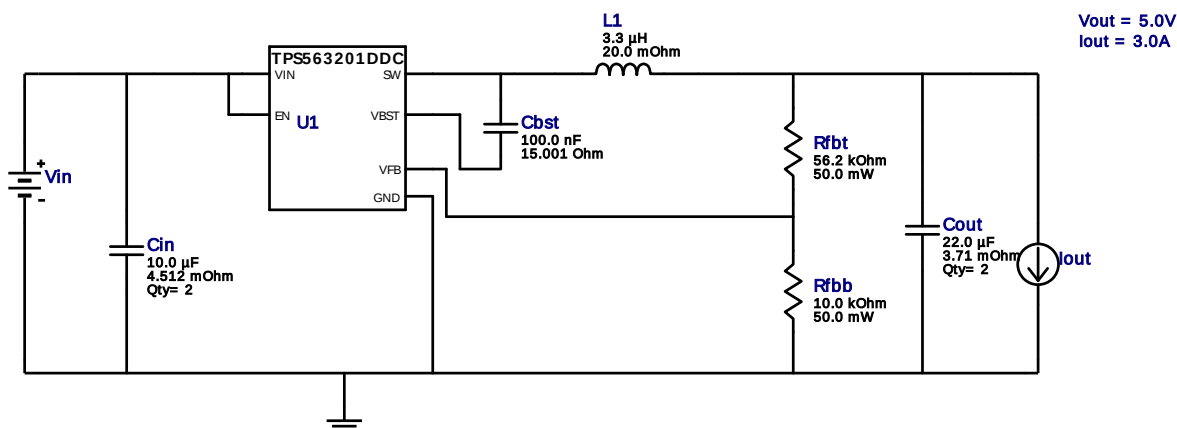








WEBENCH® Design Report

Design : 222 TPS563201DDCR
TPS563201DDCR 11V-13V to 5.00V @ 3A




Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbst	CUSTOM	CUSTOM Series= Y5V	Cap= 100.0 nF ESR= 15.001 Ohm VDC= 25.0 V IRMS= 0.0 A	1	NA	0603 0 mm ²
Cin	MuRata	GRM31CR61E106KA12L Series= X5R	Cap= 10.0 uF ESR= 4.512 mOhm VDC= 25.0 V IRMS= 2.447 A	2	\$0.12	1206_190 11 mm ²
Cout	TDK	C1608X5R1A226M080AC Series= X5R	Cap= 22.0 uF ESR= 3.71 mOhm VDC= 10.0 V IRMS= 2.69936 A	2	\$0.12	0603 5 mm ²
L1	TDK	VLP8040T-3R3N	L= 3.3 uH 20.0 mOhm	1	\$0.22	VLP8040 113 mm ²
Rfbb	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
Rfbt	Yageo	RC0201FR-0756K2L Series= ?	Res= 56.2 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
U1	Texas Instruments	TPS563201DDCR	Switcher	1	\$0.28	DDC0006A 10 mm ²

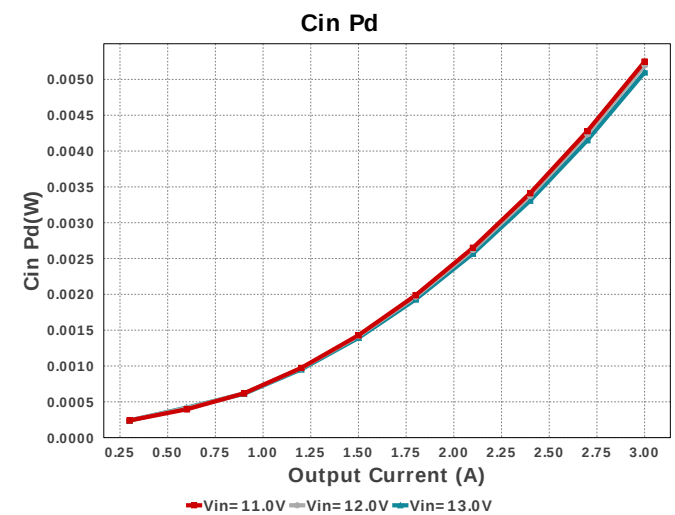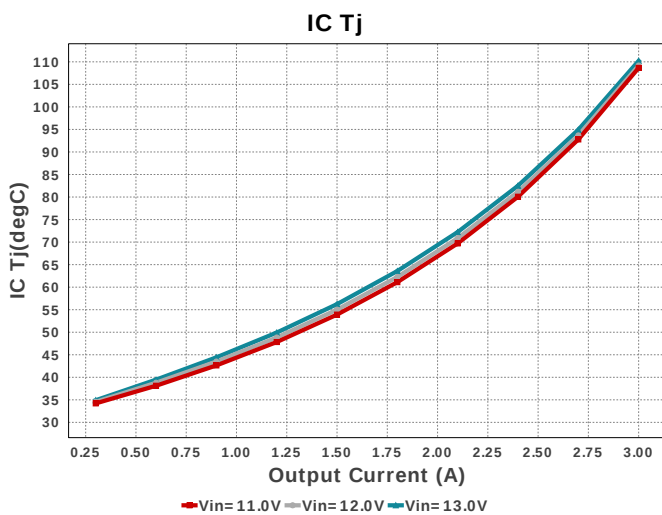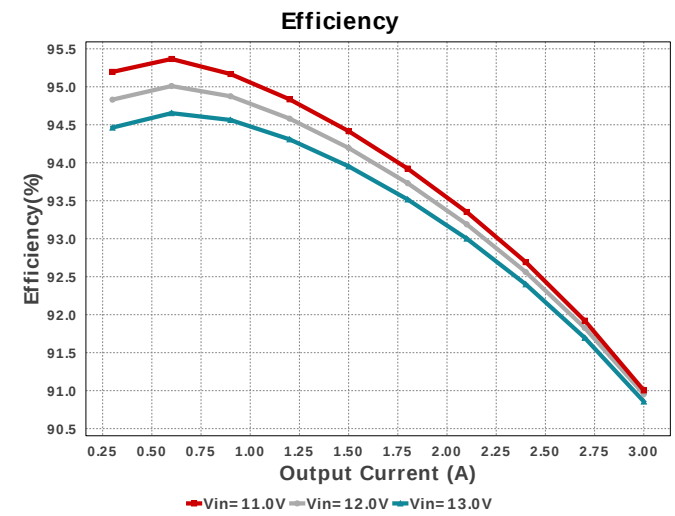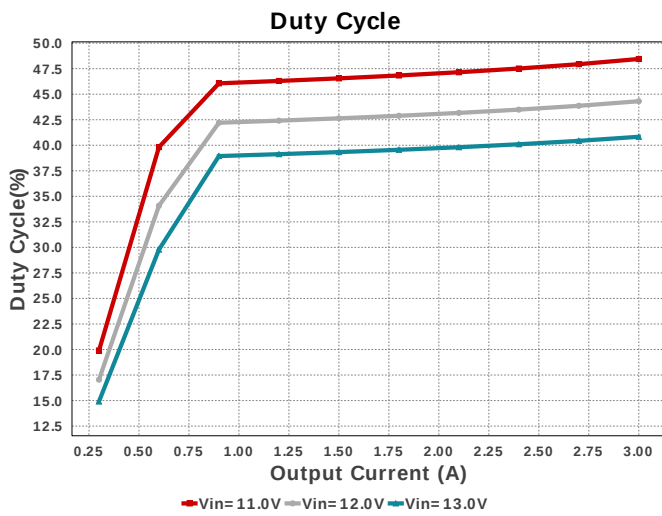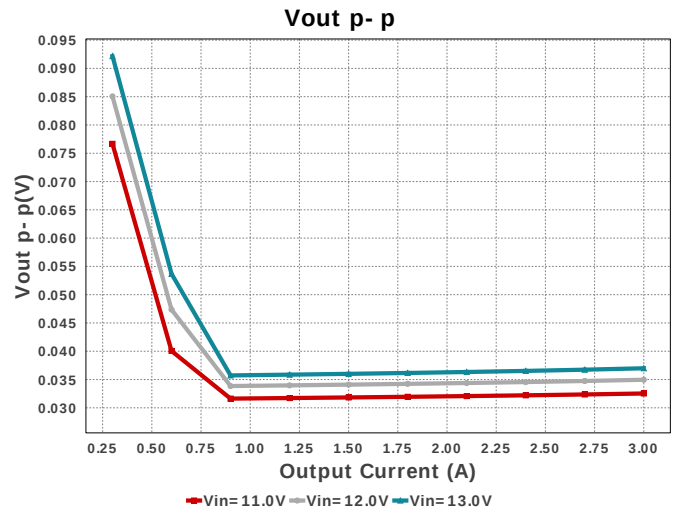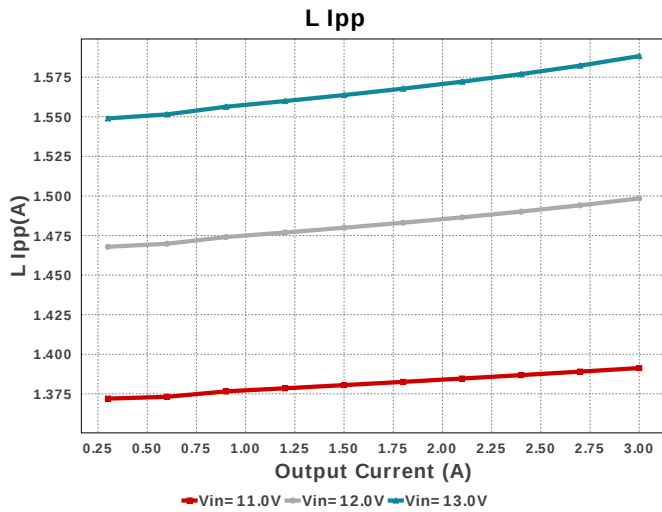


Cin IRMS

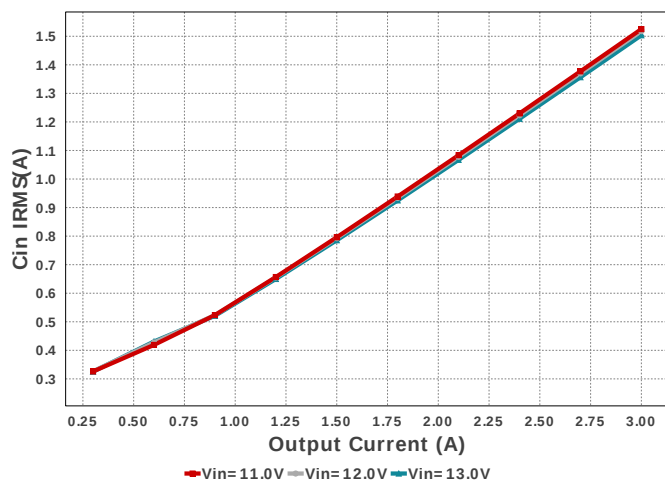


Iin Avg

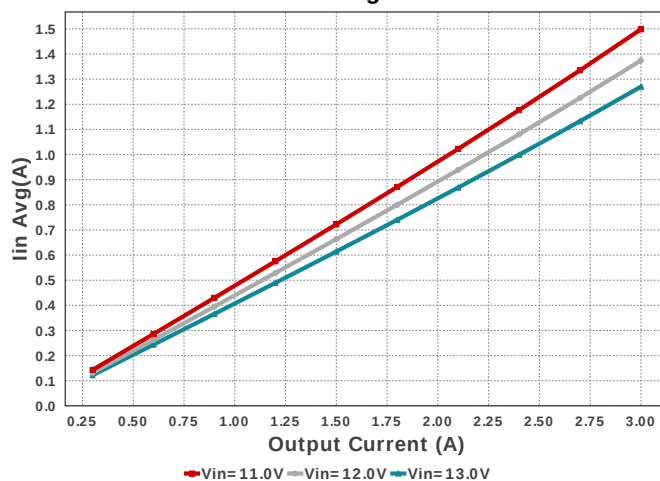


Pout

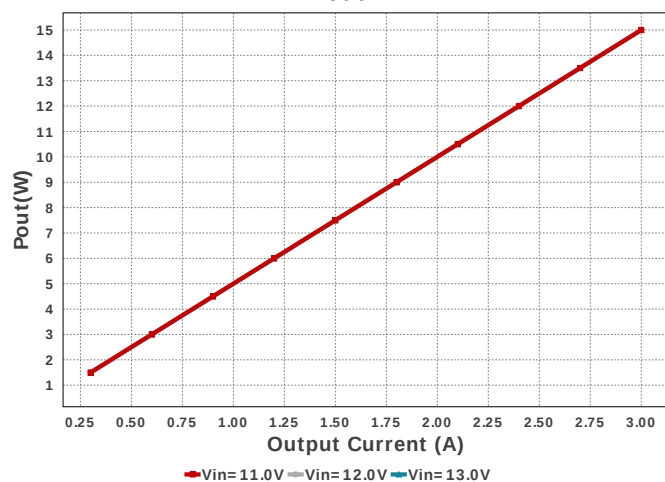


IC Ipk

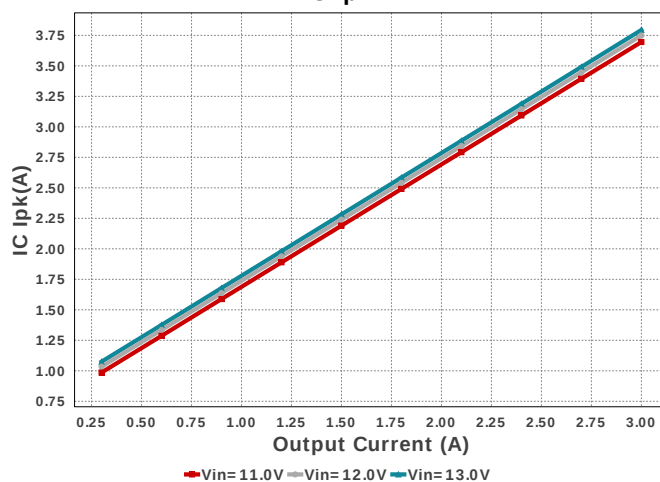


Cout IRMS

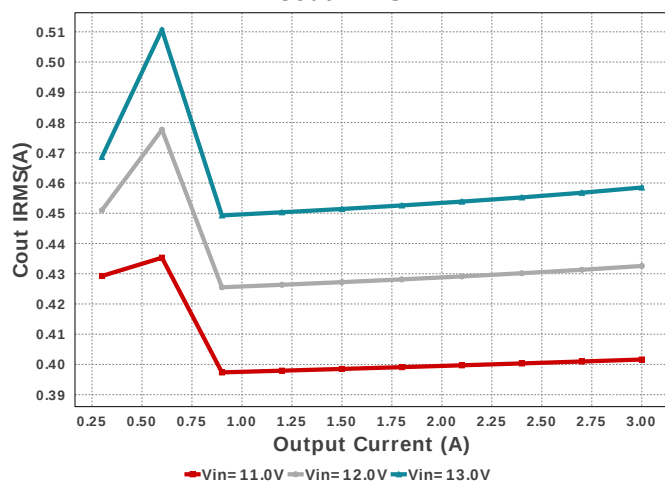

Cout Pd

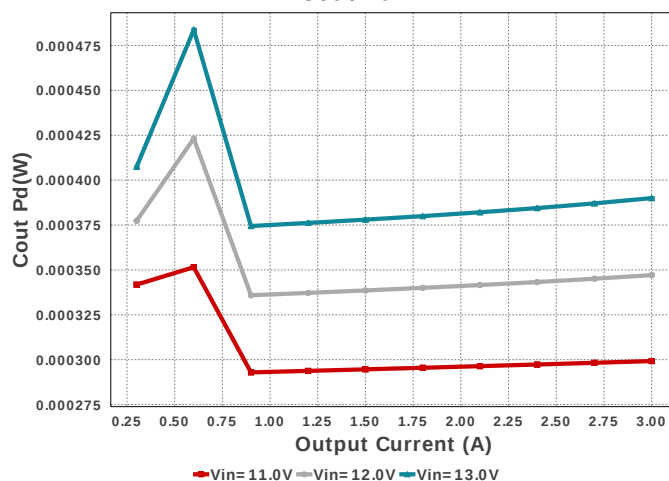

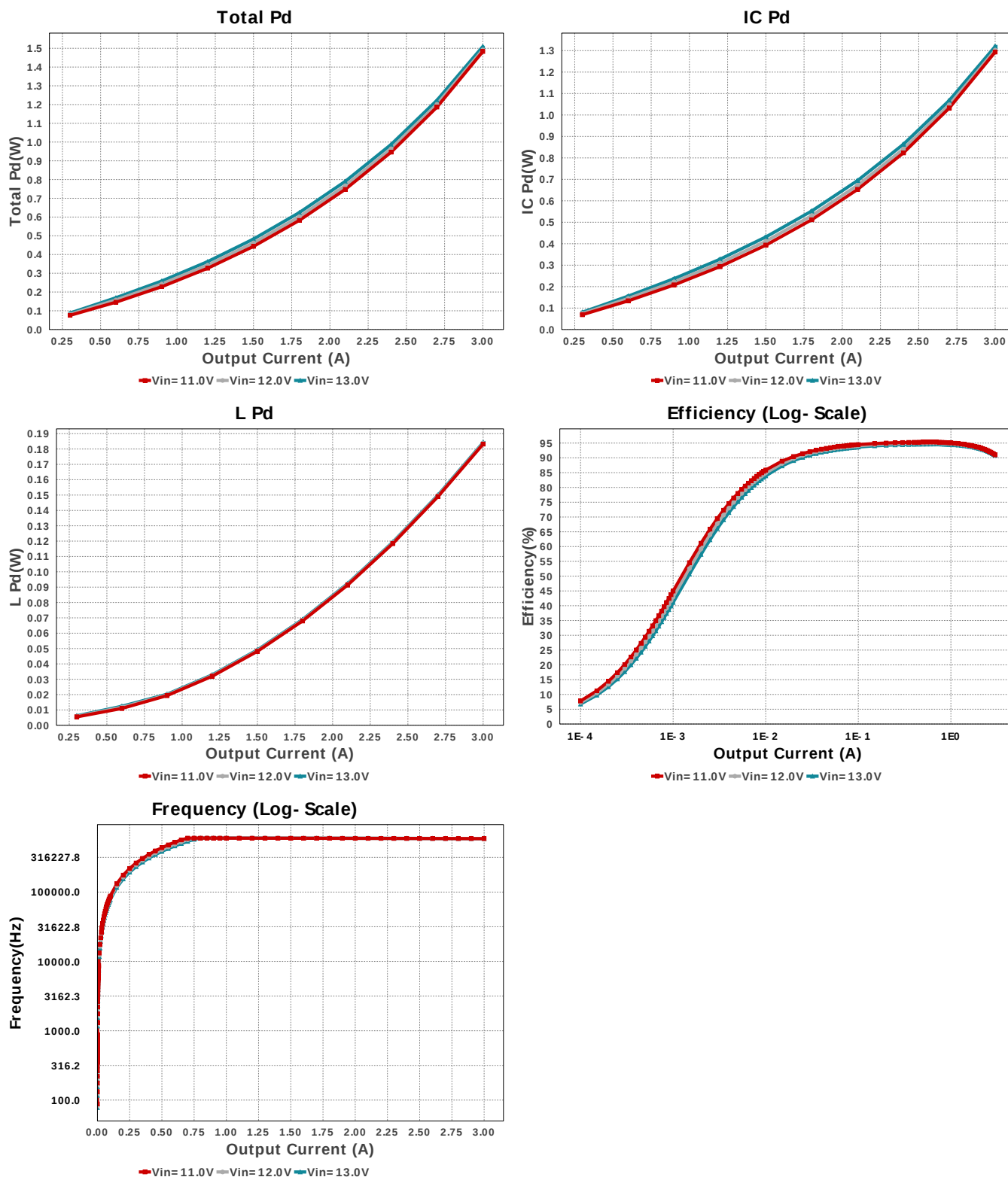

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	9		Total Design BOM count
2.	Total BOM	NA		Total BOM Cost
3.	Cin IRMS	1.503 A	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	5.099 mW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	458.515 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	389.99 μ W	Capacitor	Output capacitor power dissipation
7.	IC IpK	3.794 A	IC	Peak switch current in IC
8.	IC Pd	1.319 W	IC	IC power dissipation
9.	IC Tj	110.214 degC	IC	IC junction temperature
10.	IC Tolerance	19.0 mV	IC	IC Feedback Tolerance
11.	ICThetaJA	60.8 degC/W	IC	IC junction-to-ambient thermal resistance

#	Name	Value	Category	Description
12.	Iin Avg	1.27 A	IC	Average input current
13.	L Ipp	1.588 A	Inductor	Peak-to-peak inductor ripple current
14.	L Pd	184.2 mW	Inductor	Inductor power dissipation
15.	Cin Pd	5.099 mW	Power	Input capacitor power dissipation
16.	Cout Pd	389.99 μ W	Power	Output capacitor power dissipation
17.	IC Pd	1.319 W	Power	IC power dissipation
18.	L Pd	184.2 mW	Power	Inductor power dissipation
19.	Total Pd	1.51 W	Power	Total Power Dissipation
20.	Duty Cycle	40.83 %	System Information	Duty cycle
21.	Efficiency	90.857 %	System Information	Steady state efficiency
22.	FootPrint	164.0 mm ²	System Information	Total Foot Print Area of BOM components
23.	Frequency	591.958 kHz	System Information	Switching frequency
24.	Iout	3.0 A	System Information	Iout operating point
25.	Mode	CCM	System Information	Conduction Mode
26.	Pout	15.0 W	System Information	Total output power
27.	Vin	13.0 V	System Information	Vin operating point
28.	Vout	5.0 V	System Information	Operational Output Voltage
29.	Vout Actual	5.064 V	System Information	Vout Actual calculated based on selected voltage divider resistors
30.	Vout Tolerance	4.241 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
31.	Vout p-p	36.989 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	3.0	Maximum Output Current
VinMax	13.0	Maximum input voltage
VinMin	11.0	Minimum input voltage
Vout	5.0	Output Voltage
base_pn	TPS563201	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 11.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.


Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

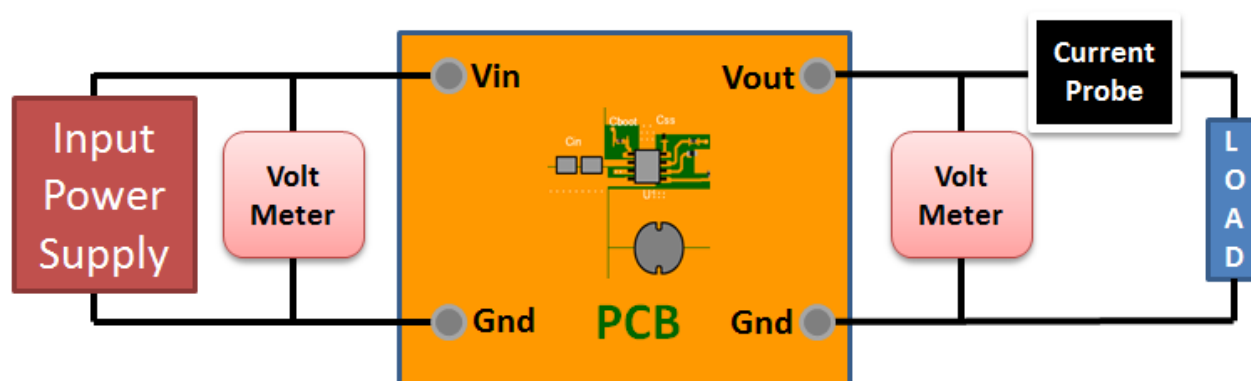


WEBENCH® Electrical Simulation Report

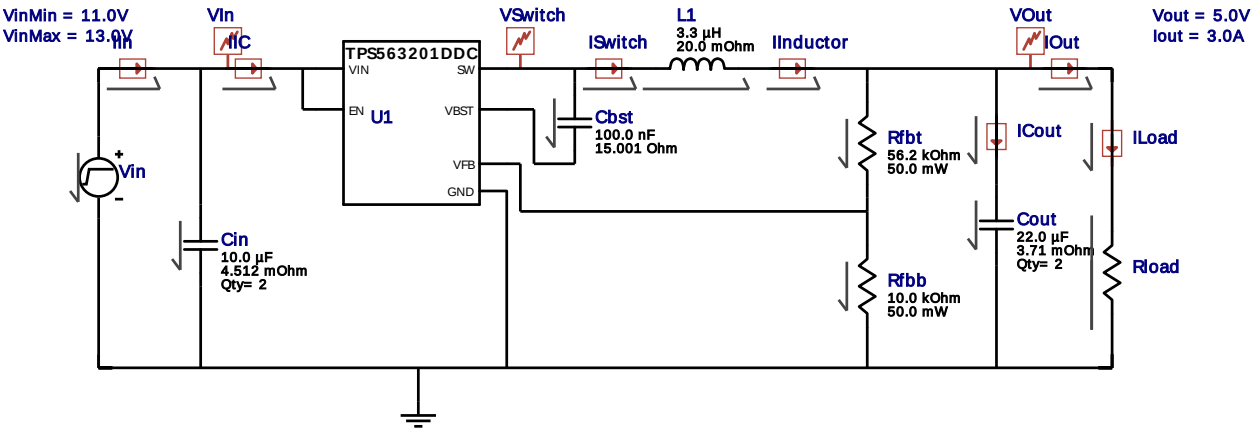Design Id = 222
sim_id = 1
Simulation Type = Startup




Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Rload	R	Load Resistance	1.666666666666667 Ohm

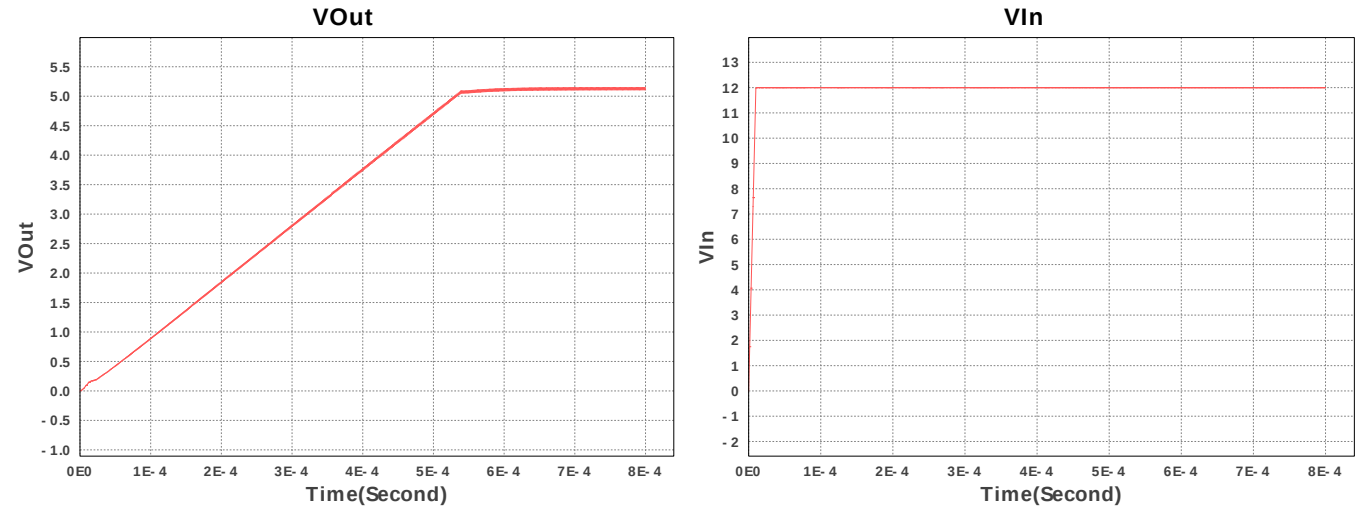


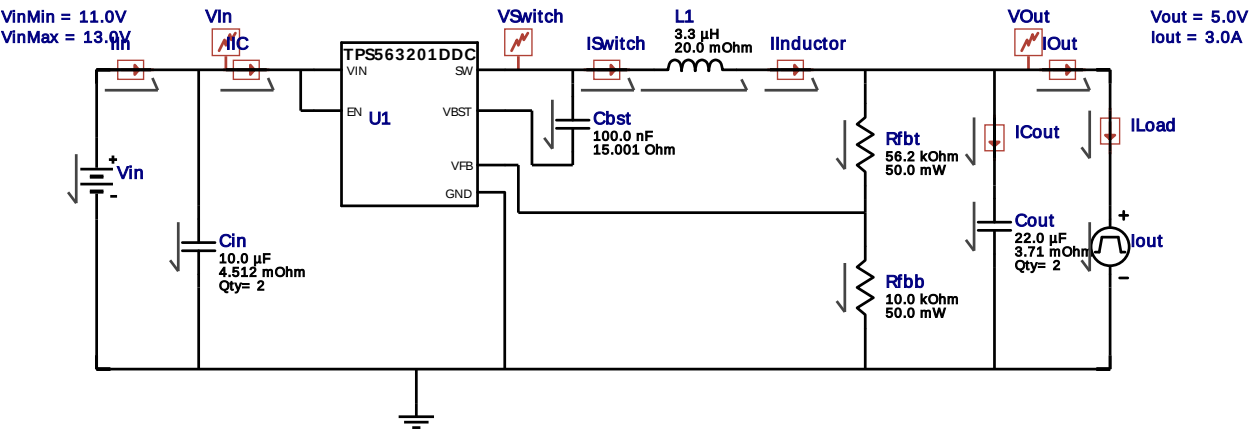Design Id = 222
sim_id = 2
Simulation Type = Load Transient




Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Cout	IC	Initial Voltage	5.0 V
2.	L1	IC	Initial Current	0 A
3.	Iout	signal_type	Signal Type	PULSE
		I1	Initial Load Current	3.0 A
		I2	Minimum Load Current	0.3 A
		Td	Initial Time Delay	300u s
		Tf	Fall Time	10u s
		Tr	Rise Time	10u s
		Pw	Pulse Width	150u s

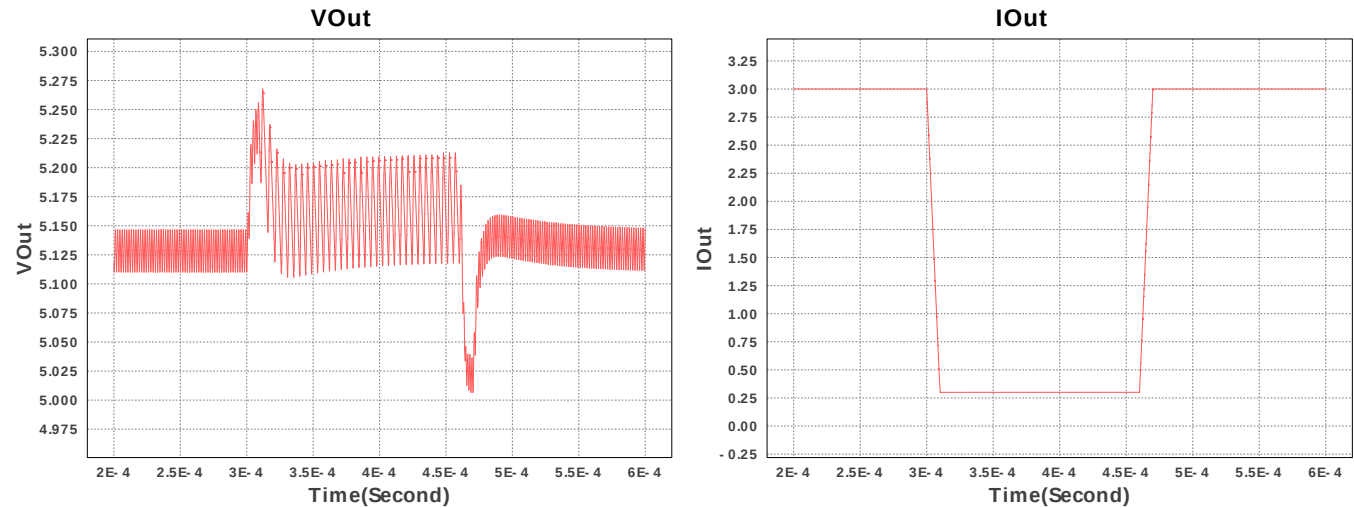


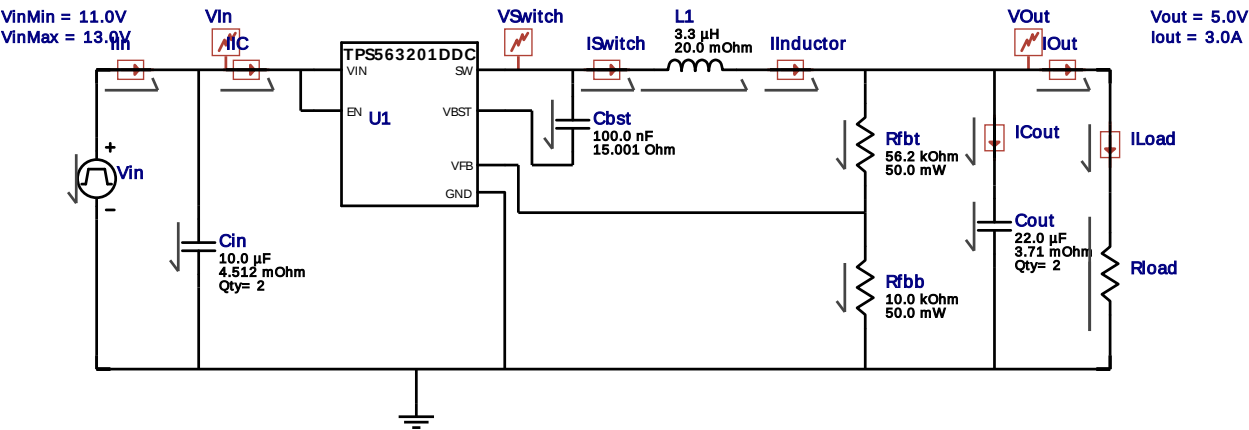Design Id = 222
sim_id = 3
Simulation Type = Input Transient



Simulation Parameters


#	Name	Parameter Name	Description	Values
1.	Cout	IC	Initial Voltage	5.0 V
2.	L1	IC	Initial Current	0 A
3.	Rload	R	Load Resistance	1.666666666666667 Ohm

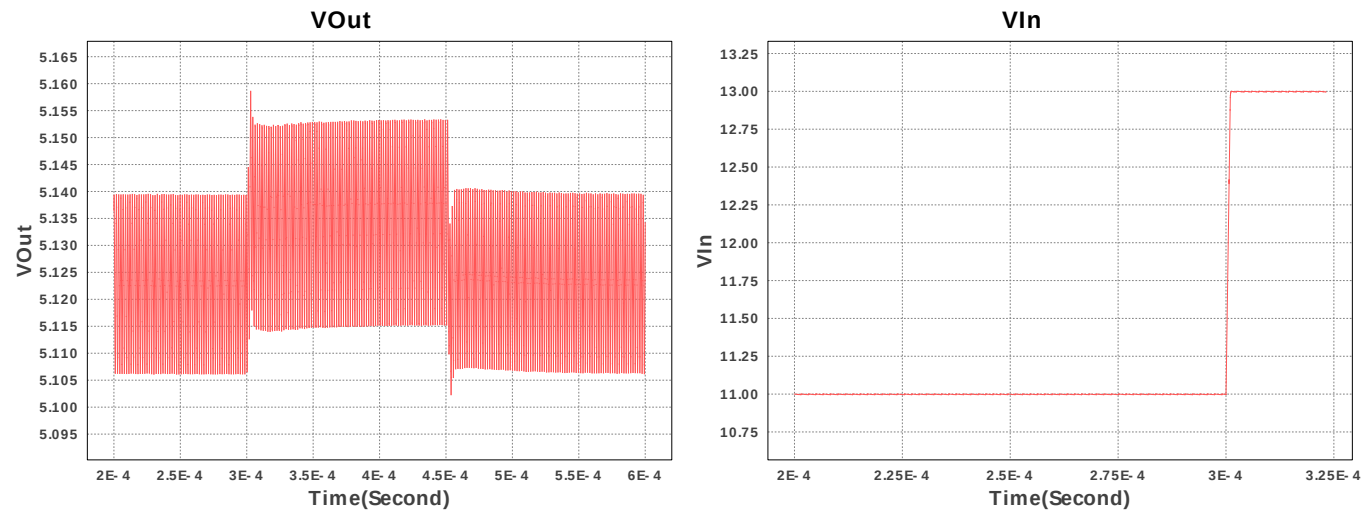

Design Id = 222


sim_id = 4

Simulation Type = Steady State

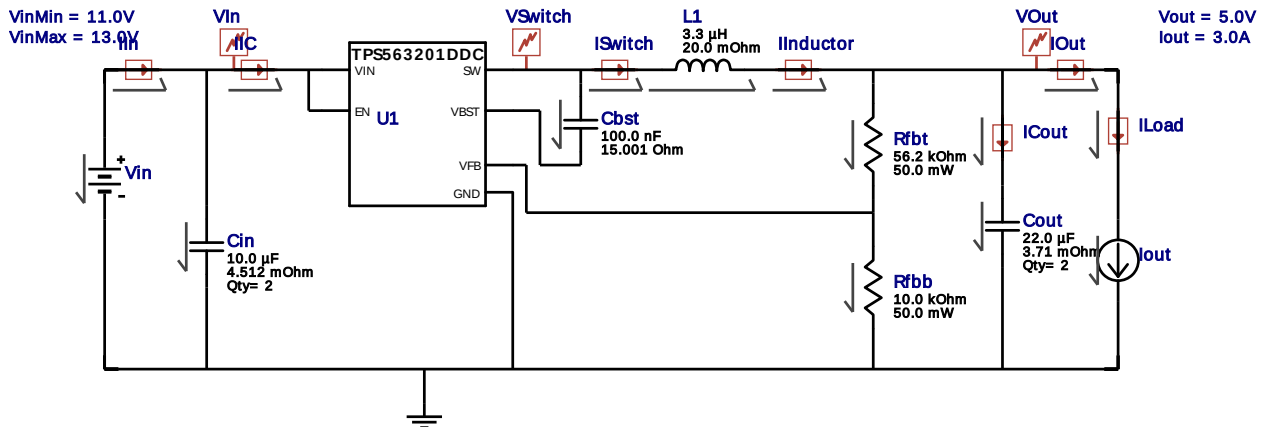

Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	IOut	IC	Initial Current	3.0 A
2.	Iout	I	Load Current	3.0 A

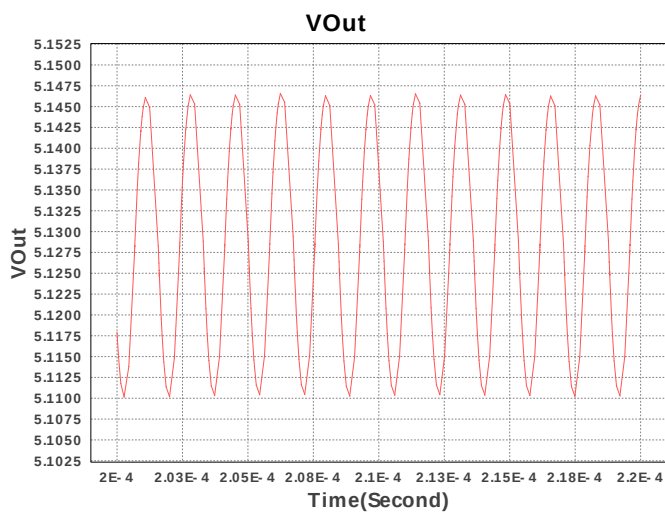

Design Assistance

- Master key : 456F448E7E1D3953[v1]
- TPS563201 Product Folder : <http://www.ti.com/product/TPS563201> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.