

Simulation conditions:



$V_{in} = V_{bat}$ (set to 3.5V) $V_{out}=6.8V$. Schematic parameters are similar with customer. The load is very light (use 1Mohm resistor as load) .

C_{out} :


22uf (GRM21BR61E226ME44L), check the datasheet on Murata website and effective capacitance @ 6.8V is only $\sim 30\% * 22uf = 6.6uf$

10uf (GRM188R61E106MA73D) check the datasheet on Murata website and effective capacitance @ 6.8V is only $\sim 30\% * 22uf = 6.6uf$

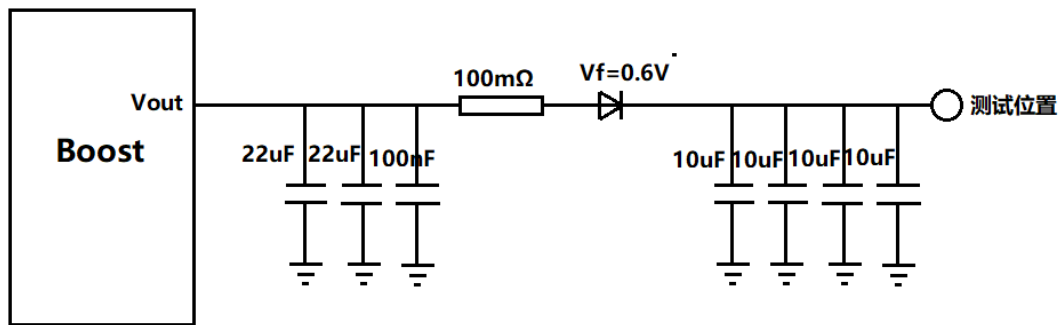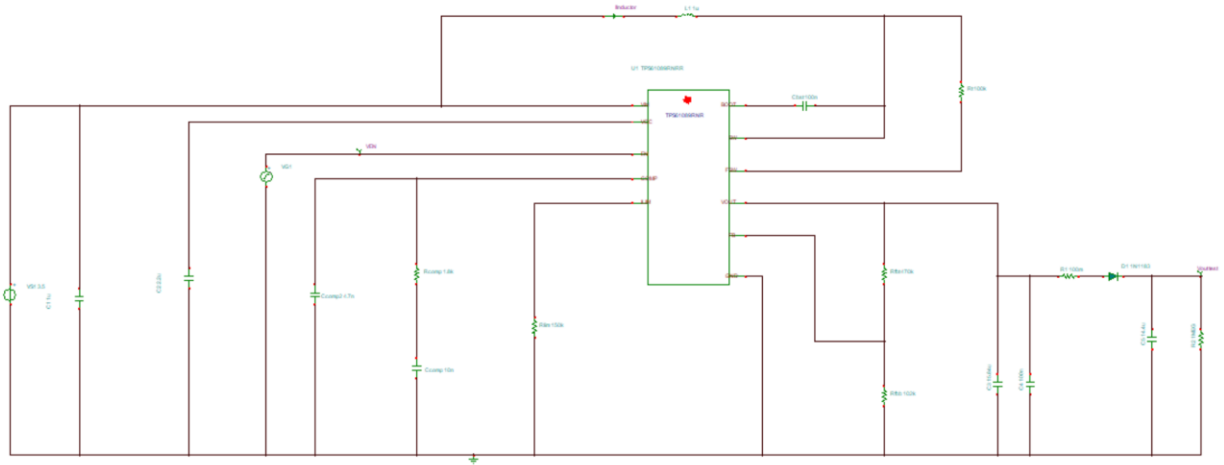
So use these effective capacitances to do simulation. Model as below, V_{out} test point is same as request shown in email.




Typical capacitance

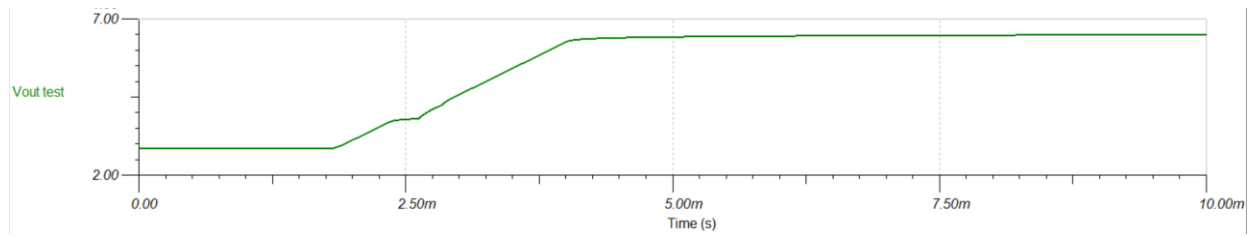

-20% decrease on capacitance

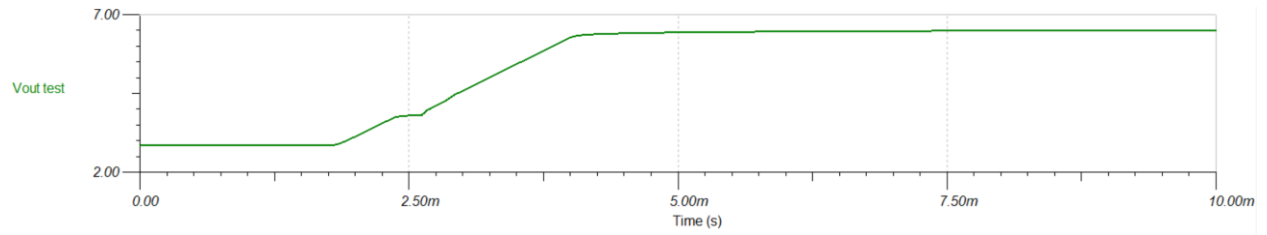

+20% increase on capacitance

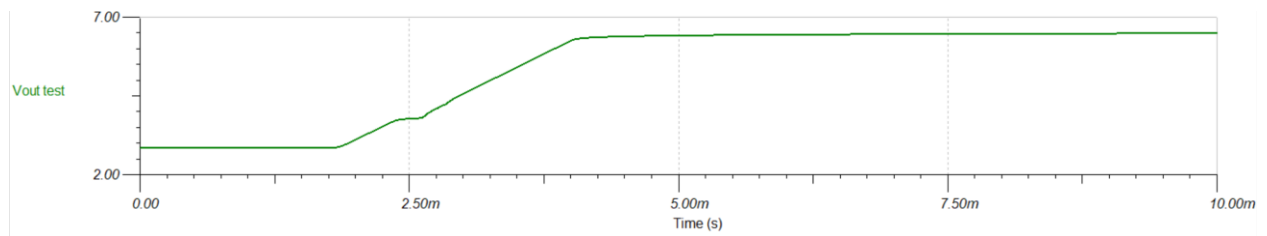

Summary:

There is no overshoot on V_{out_test} point based on simulation.