

TPS923651D1DGNR

Constant Current LED Backlight Driver

21" Display

$$V_{in} := 12 \text{ V}$$

$$f_{sw} := 400 \text{ kHz} \quad \text{Switching Frequency}$$

$$V_{ref} := 200 \text{ mV} \quad \text{Internal voltage reference}$$

$$I_{cs21} := 320 \text{ mA} \quad \text{21 Inch Monitor}$$

$$R_{cs21} := \frac{V_{ref}}{I_{cs21}} = 0.625 \Omega \quad \text{Use 634 mOhm part}$$

$$R_{cs21} := 634 \text{ m}\Omega \quad \text{Use this for Rcs}$$

$$P_{rcs21} := I_{cs21}^2 \cdot R_{cs21} = 0.0649 \text{ W} \quad \text{use .125W 0805}$$

$$\eta := 90 \% \quad \text{Expected Efficiency}$$

$$V_{oled21} := 55 \text{ V} \quad \text{Maximum Voltage on Vout for the string current}$$

$$V_{fd} := 0.6 \text{ V} \quad \text{Vorward Vf of the output schottky diode. Use 100V SMC}$$

$$P_{o21} := V_{oled21} \cdot I_{cs21} = 17.6 \text{ W} \quad \text{Output power required}$$

$$Idc_{in21} := \frac{P_{o21}}{\eta \cdot V_{in}} = 1.6296 \text{ A} \quad \text{Input current}$$

$$K_{ripple21} := 30.5 \% \quad \text{Ripple Current factor}$$

$$\Delta I_{L21} := Idc_{in21} \cdot K_{ripple21} = 0.497 \text{ A}$$

$$I_{pk21} := Idc_{in21} + \frac{\Delta I_{L21}}{2} = 1.8781 \text{ A} \quad \text{Peak Current through the switch}$$

$$L_{boost21} := \frac{V_{in} \cdot (V_{oled21} - V_{in})}{V_{oled21} \cdot K_{ripple21} \cdot Idc_{in21} \cdot f_{sw}} = 47.1887 \mu\text{H}$$

$$L_{boost} := 47 \mu\text{H}$$

$$I_{oled15r6} := 280 \text{ mA} \quad \text{15.6" Display}$$

$$V_{oled15r6} := 30 \text{ V}$$

$$R_{cs15r6} := \frac{V_{ref}}{I_{oled15r6}} = 0.7143 \Omega$$

$$P_{rcs15r6} := I_{oled15r6}^2 \cdot R_{cs15r6} = 0.056 \text{ W} \quad \text{Use 0805 .125W}$$

$$P_{o15r6} := V_{oled15r6} \cdot I_{oled15r6} = 8.4 \text{ W}$$


$$Idc_{in15r6} := \frac{P_{o15r6}}{\eta \cdot V_{in}} = 0.7778 \text{ A}$$

$$K_{ripple15r6} := 49 \%$$

$$\Delta I_{ripple15r6} := Idc_{in15r6} \cdot K_{ripple15r6} = 0.3811 \text{ A}$$

$$I_{pk15r6} := Idc_{in15r6} + \frac{\Delta I_{ripple15r6}}{2} = 0.9683 \text{ A}$$
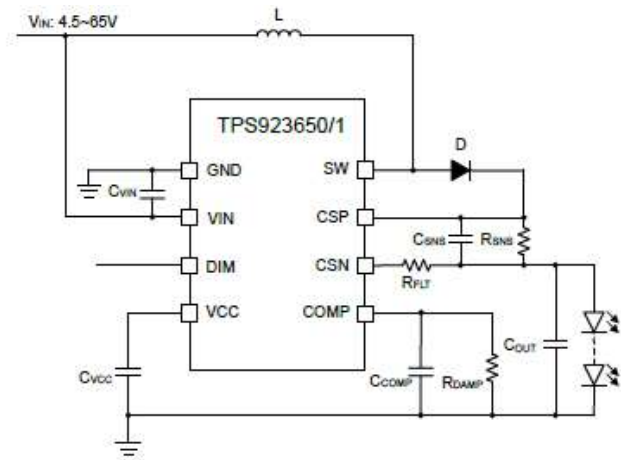
$$L_{boost15r6} := \frac{V_{in} \cdot (V_{oled15r6} - V_{in})}{V_{oled15r6} \cdot K_{ripple15r6} \cdot Idc_{in15r6} \cdot f_{sw}} = 47.2303 \mu\text{H}$$



Simplified Schematic

$$0.62 \cdot \frac{.28}{.32} = 0.5425$$

$$I_{oled12r1} := 280 \text{ mA}$$

$$V_{oled12r1} := 33 \text{ V}$$

$$R_{cs12r1} := \frac{V_{ref}}{I_{oled12r1}} = 0.7143 \text{ } \Omega$$

$$P_{rcs12r1} := I_{oled12r1}^2 \cdot R_{cs12r1} = 0.056 \text{ W} \quad \text{Use 0.125W 0805}$$

$$P_{o12r1} := V_{oled12r1} \cdot I_{oled12r1} = 9.24 \text{ W}$$

$$Idc_{in12r1} := \frac{P_{o12r1}}{\eta \cdot V_{in}} = 0.8556 \text{ A}$$

$$K_{ripple12r1} := 47.4 \text{ \%}$$

$$\Delta I_{ripple12r1} := Idc_{in12r1} \cdot K_{ripple12r1} = 0.4055 \text{ A}$$

$$I_{pk12r1} := Idc_{in12r1} + \frac{\Delta I_{ripple12r1}}{2} = 1.0583 \text{ A}$$

$$L_{boost12r1} := \frac{V_{in} \cdot (V_{oled12r1} - V_{in})}{V_{oled12r1} \cdot K_{ripple12r1} \cdot Idc_{in12r1} \cdot f_{sw}} = 47.0761 \text{ } \mu\text{H}$$

10.1" Display from +5V

$$V_{in} := 5 \text{ V}$$

$$I_{oled10r1} := 260 \text{ mA}$$

$$V_{oled10r1} := 9.6 \text{ V}$$

$$R_{cs10r1} := \frac{V_{ref}}{I_{oled10r1}} = 0.7692 \text{ } \Omega$$

$$P_{rcs10r1} := I_{oled10r1}^2 \cdot R_{cs10r1} = 0.052 \text{ W} \quad \text{Use 1206 0.25W}$$

$$P_{o10r1} := V_{oled10r1} \cdot I_{oled10r1} = 2.496 \text{ W}$$

$$Idc_{in10r1} := \frac{P_{o10r1}}{\eta \cdot V_{in}} = 0.5547 \text{ A}$$

$$K_{ripple10r1} := 23 \text{ \%}$$

$$\Delta I_{ripple10r1} := Idc_{in10r1} \cdot K_{ripple10r1} = 0.1276 \text{ A}$$

$$I_{pk10r1} := Idc_{in10r1} + \frac{\Delta I_{ripple10r1}}{2} = 0.6185 \text{ A}$$

$$L_{boost10r1} := \frac{V_{in} \cdot (V_{oled10r1} - V_{in})}{V_{oled10r1} \cdot K_{ripple10r1} \cdot Idc_{in10r1} \cdot f_{sw}} = 46.9501 \text{ } \mu\text{H}$$

8" Display from +5V

$$I_{oled8} := 600 \text{ mA}$$

$$V_{oled8} := 10.5 \text{ V}$$

$$R_{cs8} := \frac{V_{ref}}{I_{oled8}} = 0.3333 \text{ } \Omega$$

$$P_{rcs8} := I_{oled8}^2 \cdot R_{cs8} = 0.12 \text{ W} \quad \text{Use 1206, 0.25W}$$

$$P_{o8} := V_{oled8} \cdot I_{oled8} = 6.3 \text{ W}$$

$$Idc_{in8} := \frac{P_{o8}}{\eta \cdot V_{in}} = 1.4 \text{ A}$$

$$K_{ripple8} := 10 \%$$

$$\Delta I_{ripple8} := Idc_{in8} \cdot K_{ripple8} = 0.14 \text{ A}$$

$$I_{pk8} := Idc_{in8} + \frac{\Delta I_{ripple8}}{2} = 1.47 \text{ A}$$

$$L_{boost8} := \frac{V_{in} \cdot (V_{oled8} - V_{in})}{V_{oled8} \cdot K_{ripple8} \cdot Idc_{in8} \cdot f_{sw}} = 46.7687 \text{ } \mu\text{H}$$

7" Display from +5V

$$I_{oled7} := 180 \text{ mA}$$

$$V_{oled7} := 9.3 \text{ V}$$

$$R_{cs7} := \frac{V_{ref}}{I_{oled7}} = 1.1111 \text{ } \Omega$$

$$P_{rcs7} := I_{oled7}^2 \cdot R_{cs7} = 0.036 \text{ W} \quad \text{Us an 0603 0.063W}$$

$$P_{o7} := V_{oled7} \cdot I_{oled7} = 1.674 \text{ W}$$

$$Idc_{in7} := \frac{P_{o7}}{\eta \cdot V_{in}} = 0.372 \text{ A}$$

$$K_{ripple7} := 33 \%$$

$$\Delta I_{ripple7} := Idc_{in7} \cdot K_{ripple7} = 0.1228 \text{ A}$$

$$I_{pk7} := Idc_{in7} + \frac{\Delta I_{ripple7}}{2} = 0.4334 \text{ A}$$

$$L_{boost7} := \frac{V_{in} \cdot (V_{oled7} - V_{in})}{V_{oled7} \cdot K_{ripple7} \cdot Idc_{in7} \cdot f_{sw}} = 47.0802 \text{ } \mu\text{H}$$

To Decrease the likelihood of a mistake on the factory floor we will have the default configuration be the 5V rail and 180mA.

This way a 21" screen will be dim but still display something

$$R_{cs7} = 1.1111 \, \Omega$$

$$P_{rcs7} = 0.036 \, W$$

Use a 1.1 ohm 0603 for this

$$R_{cs8} = 0.3333 \, \Omega$$

$$R_{cs10r1} = 0.7692 \, \Omega$$

$$R_{cs12r1} = 0.7143 \, \Omega$$

$$R_{cs15r6} = 0.7143 \, \Omega$$

$$R_{cs21} = 0.634 \, \Omega$$

$$R_{pcs8} := \frac{R_{cs7} \cdot R_{cs8}}{R_{cs7} - R_{cs8}} = 0.4762 \, \Omega$$

Use 0.47

$$P_{prcs8} := \frac{V_{ref}^2}{R_{pcs8}} = 0.084 \, W$$

Use an 0805 0.125W

$$R_{pcs10r1} := \frac{R_{cs7} \cdot R_{cs10r1}}{R_{cs7} - R_{cs10r1}} = 2.5 \, \Omega$$

Use 2.5 ohm

$$P_{prcs10r1} := \frac{V_{ref}^2}{R_{pcs10r1}} = 0.016 \, W$$

Use an 0402 0.032W

$$R_{pcs12r1} := \frac{R_{cs7} \cdot R_{cs12r1}}{R_{cs7} - R_{cs12r1}} = 2 \, \Omega$$

Use 2 ohm

$$P_{prcs12r1} := \frac{V_{ref}^2}{R_{pcs12r1}} = 0.02 \, W$$

Use an 0603 0.063W

$$R_{pcs15r6} := \frac{R_{cs7} \cdot R_{cs15r6}}{R_{cs7} - R_{cs15r6}} = 2 \, \Omega$$

Use 2 ohm

$$P_{prcs15r6} := \frac{V_{ref}^2}{R_{pcs15r6}} = 0.02 \, W$$

Use an 0603 0.063W

$$R_{pcs21} := \frac{R_{cs7} \cdot R_{cs21}}{R_{cs7} - R_{cs21}} = 1.4765 \, \Omega$$

Use 1.47 ohm

$$P_{prcs21} := \frac{V_{ref}^2}{R_{pcs21}} = 0.0271 \, W$$

Use an 0603 0.063W

Diode Selection

$$I_{dpk} := I_{pk21} = 1.8781 \text{ A}$$

Maximum Peak Current through the diode

$$V_{rrr} := V_{oled21} = 55 \text{ V}$$

Select a 3A, 100V, SMB Diode like a SK310