

APPENDIX III - FREQUENCY RESPONSE OF THE CURRENT LOOP

- CS/A - Figure 22 shows the open-loop gain and phase response of the UC1834 CS/A. This is also a transconductance amplifier, having $g_m \approx 1/70\Omega = 14\text{ms}$. The voltage gain is analogous to that of the E/A. The E/A compensation impedance (Z_C or $Z_{R/E/A}$) is also seen by the CS/A output. For purposes of small signal AC analysis, the CS/A will always see this impedance as being returned to V_{IN} (as shown in Figures 16c, d) when the E/A is compensated by either of the methods shown in Table 2.

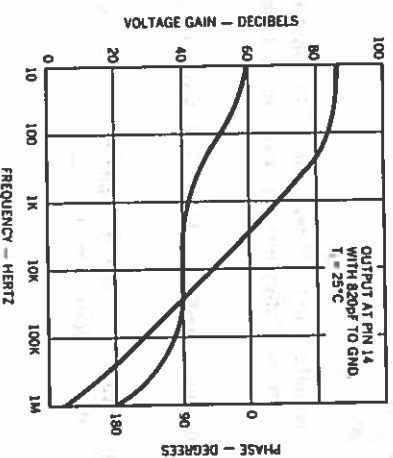


Figure 22. Current Sense Amplifier Gain and Phase Frequency Response

- Pass Transistor - Introduces current gain β to the loop transfer of both basic configurations (Figures 16c, d). Considerations outlined in Appendix I also apply here.
- Sense Resistor - Resistance value R_{SENSE} appears in transfer function for both configurations.
- Drive Transistor - In the circuit of Figure 16c, R_E allows operation of the driver as an emitter-follower. Effective conductance is $1/R_E$.

Closed-loop responses are given by the following:

for circuit of Figure 16c:

$$A_1 = g_m \cdot Z_C \cdot \frac{1}{R_E} \cdot \beta \cdot R_{SENSE} \quad \left(f < 500\text{kHz}, f < \frac{f_T}{\beta} \left(1 + \frac{\beta r_e}{R_{BE}} \right) \right)$$

for circuit of Figure 16d:

$$A_1 = g_m \cdot \frac{Z_C}{Z_C + \beta Z_L} \cdot \beta \cdot R_{SENSE} \quad \left(f < 500\text{kHz}, f < \frac{f_T}{\beta} \left(1 + \frac{\beta r_e}{R_{BE}} \right) \right)$$

Uniprobe Integrated Circuits Corporation
7 Continental Boulevard • P.O. Box 399 • Merrimack, New Hampshire • 03054-0399
Telephone 603-424-2410 • FAX 603-424-3460

9-46

A 25 WATT OFF-LINE FLYBACK SWITCHING REGULATOR

Introduction

This Application Note describes a low cost (less than \$10.00) switching power supply for applications requiring multiple output voltages, e.g. personal computers, instruments, etc... The discontinuous mode flyback regulator used in this application provides good voltage tracking between outputs, which allows the use of primary side voltage sensing. This sensing technique reduces costs by eliminating the need for an isolated secondary feedback loop.

The low cost, (8 pin) UC3844 current mode control chip employed in this power supply provides performance advantages such as:

- 1) Fast transient response
- 2) Pulse by pulse current limiting
- 3) Stable operation

To simplify drive circuit requirements, a TO-220 power MOSFET (JFN833) is utilized for the power switch. This switch is driven directly from the output of the control chip.

Power Supply Specifications

1. Input voltage: 95VAC to 130VAC (50Hz/60Hz)
2. Output voltage:
 - A. +5V, $\pm 5\%$: 1A to 4A load
 - B. +12V, $\pm 3\%$: 0.1A to 0.3A load
 - C. -12V, $\pm 3\%$: 0.1A to 0.3A load
3. Line isolation: 3750 Volts
4. Switching Frequency: 40KHz
5. Efficiency @ Full Load: 70%

Basic Circuit Operation

The 117VAC input line voltage is rectified and smoothed to provide DC operating voltage for the circuit. When power is initially applied to the circuit, capacitor C2 charges through R2. When the voltage

across C2 reaches a level of 16V the output of IC-1 is enabled, turning on power MOSFET Q1. During the on time of Q1, energy is stored in the air gap of transformer (inductor) T1. At this time the polarity of the output windings is such that all output rectifiers are reverse biased and no energy is transferred. Primary current is sensed by a resistor, R10, and compared to a fixed 1 volt reference inside IC1. When this level is reached, Q1 is turned off and the polarity of all transformer windings reverses, forward biasing the output rectifiers. All the energy stored is now transferred to the output capacitors. Many cycles of this store/release action are needed to charge the outputs to their respective voltages. Note that C2 must have enough energy stored initially to keep the control circuitry operating until C4 is charged to a level of approximately 13V. The voltage across C4 is fed through a voltage divider to the error amplifier (pin 2) and compared to an internal 2.5V reference.


Energy stored in the leakage inductance of T1 causes a voltage spike which will be added to the normal reset voltage across T1 when Q1 turns off. The clamp consisting of D4, C9 and R12 limits this voltage excursion from exceeding the BVDS rating of Q1. In addition, a turn-off snubber made up of D5, C8 and R11 keeps power dissipation in Q1 low by delaying the voltage rise until drain current has decreased from its peak value. This snubber also damps out any ringing which may occur due to parasitics.

Less than 3.5% line and load regulation is achieved by loading the output of the control winding, Nc, with R9. This resistor dissipates the leakage energy associated with this winding. Note that R9 must be isolated from R2 with diode D2, otherwise C2 could not charge to the 16V necessary for initial start-up. A small filter inductor in the 5V secondary is added to reduce output ripple voltage to less than 50mV. This inductor also attenuates any high frequency noise.


9-47

APPLICATION NOTE
U-96A

25W OFF-LINE FLYBACK REGULATOR

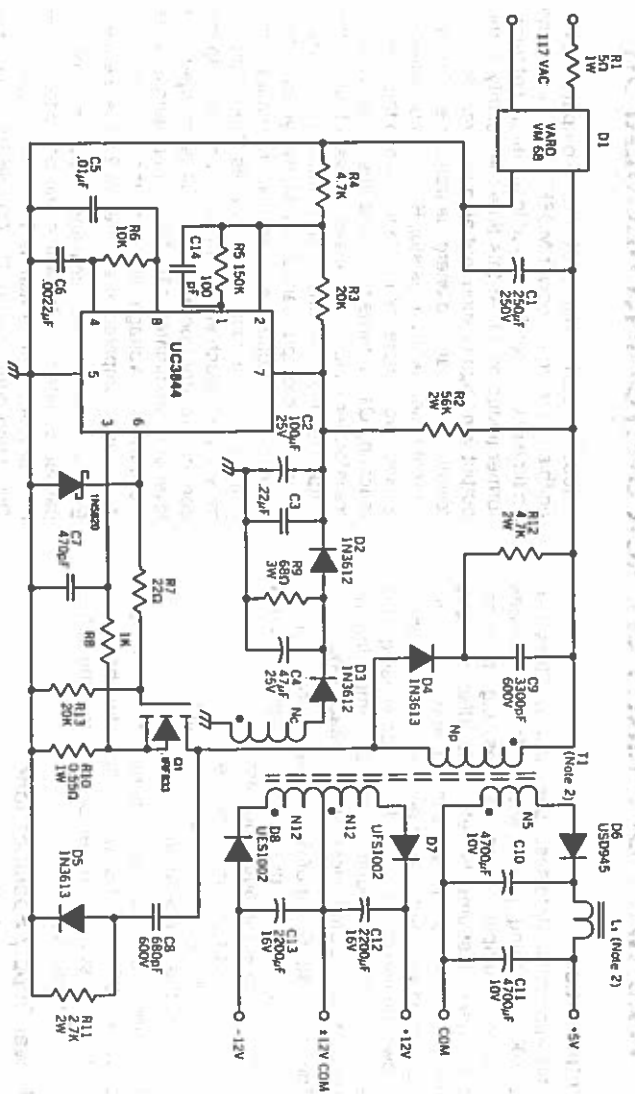

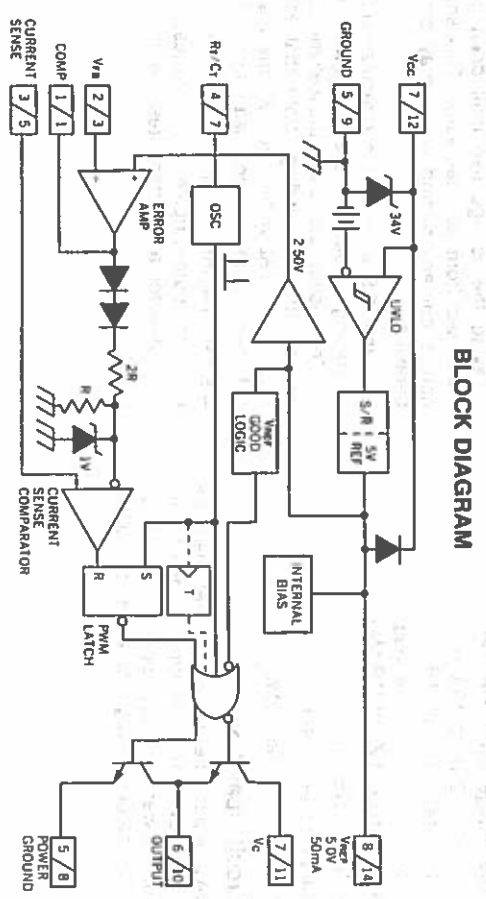Notes: 1. All resistors are 1/4 watt unless noted
2. See Appendix for construction details




Note: 1. $\frac{1}{2}$ W = DIL 8 Pin Number, 8 = SO 14 Pin Number
2. Toroid flip flop used only in 184 and 184S

UC3842/3/4/5 CURRENT MODE PWM CONTROLLER

APPLICATION NOTE


TYPICAL SWITCHING WAVEFORMS

T_{on} — Drive waveforms

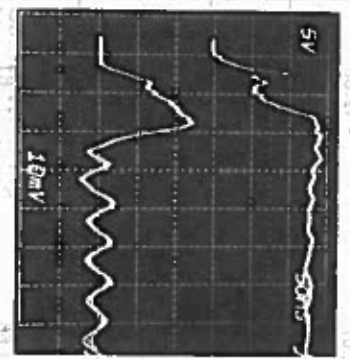


Upper trace: Q₁ — Gate to source voltage
Lower trace: Q₁ — Gate current


T_{off} — Drive waveforms

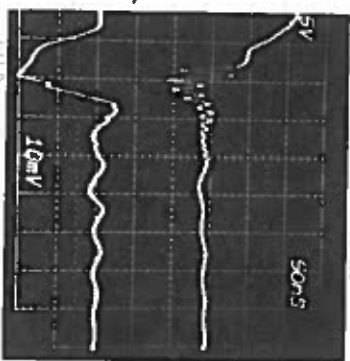

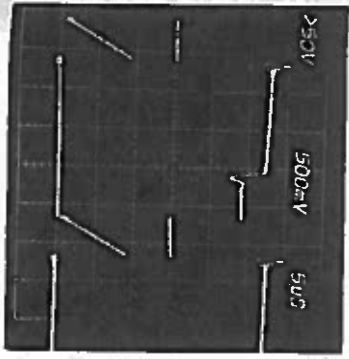Upper trace: Q₁ — Gate to source voltage
Lower trace: Q₁ — Gate current



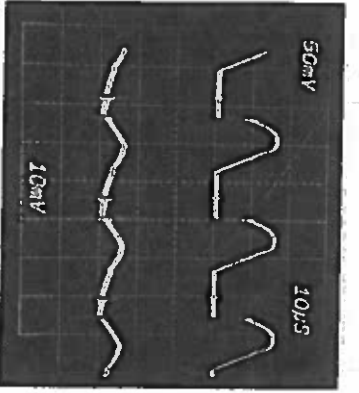Upper trace: Q₁ — Drain to source voltage
Lower trace: Primary current — I_p



Upper trace: +5V charging current
Lower trace: +5V output ripple voltage

APPLICATION NOTE

U-96A

PERFORMANCE DATA

CONDITIONS	5V out	12V out	-12V out
Low Line (95VAC)			
± 12 @ 100mA	+ 5V @ 1.0A 4.0A	5.211 4.854	12.05 12.19
± 12 @ 300mA	+ 5V @ 1.0A 4.0A	5.199 4.950	11.73 11.68
Nominal Line (120VAC)			
± 12 @ 100mA	+ 5V @ 1.0A 4.0A	5.220 4.875	12.07 12.23
± 12 @ 300mA	+ 5V @ 1.0A 4.0A	5.208 4.906	11.73 11.67
High Line (130VAC)			
± 12 @ 100mA	+ 5V @ 1.0A 4.0A	5.207 4.855	12.06 12.21
± 12 @ 300mA	+ 5V @ 1.0A 4.0A	5.200 4.902	11.71 11.66
Overall Line and Load Regulation			
		±3.5%	±2.4%

PARTS LIST

IC's	CAPACITORS	RESISTORS	MAGNETICS
IC1 UC3844	C1 250µF, 250V	C10, C11 4700µF, 10V	R7 22Ω
POWER MOSFET	C2 100µF, 25V	C12, C13 2200µF, 16V	R8 1K
Q1 UFN833	C3 0.22µF, 25V	C14 100pF, 25V	R9 68Ω, 3W
RECTIFIERS	C4 47µF, 25V	R1 5Ω, 1W	R10 0.55Ω, 1W
D1 VM68 varo	C5 .01µF, 25V	R2 56K, 2W	R11 2.7K, 2W
D2, D3 1N3612	C6 .0047µF, 25V	R3 20K	R12 4.7K, 2W
D4, D5 1N3613	C7 470pF, 25V	R4 4.7K	R13 20K
D6 USD945	C8 680pF, 600V	R5 150K	
D7, D8 UES1002	C9 3300pF, 600V	R6 10K	

APPLICATION NOTE

U-96A


APPENDIX

POWER TRANSFORMER—T1


Core: Ferroxcube EC-35/3C8
Gap: 10 mill in each outer leg

Ferroxcube EC-35/3C8

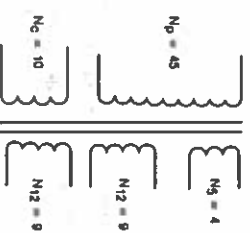NOTE: For reduced EMI put gap in center leg only.
Use 20 mil.



TRANSFORMER CONSTRUCTION

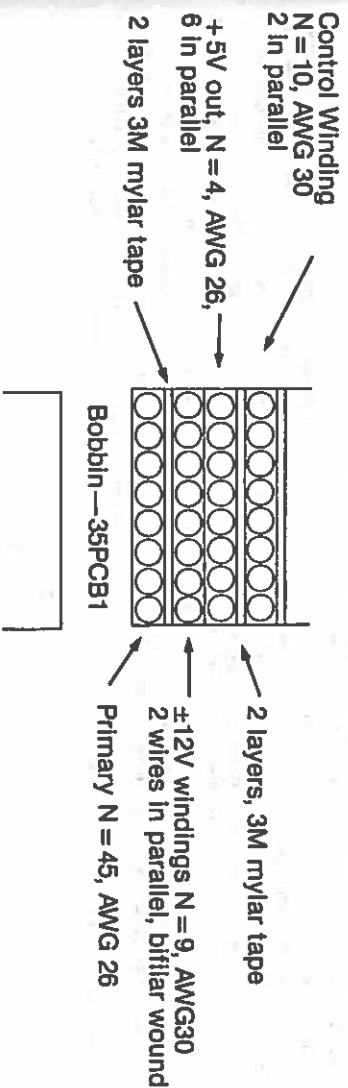

5V OUTPUT INDUCTOR

