
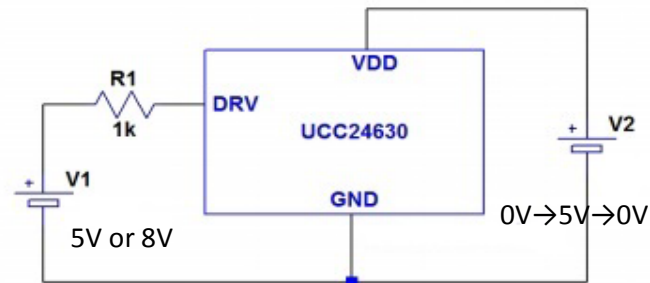


VDD, DRV voltage

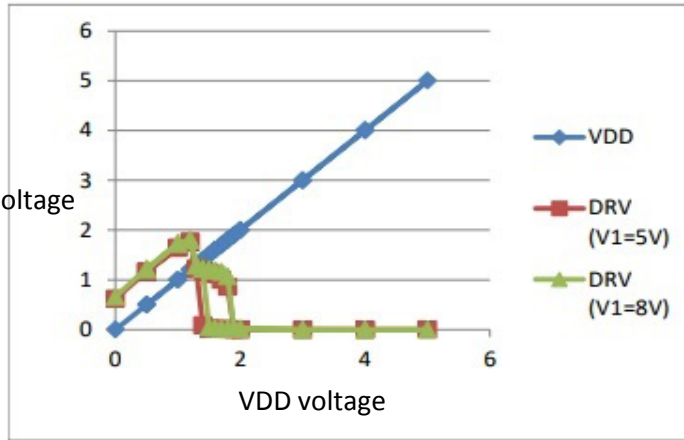

TEST circuit

Terminal voltage

VDD	DRV (V1=5V)	DRV (V1=8V)	
V	0	0.62	0.66
D	0.5	1.17	1.23
D	1	1.64	1.72
D	1.2	1.76	1.8
0	1.3	1.22	1.29
0	1.4	1.18	1.22
V	1.5	1.15	1.21
V	1.6	1.11	1.19
↓	1.7	1	1.16
5	1.8	0.86	1.07
V	1.9	0.01	0.015
V	2	0.005	0.012
	3	0	0.005
	4	0	0
	5	0	0
	4	0	0
	3	0	0
V	2	0.005	0.015
D	1.9	0.005	0.02
D	1.8	0.01	0.021
D	1.7	0.012	0.025
4	1.6	0.015	0.03
V	1.5	0.025	0.05
V	1.4	0.09	1.22
↓	1.3	1.22	1.28
0	1.2	1.76	1.8
V	1	1.64	1.74
V	0.5	1.16	1.2
0	0	0.62	0.66