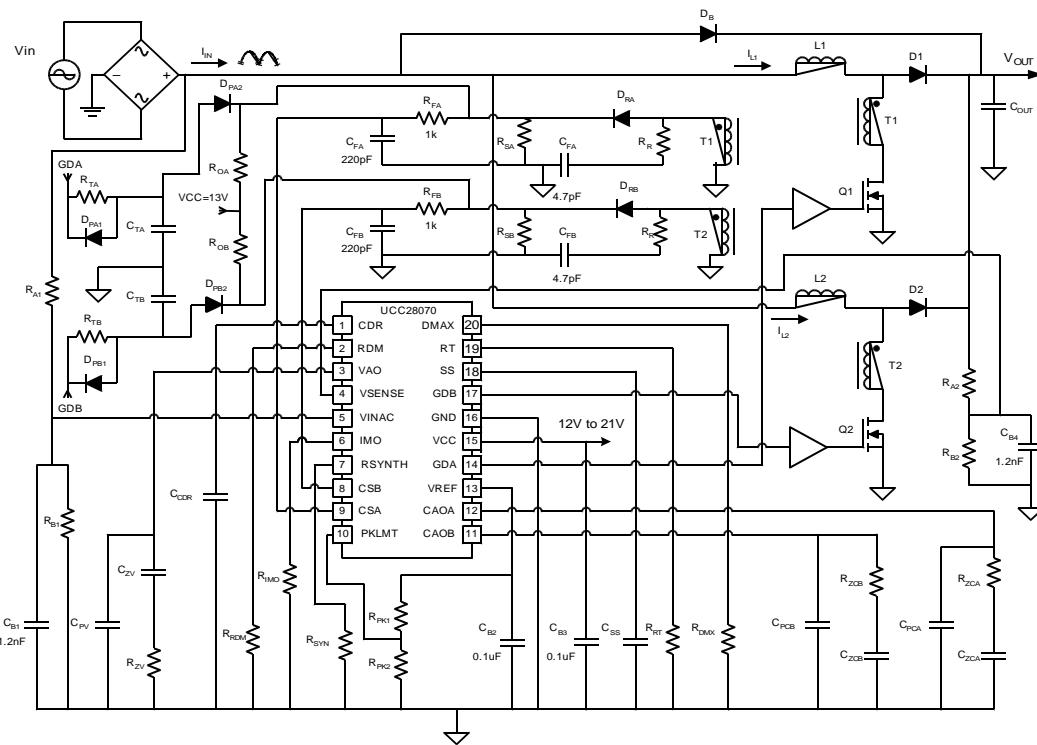


<b>UCC28070 Controller Setup Tool</b>	15/08/2008		
<b>Preliminary</b>			
Notes:			
This design tool is designed to work with the UCC28070 Application Note SLUA479			
This design tool is optimized for a Universal Input and can be used for designs where the input voltage is anywhere between 85V to 265V RMS.			
<b>Please enter design parameters into the shaded cells;</b>			
<b>Calculated results will be in GRAY</b>			
Design Parameters:	Variable Names		Units
Minimum RMS Input Voltage	V <sub>IN_MIN</sub>	85	V
Maximum RMS Input Voltage	V <sub>IN_MAX</sub>	265	V
Minimum Line Frequency	f <sub>LINE</sub>	47	Hz
Maximum Line Frequency		63	Hz
Maximum Output Power	P <sub>OUT</sub>	1900	W
Full Load Efficiency (Must be less than 0.99)	η	0,90	
Switching Frequency	f <sub>S</sub>	4,00E+04	Hz
Output Voltage	V <sub>OUT</sub>	390	V
Maximum Duty Cycle	D <sub>MAX</sub>	0,97	
Soft Start Time	t <sub>SS</sub>	0,50	s
Optional Frequency Dither Magnitude (Total Δfs)	f <sub>DM</sub>	0,00E+00	Hz
Optional Frequency Dither Rate	f <sub>DR</sub>	0,00E+00	Hz
VCC	VCC	12	V
<b>Component Selection, Trip Points and Calculated Values from the UCC28070 Design Example</b>			
Duty Cycle at the Peak of Low Line Input	D <sub>PLL</sub>	0,69	
Inductor Ripple Current Cancellation at the Peak of Low Line	K(D <sub>PLL</sub> )	0,55	
Inductor Ripple Current	ΔI <sub>L1</sub>	19,01	
Calculated Boost Inductors L <sub>1_MIN</sub> , L <sub>2_MIN</sub>	L <sub>1_MIN</sub> , L <sub>2_MIN</sub>	1,09E-04	H
Enter the Lowest Inductance Value of the Real Inductor	L <sub>1_MIN</sub> , L <sub>2_MIN</sub>	1,00E-04	H
Enter the Highest Inductance Value of the Real Inductor	L <sub>1_MAX</sub> , L <sub>2_MAX</sub>	3,50E-04	H
Average Inductance Value	L <sub>1_AVG</sub> , L <sub>2_AVG</sub>	2,25E-04	H
Inductor RMS Current	I <sub>L1_RMS</sub> , I <sub>L2_RMS</sub>	13,223	A
Output Capacitance Calculated Based on Holdup Time	C <sub>OUT</sub>	1,22E-03	F
Output Capacitance Selected	C <sub>OUT</sub>	1,41E-03	F
Output Ripple Voltage	V <sub>RIPPLE</sub>	13,0	V
Low Frequency Output Capacitor RMS Current	I <sub>COUT_LF</sub>	3,828	A
High Frequency Output Capacitor RMS Current	I <sub>COUT_HF</sub>	6,505	A
Peak Diode and FET Current	I <sub>PEAK</sub>	32,478	A
FET RMS Current (Q1 and Q2)	I <sub>DS</sub>	10,671	A
Diode Average Current (D1 and D2)	I <sub>D</sub>	2,436	A
Calculated Current Sense Transformer Turns Ratio	N <sub>CT</sub> =N <sub>S</sub> /N <sub>P</sub>	325	

Enter Current Sense Transformer Turns Ratio	$N_{CT} = N_S / N_P$	100	
Minimum Magnetizing Inductance of the Current Sense Transformer	$L_M$	9,85E-03	H
Select Current Sense Peak Voltage	$V_S$	3,70	V
Calculated Current Sense Resistor	$R_{SA} = R_{SB}$	10,3	ohm
Select Standard Current Sense Resistor	$R_{SA} = R_{SB}$	10	ohm
CalculatedReset Resistor	$R_R$	3,E+02	ohm
Select a Standard Value	$R_R$	3,30E+02	ohm
Calculated Maximum DR Reverse Voltage	$V_R$	107	V
Current Sense Offset Desired	$V_{OFF}$	0,20	V
Program Offset Bias Current to be added to $R_s$	$R_{OA} = R_{OB}$	5,90E+02	ohm
Select a Standard Value	$R_{OA} = R_{OB}$	5,90E+02	ohm
Program Current Sense PWM Ramp Resistor	$R_{TA} = R_{TB}$	7,31E+02	ohm
Select Standard Values	$R_{TA} = R_{TB}$	7,30E+02	ohm
Program Current Sense PWM Ramp Timing Capacitor	$C_{TA} = C_{TB}$	8,33E-07	F
Select Standard Values	$C_{TA} = C_{TB}$	1,00E-06	F
Select High Side Resistor on Peak Current Limit Divider	$R_{PK1}$	3,65E+03	ohm
Calculated Low Side Resistor on Peak Current Limit Divider	$R_{PK2}$	5,87E+03	ohm
Select Low Side Resistor on Peak Current Limit Divider	$R_{PK2}$	5,87E+03	ohm
Calculated Timing Resistor	$R_{RT}$	1,88E+05	ohm
Select Timing Resistor	$R_{RT}$	2,00E+05	ohm
Calculated Programmable Duty Cycle Limit Resistor	$R_{DMX}$	1,88E+05	ohm
Select Programmable Duty Cycle Limit Resistor	$R_{DMX}$	1,86E+05	ohm
Select High Side Resistor for VSENSE Voltage Divider	$R_A$	3,20E+06	ohm
Calculated Low Side Resistor on VSENSE voltage Divider	$R_B$	2,48E+04	ohm
Select Low Side Resistor on VSENSE voltage Divider	$R_B$	2,49E+04	ohm
Calculated Nominal Over Voltage Trip Point	$V_{OVP}$	412	V
Voltage Divider Gain	H	7,72E-03	
Voltage Amplifier Output Impedance at double $f_{LINE}$	$Z_o$	1,37E+04	ohm
Calculated Pole Capacitance for the Voltage Loop	$C_{PV}$	1,24E-07	F
Select a Standard Value	$C_{PV}$	1,22E-07	F
Calculated Voltage Loop Crossover Frequency	$f_{VC}$	11,6	Hz
Calculated Voltage Loop Zero Compensation Resistor	$R_{ZV}$	1,13E+05	ohm
Select a Standard Value	$R_{ZV}$	1,00E+05	ohm
Calculated Voltage Loop Zero Compensation Capacitor	$C_{ZV}$	1,37E-06	F
Select a Standard Value	$C_{ZV}$	1,22E-06	F
Calculated Current Synthesis Programmable Resistor	$R_{SYN}$	2,70E+05	ohm
Select a Standard Value	$R_{SYN}$	2,83E+05	ohm
Voltage Calculation for Selecting Multiplier Resistor	$V_1$	69,601	V
Voltage Calculation for Selecting Multiplier Resistor	$V_2$	2,359	V
Multiplier Resistor	$R_{IMO}$	1,81E+04	ohm
Select a Standard Value	$R_{IMO}$	1,82E+04	ohm

Current Loop Power Stage Gain at Loop Crossover	$G_{PSC}$	1,724	
Current Loop Zero Resistor	$R_{ZC1}=R_{ZC2}$	5,80E+03	ohm
Select a Standard Value	$R_{ZC1}=R_{ZC2}$	5,80E+03	ohm
Current Loop Zero Capacitor	$C_{ZC1}=C_{ZC2}$	6,86E-09	F
Select a Standard Value	$C_{ZC1}=C_{ZC2}$	6,90E-09	F
Current Loop Pole Capacitor	$C_{PC1}=C_{PC2}$	1,37E-09	F
Select a Standard Value	$C_{PC1}=C_{PC2}$	1,00E-09	F
Calculated Soft Start Capacitor (Be sure $C_{SS} > \text{or } = C_{ZV}$ )	$C_{SS}$	2,2222222E-006	F
Select a Standard Value (Be sure $C_{SS} > \text{or } = C_{ZV}$ )	$C_{SS}$	2,20E-06	F
Program Dither Magnitude Resistor	$R_{RDM}$	#DIV/0!	ohm
Select a Standard Value	$R_{RDM}$	0,00E+00	ohm
Program Dither Rate Capacitor	$C_{CDR}$	#DIV/0!	F
Select a Standard Value	$C_{CDR}$	0,00E+00	F
Disclaimer			

TI assumes no liability for applications assistance or customer product design. Customer is fully responsible for all design decisions and engineering with regard to its products, including decisions relating to application of TI products. By providing technical information, TI does not intend to offer or provide engineering services or advice concerning Customer's design. If Customer desires engineering services, the Customer should rely on its retained employees and consultants and/or procure engineering services from a licensed professional engineer (LPE).



Voltage Loop and Current Loop Axis Can be Adjusted Based on Individual Need

