 


# UCC28780 Debug Guide and Common Issues

# Contents

- **How to power up your board**
- **How to distinguish the protection**
- **Common issues and solutions**
- **Optimize your design**


# Before Power on : Check soldering



Specially for QFN package

- Use multi-meter “Diode” setting.
- “Red” probe → GND, “Black” probe → each Pin of IC.
- Presents a 0.5~0.7V voltage = normal.
- If not , Check soldering of pin.

 
# Before Power on : Setting Brown-in voltage



- $i_{VSL(Brown-in)}$  is start-up threshold current at VS pin
- $N_{AUX}$  and  $N_P$  are the turns of AUX and Pri. windings
- $V_{bulk(Brown-in)}$  is DC voltage on bulk at start-up
- 75Vac /106Vdc is preferred start point of Brown-in
- Large different from preferred will affect OPP curve
- Calculate  $R_{VS1}$  , then program it

$$i_{VSL(Brown-in)} = 353\mu A \approx \frac{(N_{AUX} / N_P) V_{bulk(Brown-in)}}{R_{VS1}}$$

 
# Low AC\_IN Power on : Check VDD HV start



CH1 (Yellow) : VDD

- AC input voltage = 20Vac or little more
- Capture the VDD voltage
- VDD presents a Triangle wave
- The peak ~ 17.5V , valley ~9.8V , HV start normal
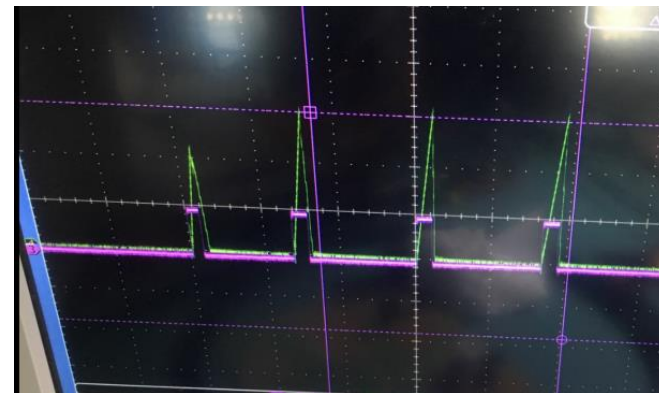
# Low AC\_IN Power on : Check low-side pulse



- Gradually increase AC input to a little lower than Brown-in
- Zoom in to low side driver pulse
- CH3 Purple : Low-side driver ,CH4 Green : VDD

- 4 pulses is normal
- CH3 Purple : Low-side driver
- CH4 Green : XFMR Ipri.

**If above steps are normal, you can power up your board to next step**

# Contents

- How to power up your board
- How to distinguish the protections
- Common issues and solutions
- Optimize your design


# Protection Features of UCC28780

Protection	Sensing	Threshold	Delay to Action	Action
VDD UVLO	V <sub>DD</sub>	V <sub>DD(on)</sub> =17.5V V <sub>DD(off)</sub> =10.5V	no	V <sub>DD</sub> restart
Over Power protection (OPP)	CS	V <sub>CST</sub> ≥V <sub>CST(OPP)</sub>	<b>1</b> 160ms	1.44s restart
Peak current limit (PCL)	CS	V <sub>CST(max)</sub> =0.8V	160ms	1.44s restart
Over current protection (OCP)	CS	V <sub>CST</sub> ≥1.2V	3 PWML pulses	1.44s restart
Short circuit protection (SCP)	CS, VS, VDD	(1) V <sub>DD</sub> =V <sub>DD(off)</sub> & V <sub>CS</sub> ≥V <sub>CS(OPP)</sub> (2) V <sub>DD</sub> =V <sub>DD(off)</sub> & VS≤0.6V	≤160ms	<b>2</b> 1.44s restart
Over voltage protection (OVP)	VS	VS≥4.6V	3 PWML pulses	1.44s restart
Brown-in detection	VS	I <sub>VSL</sub> <353μA	3 PWML pulses	V <sub>DD</sub> restart
Brown-out detection	VS	I <sub>VSL</sub> <320μA	60ms	V <sub>DD</sub> restart
Over temp. protection (OTP)	NTC	R <sub>NTC</sub> ≤10kΩ	3 PWML pulses	V <sub>DD</sub> restart until R <sub>NTC</sub> ≥22.5kΩ
Thermal shutdown	Die	T <sub>die</sub> >125°C	3 PWML pulses	V <sub>DD</sub> restart

**Note : Specially check “Delay to Action” and “Action” in your waveform  
To identify which protection occur**




# How to identify “Delay to Action”

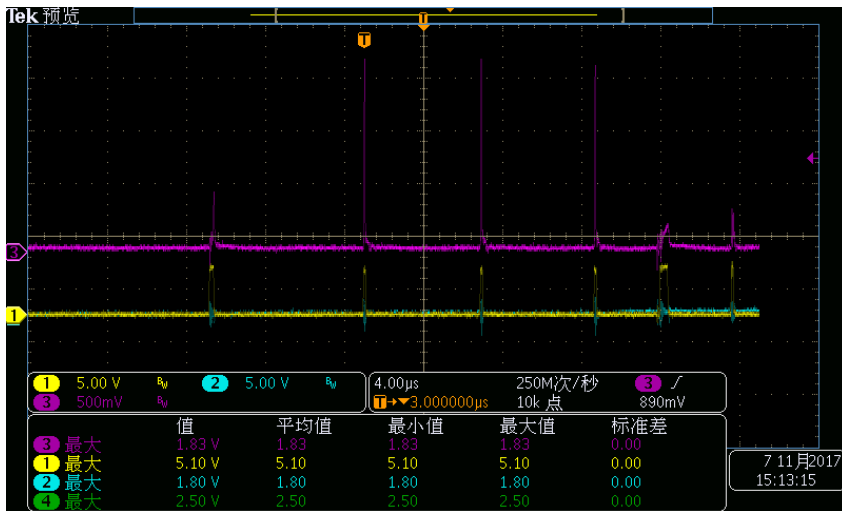


CH3 (purple): Vcs  
CH1 (Yellow): PWML

Ex: 3 pulse trigger OCP 1.2V “Delay to Action”

# How to identify “Action”

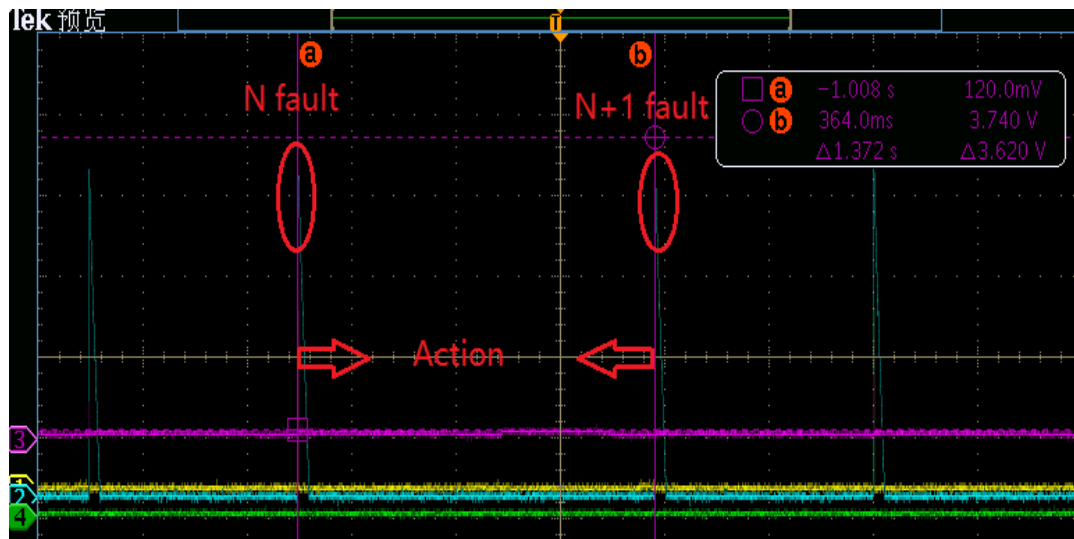

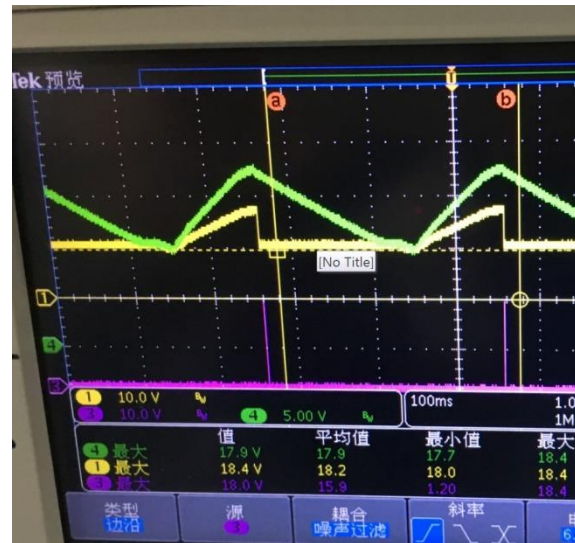The interval time of adjacent fault is “Action”  
Ex: 1.44s restart of OVP , CH2: Vout



CH4 Green VDD hiccup  
Ex: VDD restart


# Contents

- How to power up your board
- How to distinguish the protections
- **Common issues and solutions**
- Optimize your design

## VDD UVLO: VDD is clamped too low to start

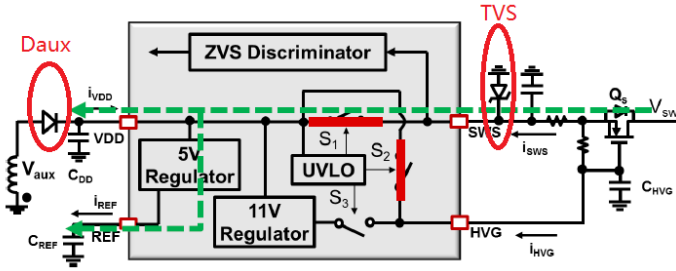
## ➤ HV Startup Mode

- S1 and S2 on, S3 off,
- S1 limits the charge current  
tens or hundreds  $\mu\text{A}$



➤ **Normal VDD start up waveform**

 - $V_{DD(on)} = 17.5V$ ,
- $V_{REF} = 5V$ ,




## ➤ Common issues

- VDD clamped to such as 9V, ---Potential reason is AUX winding rectify diode reverse current exceed S1 charge current tens or hundreds uA . **Solution:** Replace Daux and check reverse current.
- VDD be clamped to such as 15V, ---Potential reason is the TVS on SWS pin used low voltage TVS, **Solution:** suggest use 18V~20V TVS.

# VDD UVLO: AUX didn't take over VDD supply
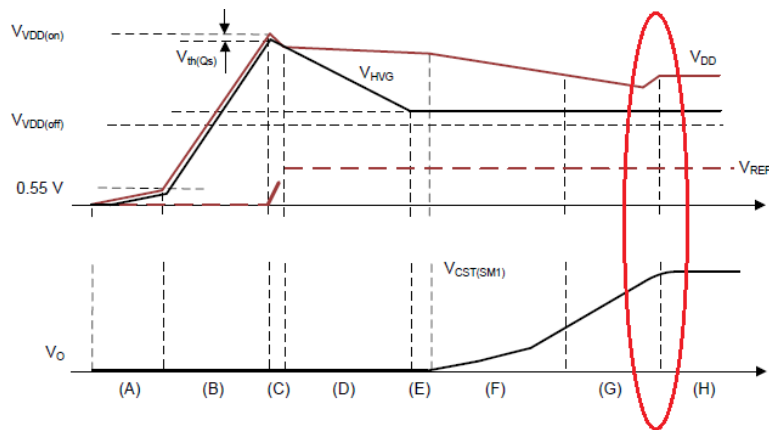
## ➤ VDD drop to UVLO

- After  $V_o$  settle, the auxiliary winding should take Over VDD supply. →
- If not ,VDD will drop to UVLO.



## ➤ Common issues

- Improper XFMR Turn ratio of  $N_s$  and  $N_{aux}$ , Specially in PD design – Large  $V_o$  range  
ex:  $N_s:N_{aux} = 4:3$ , When  $V_o=20V$ ,  $VDD=15V$  –ok, while  $V_o=9V$ ,  $VDD=6.75V$ , UVLO.
- If there are LDO or two AUX windings for VDD , check if normally operation .


# OCP: XFMR wrong polarity

## ➤ Identify if it's OCP



- "Delay to Action" -- 3 PWML pulses
- "Action" -- 1.44s restart.
- Zoom in one pulse, peak value > 1.2V
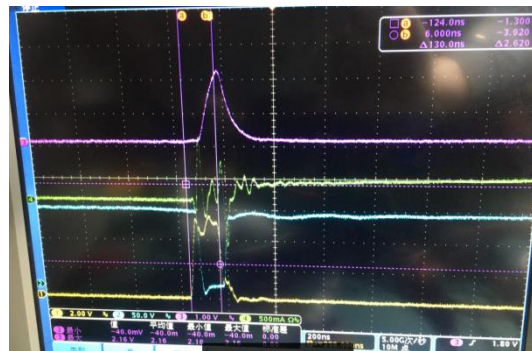
## ➤ Common issue

- Wrong polarity of XFMR winding,
- Wrong assembly or XFMR design,



Purple : Vcs, Yellow : PWML

  



# OCP: Shoot through of High&Low side FETs

## ➤ Shoot through at Burst mode


- PWML on, PWMH off --UCC28780 .
- Oscillation found at isolator driver side.
- The oscillation voltage trigger high Side GaN turn on
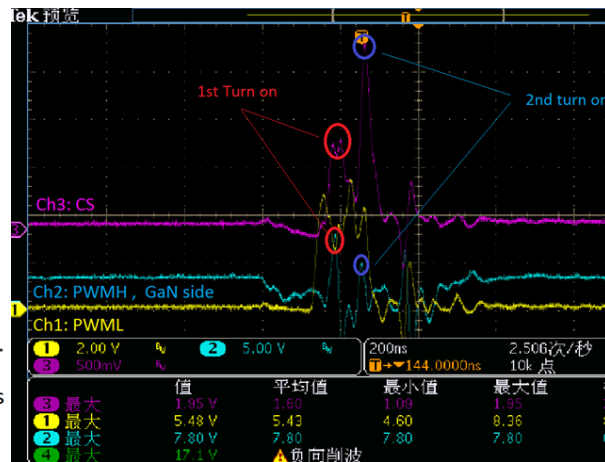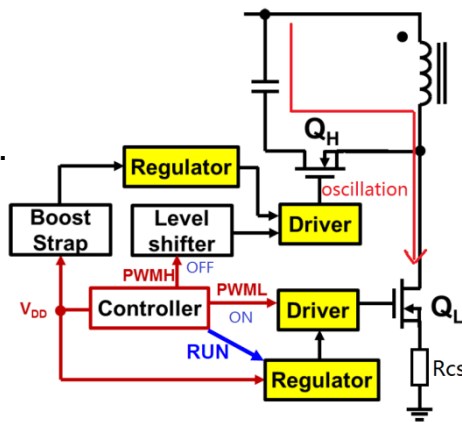
## ➤ Possible reason and solution

- Large switching noise at burst mode,
- Bad PCB layout ---large high side driver loop,



 
**Solution:** Add RC filter to suppress the oscillation



# OVP: Bad loop compensation and setting
 
## ➤ Identify if it's OVP


- “Delay to Action” -- 3 PWML pulses
- “Action” –1.44s restart.
- Capture Vout, Check if > Setting value



$$V_{VS(OVP)} = 4.5V \approx \frac{(N_{AUX} / N_S) V_{o(OVP)} \cdot R_{VS2}}{R_{VS1} + R_{VS2}}$$
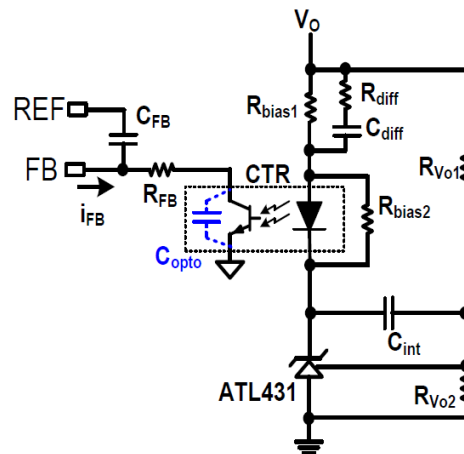
## ➤ Possible reasons and solution

- Wrong setting  $V_{OVP}$ , --Correct it
- 431 not working, --Rbias2 limits required Min.  $I_{KA}$   
Decrease Rbias2
- Too large  $R_{FB}$ . – suggest 20K ~ 39K.
- Too small CTR of opto-coupler. – Use better
- Other components failure lead to open-loop.





# Other protection: Open and Short of Pins



PROTECTION	SENSING	CONDITION	DELAY TO ACTION	ACTION
CS pin short	PWML on-time @ first PWML pulse only	$> 2 \mu\text{s}$ (SET = 5 V)	none	UVLO reset
		$> 2 \mu\text{s}$ (SET = 0 V, $R_{\text{RDM}} \geq 55 \text{ k}\Omega$ )		
		$> 1 \mu\text{s}$ (SET = 0V, $R_{\text{RDM}} < 55 \text{ k}\Omega$ )		
CS pin open	CS voltage	$V_{\text{CS}} > 1.2 \text{ V}$	3 PWML pulses	$t_{\text{FDR}}$ restart (1.5 s)
HVG pin open	HVG voltage @ $\text{UVLO}_{\text{ON}}$	$V_{\text{HVG}} < \text{or } = 12 \text{ V}$ in less than $10 \mu\text{s}$ after $V_{\text{DD}}$ reaches $V_{\text{DD(on)}}$	none	UVLO reset
HVG pin high	HVG voltage	$V_{\text{HVG}} > 14 \text{ V}$	none	UVLO reset
RDM pin short	RDM current @ $\text{UVLO}_{\text{ON}}$	$V_{\text{RDM}} = 0 \text{ V}$ , self-limited $i_{\text{RDM}}$	none	UVLO reset
RDM pin open	RDM current @ $\text{UVLO}_{\text{ON}}$	RDM = Open	none	UVLO reset
RTZ pin short	RDM current @ $\text{UVLO}_{\text{ON}}$	$V_{\text{RTZ}} = 0 \text{ V}$ , self-limited $i_{\text{RTZ}}$	none	UVLO reset
RTZ pin open	RDM current @ $\text{UVLO}_{\text{ON}}$	RTZ = Open	none	UVLO reset

**If find only 1 pulse of PWML or no pulse , the possible reason is one critical Pin was open or short**
  
# Burst mode unstable (Passive compensation)

➤ What is “unstable” ?



- In SBP,LPM,ABM mode , The count of pulse In a packet is from 2 to 9 as the load increase.
- Inconsistent pulse will lead to large ripple And audible noise



➤ Solution

- Make  $i_{FB}$  in phase with  $V_o$  “burst” ripple
- Proposed debug start point of parameters as shown in right table

  Specially add  $R_{diff}$  and  $C_{diff}$



Location	Proposed
Rbias1	11K
Rdiff	510ohm
Cdiff	4.7nF
R <sub>FB</sub>	22.1K
C <sub>FB</sub>	100pF
Cint	10nF

# Burst mode unstable (Active Ripple Compen.)

## ➤ What application should use ARC ?




- When Output capacitor  $C_{o1}$  is polymer, and No  $L_o$  and  $C_{o2}$
- With CLC filter on output -- 2<sup>nd</sup>-order filter (Secondary Resonance  $C_{o1}(\text{ceramic}) < C_{o2}$ )

## ➤ Solution :


- Active ripple compensation ( $R_{COMP}$  can be decreased but not less than 510K )



Lower ESR

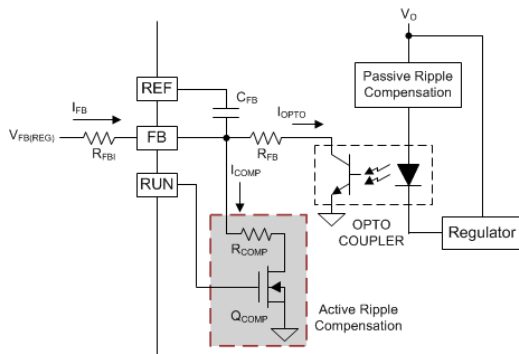  

 $Q_{COMP}$ : 2N7002;  $R_{COMP}$ =1~2M $\Omega$




# Contents

- How to power up your board
- How to distinguish the protections
- Common issues and solutions
- **Optimize your design**
 
# Audible noise reduction: ABM → AAM

Nsw higher than 9 for a smoother mode transition





## Solutions for white noise reduction:

- Transformer dip varnishing
- Lower peak magnetizing current – Minor decrease  $V_{BUR}$
- Other source of noise – MLCC capacitors of Cclamp or Sec.\_Reson. Caps
  - \* More quantity caps parallel to reduce noise
- Adjust ABM loop more stability– narrow  $i_{FB}$  range (enlarge Rbias1 page 18)
 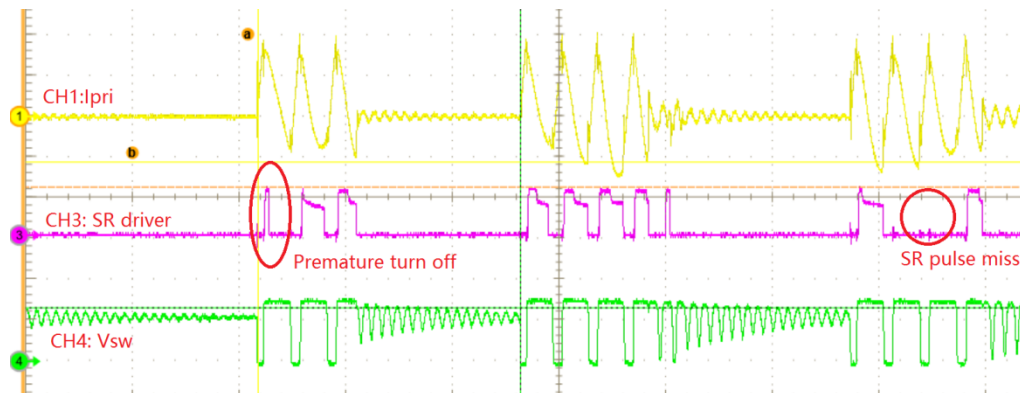
# SR driver missing pulse in burst

**Reason:** The resonance current touch demagnetizing current lead to SR current natural to zero



## Solutions :

- Higher peak magnetizing current – Increase  $V_{BUR}$
- Increase value of C<sub>clamp</sub> and decrease Sec. Resonance cap. -Co1
- Enlarge the resonant current “dip”
- \* Select smaller C<sub>oss</sub> nonlinearity of high side MOSFET --IPx60R385CP
- \* Select higher C<sub>oss</sub> nonlinearity of SR MOSFET
- \* Smaller L<sub>k</sub> of transformer

# Efficiency improve: (Specially for Si-FET)

## ➤ Transformer design considerations :



- Core material : TDK-N49, Ferroxcube-3F36
- Winding wire : Litz wire
- Delta B between 0.15~0.2T, < 0.1T more better

## ➤ MOSFET selection:

- High side : Smaller Coss, large Rdson is acceptable (Infineon CP series)
- Low side : Large Coss, smaller Rdson is prefer. (Infineon C7 series)

 
 
## ➤ RTZ resistor setting:

- High line input ,Increase RTZ until find Vsw ring back , then decrease a little



  
# Secondary Resonance (Specially for PD design)

Condition:  $V_{bulk}=325V$ ,  $V_o=5V$ ,  $I_o=3A$ ,  $C_{clamp}=0.44\mu F$



$I_o$  discharging  $C_{o1}$  every cycle allows resonance continuing even with long demagnetization time

 - Lower RMS loss on pri + sec side !!
- Better SR operation in AAM and ABM



$$L_{damp}=680nH, R_{damp}=0.68\Omega$$

**Serial damping is needed**

## ➤ Benefits of Secondary resonance

- Lowers conduction loss on primary side , results higher full load efficiency
- SR ZCS over wide output range, low turn off switching, also lower EMI
- Initial resonance current less than magnetizing current, easy SR operation
- Better for ripple




# “Tiny load ” efficiency improve

## ➤ Increasing Peak current

1. Reducing sensing resistor

$$P = \frac{1}{2} L_m i_{m(+)}^2 f_{sw}$$

2. Active voltage divider on CS Pin

 

## 1. Effect on 20V/0.25W at $V_{bulk}=325V$

Rcs	Pin	Eff	f <sub>BUR</sub>	f <sub>sw</sub>	I <sub>m(+)</sub>	OPP	P <sub>O(OPP)</sub>
0.225	0.419W	59%	5.2K	686K	0.62A	120%	54W
0.192	0.406W	61%	4.4K	660K	0.68A	145%	65W

Gain 2% efficiency results in sacrificing OPP level

## 2-1. Effect on 20V/0.25W at $V_{bulk}=325V$

R <sub>SBP</sub>	Pin	Eff	f <sub>BUR</sub>	f <sub>sw</sub>	I <sub>m(+)</sub>
Open	0.419W	59%	5.2K	686K	0.62A
1.6K	0.385W	64%	3.3K	595K	0.94A

Gain 5% efficiency with same OPP level

## 2-2. Effect on 20V/0W at $V_{bulk}=325V$

R <sub>SBP</sub>	Pin	f <sub>BUR</sub>	f <sub>sw</sub>	I <sub>m(+)</sub>
Open	55mW	790Hz	712K	0.54A
1.6K	46mW	430Hz	619K	0.74A


Gain 9mW standby power with same OPP level

# PD design considerations
 
## ➤ Balance 5V noise and 20V average efficiency

- Lower  $V_O$  results in lower  $f_{SW}$  operation
- $N_{SW}$  adjusts under lower  $f_{SW}$  case,  $f_{BUR}$  variation is larger
- Larger  $f_{BUR}$  variation force ABM loop performing different  $N_{SW}$  Among adjacent burst packets –maybe lead to audible noise

$$f_{BUR} = \frac{I_O}{I_{O(BUR)}} \left[ \frac{f_{SW}}{N_{SW}} \right]$$




# PD design considerations

## ➤ Solution (Balance 5V noise and 20V average efficiency )

- $V_o$  Feedforward Resistor to BUR Pin

$V_o$	$V_{BUR}$
20V	1.04V
5V	0.842V

 


Reducing  $V_{BUR}$  at lower  $V_{out}$  mitigates audible noise but keeping high  $V_{out}$  average effi.

## ➤ Another solution for mitigates 5V noise

- Narrow down  $\Delta I_{FB}$  (Increase  $R_{BIAS1}$ , Decrease  $C_{DIFF}$  )

$$\Delta I_{FB} = K_{RIPPLE} \times \Delta V_{O(ABM)} \approx 10 \mu A$$



$$K_{RIPPLE} \equiv \left. \frac{I_{FB}(s)}{V_o(s)} \right|_{20kHz < f < 40kHz} \approx \frac{CTR}{R_{BIAS1}} \frac{\omega_{OPTO}}{\omega_{Z1}} = \frac{CTR}{R_{BIAS1}} \frac{(R_{DIFF} + R_{BIAS1}) C_{DIFF}}{(R_{FB} + R_{FBI}) C_{OPTO}}$$

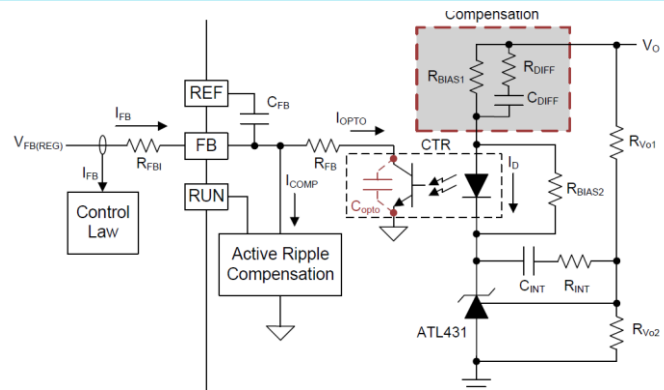


# Large Vout AC ripple improvement
  
## ➤ Choose appropriate optocoupler


- For lower standby power, UCC28780 iFB current designed to  $<0.1\text{mA}$
- The optocoupler with smaller iF current maybe have Lower CTR , Or poor performance as temperature variation .
- Lead to lower low frequency gain to suppress the AC ripple .



Not recommended

 

Proposed (5mm Creepage)

 

Proposed (8mm Creepage)



© Copyright 2018 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)