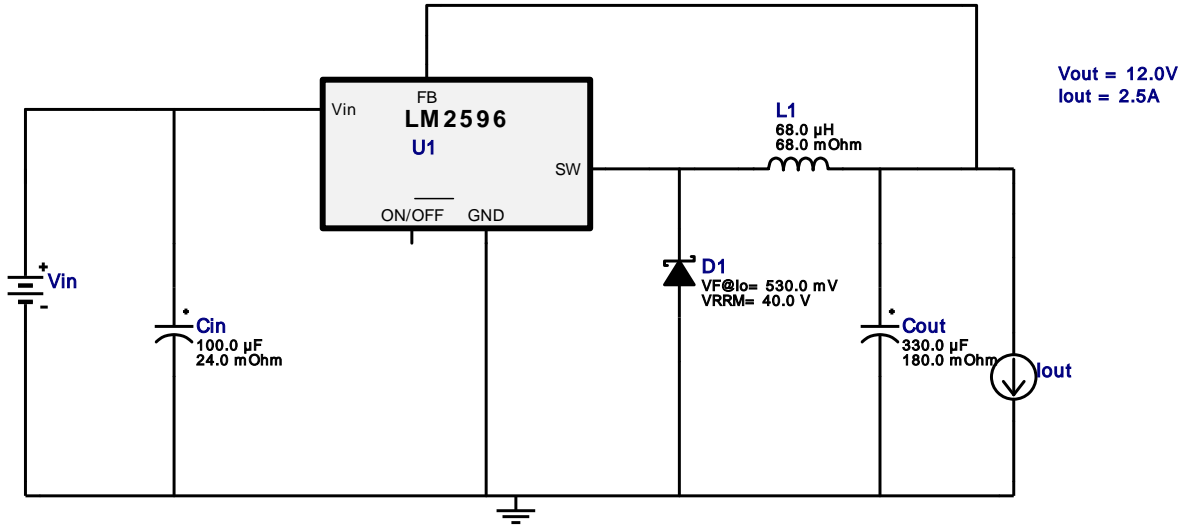


VinMin = 15.0V
 VinMax = 18.0V
 Vout = 12.0V
 Iout = 2.5A

Device = LM2596T-12/NOPB
 Topology = Buck
 Created = 2024-03-19 15:48:53.811
 BOM Cost = \$6.28
 BOM Count = 6
 Total Pd = 3.45W


WEBENCH[®] Design Report


Design : 660 LM2596T-12/NOPB
 LM2596T-12/NOPB 15V-18V to 12.00V @ 2.5A









Electrical BOM







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cf	Samsung Electro-Mechanics	CL21C332JBFNNNE Series= C0G/NP0	Cap= 3.3 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.04	0805 7 mm ²
Cin	Panasonic	25SVPF100M Series= SVPF	Cap= 100.0 uF ESR= 24.0 mOhm VDC= 25.0 V IRMS= 3.2 A	1	\$0.66	CAPSMT_62_E7 106 mm ²
Cout	Chemi-Con	EMVH630GDA331MLH0S Series= MVH	Cap= 330.0 uF ESR= 180.0 mOhm VDC= 63.0 V IRMS= 820.0 mA	1	\$2.53	CAPSMT_62_LH0 361 mm ²
D1	Vishay-Semiconductor	SL04-GS18	VF@Io= 530.0 mV VRRM= 40.0 V	1	\$0.06	DO-219AB 13 mm ²
L1	Coilcraft	MSS1210-683MEB	L= 68.0 µH 68.0 mOhm	1	\$0.81	MSS1210 204 mm ²






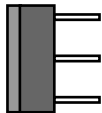
Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	LM2596T-12/NOPB	Switcher	1	\$2.18	 TA05F 127 mm ²

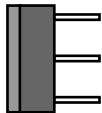

TA05F 127 mm²

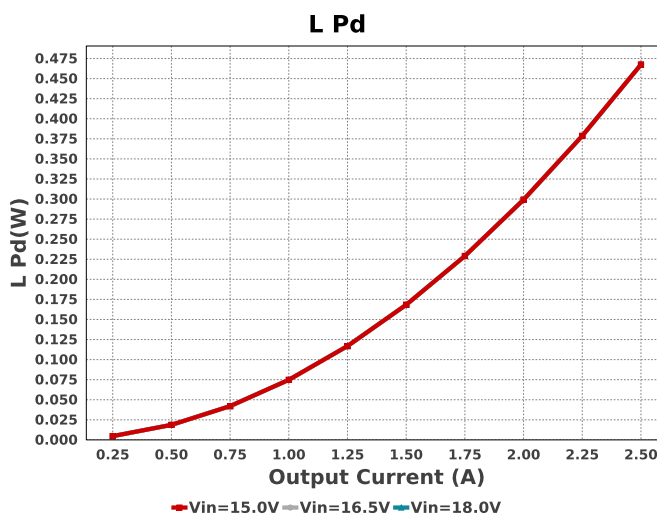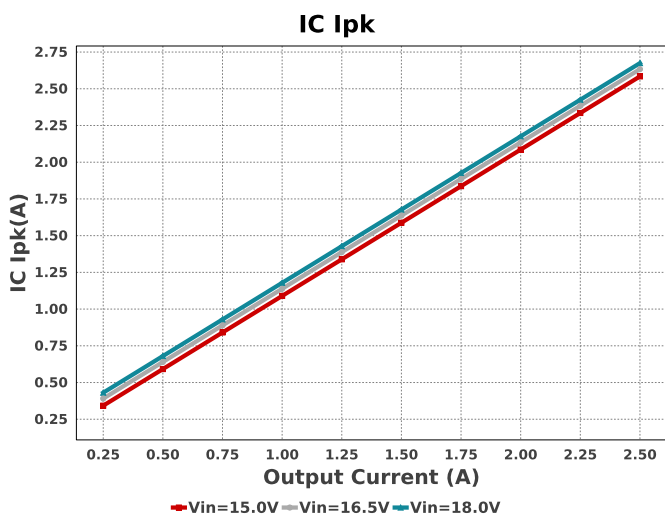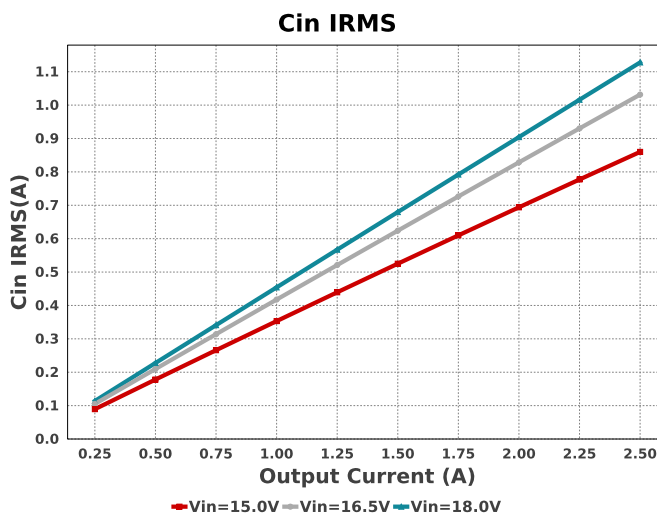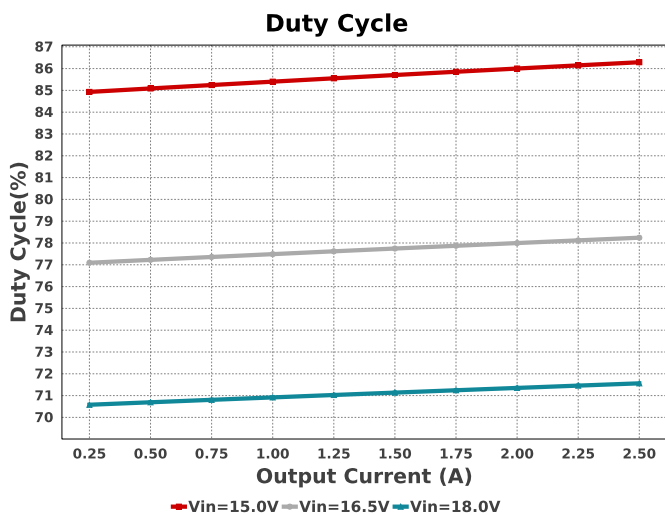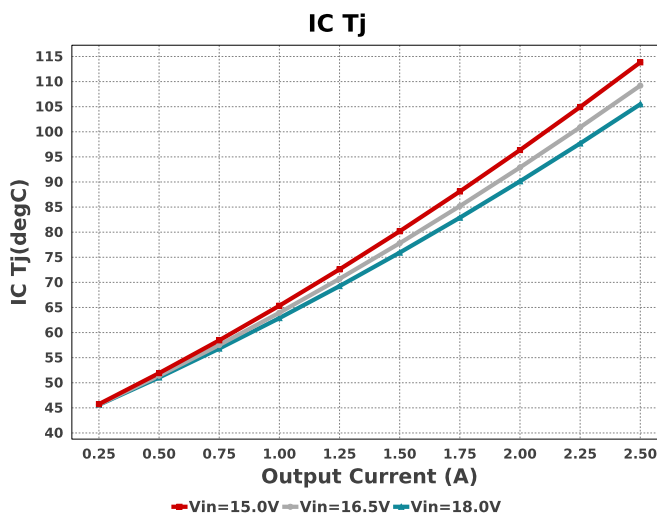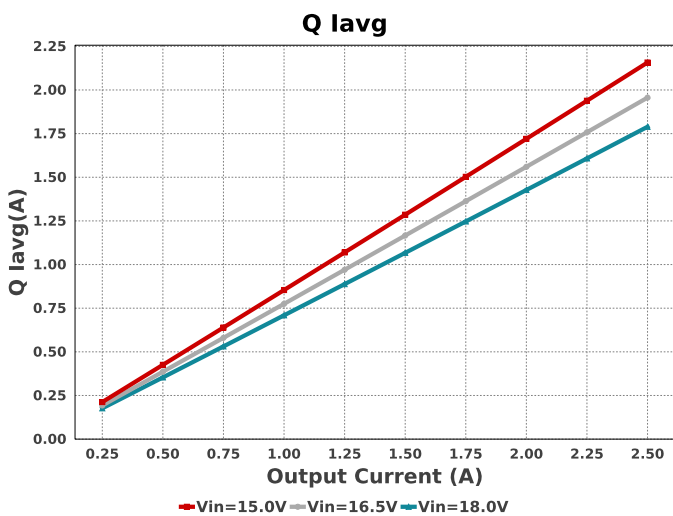

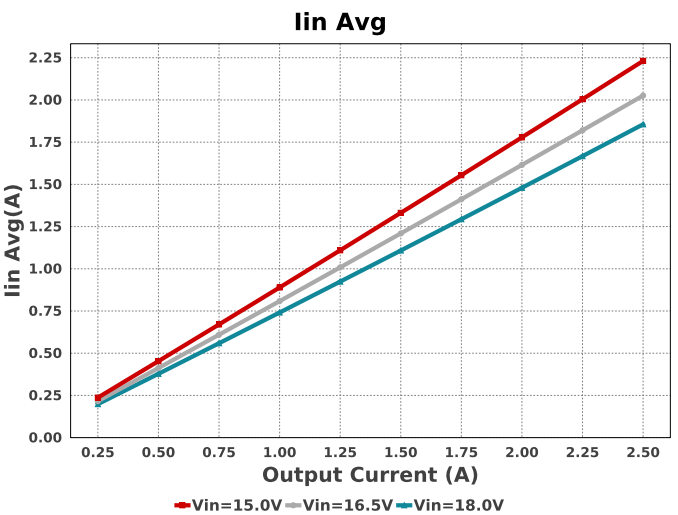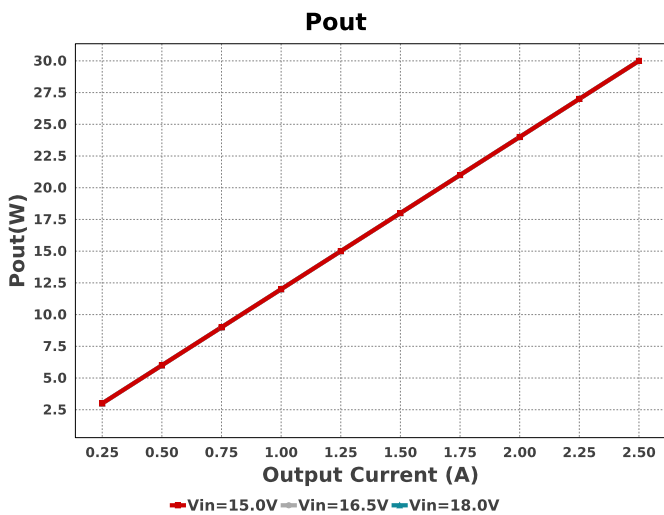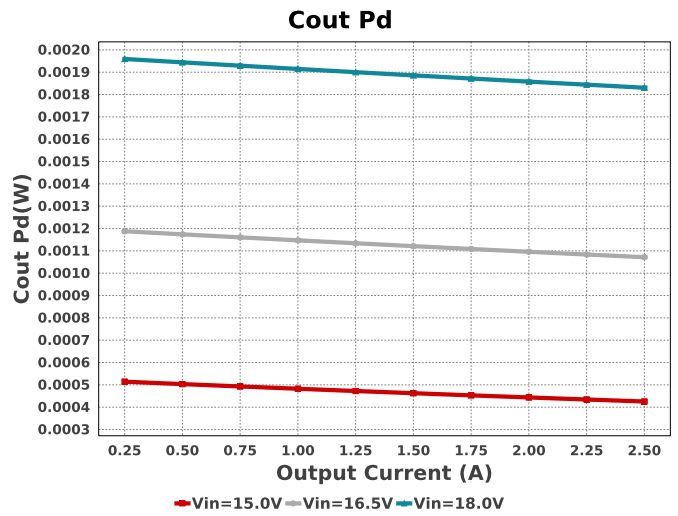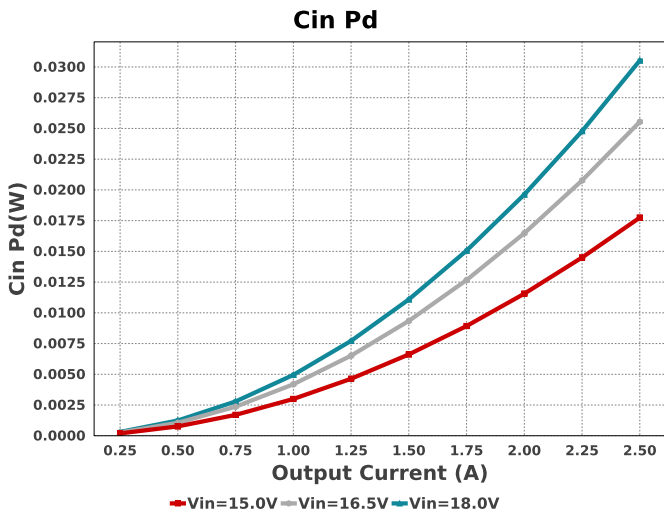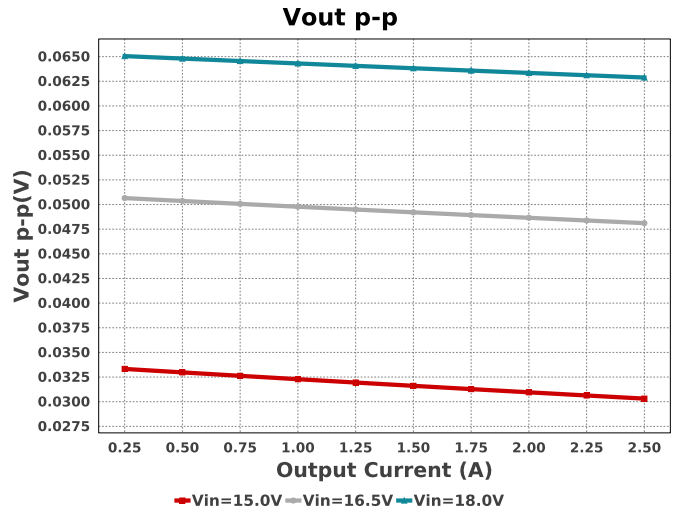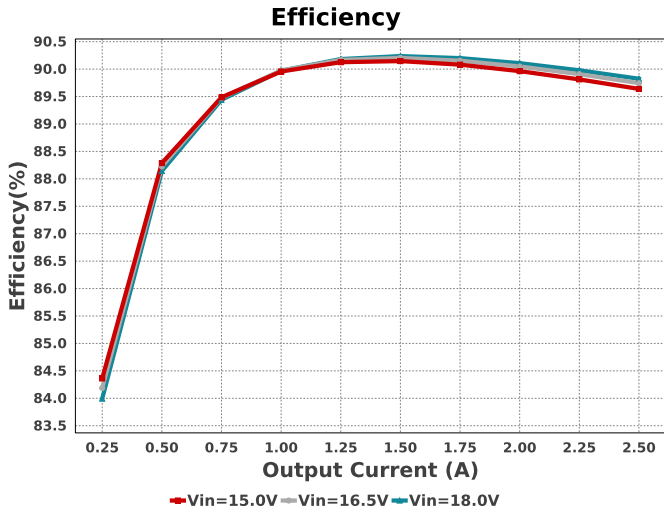

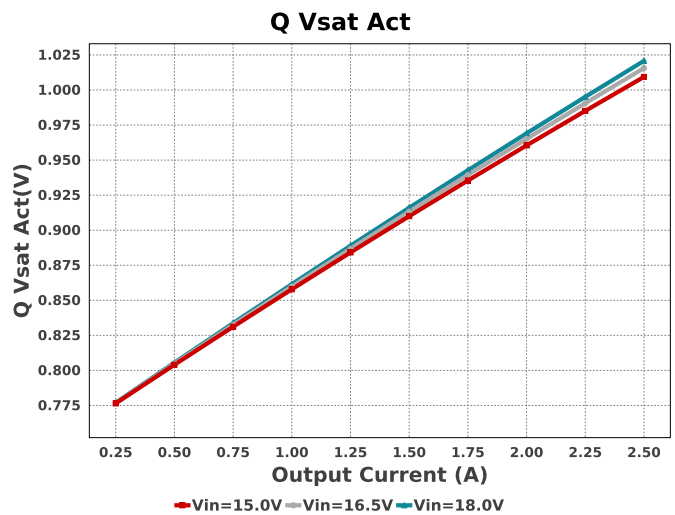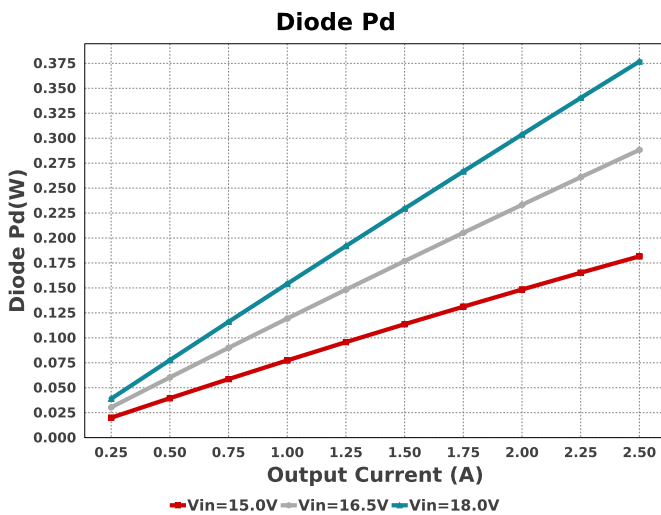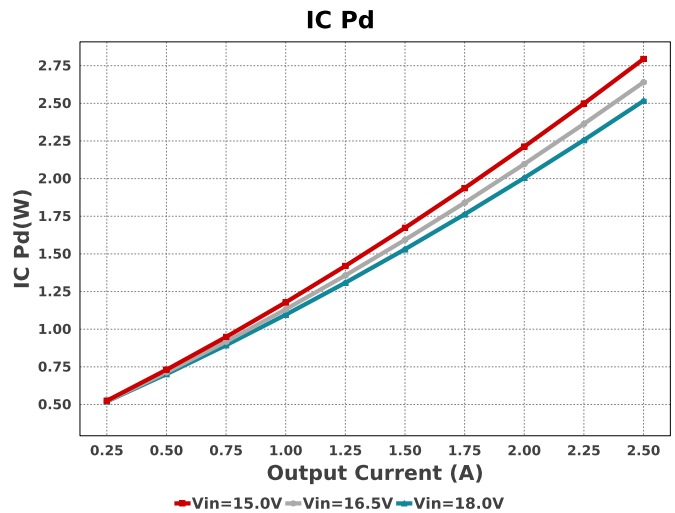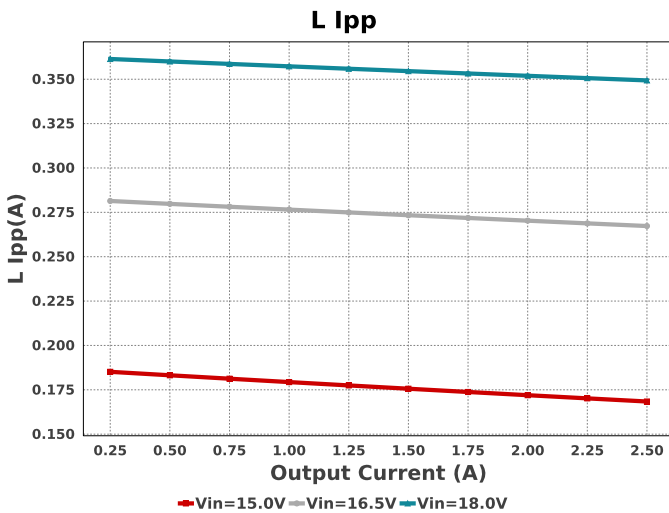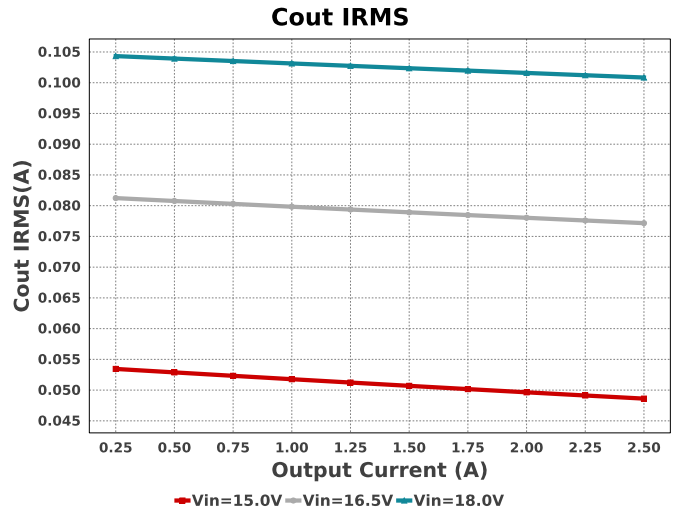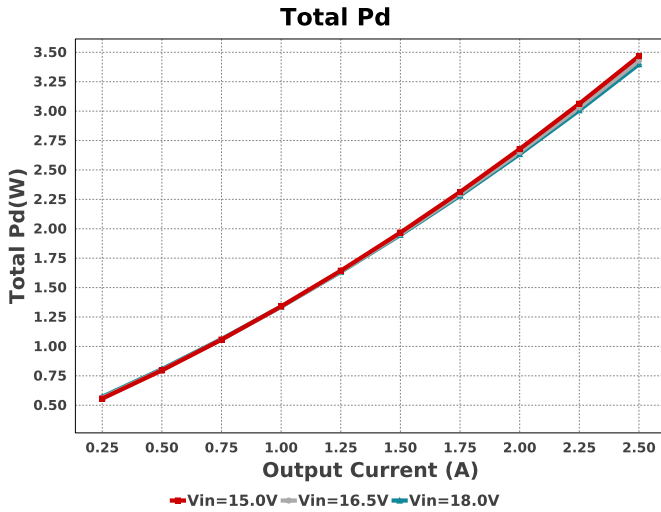

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.128 A	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	30.526 mW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	100.846 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	1.831 mW	Capacitor	Output capacitor power dissipation
5.	Diode Pd	376.8 mW	Diode	Diode power dissipation
6.	IC Ipk	2.675 A	IC	Peak switch current in IC
7.	IC Pd	2.516 W	IC	IC power dissipation
8.	IC Tj	105.478 degC	IC	IC junction temperature
9.	IC Tolerance	0.0 V	IC	IC Feedback Tolerance
10.	ICThetaJA	30.0 degC/W	IC	IC junction-to-ambient thermal resistance
11.	Iin Avg	1.858 A	IC	Average input current

#	Name	Value	Category	Description
12.	L Ipp	349.34 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	467.5 mW	Inductor	Inductor power dissipation
14.	Q Iavg	1.789 A	Mosfet	Q Iavg
15.	Cin Pd	30.526 mW	Power	Input capacitor power dissipation
16.	Cout Pd	1.831 mW	Power	Output capacitor power dissipation
17.	Diode Pd	376.8 mW	Power	Diode power dissipation
18.	IC Pd	2.516 W	Power	IC power dissipation
19.	L Pd	467.5 mW	Power	Inductor power dissipation
20.	Total Pd	3.45 W	Power	Total Power Dissipation
21.	BOM Count	6	System	Total Design BOM count
			Information	
22.	Duty Cycle	71.562 %	System	Duty cycle
			Information	
23.	Efficiency	89.686 %	System	Steady state efficiency
			Information	
24.	FootPrint	819.0 mm ²	System	Total Foot Print Area of BOM components
			Information	
25.	Frequency	150.0 kHz	System	Switching frequency
			Information	
26.	Iout	2.5 A	System	Iout operating point
			Information	
27.	Mode	CCM	System	Conduction Mode
			Information	
28.	Pout	30.0 W	System	Total output power
			Information	
29.	Total BOM	\$6.28	System	Total BOM Cost
			Information	
30.	Vin	18.0 V	System	Vin operating point
			Information	
31.	Vout p-p	62.881 mV	System	Peak-to-peak output ripple voltage
			Information	
32.	Q Vsat Act	1.021 V	Transistor	Q Vsat

Design Inputs

Name	Value	Description
Iout	2.5	Maximum Output Current
VinMax	18.0	Maximum input voltage
VinMin	15.0	Minimum input voltage
Vout	12.0	Output Voltage
base_pn	LM2596	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 15.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

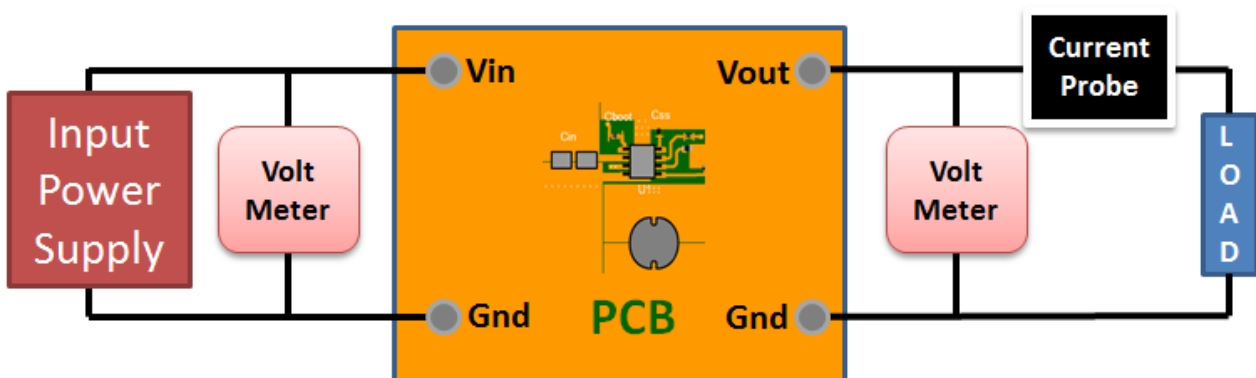

Design Assistance

1. Master key : 40EE3F1E021441DB[v1]
2. **LM2596** Product Folder : <http://www.ti.com/product/LM2596> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.