


What effects LDO PSRR?

Kyle Van Renterghem
Apps & Validation Manager

PSRR


PSRR (Power Supply Rejection Ratio) represents the ability of the LDO to filter input voltage changes. This is critical for low-noise applications.
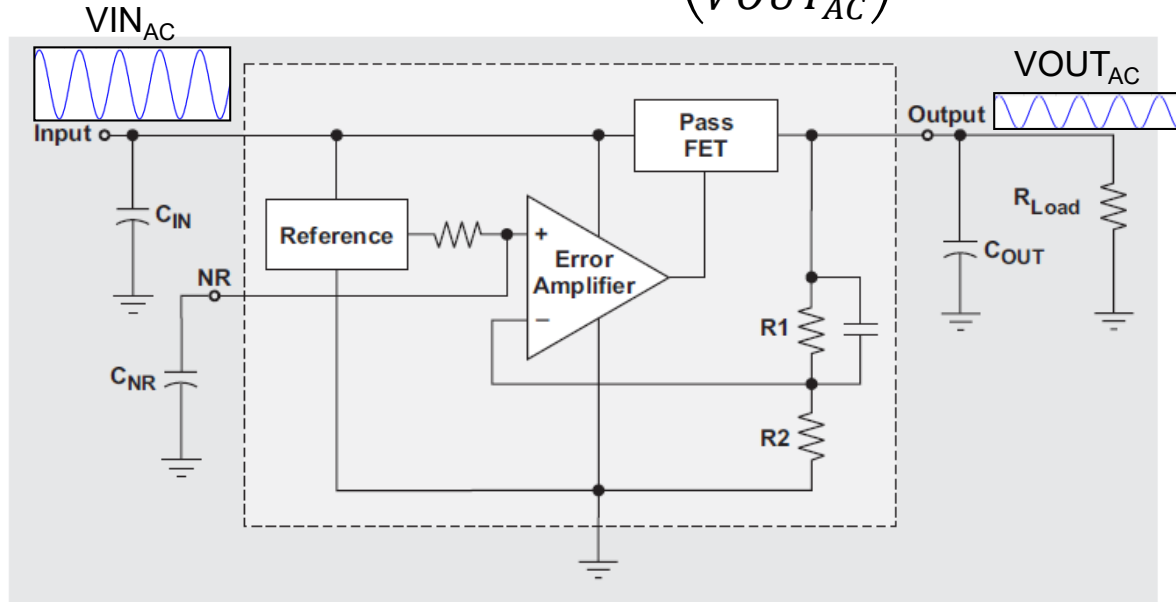
$$PSRR = 20 * \log \left(\frac{VIN_{AC}}{VOUT_{AC}} \right)$$





How PSRR/Noise Relate to the LDO AC Model

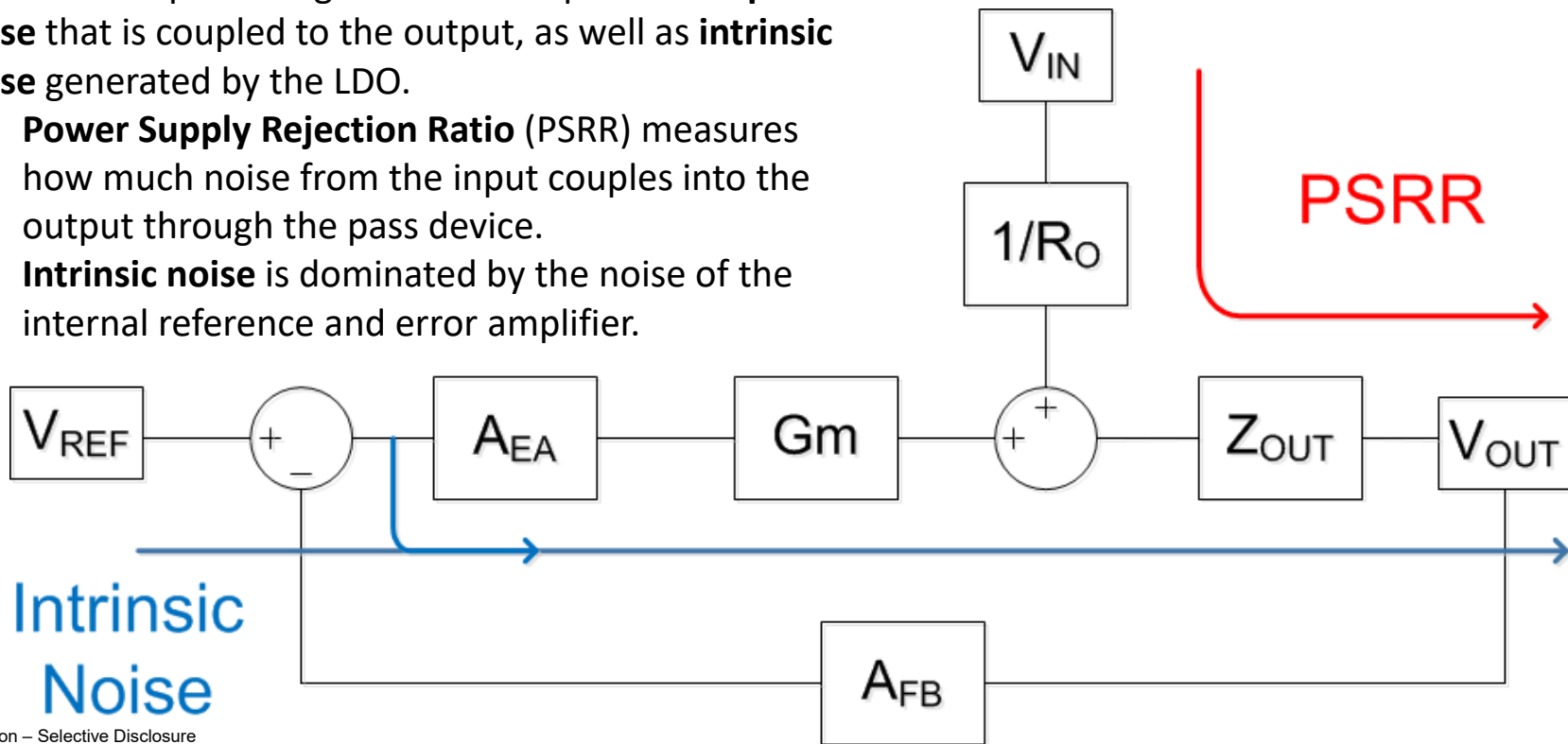- Total LDO output voltage noise is composed of **Input noise** that is coupled to the output, as well as **intrinsic noise** generated by the LDO.
 - **Power Supply Rejection Ratio (PSRR)** measures how much noise from the input couples into the output through the pass device.
 - **Intrinsic noise** is dominated by the noise of the internal reference and error amplifier.



The Importance of LDO PSRR

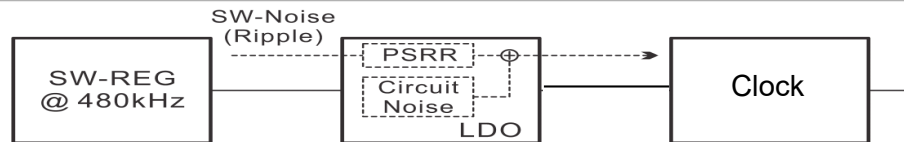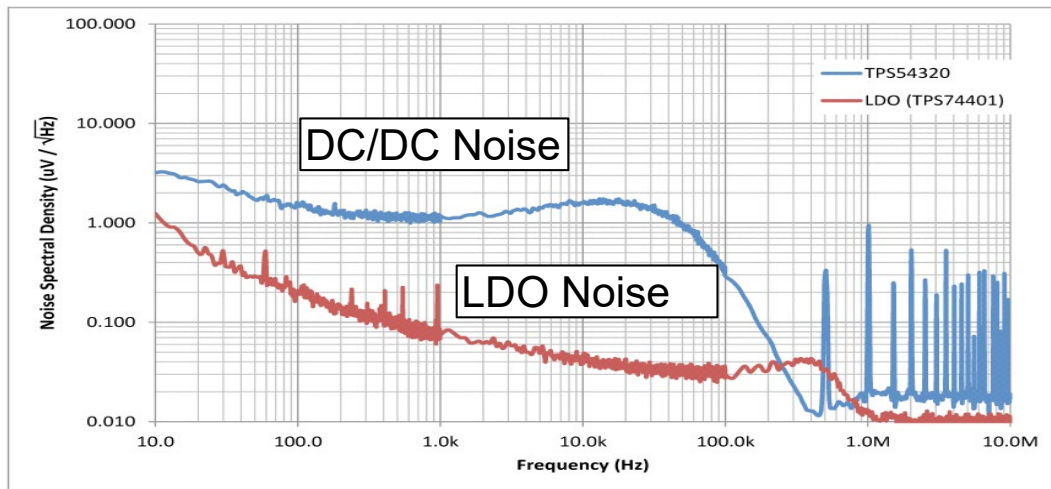- DC/DC (switching) converters are necessary for efficiency, however they are very noisy
 - most clock generators and clocking devices are very sensitive to power supply noise
 - DC/DC converters are commonly followed by an LDO to clean the supply



Typical PSRR Curve

Region 1 is determined by:



- PSRR of the Reference and the effectiveness of the RC filter

Region 2 is determined by:

- Open-Loop Gain of Error Amplifier



Region 3 is determined by:

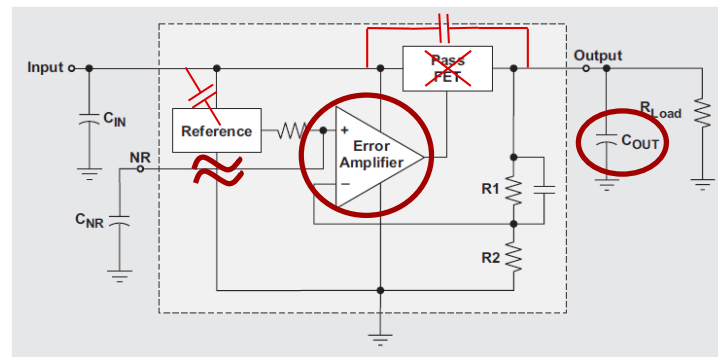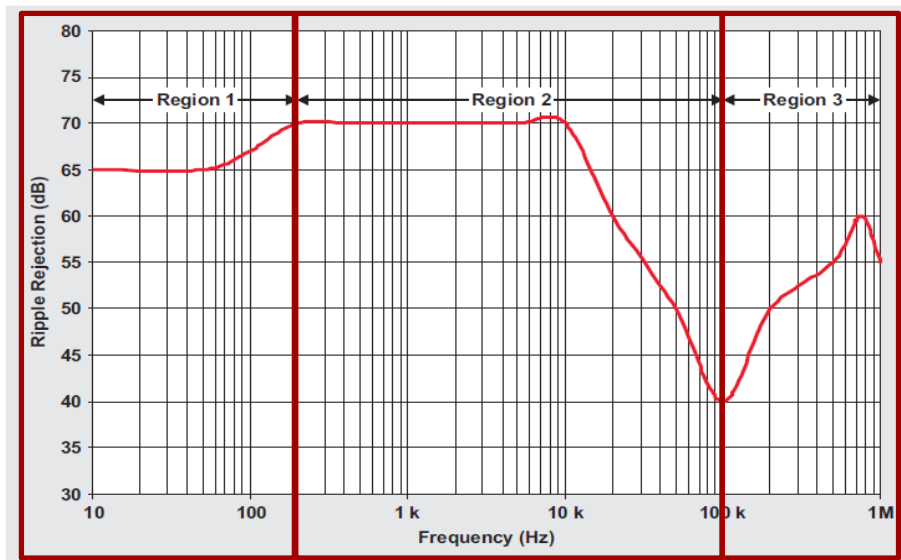- Parasitic capacitance of the FET and the output capacitor (capacitive divider)
 - The smaller the parasitic cap the less the V_{in} is AC coupled to V_{out}
 - The larger C_{out} the more noise is shunted to GND




What Conditions Effect PSRR The Most
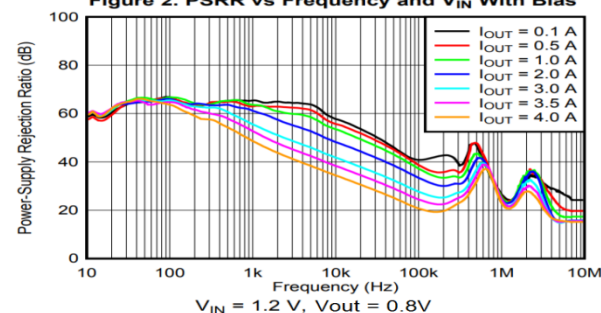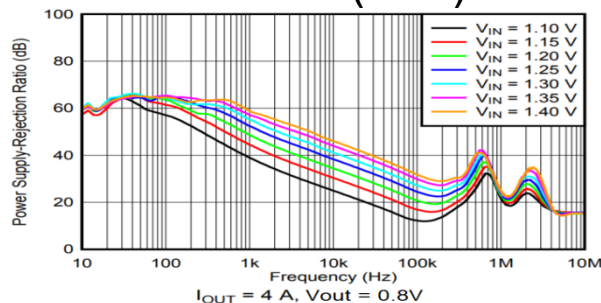
#1 thing that effects PSRR performance is the combo of V_{in}/I_{out} (V_{do})




TI Information – Selective Disclosure

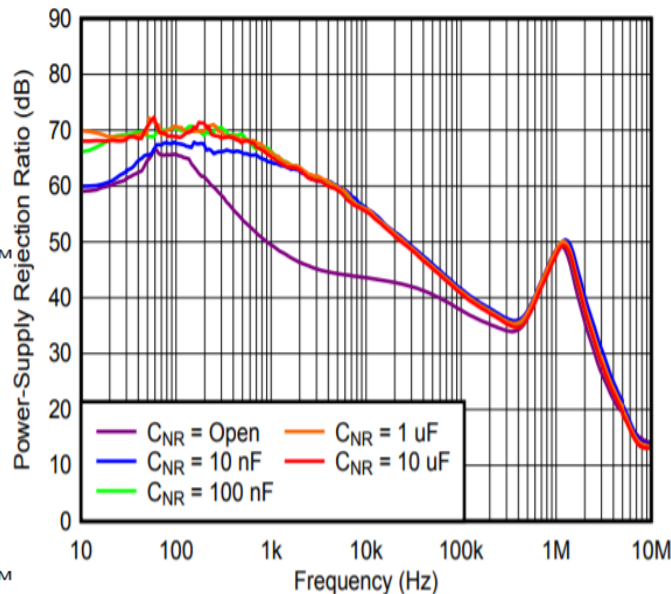The next thing that effects PSRR is the noise reduction capacitor



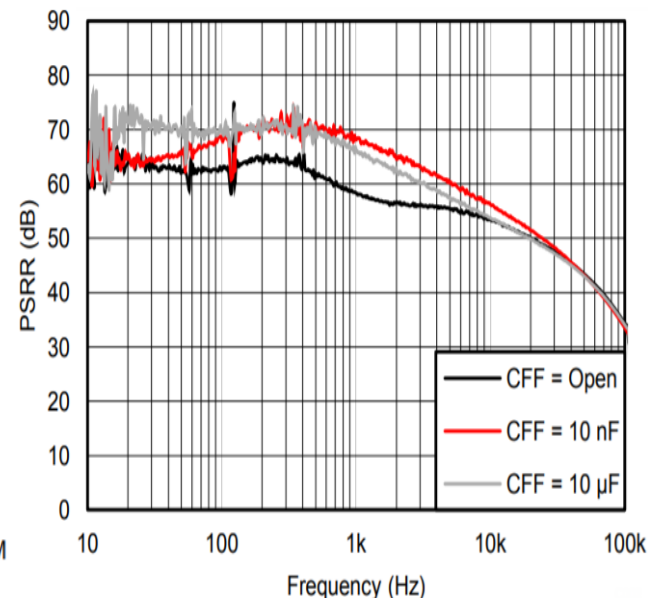The final thing that effects PSRR is the feedforward capacitor



What Conditions Do Not Effect PSRR Much

Number one thing that has almost no effect on PSRR is $V_{bias} > min$

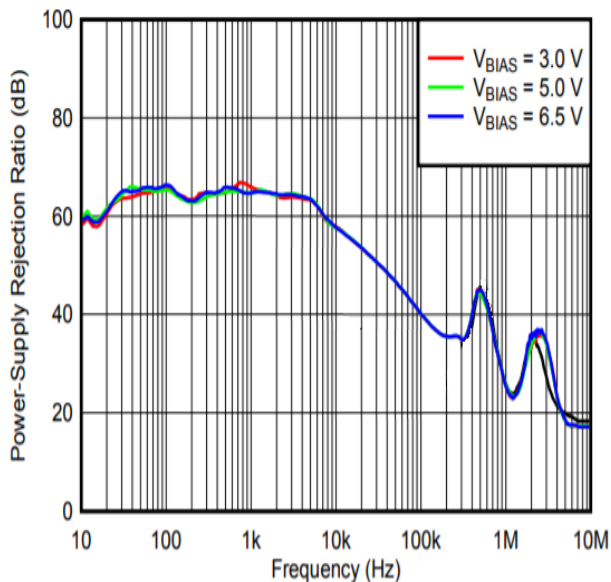


Figure 3. PSRR vs Frequency and V_{BIAS}

TI Information – Selective Disclosure

The next thing that only has a small effect on PSRR is V_{out}

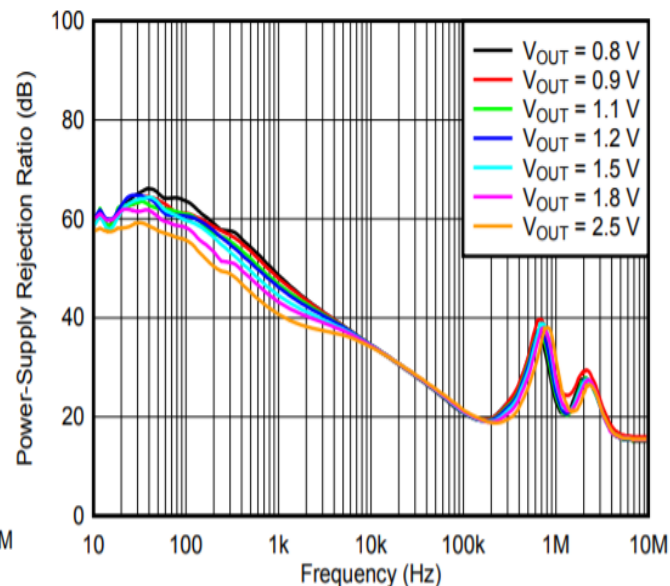


Figure 5. PSRR vs Frequency and V_{OUT} With Bias

And the final thing that has some effect (but only at high freq) is output capacitor

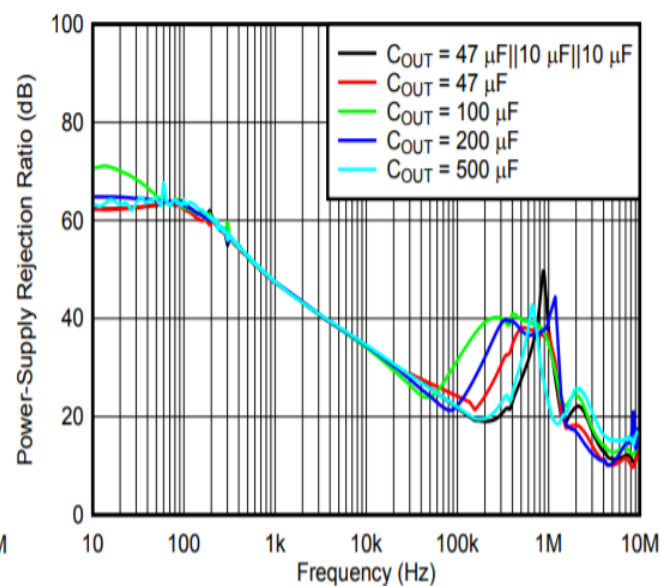


Figure 7. PSRR vs Frequency and C_{OUT}