

LM(2)5117 Wide Input Range Synchronous Buck Controller with Analog Current Monitor

Revision: 09/20/2013 ver 1.5 by Eric Lee


Note: The components calculated in this worksheet are reasonable starting values for a design using the LM(2)5117. They are not optimized for any particular performance attribute. The most recent version of this excel file can be found in the product folder of the part at national.com. Make sure to input or select values in all of the blue shaded cells even if a value already exists in that cell. Blue shaded cells require input from user. Do not over write equations in cells, as this may result in calculation errors.

To activate all functions, **Macro should be enabled and Analysis Toolpak should be added in.**

Step 1 - General Requirements

Max input voltage, $V_{IN(MAX)}$ [V]	55
Min input voltage, $V_{IN(MIN)}$ [V]	35
Target output voltage, V_{OUT} [V]	30
Full load current, I_{OUT} [A]	5
Recommended IC	LM5117

TYPICAL APPLICATION CIRCUIT

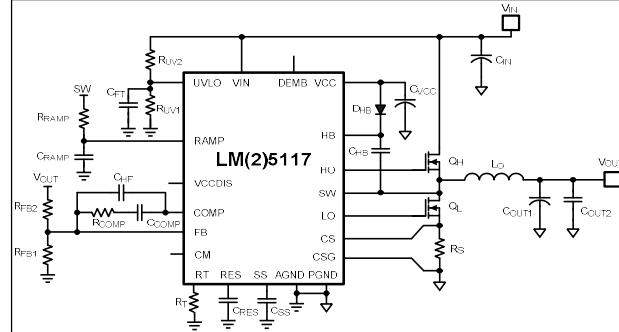

Step 2 - Switching Frequency

Switching frequency, F_{SW} [kHz]	80
Max duty cycle, D_{MAX}	0.86
Min duty cycle, D_{MIN}	0.55
RT resistor, R_T [Ω]	64.2

LIST OF COMPONENTS AND PARAMETERS

Components	Description	Value	Min Rating
IC	Buck controller	LM5117	
C_{IN}	Input capacitor	2 μ F	55V
C_{OUT1}	Output capacitor	220 μ F	30V
C_{OUT2}	Output capacitor	2 μ F	30V
C_{VCC}	VCC capacitor	0.75 μ F Min	10V
C_{HB}	Bootstrap capacitor	0.03 μ F Min	9V
C_{SS}	Softstart capacitor	0.13 μ F	6V
C_{RES}	Restart capacitor	2.00 μ F	6V
C_{RAMP}	RAMP capacitor	1000pF	16V
C_{COMP}	Compensation Capacitor	10.00nF	6V
C_{HF}	Compensation Capacitor	180pF	6V
C_{FT}	Optional filter capacitor	238pF Max	16V
R_{UV1}	UVLO divider resistor	15.15k Ω	1/16W
R_{UV2}	UVLO divider resistor	100.0k Ω	1/8W
R_{FB1}	Feedback divider resistor	2740 Ω	1/16W
R_{FB2}	Feedback divider resistor	100000 Ω	1/16W
R_S	Current sense resistor	0.0100 Ω	0.11W
R_T	Oscillator timing resistor	64.2k Ω	1/16W
R_{RAMP}	RAMP resistor	1000k Ω	1/8W
R_{COMP}	Compensation Resistor	39.00k Ω	1/16W
L_0	Output inductor	100.0 μ H	9A~12A
D_{HB}	Bootstrap diode	1A	25V
Q_H and Q_L	NMOS		55V

Step 4 - Current Limit

Target (% beyond full load @ $V_{IN(MIN)}$)	30
K Factor	1
Recommended current sense resistor, R_S [Ω]	0.0120
User selection, R_S [Ω]	0.01
Max output current @ $V_{IN(MIN)}$ [A]	8.5
Max output current @ $V_{IN(MAX)}$ [A]	9.1
Peak inductor current with output hard short [A]	12.1
Full load power dissipation of R_S @ $V_{IN(MAX)}$, P_{RS} [W]	0.11

Step 5 - Ramp Configuration


Ramp capacitor, C_{RAMP} [pF]	1000
Ramp resistor, R_{RAMP} [k Ω]	1000.0

Step 6 - VIN UV Shutdown

Desired minimum start-up voltage, $V_{IN(STARTUP)}$ [V]	9.5
Desired UV hysteresis, V_{HYS} [V]	2
R_{UV2} [k Ω]	100
R_{UV1} [k Ω]	15.15
Max C_{FT} (optional) [pF]	238

Step 7 - NMOS gate charge

High-side MOSFET Q_g @ V_{VCC} (nC)	4.3
Low-side MOSFET Q_g @ V_{VCC} (nC)	108
Gate charging current [mA]	9

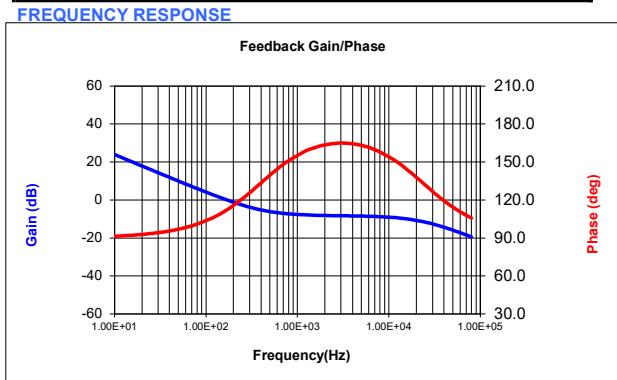


Step 8 -Bootstrap capacitor and VCC capacitor

Min C _{HB} [μ F]	0.03
Min C _{VCC} [μ F]	0.75

Step 9 -Output Capacitors

Output capacitor with ESR, C _{OUT1} [μ F]	220
Ceramic output capacitor, C _{OUT2} [μ F]	2
Max ESR of C _{OUT1} , R _{ESR} [Ω]	0.02
Effective total C _{OUT} [μ F]	222
Peak-Peak output voltage ripple @V _{IN(MAX)} [mV]	36
RMS output current ripple [A]	0.5

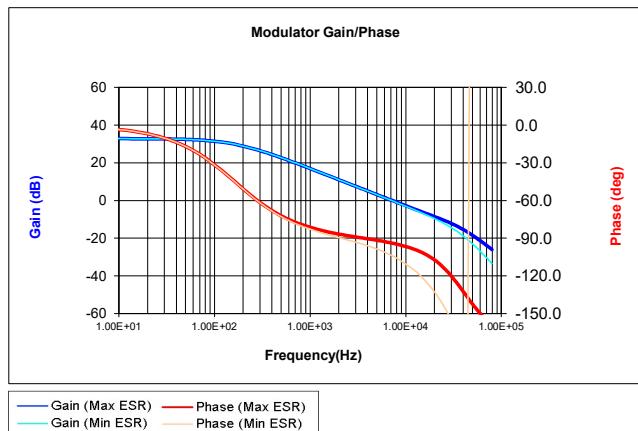**Step 10 -Input Capacitors**

Input capacitor(ceramic), C _{IN} [μ F]	2
Peak-Peak input voltage ripple [V]	7.81
RMS input current ripple [A]	2.5

Step 11 -Soft Start


Desired soft-start time, T _{SS} [ms]	10
Soft-start capacitor, C _{SS} [μ F]	0.125

Step 12 - Hiccup mode restart time

Desired restart time, T _{RES} [ms]	250
Restart capacitor, C _{RES} [μ F]	2.00


Step 13 - Feedback Resistors

R _{FB2} [Ω]	100000
R _{FB1} [Ω]	2740

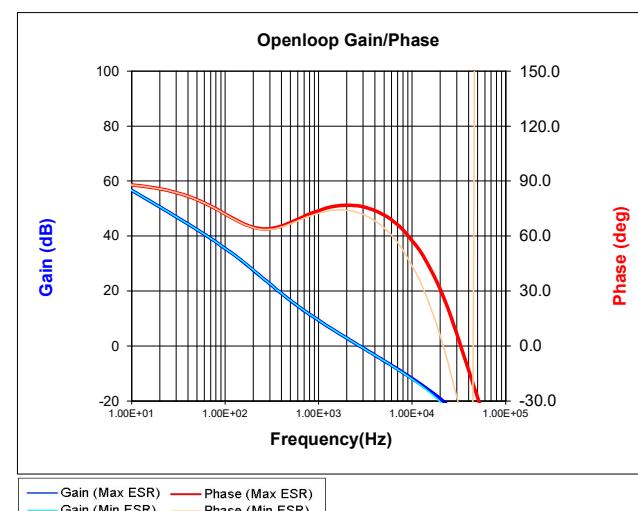**Step 14 - Compensation Network**

Openloop crossover frequency, F _{CROSS} [kHz]	2.8
R _{COMP} [Ω]	39036
User selection, R _{COMP} [Ω]	39000
C _{COMP} [μ F]	12000
User selection, C _{COMP} [μ F]	10000

User selection, C _{HF} [μ F]	180
--------------------------------------------	-----

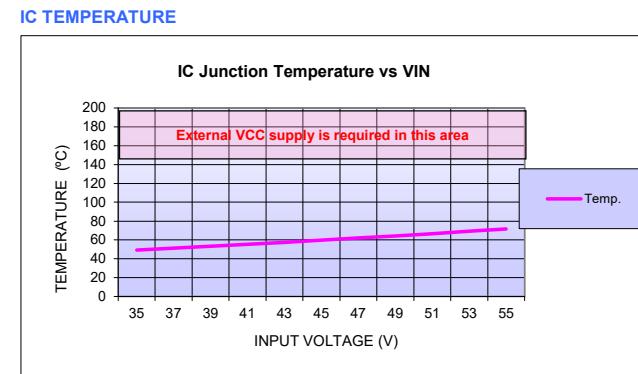**PRINT****Simulate This Design Using WEBENCH® Tools**

To further optimize the design, please visit:

<http://webench.national.com/>

Optimization graphs, charts, and electrical/thermal simulation capabilities are available.

Note: The WEBENCH recommended BOM may be different than what is recommended in this spreadsheet.