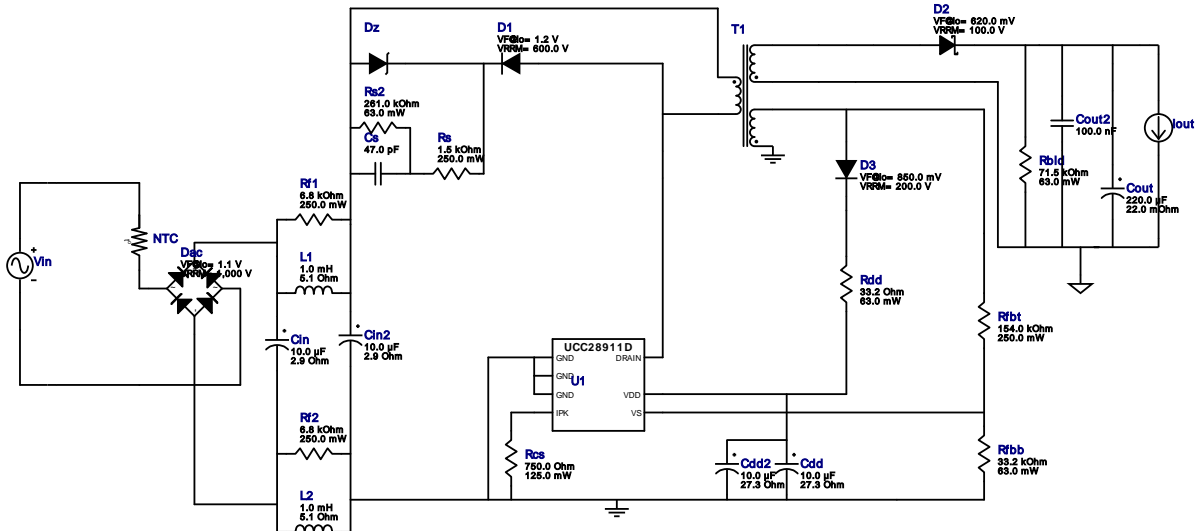








## WEBENCH® Design Report


 Design : 10925/22 UCC28911D  
 UCC28911D 85.0V-265.0V to 12.00V @ 0.5A

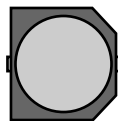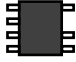
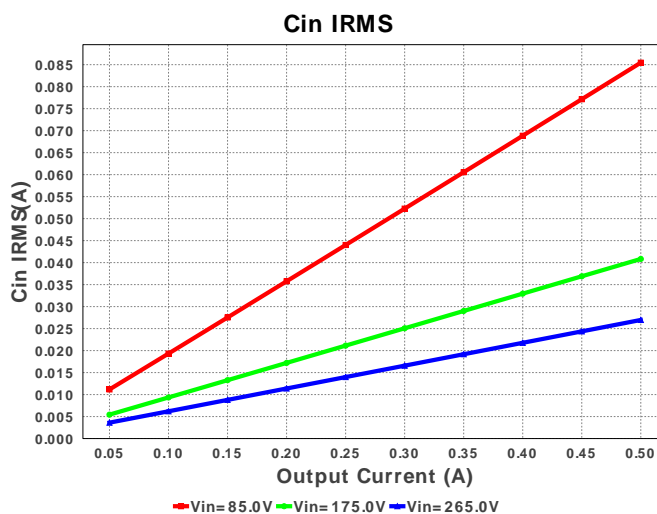
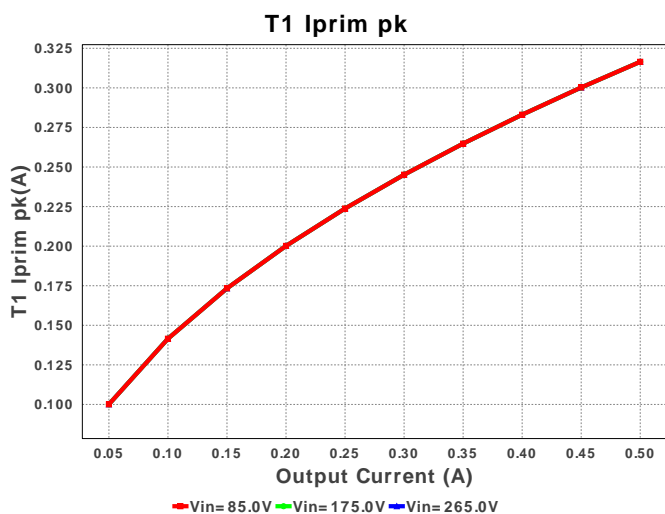
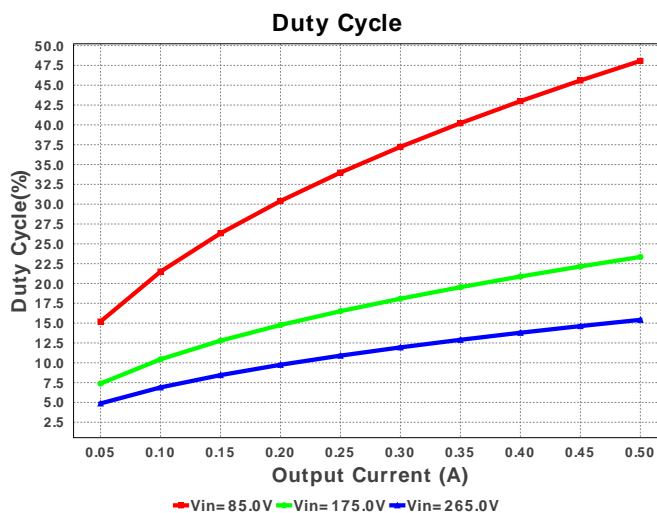
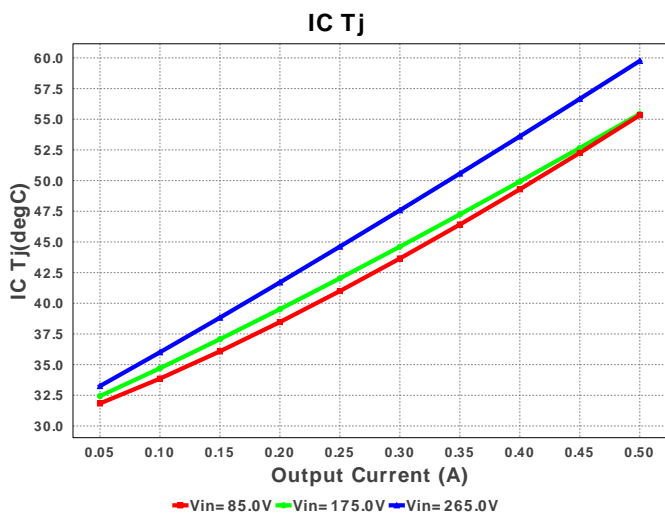
1. Click on the transformer symbol and select 'Design Transformer' to design using specific transformer cores and bobbin







### Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cdd	Nichicon	UVR1V100MDD1TA Series= ?	Cap= 10.0 uF ESR= 27.3 Ohm VDC= 35.0 V IRMS= 0.0 A	1	\$0.03	 CAPPR2-5X11 49 mm <sup>2</sup>
2.	Cdd2	Nichicon	UVR1V100MDD1TA Series= ?	Cap= 10.0 uF ESR= 27.3 Ohm VDC= 35.0 V IRMS= 0.0 A	1	\$0.03	 CAPPR2-5X11 49 mm <sup>2</sup>
3.	Cin	Kemet	ESG106M400AH4AA Series= 2334	Cap= 10.0 uF ESR= 2.9 Ohm VDC= 400.0 V IRMS= 100.0 mA	1	\$0.19	ESG106 144 mm <sup>2</sup>
4.	Cin2	Kemet	ESG106M400AH4AA Series= 2334	Cap= 10.0 uF ESR= 2.9 Ohm VDC= 400.0 V IRMS= 100.0 mA	1	\$0.19	ESG106 144 mm <sup>2</sup>
5.	Cout	Chemi-Con	APXE160ARA221MJ80G Series= PXE	Cap= 220.0 uF ESR= 22.0 mOhm VDC= 16.0 V IRMS= 3.45 A	1	\$0.77	 CAPSMT_62_J80 156 mm <sup>2</sup>
6.	Cout2	MuRata	GRM155R61C104KA88D Series= X5R	Cap= 100.0 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm <sup>2</sup>
7.	Cs	MuRata	GRM21A5C2E470JW01D Series= C0G/NP0	Cap= 47.0 pF VDC= 250.0 V IRMS= 0.0 A	1	\$0.06	 0805 7 mm <sup>2</sup>
8.	D1	ON Semiconductor	1N4937G	VF@Io= 1.2 V VRRM= 600.0 V	1	\$0.04	 DO-41 43 mm <sup>2</sup>


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	D2	Vishay-Semiconductor	SS2PH10-M3	VF@Io= 620.0 mV VRRM= 100.0 V	1	\$0.14	 DO-220AA 0 mm <sup>2</sup>
10.	D3	Rohm	RF071M2S	VF@Io= 850.0 mV VRRM= 200.0 V	1	\$0.09	 SOD-123 13 mm <sup>2</sup>
11.	Dac	Vishay-Semiconductor	DF10SA	VF@Io= 1.1 V VRRM= 1,000.0 V	1	\$0.24	 DF-S 99 mm <sup>2</sup>
12.	Dz	ON Semiconductor	1SMB5949BT3G	Zener	1	\$0.10	 SMB 44 mm <sup>2</sup>
13.	L1	Coilcraft	LPS5030-105MRB	L= 1.0 mH DCR= 5.1 Ohm	1	\$0.44	 LPS5030 34 mm <sup>2</sup>
14.	L2	Coilcraft	LPS5030-105MRB	L= 1.0 mH DCR= 5.1 Ohm	1	\$0.44	 LPS5030 34 mm <sup>2</sup>
15.	NTC	Ametherm	SL0310001 Series= miniAMP	Thermistor	1	\$0.23	SL03 6 mm <sup>2</sup>
16.	Rbld	Vishay-Dale	CRCW040271K5FKED Series= CRCW..e3	Res= 71.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm <sup>2</sup>
17.	Rcs	Vishay-Dale	CRCW0805750RFKEA Series= CRCW..e3	Res= 750.0 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm <sup>2</sup>
18.	Rdd	Vishay-Dale	CRCW040233R2FKED Series= CRCW..e3	Res= 33.2 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm <sup>2</sup>
19.	Rf1	Yageo America	RC1206FR-076K8L Series= ?	Res= 6.8 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm <sup>2</sup>
20.	Rf2	Yageo America	RC1206FR-076K8L Series= ?	Res= 6.8 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm <sup>2</sup>
21.	Rfbb	Vishay-Dale	CRCW040233K2FKED Series= CRCW..e3	Res= 33.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm <sup>2</sup>
22.	Rfbt	Panasonic	ERJ-8ENF1543V Series= ERJ-8E	Res= 154.0 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm <sup>2</sup>
23.	Rs	Panasonic	ERJ-8ENF1501V Series= ERJ-8E	Res= 1.5 kOhm Power= 250.0 mW Tolerance= 1.0%	1	\$0.01	 1206 11 mm <sup>2</sup>
24.	Rs2	Vishay-Dale	CRCW0402261KFKED Series= CRCW..e3	Res= 261.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm <sup>2</sup>
25.	T1	Core=TDK , CoilFormer=TDK	Core=B66413G0000X197 , CoilFormer=B66414W1008D001	Lp= 1.2 mH Turns Ratio(Nas)= 8:5 Turns Ratio(Nps)= 38:5 Npri= 38.0 Naux= 8.0 Nsec= 5.0	1	\$0.86	 TDK_B66305 248 mm <sup>2</sup>

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
26.	U1	Texas Instruments	UCC28911D	Switcher	1	\$0.98	 D0007A 55 mm <sup>2</sup>




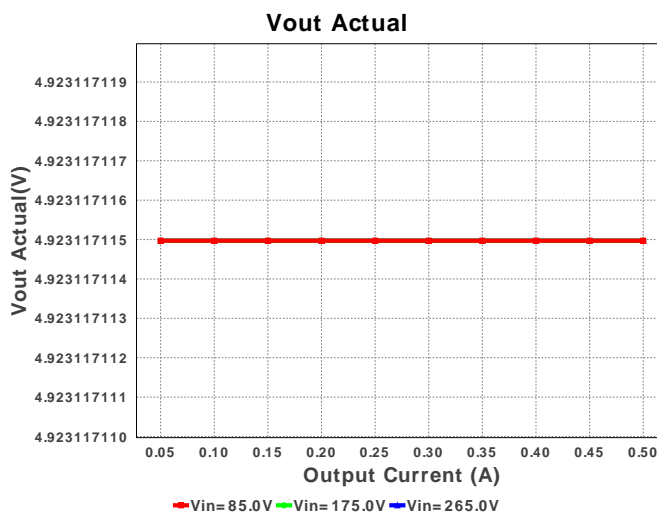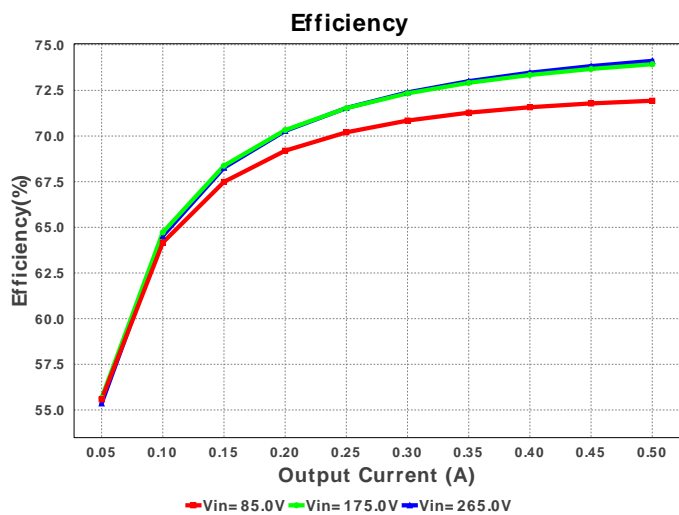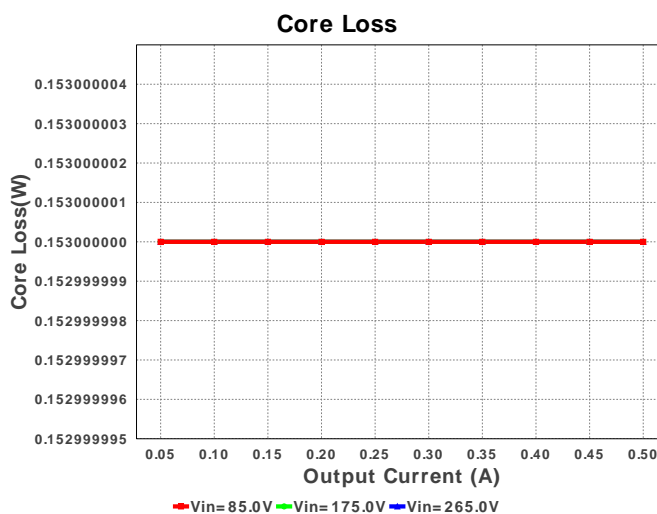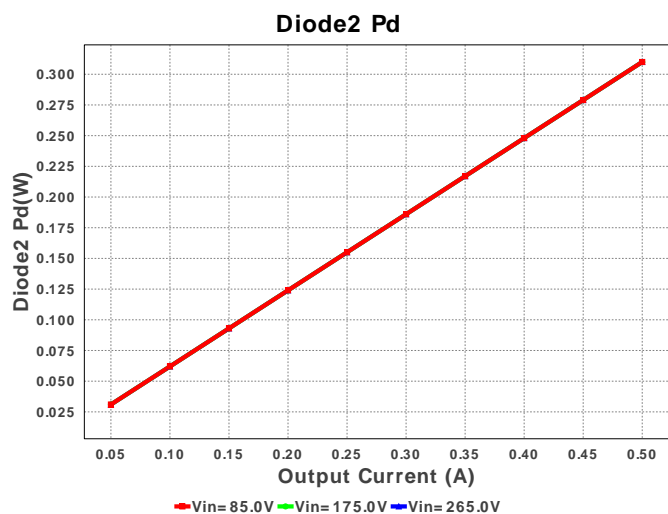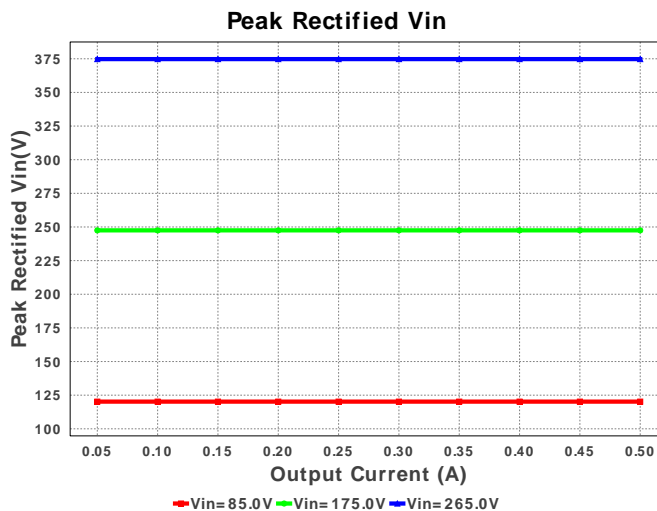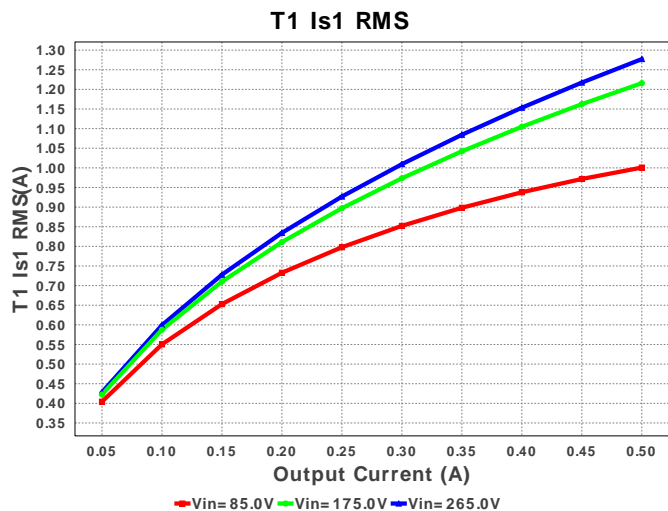


**Cin2 IRMS**

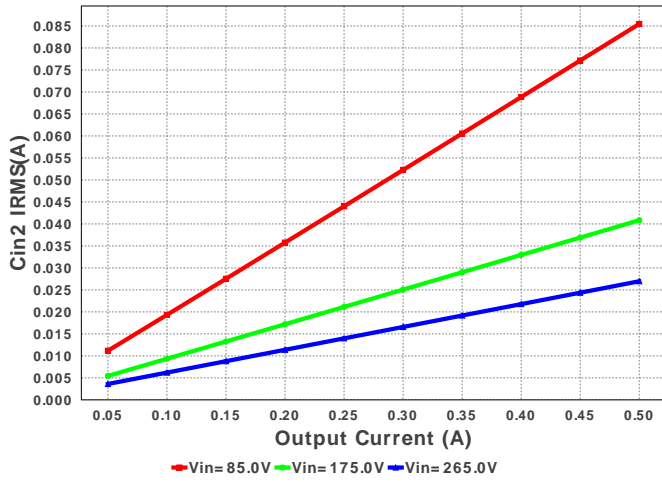


**Vout p- p**

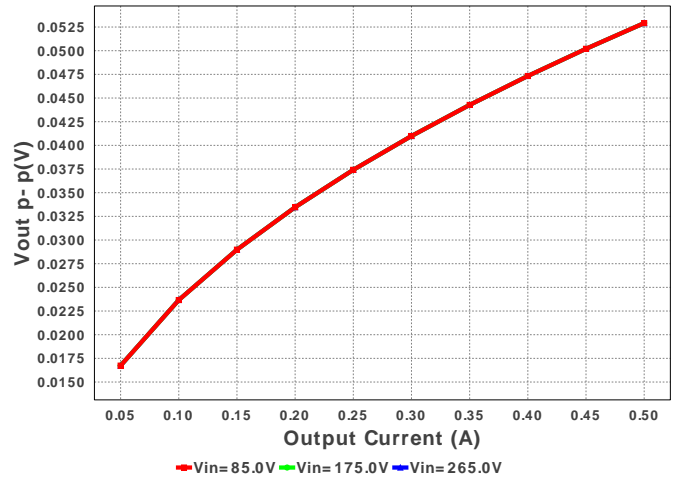


**T1 Iprim RMS**

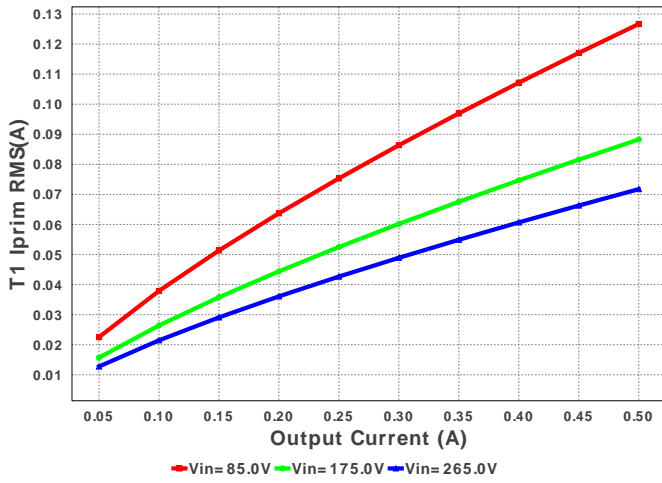


**Iin rms**






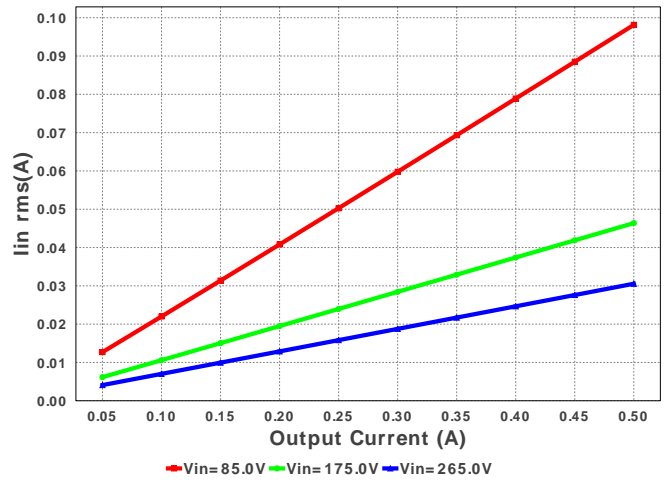



**Cin Pd**

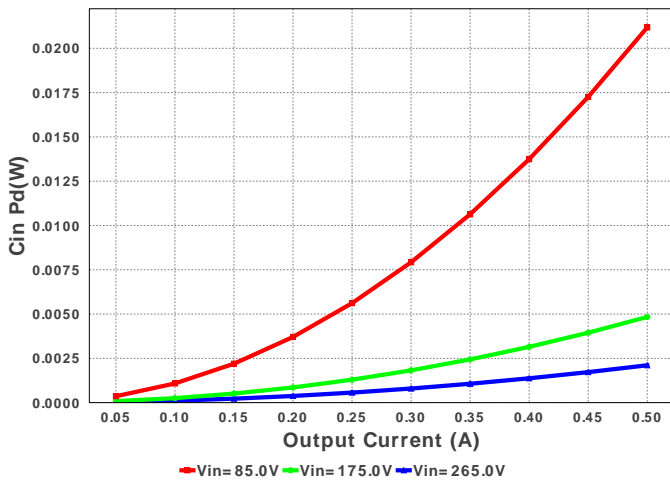

**Cout Pd**

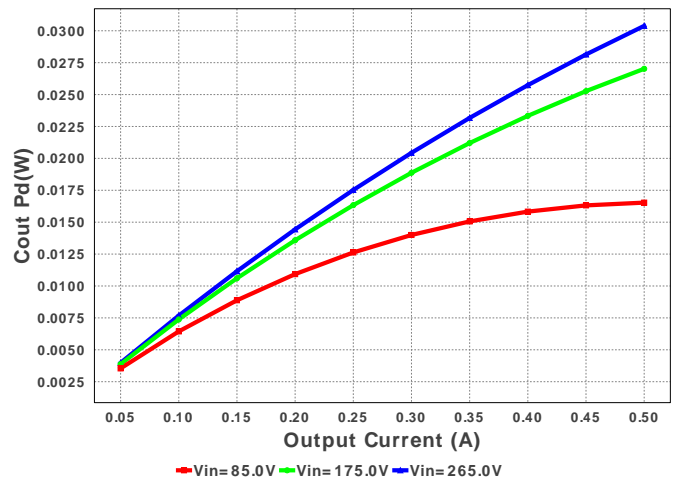

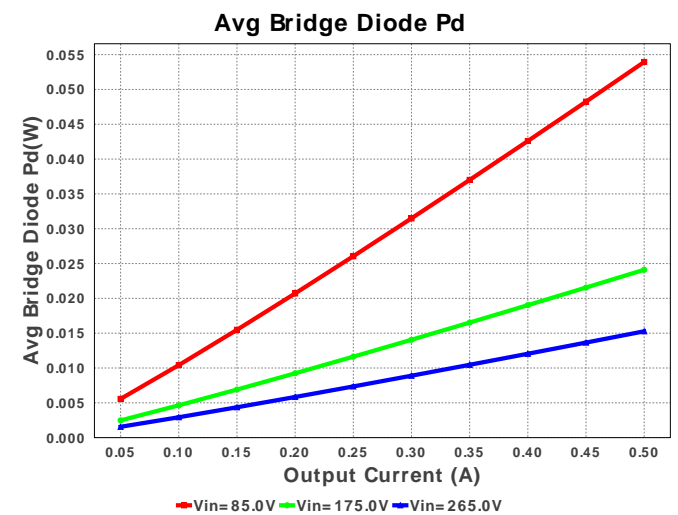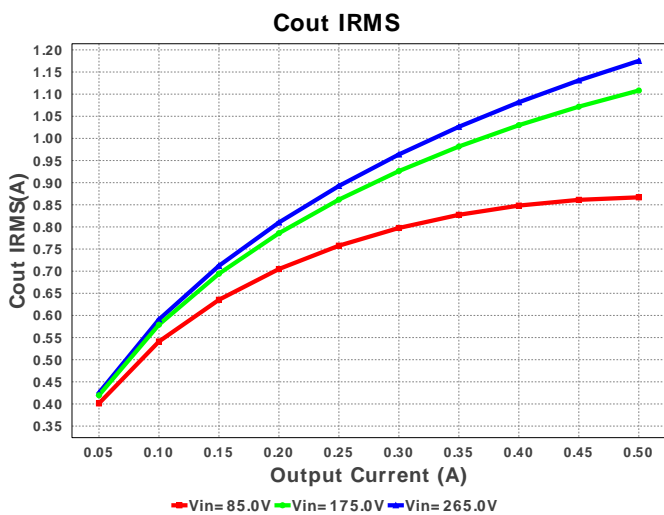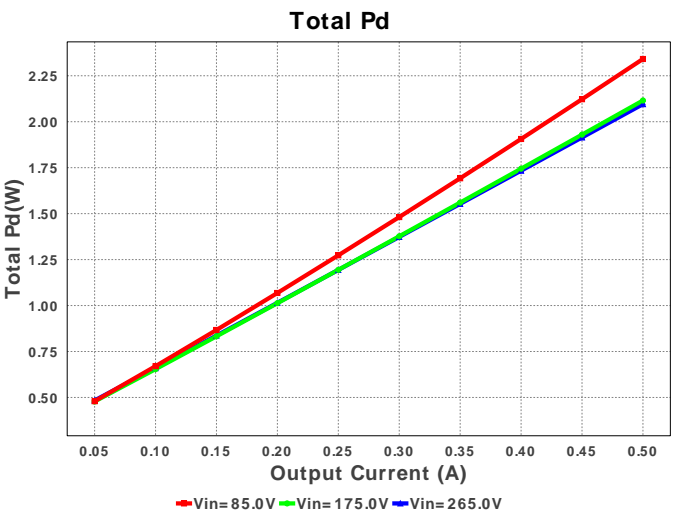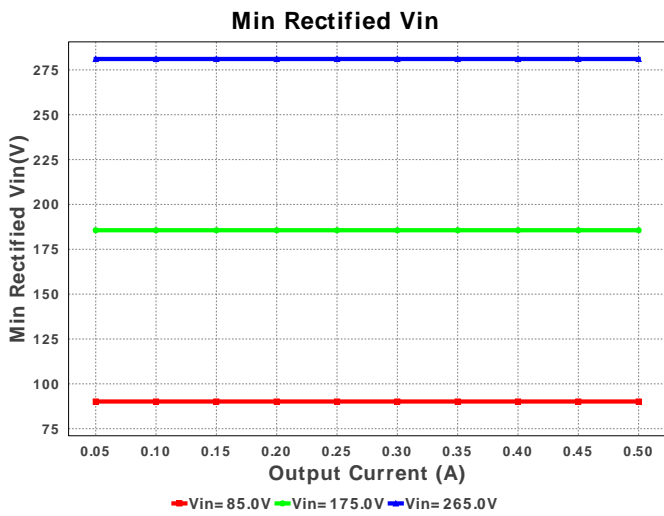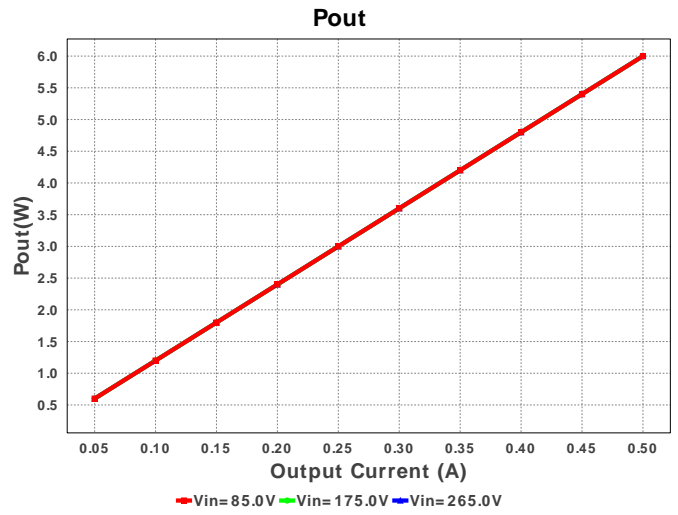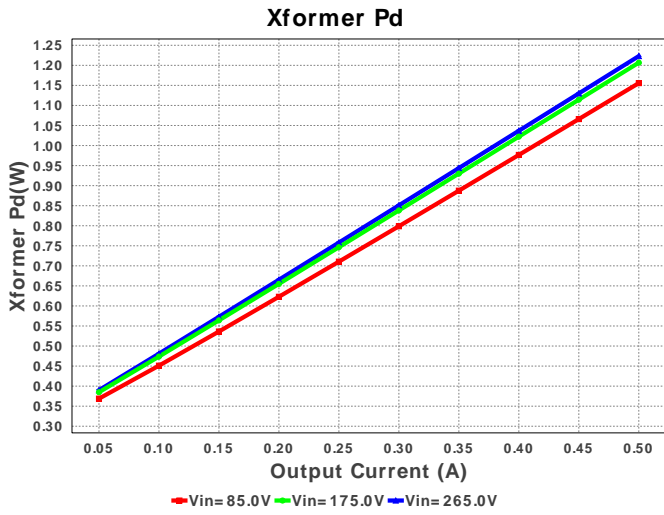

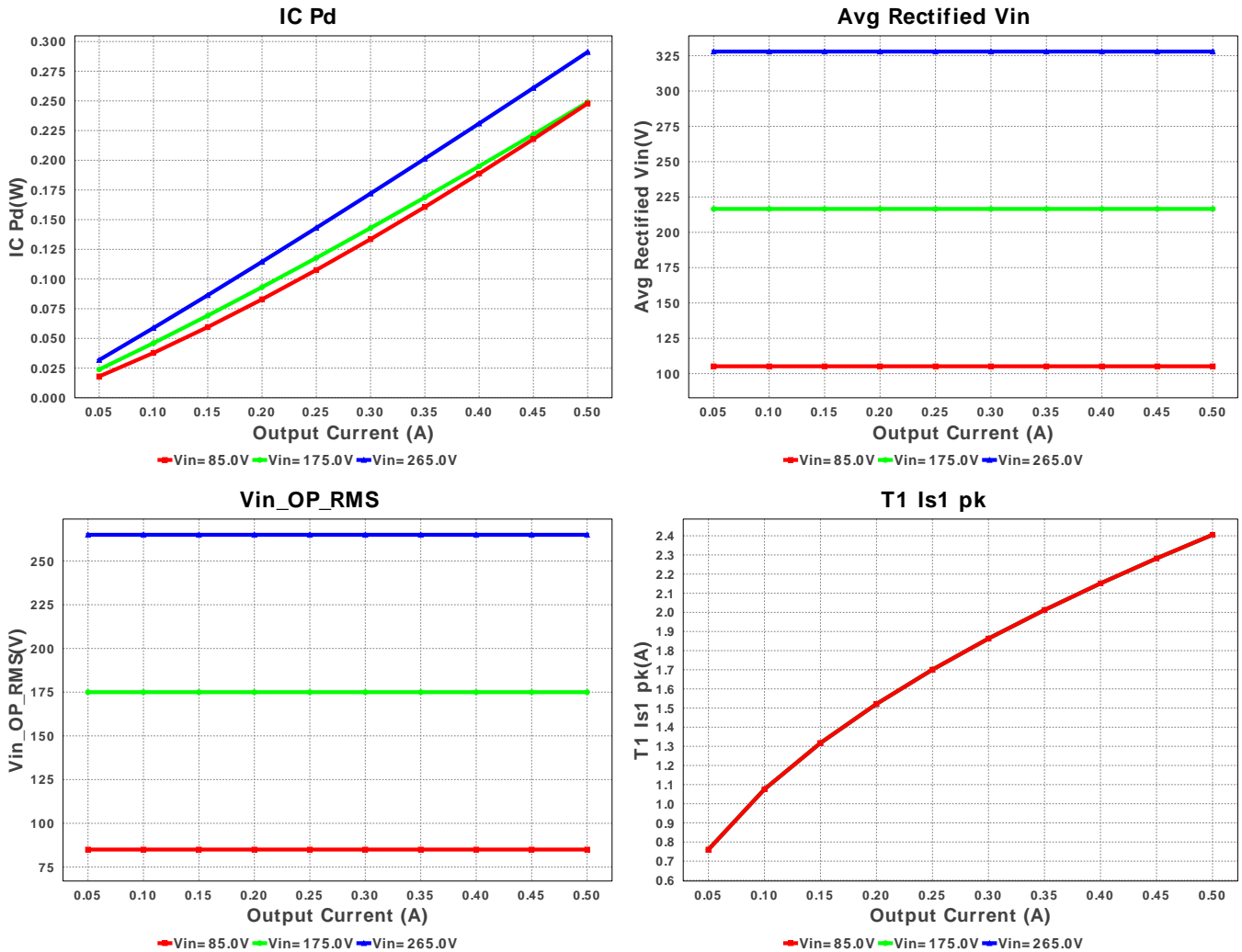

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	77.497 mA	Current	Input capacitor RMS ripple current
2.	Cin2 IRMS	77.497 mA	Current	Input Capacitor Cin2 RMS Ripple Current
3.	Cout IRMS	451.471 mA	Current	Output capacitor RMS ripple current
4.	Iin rms	89.292 mA	Current	RMS Input Current
5.	T1 Iprim RMS	111.576 mA	Current	Transformer Primary RMS Current
6.	T1 Iprim pk	245.517 mA	Current	Transformer Primary Peak Current
7.	T1 Is1 RMS	673.666 mA	Current	Transformer Secondary1 RMS Current
8.	T1 Is1 pk	1.892 A	Current	Transformer Secondary1 Peak Current
9.	Avg Rectified Vin	105.181 V	General	Average Rectified Voltage for the AC Line Period
10.	BOM Count	26	General	Total Design BOM count
11.	D1 trr	300.0 ns	General	D1 Reverse Recovery Time
12.	D2 trr	0.0 ns	General	Output Diode Reverse Recovery Time
13.	D3 trr	25.0 ns	General	Auxiliary Diode Reverse Recovery Time
14.	FootPrint	1.29 k mm <sup>2</sup>	General	Total Foot Print Area of BOM components
15.	Frequency	105.0 kHz	General	Switching frequency
16.	Pout	6.0 W	General	Total output power
17.	Total BOM	\$4.92	General	Total BOM Cost
18.	Vout Actual	4.923 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
19.	Vout OP	12.0 V	Op_Point	Operational Output Voltage
20.	Duty Cycle	61.959 %	Op_point	Duty cycle
21.	Efficiency	79.053 %	Op_point	Steady state efficiency
22.	IC Tj	61.486 degC	Op_point	IC junction temperature
23.	ICThetaJA	102.2 degC/W	Op_point	IC junction-to-ambient thermal resistance
24.	IOUT_OP	500.0 mA	Op_point	Iout operating point
25.	Min Rectified Vin	90.155 V	Op_point	Minimum voltage seen at rectified input
26.	Peak Rectified Vin	120.207 V	Op_point	Peak voltage seen at rectified input
27.	Vin_OP_RMS	85.0 V	Op_point	AC Input RMS Voltage
28.	Vout p-p	41.62 mV	Op_point	Peak-to-peak output ripple voltage
29.	Avg Bridge Diode Pd	48.921 mW	Power	Average Power Dissipation in the Bridge Diode over the AC Line Period
30.	Cin Pd	17.417 mW	Power	Input capacitor power dissipation
31.	Core Loss	39.905 mW	Power	

#	Name	Value	Category	Description
32.	Cout Pd	4.484 mW	Power	Output capacitor power dissipation
33.	Diode2 Pd	310.0 mW	Power	Diode2 power dissipation
34.	IC Pd	308.077 mW	Power	IC power dissipation
35.	Total Pd	1.59 W	Power	Total Power Dissipation
36.	Xformer Pd	347.765 mW	Power	Transformer power dissipation
37.	Vout Tolerance	8.64 %		Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable

## Design Inputs

#	Name	Value	Description
1.	Iout	500.0 m	Maximum Output Current
2.	VinMax	265.0	Maximum input voltage
3.	VinMin	85.0	Minimum input voltage
4.	Vout	12.0	Output Voltage
5.	line_fsw	60.0	Light Output in Lumen
6.	base_pn	UCC28911	Base Product Number
7.	source	AC	Input Source Type
8.	Ta	30.0	Ambient temperature

## Design Assistance

1. **UCC28911** Product Folder : <http://www.ti.com/product/UCC28911> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).