

## TIDA-01513 insulation resistance calculation formula

- Get both resistance of HV positive to chassis ground(Risop) and HV negative to chassis ground(Rison)

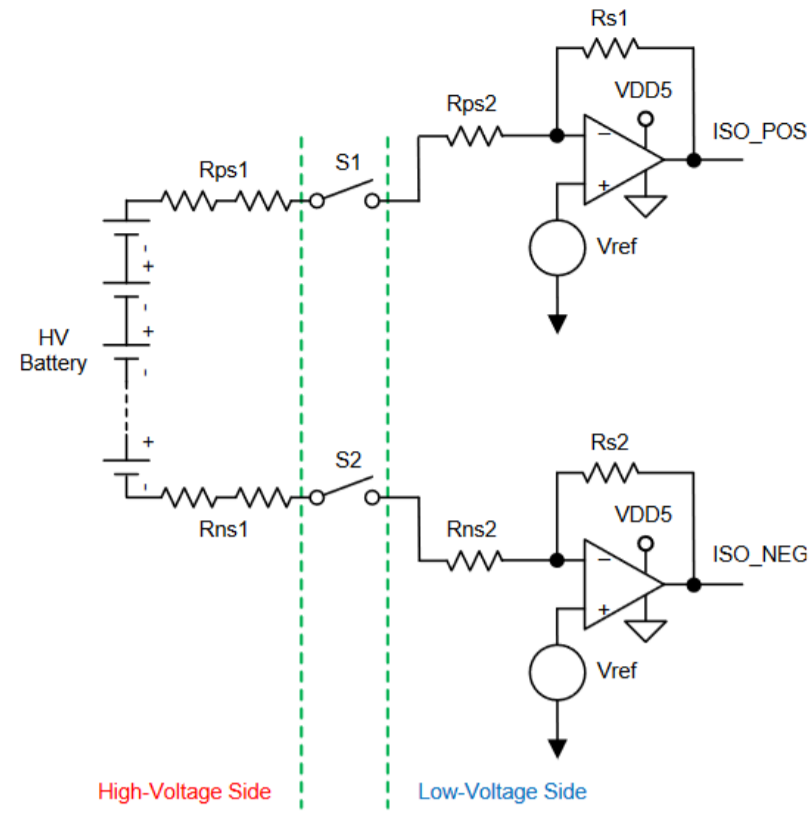


Figure 6. HEV and EV Isolation

**Status 1:** Close S1 and remain S2 open, ISO\_POS and HV\_BATT1(Simultaneous with ISO\_POS) can be read by the ADC while ISO\_NEG remains equal to Vref. For simplify,  $\alpha$  is stipulated as below.

$$\alpha = V_{ref} \left( 1 + \frac{R_{ps}}{R_s} \right) - \frac{R_{ps}}{R_s} \cdot ISO\_POS$$

Then equation 1 can be got.

$$\frac{\frac{V_{ref}}{R_{ps}} + \frac{HV\_BATT1}{R_{ison}}}{\frac{1}{R_{ps}} + \frac{1}{R_{ison}} + \frac{1}{R_{isop}}} = \alpha \quad \text{equation 1}$$

**Status 2:** Close S2 and open S1, ISO\_NEG and HV\_BATT2(Simultaneous with ISO\_NEG) can be read by the ADC while ISO\_POS remains equal to Vref. For simplify,  $\beta$  is stipulated as below.

$$\beta = V_{ref} \left( 1 + \frac{R_{ps}}{R_s} \right) - \frac{R_{ps}}{R_s} \cdot ISO\_NEG$$

Then equation 2 can be got.

$$\frac{\frac{V_{ref}}{R_{ps}} - \frac{HV\_BATT2}{R_{isop}}}{\frac{1}{R_{ps}} + \frac{1}{R_{ison}} + \frac{1}{R_{isop}}} = \beta \quad \text{equation 2}$$

Here,  $R_{ps} = R_{ps1} + R_{ps2} = R_{ns1} + R_{ns2}$ ,  $R_s = R_{s1} = R_{s2}$ .

By these two equations, Risop and Rison can be got separately.

$$R_{isop} = \frac{HV\_BATT1 \cdot HV\_BATT2 \cdot R_{ps} + HV\_BATT1 \cdot R_{ps} \cdot \beta - HV\_BATT2 \cdot R_{ps} \cdot \alpha}{HV\_BATT1 \cdot V_{ref} - HV\_BATT1 \cdot \beta + V_{ref} \cdot \beta - V_{ref} \cdot \alpha}$$

$$R_{ison} = \frac{HV\_BATT1 \cdot HV\_BATT2 \cdot R_{ps} + HV\_BATT1 \cdot R_{ps} \cdot \beta - HV\_BATT2 \cdot R_{ps} \cdot \alpha}{HV\_BATT2 \cdot V_{ref} - HV\_BATT2 \cdot \alpha + V_{ref} \cdot \beta - V_{ref} \cdot \alpha}$$

## Double check Risop and Rison with simulation


$$R_{ps} := 1.18 \cdot 10^6$$


$$R_s := 5000$$

$$HV\_BATT1 := 400$$

$$HV\_BATT2 := 400$$

$$V_{ref} := 2.5$$

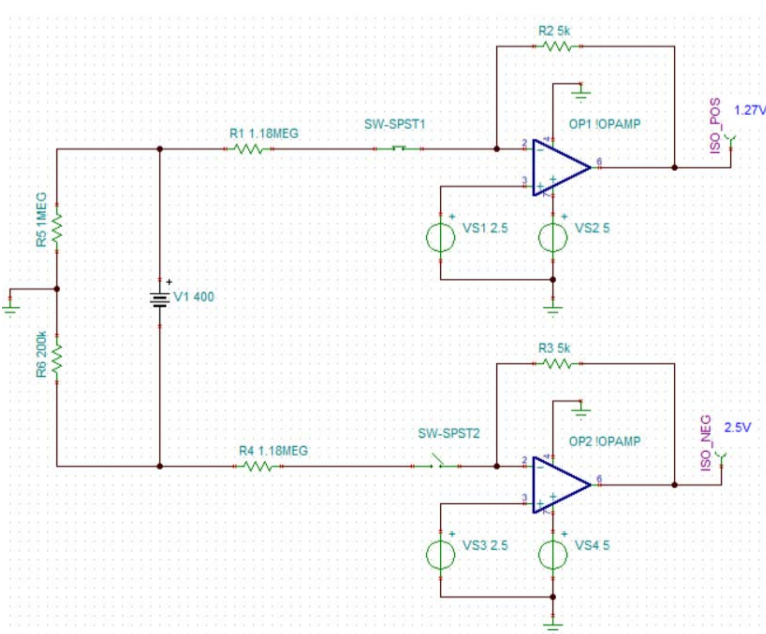

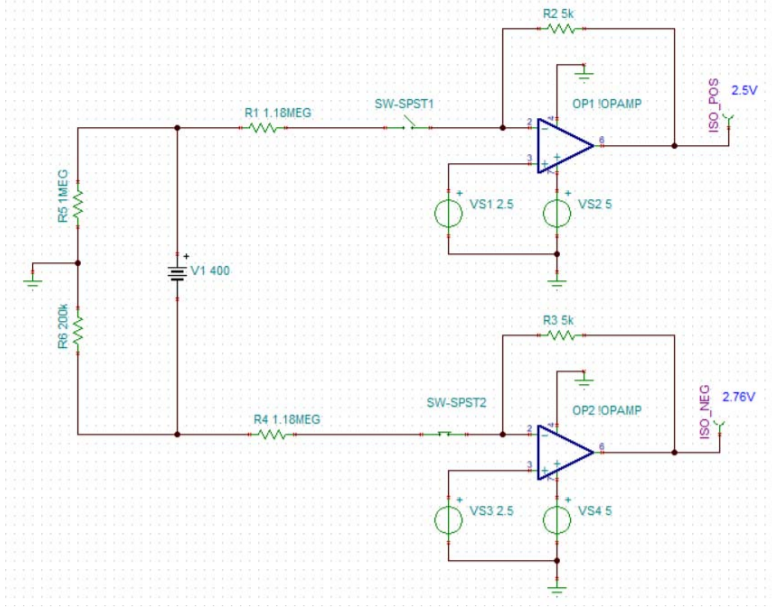

$$\text{ISO\_POS} := 1.27$$

$$\alpha := V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{R_{\text{ps}}}{R_{\text{s}}} \cdot \text{ISO\_POS} = 292.78$$

$$\text{ISO\_NEG} := 2.76$$

$$\beta := V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{R_{\text{ps}}}{R_{\text{s}}} \cdot \text{ISO\_NEG} = -58.86$$

$$R_{\text{isop}} := \frac{\text{HV\_BATT1} \cdot \text{HV\_BATT2} \cdot R_{\text{ps}} + \text{HV\_BATT1} \cdot R_{\text{ps}} \cdot \beta - \text{HV\_BATT2} \cdot R_{\text{ps}} \cdot \alpha}{\text{HV\_BATT1} \cdot V_{\text{ref}} - \text{HV\_BATT1} \cdot \beta + V_{\text{ref}} \cdot \beta - V_{\text{ref}} \cdot \alpha} = 9.645 \times 10^5$$

$$R_{\text{ison}} := \frac{\text{HV\_BATT1} \cdot \text{HV\_BATT2} \cdot R_{\text{ps}} + \text{HV\_BATT1} \cdot R_{\text{ps}} \cdot \beta - \text{HV\_BATT2} \cdot R_{\text{ps}} \cdot \alpha}{\text{HV\_BATT2} \cdot V_{\text{ref}} - \text{HV\_BATT2} \cdot \alpha + V_{\text{ref}} \cdot \beta - V_{\text{ref}} \cdot \alpha} = 1.951 \times 10^5$$

### Get ISO\_POS and ISO\_NEG from known Risop and Rison

**Status 1:** Close S1 and remain S2 open, ISO\_POS and HV\_BATT1 (Simultaneous with ISO\_POS) can be read by the ADC while ISO\_NEG remains equal to Vref. The formula of getting ISO\_POS is the reverse calculation of equation 1.

$$\text{ISO\_POS} = \left[ V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{\frac{V_{\text{ref}} + \text{HV\_BATT1}}{R_{\text{ps}} + \frac{R_{\text{ps}}}{R_{\text{ison}}}}}{\frac{1}{R_{\text{ps}}} + \frac{1}{R_{\text{ison}}} + \frac{1}{R_{\text{isop}}}} \right] \cdot \frac{R_{\text{s}}}{R_{\text{ps}}}$$

**Status 2:** Close S2 and open S1, ISO\_NEG and HV\_BATT2 (Simultaneous with ISO\_NEG) can be read by the ADC while ISO\_POS remains equal to Vref. The formula of getting ISO\_NEG is the reverse calculation of equation 2.

$$\text{ISO\_NEG} = \left[ V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{\frac{V_{\text{ref}} - \text{HV\_BATT2}}{R_{\text{ps}} - \frac{R_{\text{ps}}}{R_{\text{ison}}}}}{\frac{1}{R_{\text{ps}}} + \frac{1}{R_{\text{ison}}} + \frac{1}{R_{\text{isop}}}} \right] \cdot \frac{R_{\text{s}}}{R_{\text{ps}}}$$

**Status 3:** Close both S1 and S2, ISO\_POS, ISO\_NEG and HV\_BATT2 (Simultaneous with ISO\_POS and ISO\_NEG) can be read by the ADC. Equation 3 and equation 4 represent ISO\_POS and ISO\_NEG with known Risop and Rison.

$$\text{ISO\_POS} = \frac{R_{\text{ps}}^2 \cdot R_{\text{ison}} \cdot V_{\text{ref}} + R_{\text{ps}}^2 \cdot R_{\text{isop}} \cdot V_{\text{ref}} - \text{HV\_BATT} \cdot R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{isop}} - \text{HV\_BATT} \cdot R_{\text{s}} \cdot R_{\text{ison}} \cdot R_{\text{isop}} + R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot V_{\text{ref}} + R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{isop}} \cdot V_{\text{ref}} + 2 \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot R_{\text{isop}} \cdot V_{\text{ref}}}{R_{\text{ps}}^2 \cdot R_{\text{ison}} + R_{\text{ps}}^2 \cdot R_{\text{isop}} + 2 \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot R_{\text{isop}}} \quad \text{equation 3}$$

$$\text{ISO\_NEG} = \frac{R_{\text{ps}}^2 \cdot R_{\text{ison}} \cdot V_{\text{ref}} + R_{\text{ps}}^2 \cdot R_{\text{isop}} \cdot V_{\text{ref}} + \text{HV\_BATT} \cdot R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{ison}} + \text{HV\_BATT} \cdot R_{\text{s}} \cdot R_{\text{ison}} \cdot R_{\text{isop}} + R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot V_{\text{ref}} + R_{\text{s}} \cdot R_{\text{ps}} \cdot R_{\text{isop}} \cdot V_{\text{ref}} + 2 \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot R_{\text{isop}} \cdot V_{\text{ref}}}{R_{\text{ps}}^2 \cdot R_{\text{ison}} + R_{\text{ps}}^2 \cdot R_{\text{isop}} + 2 \cdot R_{\text{ps}} \cdot R_{\text{ison}} \cdot R_{\text{isop}}} \quad \text{equation 4}$$

### Double check ISO\_POS and ISO\_NEG by simulation

$$R_{\text{ps}} := 1.18 \cdot 10^6$$

$$R_{\text{s}} := 5000$$

$$\text{HV\_BATT1} := 400$$

$$\text{HV\_BATT2} := 450$$



$$V_{\text{ref}} := 2.5$$

$$R_{\text{isop}} := 1 \cdot 10^6$$

$$R_{\text{ison}} := 200 \cdot 10^3$$

$$\text{ISO\_POS} := \left[ V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{\frac{V_{\text{ref}} + \text{HV\_BATT1}}{R_{\text{ps}} + \frac{R_{\text{ps}}}{R_{\text{ison}}}}}{\frac{1}{R_{\text{ps}}} + \frac{1}{R_{\text{ison}}} + \frac{1}{R_{\text{isop}}}} \right] \cdot \frac{R_{\text{s}}}{R_{\text{ps}}} = 1.272$$
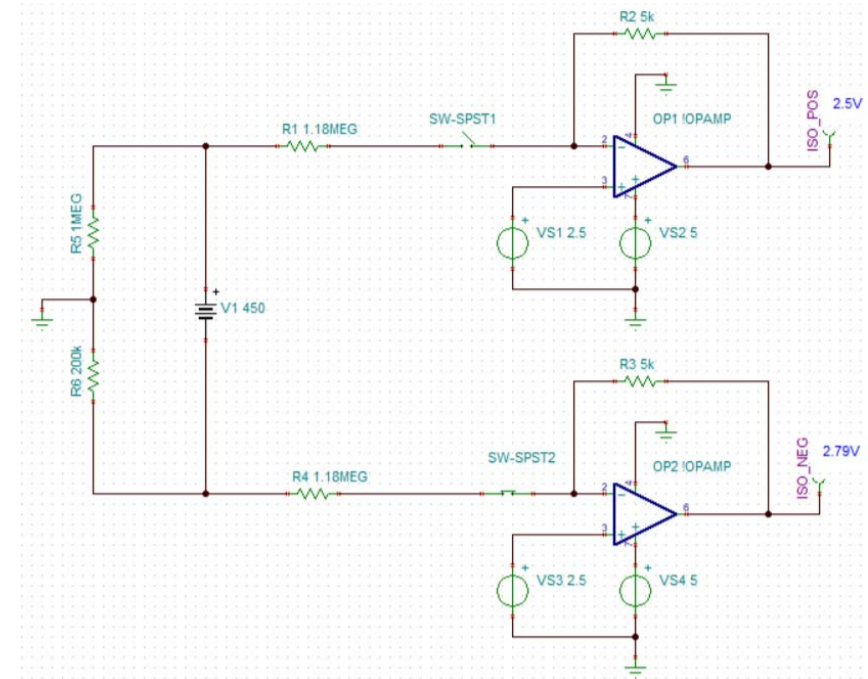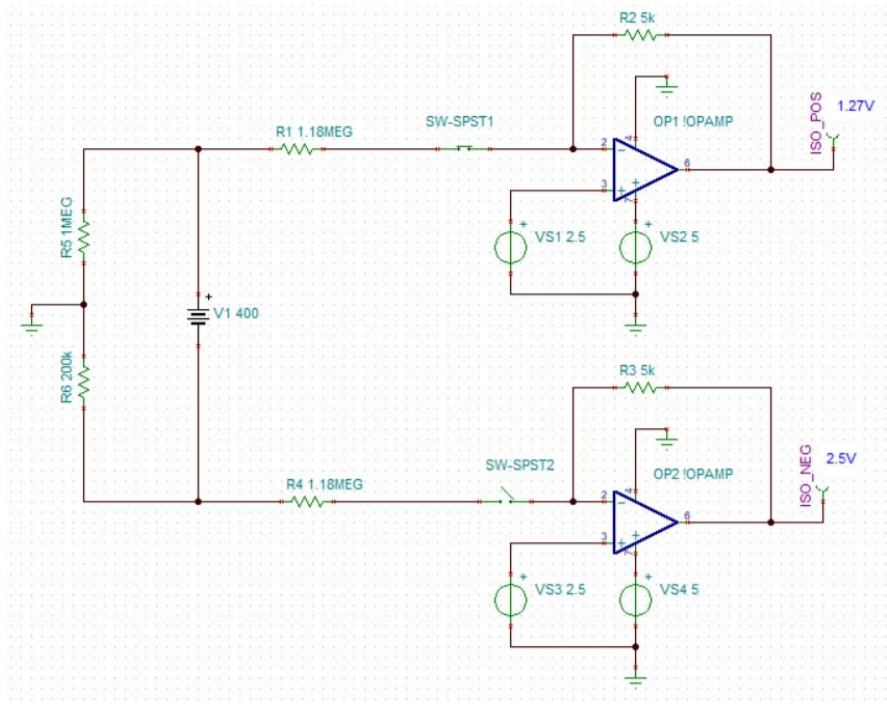
$$\text{ISO\_NEG} := \left[ V_{\text{ref}} \cdot \left( 1 + \frac{R_{\text{ps}}}{R_{\text{s}}} \right) - \frac{\frac{V_{\text{ref}} - \text{HV\_BATT2}}{R_{\text{ps}} - \frac{R_{\text{ps}}}{R_{\text{ison}}}}}{\frac{1}{R_{\text{ps}}} + \frac{1}{R_{\text{ison}}} + \frac{1}{R_{\text{isop}}}} \right] \cdot \frac{R_{\text{s}}}{R_{\text{ps}}} = 2.788$$



$$R_{ps} := 1.18 \cdot 10^6$$

$$R_s := 5000$$

$$HV\_BATT := 500$$

$$V_{ref} := 2.5$$

$$R_{isop} := 500 \cdot 10^3$$

$$R_{ison} := 200 \cdot 10^3$$

$$ISO\_POS := \frac{R_{ps}^2 \cdot R_{ison} \cdot V_{ref} + R_{ps}^2 \cdot R_{isop} \cdot V_{ref} - HV\_BATT \cdot R_s \cdot R_{ps} \cdot R_{isop} - HV\_BATT \cdot R_s \cdot R_{ison} \cdot R_{isop} + R_s \cdot R_{ps} \cdot R_{ison} \cdot V_{ref} + R_s \cdot R_{ps} \cdot R_{isop} \cdot V_{ref} + 2 \cdot R_{ps} \cdot R_{ison} \cdot R_{isop} \cdot V_{ref}}{R_{ps}^2 \cdot R_{ison} + R_{ps}^2 \cdot R_{isop} + 2 \cdot R_{ps} \cdot R_{ison} \cdot R_{isop}} = 1.084$$

$$ISO\_NEG := \frac{R_{ps}^2 \cdot R_{ison} \cdot V_{ref} + R_{ps}^2 \cdot R_{isop} \cdot V_{ref} + HV\_BATT \cdot R_s \cdot R_{ps} \cdot R_{ison} + HV\_BATT \cdot R_s \cdot R_{ison} \cdot R_{isop} + R_s \cdot R_{ps} \cdot R_{ison} \cdot V_{ref} + R_s \cdot R_{ps} \cdot R_{isop} \cdot V_{ref} + 2 \cdot R_{ps} \cdot R_{ison} \cdot R_{isop} \cdot V_{ref}}{R_{ps}^2 \cdot R_{ison} + R_{ps}^2 \cdot R_{isop} + 2 \cdot R_{ps} \cdot R_{ison} \cdot R_{isop}} = 3.202$$

