

**POWER
MANAGEMENT
DesignLine**

☒ All ☐ Articles ☐ Products ☐ Courses ☐ Papers ☐ News ☐ Webinars

Site Search:

[LOGIN](#) [REGISTER](#) [Welcome, Guest](#) [Home](#) [RSS](#) [Design Center](#) [Learning Center](#) [Product Center](#) [News](#) [Blogs](#) [Forums](#) [Careers](#)

**The power to go from line to load**
Click here for TI's broad line-power portfolio

 **TEXAS
INSTRUMENTS**

**Register
for
Newsletters**

September 30, 2008

Power Tip #4: Damping an Input Filter " Part 2 of 2

Controlling the source impedance

By Robert Kollman, Texas Instruments

In Power Tip #3, we discussed how the source impedance of an input filter can turn resistive, and how it can interact with the negative input impedance of a switching regulator. At worst case, these impedances can be equal in magnitude, but opposite in sign to make an oscillator. A general criterion has been established that the source impedance of an input filter should be at least 6dB less than the [input](#) impedance of a switching regulator as a safety margin to minimize the chance for oscillation.

The design of an input filter usually begins with selection of an input capacitor (CO of Figure 1) based on ripple current rating or hold-up requirements. The next step usually involves selecting an inductor (LO) based on the system's EMI requirements. As we saw last month, near resonance the source impedance of these two elements can be quite high, leading to an unstable system. Figure 1 presents a method to control this impedance by placing a series resistor (RD) and [capacitor](#) (CD) in parallel with the input filter. The filter could be damped with just a resistor across CO. However, in most cases the power loss would be unacceptable. An alternative method is to add a series connection of an inductor and resistor across the filter inductor.

Interestingly, there is an optimum choice of damping resistance once the four other [circuit](#) elements are

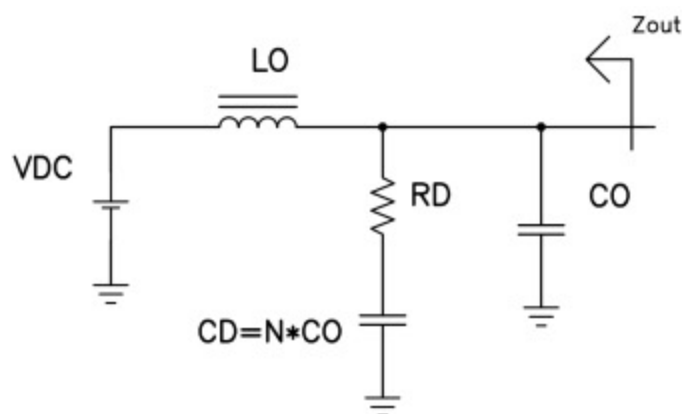


Figure 1: CD and RD damp the [output](#) filter source impedance.
(Click this image to view a larger, more detailed version)

picked. Figure 2 shows the output impedance of this type of filter as the damping resistor is varied. The red curve shows a damping resistor that is too large. Consider an extreme case. If the damping resistor was open, then the peak would be quite high and would be set only by CO and LO. The blue curve shows a damping resistor that is too low. If the resistor was made a short, the resonance would be set by the parallel combination of the two capacitors and the inductor. The green curve represents the optimum value of damping. This value is easily found by numerical methods (Reference 1) that contain the closed form solution.

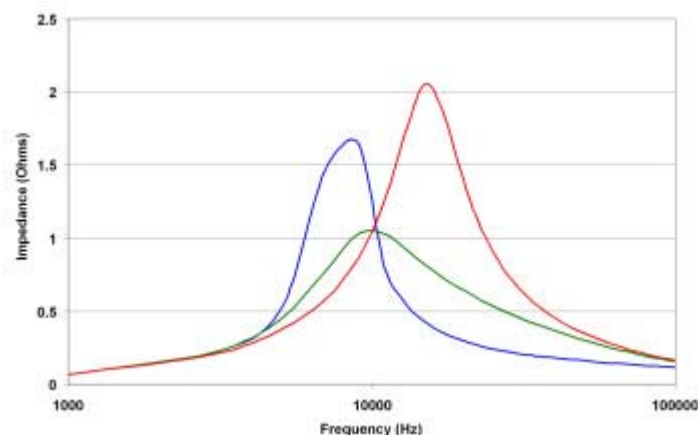


Figure 2: For a given CD to CO ratio, there is an optimum damping resistor.
(Click this image to view a larger, more detailed version)

Figure 3 can be quite useful in selecting the damping components. This chart was prepared using the closed form solution developed by RD Middlebrook. The abscissa is the ratio of the damped filter output impedance to the characteristic impedance of the undamped filter ($Z_O = (LO/CO)^{1/2}$). There are two ordinate values: the ratio of damping capacitor to filter capacitor (N); and the ratio of the damping resistor to the characteristic impedance. To use this chart, first pick LO and CO based on circuit requirements to establish Z_O . Next, establish your maximum input filter source impedance by dividing the minimum [power supply](#) input

impedance by two (or 6dB).

The minimum power supply input impedance is equal to V_{inmin}^2/P_{max} . This lets you calculate an abscissa value. Then simply read the ratio of the damping capacitor to the filter capacitor, and the ratio of the damping resistor to the characteristic impedance. For example, a filter with a 10μH inductor and a 10μF capacitor will have a characteristic impedance of $Z_o = (10\mu H/10\mu F)^{1/2} = 1\text{ Ohm}$. If it were filtering a 12W power supply with 12V minimum input, the power supply input impedance would be $Z = V^2/P = 12^2/12 = 12\text{ Ohms}$. The maximum source impedance should then equal half that, or 6 Ohms. Now enter the chart on the x-axis at $6/1 = 6$. Then read $CD/CO = 0.1$ or 1 μF and $RD/ZO = 3$, or 3 Ohms.

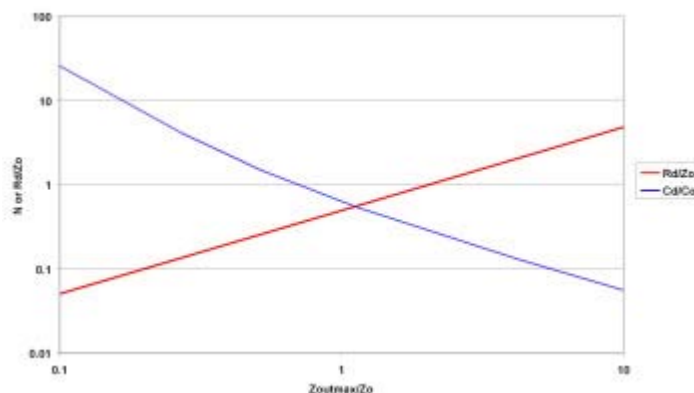


Figure 3: Once you pick LO and Co, choose CD and RD from maximum allowable source impedance.
(Click this image to view a larger, more detailed version)

In Power Tip #5, we will discuss using a buck [controller](#) in a buck-boost power supply.

Reference

1. R.D. Middlebrook, "Design Techniques for Preventing Input-Filter Oscillations in Switched-Mode Regulators," Proceedings Powercon 5, 1978.

The Power Tips! series

- #1, July: [Picking the right operating frequency for your power supply](#)
- #2, August: [Taming a noisy power supply](#)
- #3, September: [Damping the input filter --- Part 1](#)



Robert Kollman is a Senior Applications Manager and Distinguished Member of Technical Staff at Texas Instruments. He has more than 30 years of experience in the power electronics business and has designed magnetics for power electronics ranging from sub-watt to sub-megawatt with operating frequencies into the [megahertz](#) range. Robert earned a BSEE from Texas A&M University, and a MSEE from Southern Methodist University.

Portable Power Applications
Portable power made simple
Click here for TI's portable power IC portfolio

TechOnline Communities

Audio DesignLine | Automotive DesignLine | CommsDesign | Digital Home DesignLine | DSP DesignLine | EDA DesignLine
eeProductCenter | [Green SupplyLine](#) | Industrial Control DesignLine | Mobile Handset DesignLine | Planet Analog | Power Management DesignLine
Programmable Logic DesignLine | RF DesignLine | Teardown.com | TechOnline | Video/Imaging DesignLine | Wireless Net DesignLine

EE Times

United States | Asia | China | Europe | France | Germany | India | Japan | Korea | Taiwan | United Kingdom | EE Times Supply Network

Additional Network Sites

Analog Europe | Automotive Designline Europe | DeepChip | Design & Reuse | Elektronik iNorden | Embedded.com

| Microwave Engineering Europe | Portelligent | Power Management Designline Europe
The RF Edge | Semiconductor Insights | Embedded-europe.com | Mechanical Design | TechOnline India

All materials on this site [Copyright © 2009 TechInsights, a Division of United Business Media LLC](#) All rights reserved.

[Privacy Statement](#) | [Terms of Service](#)