

Design Methods of Modern Ultra-Low-Noise Synthesizers

This first article in a multi-part series on modern synthesizers describes basic phase-locked-loop operation along with various topologies.


Recent years have seen major changes in the frequency synthesis art. Ultra-low-noise discrete VCOs, the heart of low noise synthesizers for decades, now find themselves challenged by integrated VCOs. The best discrete VCOs still enjoy 20-30 dB phase-noise superiority, but IC companies are conducting an asymmetric battle to dominate the market with full integration based not on the best VCO noise, but on architectural innovations that often render free-running VCO noise less important.

This is achieved by putting good VCOs on die, suppressing that noise down to a very low level via feedback, and then dividing down to the application band for a further phase noise reduction. The challenge now facing discrete VCO suppliers is to extend the outstanding phase noise they get in application bands to higher frequency where they also can get the full architectural benefit of the latest synthesizer innovations.

This first article of a five-article series will review modern advanced design methods. This is the on-line version, which is moderately more complete than the printed version. See the publications page at www.longwingtech.com for considerably more detailed versions of these articles. The next four articles in this series will cover detailed noise analysis (2 articles), key parts and tools for low noise implementation, and examples requiring low noise that illustrate current state of the art performance.

Basic PLL Operation and 2nd-Order Normalized Form

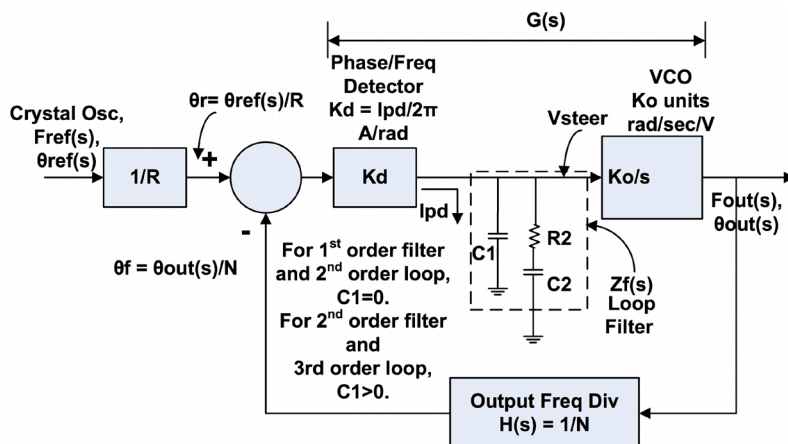The standard second-order form of PLL design that is presented in most classic text books allows for approximate but still useful design and analysis equations, and a simple de-




1. This is a depiction of the second- and third-order charge pump PLL synthesizer ($C_1 = 0$ for second-order). Frequency is set by firmware via the programmable R and N dividers.

scription of loop operation.

We are used to thinking primarily of voltage and current as the feedback quantities, but in addition to those the PLL also treats phase and frequency as small signal frequency domain variables. When seeking lock over a wide frequency range, the modern phase/frequency detector (PFD) acts as a frequency detector to steer the voltage-controlled oscillator (VCO) towards lock. As frequency converges, the loop transitions to a phase locked mode where phase as a time difference between digital edges is driven to zero.

Since frequency is the time derivative of changing phase ($\omega = d\theta/dt$), phase is the integral of frequency. Thus, the VCO acts as an integrator of input voltage to output phase, which introduces -90 degrees of phase shift. That is why its transfer function is in the form K_o / s , the standard frequency domain representation of an integrator. K_o is here given in units of rad/sec/volt. VCO datasheets will normally give K_o in units of MHz/V. To be clear in this article series, we will refer to the Hz/V form as K_{Hz} and the radian form as K_o , so $K_o = 2\pi K_{Hz}$.

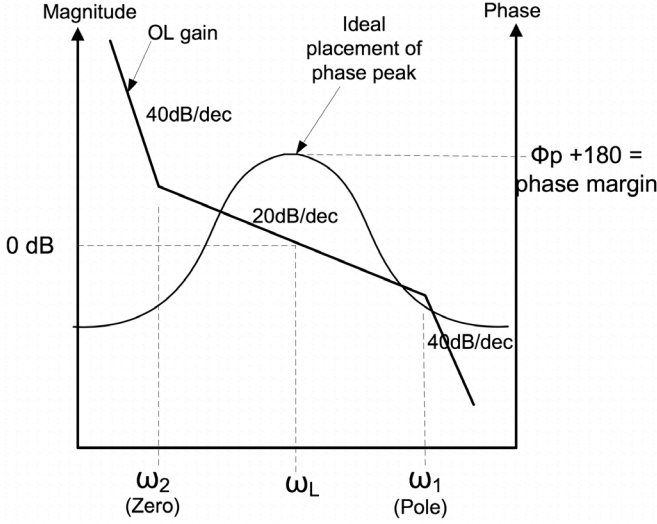

2. Shown is open-loop gain and phase in the properly designed third-order PLL. The maximum phase is forced to occur at the loop bandwidth by the design.

With the -90 deg phase shift and the -180 degrees of negative feedback, we only have a maximum of 90 degrees of filtering phase shift allowed before -360 degrees total would result in instability. We normally leave a minimum of 40 degrees of “phase margin” at the loop bandwidth. This margin comes from the zero introduced by resistor R_2 , as without it the charge pump driving a capacitor would also be an integrator.

Now we may review basic analysis. The classic “phase transfer function” of the loop as given in older references (such as Refs. 8 and 9) is defined here as:

$$H_{classic}(s) = \frac{\theta_{out}/N}{\theta_{ref}} \quad (1)$$

$H_{classic}(s)$ is the *closed-loop* transfer function from the reference input on the phase detector to the feedback input, usually referred to as simply “H(s)” in classic references. This subscript is used to clearly distinguish from the “H” that is used as part of the *open-loop* transfer function in most modern literature. From the figure above, if we solve for this relationship by “substituting around the loop” using the relations established in the figure, we obtain:

$$H_{classic}(s) = \frac{\frac{K_{ol}I_{pd}R}{2\pi N}s + \frac{K_{ol}I_{pd}}{2\pi NC}}{s^2 + \frac{K_{ol}I_{pd}R}{2\pi N}s + \frac{K_{ol}I_{pd}}{2\pi NC}} \quad (2)$$

This equation is in a familiar control system form where we may extract standard parameters that aid in understanding and in calculations. The standard normalized form of the second-order system is given by:

$$H_{classic}(s) = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (3)$$

The two equations are in the same form, and by equating terms we obtain the following analysis equations:

$$\omega_n = \sqrt{\frac{K_{ol}I_{pd}}{2\pi NC}} = \sqrt{\frac{K_{Hz}I_{pd}}{NC}} \quad (4)$$

$$\zeta = \frac{K_{ol}I_{pd}R}{4\pi N\omega_n} = \frac{K_{Hz}I_{pd}R}{2N\omega_n} \quad (5)$$

The term ω_n is the “natural” frequency, and is close to but generally not equal to the open-loop bandwidth (see the publications page at www.longwingtech.com for the long form of this article giving the exact relationship between ω_n , ζ , and loop bandwidth). When settling, the transient response “rings down” at the natural frequency. The term ζ is the “damping factor” and must be greater than zero for stability. Normally damping factor is set to about 0.5, which will give about 45 degrees of phase margin, or about 0.7 to 1 when an additional filtering pole is added.

Again, referring to Refs. 8 and 9, the common PLL “error transfer function” is defined as:

$$H_e(s) = \frac{\theta_{ref} - (\theta_{out}/N)}{\theta_{ref}} \quad (6)$$

$H_e(s)$ may also be represented in the standard normalized form of control theory as:

$$H_e(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (7)$$

$H_e(s)$ is a high pass function, whereas the phase transfer function $H_{classic}(s)$ is low pass. It is quickly shown from above that:

$$H_e(s) = 1 - H_{classic}(s) \quad (8)$$

It will turn out that many of the modulation and noise responses of PLLs can be conveniently expressed using these functions, which is a great aid in understanding how the loop shapes noise. For example, phase or phase noise variation on the reference input to the phase detector will transfer to the VCO output proportional to the phase transfer function. Since phase transfer function is low pass, above the loop bandwidth there will be suppression of this noise or modulation. The suppression of voltage-controlled oscillator phase noise inside the loop bandwidth will be according to the $H_e(s)$ function given just above, down to the limits of divider noise, charge pump noise, and crystal reference noise (to be analyzed in articles 2 and 3).

From the analysis equations just above, we obtain the following design equations:

$$C_2 = \frac{K_o I_{pd}}{2\pi N \omega_n^2} = \frac{K_{Hz} I_{pd}}{N \omega_n^2} \quad (9)$$

$$R_2 = \frac{4\pi N \omega_n \zeta}{K_o I_{pd}} = \frac{2N \omega_n \zeta}{K_{Hz} I_{pd}} \cong \frac{N \omega_L}{K_{Hz} I_{pd}} \quad (10)$$

These equations are used to determine R and C based upon chosen values for natural frequency and damping factor. When extra filtering poles are introduced these values will change (particularly the capacitor), but they are still very useful starting points and serve well for many approximations such as settling time, pull out range, and finding minimum possible thermal noise in the loop filter.

The 3rd-Order Passive Filter PLL

This form is the simplest highly usable form, and is attained by adding another capacitor C_1 as shown in Refs 6 and 7. Introducing another filter pole will eventually cancel out the zero. This means that there will be a frequency where phase peaks and then declines, as shown in Figure 2.

The loop filter impedance is:

$$Z(s) = \frac{1+sT_2}{s A_0(1+sT_1)} \quad (11)$$

A half page of circuit analysis will establish:

$$T_2 = R_2 C_2 \quad (12)$$

$$T_1 = \frac{R_2 C_2 C_1}{A_0} \quad (13)$$

$$A_0 = C_1 + C_2 \quad (14)$$

The open-loop gain function is given by (see figures for G and H):

$$GH(j\omega) = \frac{K_d K_o}{-N} \frac{1+j\omega T_2}{\omega^2 A_0(1+j\omega T_1)} \quad (15)$$

We know K_d , K_o , and N , and choose loop bandwidth ω_L and phase margin ϕ_m . To find our three unknowns A_0 , T_1 and T_2 , we need three equations. We get them from the magnitude of GH (which is 1 at ω_L), the phase of GH (which gives ϕ_m at ω_L), and the derivative of the phase of GH with respect to ω (which is zero at ω_L). This is the basic methodology referred to here as the modern technique.

The magnitude of GH is:

$$|GH(j\omega)| = \frac{K_d K_o}{N A_0 \omega^2} \frac{\sqrt{1+\omega^2 T_2^2}}{\sqrt{1+\omega^2 T_1^2}} \quad (16)$$

At $\omega = \omega_L$ this magnitude is 1, and we have:

$$A_0 = \frac{K_d K_o}{N \omega_L^2} \frac{\sqrt{1+\omega_L^2 T_2^2}}{\sqrt{1+\omega_L^2 T_1^2}} \quad (17)$$

The phase margin expressed as a positive number from 0 to 90 degrees is the difference between the open-loop phase and 180 degrees, which is:

$$\phi_m = \tan^{-1}(\omega_L T_2) - \tan^{-1}(\omega_L T_1) \quad (18)$$

Taking the derivative of phase margin with respect to variable frequency, and setting it to zero at $\omega = \omega_L$:

$$\frac{T_2}{1+\omega_L^2 T_2^2} - \frac{T_1}{1+\omega_L^2 T_1^2} = 0 \quad (19)$$

We now have two nonlinear equations in the two unknowns T_1 and T_2 . We may solve these numerically, but there is a closed form solution (Ref. 3, pp. 32-36):

$$T_1 = \frac{\frac{1}{\cos \phi_m} - \tan \phi_m}{\omega_L} \quad (20)$$

$$T_2 = \frac{1}{\omega_L^2 T_1} \quad (21)$$

$$\omega_L = \sqrt{\omega_1 \omega_2} \quad (22)$$

Now we may find the circuit values:

$$C_2 = A_0 \left(1 - \frac{T_1}{T_2}\right) \quad (23)$$

$$C_1 = A_0 - C_2 \quad (24)$$

$$R_2 = \frac{T_2}{C_2} \quad (25)$$

The 2nd-order filter (3rd-order loop) is the lowest noise filter form. However, pushing bandwidth out typically requires additional poles of filtering to keep phase detector noise from contaminating VCO noise.

The 4th-Order Passive Filter PLL

This form uses the 3rd-order filter shown in Figure 3, and is likely the most common filter form.


The open-loop transfer function is given by:

$$GH(j\omega) = \frac{K_d K_o}{-N} \frac{1+j\omega T_2}{\omega^2 A_0(1+j\omega T_1)(1+j\omega T_3)} \quad (26)$$

The filter (transfer) impedance that is part of the above is given by:

$$Z(s) = \frac{1+sT_2}{s A_0(1+sT_1)(1+sT_3)} = \frac{1+sC_2 R_2}{s (A_2 s^2 + A_1 s + A_0)} \quad (27)$$

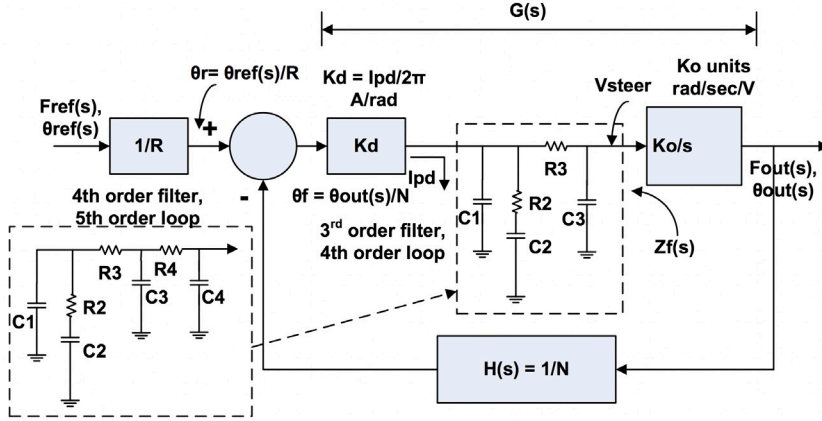The coefficients A_1 and A_2 are useful abbreviations for lengthy functions of parts values. (see long version)



3. Here are the fourth- and fifth-order PLL forms.

$$A_0 = C_1 + C_2 + C_3 \quad (28)$$

Using the magnitude function of the open-loop transfer function:

$$A_0 = \frac{K_d K_o}{N \omega_L^2} \frac{\sqrt{1 + \omega_L^2 T_2^2}}{\sqrt{(1 + \omega_L^2 T_1^2)(1 + \omega_L^2 T_3^2)}} \quad (29)$$

We next define what Banerjee calls “pole ratios,” which shall be selected by the designer based upon factors such as spur rejection. Technically these would be more properly referred to as time constant ratios, but we shall stay with the now established terminology of calling them pole ratios.

$$T_{31} = \frac{T_3}{T_1} = \frac{\omega_1}{\omega_3} = \frac{f_1}{f_3} \quad (30)$$

T_{31} is determining how spaced out the added pole is. We must use $T_{31} < 1$, and find that 0.5 buys almost all the possible spur suppression that is practically possible.

The phase margin of the open-loop transfer function is given by:

$$\phi_m = \tan^{-1}(\omega_L T_2) - \tan^{-1}(\omega_L T_1) - \tan^{-1}(\omega_L T_{31} T_1) \quad (31)$$

The phase margin occurs at the peak of the phase-margin function. Taking this derivative with variable frequency, and then applying the first derivative test with $\omega = \omega_L$:

$$\frac{T_2}{1 + \omega_L^2 T_2^2} - \frac{T_1}{1 + \omega_L^2 T_1^2} - \frac{T_{31} T_1}{1 + \omega_L^2 T_{31}^2 T_1^2} = 0 \quad (32)$$

After selecting the pole ratio T_{31} , the above two equations may be solved numerically for T_2 and T_1 , thus allowing $T_3 = T_{31} T_1$.

Now we come to the “Gamma Optimization Factor” used by Banerjee. This quantity allows approximation, with addi-

tional information on its importance given in the long version at www.longwingtech.com. We may extend the earlier expressions for T_2 in approximate form to higher-order loops (Ref. 7, 5th ed, p.309), at the same time defining γ :

$$T_2 = \frac{\gamma}{\omega_L^2 (T_1 + T_3)} = \frac{\gamma}{\omega_L^2 T_1 (1 + T_{31})} \quad (33)$$

This parameter is normally close to 1 in practical designs—in the range of 0.7 to 1.3.

Substituting, we get this approximation (leaving the 180 deg. off to convert from phase to phase margin):

$$\phi_m = \tan^{-1}\left(\frac{\gamma}{\omega_L T_1 (1 + T_{31} + T_{41})}\right) - \tan^{-1}(\omega_L T_1) - \tan^{-1}(\omega_L T_{31} T_1) \quad (34)$$

The above has only T_1 to be solved for. An approximation can be found using $\tan^{-1}(x) \sim x$ for small x . The result is:

$$T_1 \cong \frac{\frac{1}{\cos \phi_m} - \tan \phi_m}{\omega_L (1 + T_{31})} \quad (35)$$

The other two time constants follow immediately.

$$T_3 = T_1 T_{31} \quad (36)$$

When using the approximate approach:

$$T_2 \cong \frac{\gamma}{\omega_L^2 (T_1 + T_3)} \quad (37)$$

We find A_1 and A_2 from:

$$A_1 = A_0 (T_1 + T_3) = C_2 C_3 R_2 + C_1 C_2 R_2 + C_1 C_3 R_3 + C_2 C_3 R_3 \quad (38)$$

$$A_2 = A_0 T_1 T_3 = C_1 C_2 C_3 R_2 R_3 \quad (39)$$


We have the four equations for five values C_1 , C_2 , C_3 , R_2 , and R_3 . The method adopted by Banerjee to get a 5th equation is to find the largest C_3 that satisfies these equations. The above may be manipulated to find C_3 :

$$C_3 = \frac{-T_2^2 C_1^2 + T_2 A_1 C_1 - A_2 A_0}{T_2^2 C_1 - A_2} \quad (40)$$

Applying the first derivative test for the value of C_1 that peaks C_3 :

$$C_1(\max C_3) = \frac{A_2}{T_2^2} \left(1 + \sqrt{1 + \frac{T_2}{A_2} (T_2 A_0 - A_1)}\right) \quad (41)$$

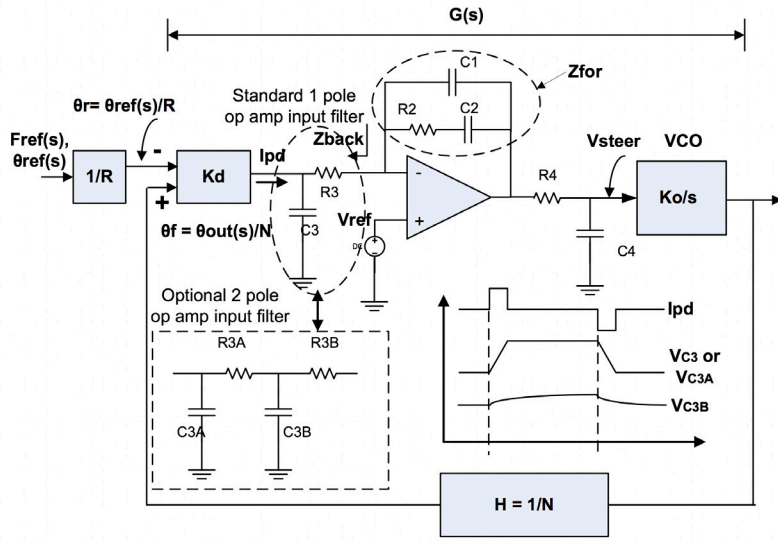Everything needed to find C_1 is known, and it may be



4. This is the active fourth-order filter and fifth-order PLL, with option for fifth-order filter. This filter is referred to as a “slow slew” active filter, as the input RC reduces speed requirements. Bandwidth limits of the op amp may still make it advantageous to use the two-pole input filter option, converting the filter to fifth order and the loop to sixth order.

plugged into Equation 40 to find C_3 . Then the final values are found from:

$$C_2 = A_0 - C_1 - C_3 \quad (42)$$

$$R_2 = \frac{T_2}{C_2} \quad (43)$$

$$R_3 = \frac{A_2}{C_1 C_3 T_2} \quad (44)$$

Passive Filter 5th-Order PLLs

The addition of an extra RC stage can provide moderate improvement in far out spur rejection over the 3rd-order filter. Speaking very approximately, the benefit of the 3rd-order loop filter over the 2nd is about 2 to 7 dB, while the benefit of the 4th-order filter over the 3rd is about 1-3 dB (Ref. 7, 5th ed, p. 324). See the long version of this article at www.longwingtech.com for more details.

Op-Amp Active Filter PLLs

The primary reason for using an op amp is to extend the voltage range of the loop filter to allow VCOs with large tune ranges (since passive loop filters are limited to the relatively low synthesizer IC charge pump output range). This allows for lower K_0 and lower noise, as will be shown in articles 2 and 3. The op amp also allows smaller, lower noise resistors and placing the lowest pole after the op amp. There are several topologies for active loop filters, but here a single preferred version (Fig. 4) is given in full 4th-order form.

A low-noise dc reference voltage is provided at the positive input of the op amp, and the combination of loop action

and op amp action will be to keep the negative input of the op amp at this same voltage. In this form the op amp output will “pump up” via current flowing through Z_{for} to assume whatever voltage is needed to maintain lock. The part values can be selected so that this inverting form suffers only small noise gain (to come in article 2).

For transfer impedance $Z(f)$ we find:

$$Z(s) = \frac{V_{out}}{I_{pd}} = \frac{1+sT_2}{s A_0(1+sT_1)(1+sT_3)(1+sT_4)} \quad (45)$$

An importance point is that T_4 shall be the lowest frequency pole.

We also find:

$$A_0 = C_1 + C_2 \quad (46)$$

The open-loop gain as a function of $j\omega$ is:

$$GH(j\omega) = \frac{K_d K_0}{-N} \frac{1+j\omega T_2}{\omega^2 A_0 (1+j\omega T_1)(1+j\omega T_3)(1+j\omega T_4)} \quad (47)$$

Using the magnitude function of the open-loop transfer function (1 at loop BW):

$$A_0 = \frac{K_d K_0}{N \omega_L^2} \frac{\sqrt{1+\omega_L^2 T_2^2}}{\sqrt{(1+\omega_L^2 T_1^2)(1+\omega_L^2 T_3^2)(1+\omega_L^2 T_4^2)}} \quad (48)$$

To maintain one set of equations whether f_1 or f_3 is lower, we refer both higher frequency poles to the lowest pole f_4 .

To evaluate A_0 , we need T_4 and T_2 , and then use the selected pole ratios to get T_1 and T_3 . The exact equations are:

$$\phi_m = \tan^{-1}(\omega_L T_2) - \tan^{-1}(\omega_L T_4) - \tan^{-1}(\omega_L T_{14} T_4) - \tan^{-1}(\omega_L T_{34} T_4) \quad (49)$$

The max phase margin occurs at the peak of the phase margin function, where we substitute $\omega = \omega_L$ after taking the derivative in the first derivative test:

$$\frac{T_2}{1+\omega_L^2 T_2^2} - \frac{T_1}{1+\omega_L^2 T_4^2} - \frac{T_{14} T_4}{1+\omega_L^2 T_{14}^2 T_4^2} - \frac{T_{34} T_4}{1+\omega_L^2 T_{34}^2 T_4^2} = 0 \quad (50)$$

Now these two may be solved numerically for T_2 and T_4 , leading then to T_1 and T_3 via the selected pole ratios (usually around 0.5 for the lowest pole above f_4 and 0.25 for the next pole, relative to T_4). The below approximations may be used as starting points for the numerical solutions, or used as is.

$$\phi_m = \tan^{-1}\left(\frac{\gamma}{\omega_L T_4(1+T_{14}+T_{34})}\right) - \tan^{-1}(\omega_L T_4) - \tan^{-1}(\omega_L T_{14} T_4) \tan^{-1}(\omega_L T_{34} T_4) \quad (51)$$

We may use $\gamma = 1$, or alter it from 1 based on the optimiza-

tion criteria in Banerjee 5th ed, chapter 36. The only variable remaining is T_4 , which may be solved numerically, or approximately:

$$T_4 \cong \frac{\frac{1}{\cos \phi_m} - \tan \phi_m}{\omega_L(1+T_{14}+T_{34})} \quad (52)$$

If the approximate form is used, then:

$$T_2 \cong \frac{\gamma}{\omega_L^2(T_1+T_3+T_4)} \quad (53)$$

In either case:

$$T_1 = T_{14} T_4 \quad (54)$$

$$T_3 = T_{34} T_4 \quad (55)$$

We now have all the variables needed to find $A_0 = C_1 + C_2$. We may then find all the part values in Z_{for} from:

$$C_1 = \frac{T_1 A_0}{T_2} \quad (56)$$

$$C_2 = A_0 - C_1 \quad (57)$$

$$R_2 = \frac{T_2}{C_2} \quad (58)$$

Now we select the values for R_3 , C_3 , R_4 , and C_4 , which seems easy as we have their time constants, but there are some subtle complexities at work here, including op amp limits to deal with.

On the input side of the op amp it might seem that smaller R_3 would help with noise, but actually the opposite is true. The thermal noise of R_3 is going up with its square root, whereas its noise gain is going down with R_3 , so that the noise of R_3 on the op amp output is going down with its square root. So, we tend to select the largest R_3 that other limits allow, as follows.

Banerjee gives (Ref. 7, 5th ed, p.38) the duty cycle of the phase-frequency detector in frequency-lock mode as a function of the ratio of f_{ref} and f_{out}/N as:

$$D_c = 1 - \frac{f_{\text{lower}}}{f_{\text{upper}}} \quad (59)$$

In the above f_{lower} is the smaller of f_{ref} and f_{out}/N . Since most VCOs do not steer far in a fractional sense from their center frequency, the duty cycle would seldom range above 10% (octave-type VCOs being the exception).

Let us define ΔV_{mc3} as the max filtered voltage change from V_{ref} that we wish to be imposed (such as to comply with op amp input requirements) on C_3 during a frequency-lock acquisition event. We may thus write a relationship for $R_{3\text{max}}$ as:

$$R_{3\text{max}} = \frac{\Delta V_{\text{mc3}}}{D_c I_{\text{pd}}} \quad (60)$$

Additionally, we need to beware of slew rate limits. Banerjee

offers experimental evidence (Ref. 7, 5th ed., pp.371-372) that if the op amp is not fast enough there will be worsening of 1/f phase noise inside the loop bandwidth (typically a few dB). There are four slew rate cases derived in long version (see the publications page at www.longwingtech.com), two in frequency acquisition mode (for lock speed) and two in PLL mode (for noise control). The worst case (highest) requirement on slew rate is usually the frequency-locking case towards the end of the frequency lock process given by:

$$\text{ReqSlewRateFLL}(R_2 \text{ limited}) \cong \frac{D_{c\text{max}} I_{\text{pd}} R_2}{C_3 R_3} \quad (61)$$

Furthermore, bandwidth limits of the op amp are an issue, but this can be mitigated by the two-pole input filter option. This allows the op amp to be “cocooned” within filtering that prevents signals beyond its specified bandwidth from reaching it. This would seem to be a more logical strategy than the typical GBW > 10X loop bandwidth that is often assumed with op amp circuits. See the long version for further discussion.

Next, we consider the op amp output current limits on C_4 . We are used to seeing strict load limits on op amps, but many can drive loads of 10 Ω and even less when those loads are DC isolated, even against large capacitance. But, with a large frequency change on the PLL, that capacitance does take large current that may exceed the op amp max in the range of 10mA to 100mA. Fundamentally, we desire the op amp max current I_{opmax} to be able to charge C_4 at the same rate that $D_c \cdot I_{\text{pd}}$ charges C_2 during a large frequency change. Using $I \cdot t = CV$:

$$C_{4\text{max}} = \frac{I_{\text{opmax}} C_2}{D_c I_{\text{pd}}} \quad (62)$$

This maximum is sometimes more than we would like to use for reasons of size and cost, and may lead to resistor values too small for the op amp even when dc isolated. In that case we select a value of R_4 whose thermal noise is considerably less than the noise of the op amp, and then find $C_4 = T_4/R_4$.

What's Next

The transfer function approach shown here is enabling to showing noise sources and shaping in articles 2 and 3, along with showing the key innovations driving full integration, and how discrete VCO makers can fight back. Article 4 will show key parts and CAD tools that are the weapons of the low noise synthesizer designer. Article 5 will put it all together with requirements and examples of integrated and discrete VCO synthesizers to meet them.

Acknowledgments

The author expresses his appreciation for the valuable reviews, comments and information provided by Adnaan Khan, Joe Bouchez of Lonestar III Five Designs, Dean Banerjee at

Texas Instruments, C.Y. Teng and Miguel Troester at Taitien, and Ulrich Rohde, Ajay Poddar, and Bill Becker at Synergy Microwave.

FARRON DACUS is an RF design consultant in Dallas, Texas. He received his BSEE and MSEE from the University of Texas, and he has over 30 years of experience ranging from ICs to circuits to systems in low noise RF, short range radio/IoT, cellular, military communications, and aircraft radios. He may be reached at farron.dacus@longwingtech.com.

References

1. “Analyze, Don’t Estimate Phase-Locked Loop Performance of Type 2 Third Order Systems,” *Electronic Design*, May 1978. This is one of the earliest public references to design with higher-order loop filters.

2. “Digital PLL Synthesis,” National Semiconductor Application Note 335, 1983.

3. *Digital PLL Frequency Synthesizers: Theory and Design*, Ulrich L. Rohde, Prentice-Hall, 1983. This excellent book is a rare example of a classic reference that presents higher-order loop filters in addition to 2nd-order normalized form, and also presents the closed loop suppression of free running VCO phase noise. Rohde is one of the historical leaders of the frequency source field both in publications and in industry.

4. *Microwave and Wireless Synthesizers: Theory and Design*, Ulrich L. Rohde, John Wiley and Sons, 1997. This book is an update to the Rohde text just above.

5. “Introduction to Modern Signal Generation; from Analog to Digital: Needs, Advantages, Disadvantages, and “Solutions,” Ulrich L. Rohde, an extensive industry white paper, available from https://badw.de/fileadmin/members/R/3685/6_4_18_UNI_BW_June18-safe.pdf. This reference is particularly valuable for its combination of methods from basic to advanced, and resulting final limits.

6. “An Analysis and Performance Evaluation of a Passive Filter Design Technique for Charge Pump PLL’s,” National Semiconductor Application Note 1001, 1996, by Bill Keese. Though this reference was not the first to analytically present higher-order loop filters, it became widely available via the early internet and had a strong influence.

7. *PLL Performance, Simulation, and Design*, Dean Banerjee, first edition 1998 and 2001. The focus of this outstanding book is modern design focusing on synthesizers with high-order loops and noise prediction using the normalized noise floor of the particular synthesizer chip to take into account divider and charge pump noise. It is currently in its 5th edition, published 2017, covering sigma delta synthesizers and their spur control methods in high detail. Author Dean Banerjee is an electrical engineer and applied mathematician who was deeply involved in the National Semiconductor effort to build a powerhouse synthesizer IC business (now owned by Texas

Instruments), and this groundbreaking book reflects both his detailed insider knowledge and his ability to distill practical design methods with tractable mathematics from the complexity of low noise synthesizer design. The 5th edition of 2017 may be freely downloaded in PDF form at: http://www.ti.com/tool/pll_book.

8. *Phaselock Techniques*, 2nd Ed, Floyd Gardner, John Wiley and Sons, 1979. A highly respected classic work, though lacking in modern filter and noise analysis methods in early versions. The 3rd edition of 2005 does cover 3rd-order loops (the addition of one filter pole to the 2nd-order form).

9. *Phase Locked Loops, Third Edition*, Roland Best, McGraw-Hill, 1997. A valuable classic reference, though lacking coverage of higher-order loop filter methods in early editions. The 5th edition of 2003 has a chapter devoted to higher-order loops, and is available online for free download in PDF form at <http://ebook-dl.com/book/90836>. The 6th edition came out in 2007 and is still in print.