

CDCI6214 and CDCE6214-Q1 design with crystal input

Hao Zheng

ABSTRACT

CDCI6214 and CDCE6214-Q1 incorporate a crystal driver circuit that can drive an external crystal resonator (XTAL). Design procedures related to crystal input are explained in this article. Both CDCI6214 and CDCE6214-Q1 share the same crystal driver circuit. This appnote assumes basic understanding of crystal resonators and crystal oscillators.

Contents

| | | |
|---|--|---|
| 1 | Introduction | 1 |
| 2 | Crystal circuit design description | 2 |
| 3 | Bench measurement examples | 5 |
| 4 | Design procedures summary..... | 6 |

List of Figures


| | | |
|---|--|---|
| 1 | XTAL input schematic..... | 2 |
| 2 | XTAL equivalent circuit | 2 |
| 3 | Load capacitance illustration diagram..... | 5 |

List of Tables

| | | |
|---|--|---|
| 1 | g_m table..... | 3 |
| 2 | Available negative resistance divided by 3..... | 3 |
| 3 | Drive Level vs Bias Current With 25MHz crystal | 4 |
| 4 | Drive level vs bias current with 50MHz crystal | 4 |
| 5 | Measured maximum ESR to start oscillation..... | 6 |

1 Introduction

A simplified circuit for crystal input is shown in [Figure 1](#). A crystal in series with R_s is connected to Pin 1 and Pin 2 of CDCI6214 / CDCE6214-Q1, where R_s is series resistor used to reduce drive level. C_{L1} and C_{L2} are two single ended load capacitors used to control initial frequency accuracy of the crystal. $-R$ is called "negative resistance". It's generated by the active circuit inside the chip and can effectively "cancel out" the positive resistance in order for the crystal to start and maintain oscillation.

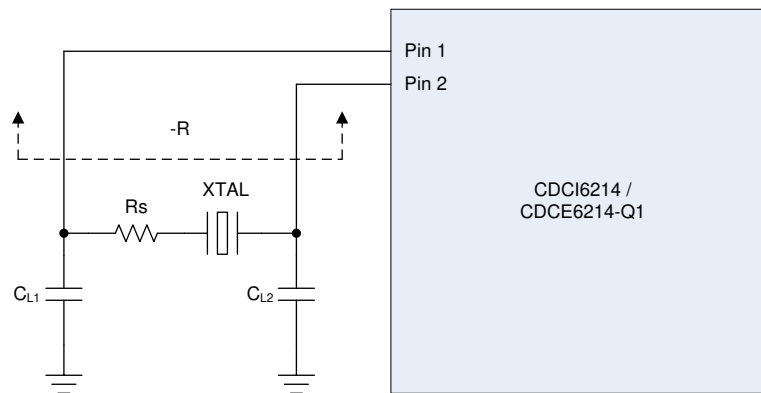
Figure 1. XTAL input schematic

The goals of crystal circuit design are:

1. To make sure that crystal oscillates. This requires the $-R$ to be large enough to provide sufficient power for crystal to oscillate.
2. Not to overdrive the crystal. This requires the $-R$ not to be so large that crystal is overdriven. The consequences of overdriving a crystal are reduced lifetime, accelerated aging and unwanted spurs. R_s is used to reduce power dissipation when drive level is too high. Crystal vendors typically specify maximum drive level which should not be violated.
3. To minimize crystal frequency error. Crystal vendors typically require load capacitance (C_L) of a certain value in order to achieve frequency accuracy. If C_L is too low, actual frequency will be higher than the target frequency, and vice versa.


Based on above discussion, in order to design a circuit for crystal input, designer needs to decide the value of R_s as well as C_{L1} and C_{L2} . Further, CDCI6214 / CDCE6214-Q1 provide controllable driver bias current and programmable internal load capacitance, which make the design much easier once the user understands how it works. This will be explained in detail in later sections.

2 Crystal circuit design description

2.1 Negative resistance and oscillation criteria

For a successful crystal circuit design, the first step is to make the crystal oscillate. This subsection explains the oscillation criteria of a crystal and how to design with sufficient margin. To start with, let's review the concepts of ESR (Equivalent Series Resistance) and negative resistance.

Shown in [Figure 2](#), a crystal resonator can be modeled as an RLC circuit. An RLC circuit cannot start or maintain oscillation without external supply because motional resistance (R_m) is lossy and dissipates power. Therefore, an active network is needed for crystal to oscillate.

 
Figure 2. XTAL equivalent circuit

As mentioned before, a crystal driver provides an equivalent "negative resistance" ($-R$) to effectively eliminate the real part ($ESR + R_s$). Although *during* oscillation the total impedance is purely imaginary -- meaning that magnitude of $-R$ is equal to $ESR + R_s$, in order for the XTAL to *start* oscillation, $-R$ needs to be larger than that. A rule of thumb for an oscillator to start oscillating is:

$$\text{abs}(-R) = (3 \sim 5) * (ESR + R_s) \quad (1)$$

Meaning that the magnitude of -R should be 3 to 5 times larger than the real part of crystal + Rs. A factor of 3 is the minimum requirement. A factor of 5 is usually recommended for good margin.

ESR can be estimated using [Equation 2](#), where C_0 is shunt capacitance shown in [Figure 2](#). If R_m or C_0 values are unavailable, simply use the max ESR specified in crystal datasheet for a rough estimation.

$$ESR = R_m \left(1 + \frac{C_0}{C_L} \right)^2 \quad (2)$$

-R can be calculated using [Equation 3](#), where ω is angular resonant frequency in rad/s, and g_m values for CDCI6214 / CDCE6214-Q1 are provided in [Table 1](#).

$$-R = - \frac{g_m}{(2\omega C_L)^2} \quad (3)$$

Notice how -R is related to resonant frequency and load capacitance. The higher the frequency and the larger the C_L , the smaller the magnitude of -R, meaning that there is typically less margin of negative resistance at high frequency and with large load capacitance and vice versa.

Table 1. g_m table

| R26[5:2] of CDCI6214 or R24[5:2] of CDCE6214-Q1 | Bias Current (uA) | gm (mS) |
|---|-------------------|---------|
| 0x0 | 0 | NA |
| 0x1 | 14 | 0.02 |
| 0x2 | 29 | 0.38 |
| 0x3 | 44 | 0.71 |
| 0x4 | 59 | 1.01 |
| 0x5 | 148 | 1.3 |
| 0x6 | 295 | 2.83 |
| 0x7 | 443 | 4.92 |
| 0x8 | 591 | 6.66 |
| 0x9 | 884 | 8.18 |
| 0xA | 1177 | 10.7 |
| 0xB | 1468 | 12.78 |
| 0xC | 1758 | 14.53 |

[Table 2](#) shows calculation results using common resonant frequencies (25MHz, 40MHz and 50MHz) and load capacitances (18pF, 12pF and 8pF) based on [Equation 3](#) with a factor of 3. The max ESR of a crystal should not be higher than the numbers listed in this table. A factor of 4 or 5 is recommended for sufficient margin.

Keep in mind that the crystal driver starts to saturate when 1177uA or higher bias current is chosen. [Equation 3](#) should only be applied to bias current below 1177uA. Avoid using 1468uA and 1758uA unless necessary, because with these bias currents, the magnitude of actual -R is lower than what is predicted using the equation. This will be better demonstrated with bench measurement results in later sections.

Table 2. Available negative resistance divided by 3

| Bias current (uA) | $C_L = 18pF$ | | | $C_L = 12pF$ | | | $C_L = 8pF$ | | |
|--------------------|--------------|-------|-------|--------------|-------|-------|-------------|-------|-------|
| | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz |
| 295 ⁽¹⁾ | 30 | 12 | 7 | 66 | 26 | 17 | 149 | 58 | 37 |
| 443 | 51 | 20 | 13 | 116 | 45 | 29 | 260 | 102 | 65 |
| 591 | 69 | 27 | 17 | 156 | 61 | 39 | 352 | 137 | 88 |
| 884 | 85 | 33 | 21 | 192 | 75 | 48 | 432 | 169 | 108 |
| 1177 | 112 | 44 | 28 | 251 | 98 | 63 | 565 | 221 | 141 |
| 1468 | 133 | 52 | 33 | 300 | 117 | 75 | 675 | 264 | 169 |

⁽¹⁾ Bias current below 295uA is not recommended, because phase noise performance with 148uA or lower is inferior. In general, phase noise performance achieves optimum at and above 295uA. It gets slightly better with increase of bias current.

Table 2. Available negative resistance divided by 3 (continued)

| Bias current (uA) | C _L = 18pF | | | C _L = 12pF | | | C _L = 8pF | | |
|-------------------|-----------------------|-------|-------|-----------------------|-------|-------|----------------------|-------|-------|
| | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz |
| 1758 | 152 | 59 | 38 | 341 | 133 | 85 | 768 | 300 | 192 |

2.2 R_s, bias current and drive level

According to [Table 1](#) and [Table 2](#), higher bias current provides larger g_m, and hence more negative resistance and more margin for max ESR. Then why not choose the maximum bias current? Because higher bias current also means higher drive level, and as mentioned earlier, if drive level is too high, it will lead to reduced lifetime, accelerated aging and unwanted spurs. In this subsection, we will discuss how to control the drive level so that it is within the max drive level specified in crystal datasheet (typical 100uW or 200uW). To start with, let's review the concept of drive level and the effect of R_s.

Drive level is the amount of power dissipated in a crystal. It is calculated using:

$$DL = I_{rms}^2 ESR \quad (4)$$

Where I_{rms} is the RMS current flowing through the crystal. It can be measured using a current probe with crystal deadbugged or flywired. ESR should be calculated using [Equation 2](#). Max ESR in the datasheet is not acceptable for drive level calculation because it may lead to a much larger value than the actual one. A series resistor R_s can decrease the drive level because I_{rms} is reduced while ESR is unchanged. However, there is hardly any equation that can predict the relationship between R_s and I_{rms} because it is very much dependent on the internal driver circuit which is not disclosed to users. Most of the times board designers either do trial and error or do not know whether or not the crystal has been overdriven at all.

Fortunately, the crystal driver of CDCI6214 / CDCE6214-Q1 was designed in a way such that no R_s is needed. The programmable bias current makes sure that drive level can be controlled within an acceptable range. An example measurement was done using a certain family of crystals (similar C₀ and R_m across frequency). Drive level vs bias current for 25MHz and 50MHz crystal are shown in [Table 3](#) and [Table 4](#). Note that drive level measured with these crystals is quite high, because the R_m of the crystal is very low and C₀ is small, resulting in a small ESR. For crystals with higher ESR, the drive level may be lower.

Table 3. Drive Level vs Bias Current With 25MHz crystal

| Bias current (uA) | R _m (Ω) | C ₀ (pF) | C _L (pF) | ESR (Ω) | 3.3V | | 1.8V | |
|-------------------|--------------------|---------------------|---------------------|---------|-----------------------|------------------|-----------------------|------------------|
| | | | | | I _{rms} (mA) | Drive level (uW) | I _{rms} (mA) | Drive level (uW) |
| 295 | 12.6 | 1.3 | 8.0 | 17.0 | 1.9 | 59.2 | 1.8 | 52.6 |
| 443 | 12.6 | 1.3 | 8.0 | 17.0 | 2.3 | 91.2 | 1.9 | 64.7 |
| 591 | 12.6 | 1.3 | 8.0 | 17.0 | 2.7 | 122.2 | 2.2 | 84.6 |
| 884 | 12.6 | 1.3 | 8.0 | 17.0 | 2.9 | 144.6 | 2.7 | 126.1 |
| 1177 | 12.6 | 1.3 | 8.0 | 17.0 | 2.9 | 146.7 | 2.8 | 136.2 |
| 1468 | 12.6 | 1.3 | 8.0 | 17.0 | 2.8 | 136.2 | 2.8 | 136.2 |
| 1758 | 12.6 | 1.3 | 8.0 | 17.0 | 2.7 | 128.1 | 2.8 | 136.2 |

Table 4. Drive level vs bias current with 50MHz crystal

| Bias current (uA) | R _m (Ω) | C ₀ (pF) | C _L (pF) | ESR (Ω) | 3.3V | | 1.8V | |
|-------------------|--------------------|---------------------|---------------------|---------|-----------------------|------------------|-----------------------|------------------|
| | | | | | I _{rms} (mA) | Drive level (uW) | I _{rms} (mA) | Drive level (uW) |
| 295 | 13.4 | 1.3 | 8.0 | 18.1 | 1.1 | 20.8 | 0.4 | 3.3 |
| 443 | 13.4 | 1.3 | 8.0 | 18.1 | 1.4 | 37.3 | 1.1 | 22.5 |
| 591 | 13.4 | 1.3 | 8.0 | 18.1 | 1.9 | 67.3 | 1.3 | 29.9 |
| 884 | 13.4 | 1.3 | 8.0 | 18.1 | 2.4 | 108.1 | 1.5 | 39.6 |

Table 4. Drive level vs bias current with 50MHz crystal (continued)

| Bias current (uA) | R _m (Ω) | C ₀ (pF) | C _L (pF) | ESR (Ω) | 3.3V | | 1.8V | |
|-------------------|--------------------|---------------------|---------------------|---------|-----------------------|------------------|-----------------------|------------------|
| | | | | | I _{rms} (mA) | Drive level (uW) | I _{rms} (mA) | Drive level (uW) |
| 1177 | 13.4 | 1.3 | 8.0 | 18.1 | 2.7 | 134.1 | 1.6 | 49.3 |
| 1468 | 13.4 | 1.3 | 8.0 | 18.1 | 2.8 | 147.1 | 1.8 | 60.1 |
| 1758 | 13.4 | 1.3 | 8.0 | 18.1 | 2.9 | 156.1 | 2.0 | 70.4 |

Since no R_s is required, drive level should typically fall below 100uW automatically once a proper bias current is selected based on negative resistance needed. Even if drive level is somehow higher than the crystal limit, it can be easily reduced by adjusting bias current.

2.3 Load capacitance

Crystal vendors require a specific load capacitance value in order for the resonator to resonate with minimal frequency error. C_L is defined as equivalent capacitance seen by the crystal. Shown in Figure 3, C_L consists of three parts: external load capacitance (C_{L1} and C_{L2}), internal load capacitance (C_{int_L1} and C_{int_L2}) and stray capacitance (C_{stray}) that includes all kinds of pin and PCB parasitics.

 


Figure 3. Load capacitance illustration diagram

The equivalent capacitance seen by XTAL is (C_{int_L1} in series with C_{int_L2}) in parallel with (C_{L1} in series with C_{L2}) in parallel with C_{stray}. Therefore, C_L can be calculated using:

$$C_L = \frac{C_{L1}C_{L2}}{C_{L1} + C_{L2}} + \frac{C_{int_L1}C_{int_L2}}{C_{int_L1} + C_{int_L2}} + C_{stray} \tag{5}$$

C_{int_L1} is equal to C_{int_L2}, and normally, C_{L1} and C_{L2} are also equal. Therefore, above equation can be simplified to:

$$C_L = \frac{C_{L1}}{2} + \frac{C_{int_L1}}{2} + C_{stray} \tag{6}$$

Programmable C_{int_L1} and C_{int_L2} are controlled by R26[12:8] of CDCI6214 or R24[12:8] of CDCE6214-Q1. Generally, it is recommended to first estimate the stray capacitance, calculate the sum of extra load capacitance needed, then make external load capacitance lower than that value in case the stray capacitance is higher than estimated. If the load capacitance turns out to be lower, then fine tune it using programmable internal load capacitance.

For example, if required load capacitance is 12pF and PCB stray capacitance is estimated to be 3pF, then 9pF of extra capacitance is needed. Set C_{L1} and C_{L2} to 12pF so that there is still 3pF margin. Fine tune the capacitance using internal load cap.

3 Bench measurement examples

In this section, we use bench measurement results to verify Equation 1 and Equation 3. To do so, measure the maximum series resistance with which the crystal can start oscillating, then add to that the ESR of the crystal. The result is the max acceptable ESR with 0 margin.

Table 5. Measured maximum ESR to start oscillation

| Bias current (uA) | Measured maximum ESR (Ω) | | | | | | | | |
|-------------------|-----------------------------------|-------------------|-------------------|-----------|-------|-------|----------|-------|-------|
| | CL = 18pF | | | CL = 12pF | | | CL = 8pF | | |
| | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz | 25MHz | 40MHz | 50MHz |
| 295 | 45 | NA ⁽¹⁾ | NA ⁽¹⁾ | 85 | 45 | 23 | 215 | 75 | 40 |
| 443 | 65 | 27 | 17 | 135 | 55 | 35 | 335 | 120 | 65 |
| 591 | 85 | 30 | 19 | 165 | 85 | 43 | 415 | 145 | 90 |
| 884 | 105 | 33 | 21 | 255 | 100 | 53 | 515 | 185 | 100 |
| 1177 | 135 | 37 | 23 | 315 | 115 | 55 | 615 | 220 | 105 |
| 1468 | 135 | 41 | 25 | 315 | 120 | 56 | 615 | 225 | 115 |
| 1758 | 135 | 43 | 27 | 315 | 120 | 57 | 615 | 225 | 120 |

⁽¹⁾ Crystal does not oscillate.

Comparing [Table 5](#) with [Table 2](#), it can be found that the numbers predicted in [Table 2](#) are quite accurate but not with much margin. That's why a factor of 4 or 5 is recommended considering process, voltage and temperature variation.

Notice how available negative resistance stops increasing or increases slowly beyond 1177uA because of crystal driver saturation.

4 Design procedures summary

1. Set $R_s = 0$. Based on information provided in [Section 2.1](#), determine the negative resistance value and find out the bias current that can provide that.
2. According to [Section 2.3](#), set internal and external load capacitance.
3. After the board is built, send it to crystal vendor to generate a test report. Make sure that $-R$ is 3~5 times of *measured* ESR and drive level is less than what is specified in the crystal datasheet. Adjust the bias current if necessary. Measure the output frequency. Fine tune the frequency by adjusting the internal load cap. Increment frequency by reducing load cap and decrement the frequency by increasing the load cap.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated

DRAFT
TI Confidential – NDA Restriction