

CC13xx/CC26xx Hardware Configuration and PCB Design Considerations

ABSTRACT

This application report provides design guidelines for the CC13xx/CC26xx SimpleLink™ ultra-low-power wireless MCU platform. There is an overview of the different reference designs followed by RF front-end, schematic, PCB, and antenna design considerations. The report also covers crystal oscillator tuning, optimum load impedance as well as a brief explanation of the different power supply configurations. At the end there is a summary of steps to carry out at board bring-up.

Contents

1	Reference Design.....	2
2	Front-End Configurations	6
3	Schematic	10
4	PCB Layout	14
5	Antenna.....	20
6	Crystal Tuning	25
7	Integrated Passive Component (IPC).....	29
8	Optimum Load Impedance	30
9	Power Supply Configuration	31
10	Board Bring-Up	34
11	References	37

List of Figures

1	CC13xx/CC26xx Front-End Options (red = required if external bias is used)	7
2	Comparison of CC13xx/CC26xx Front-End Options	8
3	CC13xx TX Only Matching (868/915 MHz).....	9
4	CC13xx RX Only Matching (868/915 MHz)	9
5	CC1312R 7x7 RF Part Schematic Overview	10
6	CC1312R 7x7 Decoupling Capacitors.....	11
7	CC1312R Board Stack Up	14
8	CC1312R Balun and LC Filter PCB Layout	15
9	LC Filter PCB Layout Design Guideline	16
10	Decoupling Capacitors and VIA to Ground	17
11	Current Return Path	18
12	CC1312R DC/DC Regulator PCB Layout	19
13	Recommended Antenna PI-Match Network for Single-Band Antennas.....	20
14	Recommended Antenna Match Network for Dual-Band Antennas	20
15	Matching the Low-Band With C_{LOW} : 5.6 pF and L_{LOW} : NC	21
16	Matching the High-Band With an Ideal Value of L_{HIGH} : 2.2 nH and C_{HIGH} : NC	22
17	Smith Chart With Final Match Values of L_{HIGH} : 3.3 nH and C_{LOW} : 5.6 pF.....	22
18	VSWR Chart With Final Match Values of L_{HIGH} : 3.3 nH and C_{LOW} : 5.6 pF.....	23
19	Recommended Antenna Match Network for Dual-Band Antennas (433-510 MHz & 2.4 GHz).....	24

20	VSWR Chart With Final Match Values of L_{ANT} : 33 nH L_{HIGH} : 3.9 nH and C_{LOW} : 0 Ω	24
21	CC1312R With 32 kHz and 48 MHz Crystals	25
22	Pierce Type Oscillator	26
23	DC/DC Mode	31
24	Global LDO Mode	32
25	External Regulator Mode	33

List of Tables

1	CC13xx/CC26xx Reference Design Overview	6
2	CC26x0/CC13x0 and CC26x2/CC13x2 Pins With up to 8 mA Drive Strength	11
3	CC13x0/CC26x0 and CC13x2/CC26x2 Configuration of Signal Interfaces	12
4	CC13x2/CC26x2 Pin Mapping	12
5	CC13x0/CC26x0 Pin Mapping	13
6	CC26x0/CC13x0 and CC26x2/CC13x2 JTAG Pins	13
7	Cap-Array Delta	27
8	Available IPC's	29

Trademarks

SimpleLink, LaunchPad, SmartRF are trademarks of Texas Instruments.
Bluetooth is a registered trademark of Bluetooth SIG, Inc and used by Motorola, Inc. under license.
All other trademarks are the property of their respective owners.

1 Reference Design

A TI LaunchPad™ is the main development platform for CC13xx and CC26xx devices. A LaunchPad includes optimized external RF components on-board, PCB antenna and built-in debugger providing an easy-to-use development environment with a single core software development kit (SDK) and rich tool set. Each CC13xx/CC26xx family member is featured on a dedicated LaunchPad with RF matching network and an antenna optimized for operation at one or more of the supported ISM bands. All TI LaunchPad design files, including Gerber-files and CAD source, are available for download at ti.com and can be used as a reference design when integrating CC13xx/CC26xx into custom hardware.

1.1 Sub-1 GHz LaunchPads

This section provides the different LaunchPad designs and which design to follow for a specific CC13xx/CC26xx device and ISM band.

1.1.1 LAUNCHXL-CC1310

Featured device:	CC1310
ISM band:	868 MHz and 915 MHz
Antenna:	Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	LAUNCHXL-CC1310 Design Files

1.1.2 LAUNCHXL-CC1312R

Featured device:	CC1312R
ISM band:	868 MHz and 915 MHz
Antenna:	Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	SimpleLink Sub-1 GHz CC1312R Wireless (MCU) LaunchPad Dev Kit 868MHz/915MHz App

1.2 2.4 GHz LaunchPads

1.2.1 LAUNCHXL-CC2640R2

Featured device:	CC2640R2F
ISM band:	2.4 GHz
Antenna:	2.4-GHz Inverted F Antenna
RF front end:	Differential, internal bias
Design files:	LAUNCHXL-CC2640R2 Design Files

1.2.2 LAUNCHXL-CC26x2R

Featured device:	CC2652R
ISM band:	2.4 GHz
Antenna:	2.4-GHz Inverted F Antenna
RF front end:	Differential, internal bias
Design files:	CC26x2R LaunchPad Design Files

This LaunchPad can also be used for development with CC2642R.

1.3 Dual-Band LaunchPads

1.3.1 LAUNCHXL-CC1350EU/US

This LaunchPad uses an RF switch to select either the 868 MHz/915 MHz RF front end and antenna or the 2.4 GHz front end and antenna. Note that the LaunchPad comes in two different versions: EU and US. The only difference between the two is the antenna matching components that are optimized for either 868 MHz (EU) or 915 MHz (US) operation.

Featured device:	CC1350
ISM band:	868 MHz/915 MHz and 2.4 GHz
Antenna:	• Miniature Helical PCB Antenna for 868 MHz or 915/920 MHz • 2.4-GHz Inverted F Antenna
RF front end:	Differential, external bias
Design files:	LAUNCHXL-CC1350 Design Files

1.3.2 LAUNCHXL-CC1350-4

This LaunchPad uses an RF switch to select either the 433 MHz RF front end and antenna or the 2.4 GHz front end and antenna.

Featured device:	CC1350
ISM band:	433 MHz and 2.4 GHz
Antenna:	• Miniature Helical PCB Antenna for 868 MHz or 915/920 MHz • 2.4-GHz Inverted F Antenna
RF front end:	Differential, external bias
Design files:	CC1350 Dual Band Launchpad for 433 MHz/ 2.4 GHz Band Rev A

1.3.3 LAUNCHXL-CC1352R

Revision A of this LaunchPad uses an RF switch to route either the 868 MHz/915 MHz or 2.4 GHz RF front end into the shared tri-band antenna. For more information about the antenna, see [Section 5.2.1](#). Revision B of this LaunchPad uses a diplexer instead of a switch to combine the two RF paths into the shared antenna, which frees up one DIO as a control signal for the switch is no longer needed.

Featured device:	CC1352R
ISM band:	868 MHz, 915 MHz and 2.4 GHz
Antenna:	Based on Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	CC1352R LaunchPad Design Files

1.3.4 LAUNCHXL-CC1352P1

This LaunchPad has an 868 MHz/915 MHz RF front end at the high power PA port, which enables up to +20 dBm output power in the respective ISM bands. The regular sub-1 GHz port also has an 868 MHz/915 MHz RF front end to be able to receive and transmit at up to +14 dBm output power in the 868 MHz/915 MHz bands. Also, a 2.4 GHz RF front end is available at the 2.4 GHz port to be able to receive and transmit at up to +5 dBm output power in the 2.4 GHz band. All three paths share the same antenna and an RF switch selects which RF path to connect to the antenna. The switch has an insertion loss of approximately 0.5 dB. This is accounted for in the [CC1352P SimpleLink™ High-Performance Dual-Band Wireless MCU With Integrated Power Amplifier Data Sheet](#) RF performance figures. For more information about the antenna, see [Section 5.2.1](#).

Featured device:	CC1352R
ISM band:	868 MHz, 915 MHz and 2.4 GHz
Antenna:	Based on Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	CC1352R LaunchPad Design Files

1.3.5 LAUNCHXL-CC1352P-2

This LaunchPad has a 2.4 GHz RF front end at the high power PA port, which enables up to +20 dBm output power in the respective ISM band. The regular 2.4 GHz port has a 2.4 GHz RF front end to be able to receive and transmit at up to +5 dBm output power in the 2.4 GHz band. Also, an 868 MHz/915 MHz RF front end is available at the sub-1 GHz port to be able to receive and transmit up to +14 dBm output power in the 868 MHz/915 MHz bands. All three paths share the same antenna and an RF switch selects which RF path to connect to the antenna. The switch has an insertion loss of approximately 0.5 dB. This is accounted for in the [CC1352P SimpleLink™ High-Performance Dual-Band Wireless MCU With Integrated Power Amplifier Data Sheet](#) RF performance figures. For more information about the antenna, see [Section 5.2.1](#).

Featured device:	CC1352P
ISM band:	868 MHz, 915 MHz and 2.4 GHz
Antenna:	Based on Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	LAUNCHXL-CC1352P-2 Design Files

1.3.6 LAUNCHXL-CC1352P-4

This LaunchPad has a 470 MHz/510 MHz RF front end on the high power PA port, which enables up to +20 dBm output power in the respective ISM bands. The regular sub-1 GHz port has an RF front end to be able to receive and transmit at up to +14 dBm output power in the 433 MHz, 470 MHz and 510 MHz ISM bands. Also, a 2.4 GHz RF front end is available to be able to receive and transmit at up to +5 dBm output power in the 2.4 GHz band. All three paths share the same antenna and an RF switch selects which RF path to connect to the antenna. The switch has an insertion loss of approximately 0.5 dB. This is accounted for in the [CC1352P SimpleLink™ High-Performance Dual-Band Wireless MCU With Integrated Power Amplifier Data Sheet](#) RF performance figures. The antenna is dual-band and supports operation at one sub-1 GHz frequency in addition to 2.4 GHz. The antenna must be tuned to work with either 433 MHz and 2.4 GHz, 470 MHz and 2.4 GHz, or 510 MHz and 2.4 GHz. For more information, see the device-specific design files. For more information about the antenna, see [Section 5.2.2](#).

Featured device:	CC1352P
ISM band:	433 MHz, 470 MHz, 510 MHz and 2.4 GHz
Antenna:	Based on Monopole PCB Antenna with Single or Dual Band Option
RF front end:	Differential, external bias
Design files:	LAUNCHXL-CC1352P-4 Design Files

1.4 Reference Design Overview

When designing a custom board, the reference design should be followed as much as possible. Not all combinations of CC13xx/CC26xx devices and ISM bands are covered by a reference design, but it is possible to use an RF front end from one reference design and combine it with a compatible CC13xx/CC26xx device. [Table 1](#) shows which CC13xx/CC26xx reference design to use for a given ISM band.

As an example, if the application requires operation in the 433 MHz band, but does not need 2.4 GHz operation or +20 dBm transmit power, the CC1312R device can be used instead of CC1352P. Then, the LAUNCHXL-CC1352P-4 reference design should be followed, but only the RF front end on the SUB-1_GHZ_RF_P/N pins is required.

Table 1. CC13xx/CC26xx Reference Design Overview

ISM Band	Supported Device	Reference Design	Comment
433 MHz 470 MHz 510 MHz	CC1310	CC13xxEM-7XD-4251	
	CC1350	LAUNCHXL-CC1350-4	
	CC1312R	LAUNCHXL-CC1352P-4	Use the sub-1 GHz front end from the reference design
	CC1352R		
	CC1352P		
779 MHz 868 MHz 915 MHz	CC1310	LAUNCHXL-CC1310	For other reference designs, see the following link
	CC1350	LAUNCHXL-CC1350	
	CC1312R	LAUNCHXL-CC1312R1	
	CC1352R	LAUNCHXL-CC1352R1	
	CC1352P	LAUNCHXL-CC1352P1	
		LAUNCHXL-CC1352P-2	
2.4 GHz	CC1350	LAUNCHXL-CC1350	For other reference designs, see the following link
		LAUNCHXL-CC1350-4	
	CC2640R2	LAUNCHXL-CC2640R2	
	CC1352R	LAUNCHXL-CC1352R1	
	CC1352P	LAUNCHXL-CC1352P1	
		LAUNCHXL-CC1352P-2	
		LAUNCHXL-CC1352P-4	
	CC2642R	LAUNCHXL-CC26x2R1	
	CC2652R		

2 Front-End Configurations

2.1 CC13xx/CC26xx

CC13xx and CC26xx have the following front-end modes:

- Single ended: Either the RF_P pin or the RF_N pin is used as the RF path.
- Differential: Both RF_P and RF_N are used as a differential RF interface.
- Internal or external bias of the LNA: The LNA can be biased by an internal or external inductor. Both types of biasing can be selected for single-ended and differential configuration.

Figure 1 shows the front-end options. In the figure components and lines in red color are not required if external bias is used. The component values depend on the frequency band of operation.

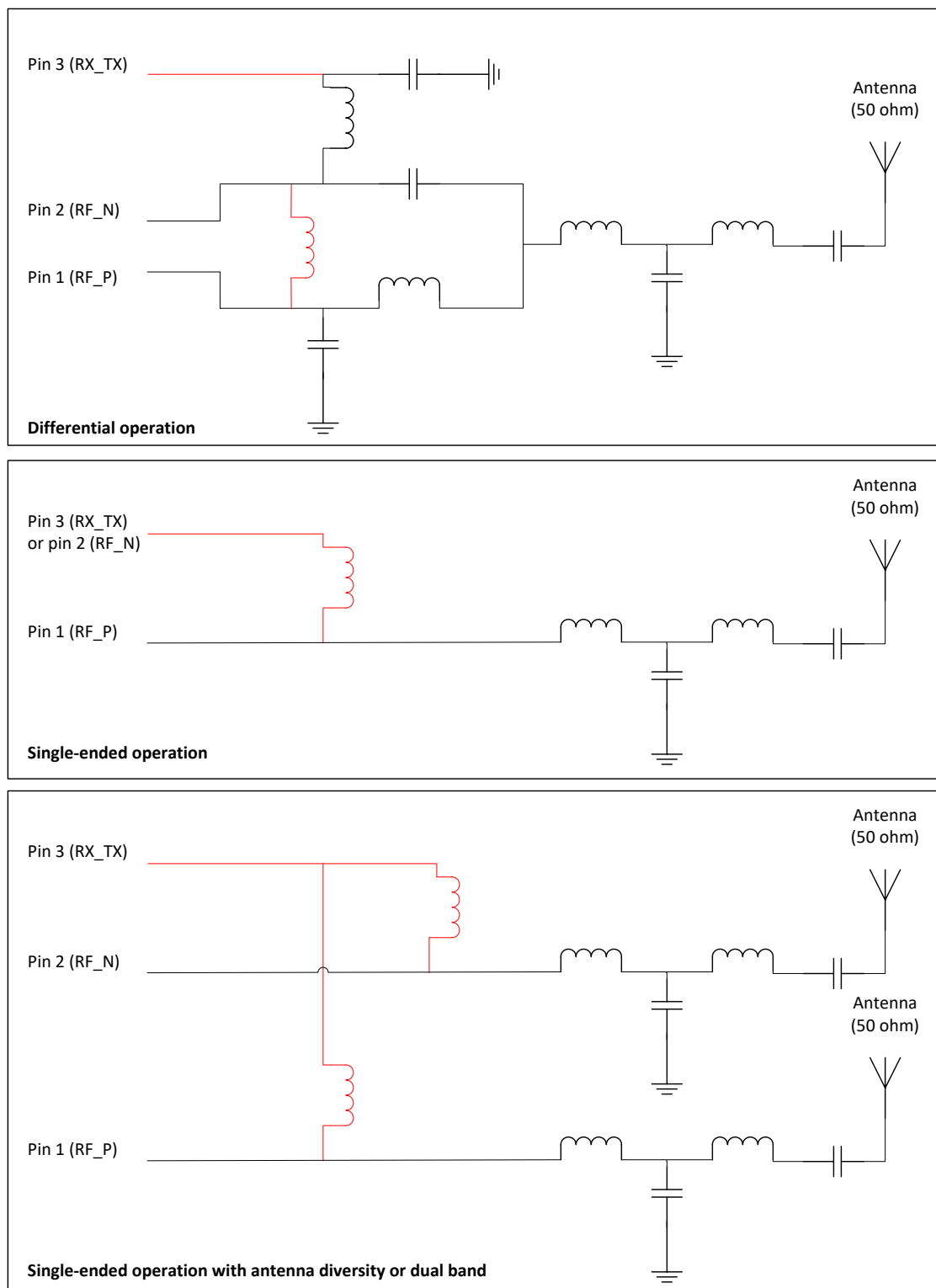


Figure 1. CC13xx/CC26xx Front-End Options (red = required if external bias is used)

Figure 2 summarizes the pros and cons of the different solutions. All numbers in the figure are compared to a differential front end and external biasing.

	External Bias	Internal Bias
Differential	Pros • Best RX performance • Best TX performance Cons • Biggest footprint • Highest BOM cost	Pros • Slightly smaller footprint • Slightly lower BOM cost Cons • 1 dB lower sensitivity
Single-Ended	Pros • Small footprint • Lower BOM cost Cons • 1 dB lower sensitivity • 3 dB lower output power	Pros • Smallest footprint • Lowest BOM cost Cons • 2 dB lower sensitivity • 3 dB lower output power

Figure 2. Comparison of CC13xx/CC26xx Front-End Options

2.2 Configuring Front-End Mode

The front-end mode is set in the CMD_RADIO_SETUP command:

- Config.frontEndMode = 0x00: Differential mode
- Config.frontEndMode = 0x01: Single-ended mode RFP
- Config.frontEndMode = 0x02: Single-ended mode RFN

For single-ended operation that uses one RF pin in RX and the other RF pin in TX, an additional override has to be set:

ADI_HALFREG_OVERRIDES(0, 16, 0x7, x) (1)

where, x = 1 configures the PA output on RFP and x = 0 configures the PA output on RFN.

For single-ended operation, the pin set by CMD_RADIO_SETUP Config.frontEndMode will be used in RX and the pin set by the ADI_HALFREG_OVERRIDE override will be used in TX.

The LNA biasing is set in the CMD_RADIO_SETUP command:

- config.biasMode = 0: Internal bias
- config.biasMode = 1: External bias

2.3 CC13xx Single-Ended Mode

2.3.1 Single-Ended RX/TX

A typical sub-1 GHz design usually requires long range and a differential design is typically used. For lower cost and a smaller footprint, a single-ended design can be used at the expense of shorter range. The sub-1 GHz part from [CC1350STK Design Files](#) can be used for a single ended-design.

If CC13xx is interfaced to a front-end module (FEM) with dedicated 50 Ω ports for RX and TX, fewer components than in the single-ended RX/TX design are needed. This is covered in [Section 2.3.2](#) and [Section 2.3.3](#) for TX and RX only.

2.3.2 Single-Ended TX Only

Load pull measurements show that maximum output power can be achieved if the single-ended RF pin sees $14 - j20\Omega$. A suggested matching network is shown [Figure 3](#). This match gives an output power of 11.8 dBm, 2nd harmonic of -39 dBm, and 3rd harmonic of -42 dBm (measured on 3 units @25°, 3.0 V, 868 MHz). Note that single-ended measurements have not been done for 433 MHz.

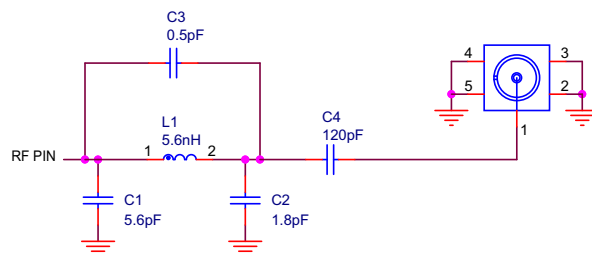


Figure 3. CC13xx TX Only Matching (868/915 MHz)

2.3.3 Single-Ended RX Only

Source pull measurements show that best sensitivity can be achieved if the single-ended RF pin sees $47 + j26\Omega$. A suggested matching network is shown [Figure 4](#). Using this match gives sensitivity of -110 dBm (measured on 3 units @25°, 3.0 V, 868 MHz). Note that single-ended measurements have not been done for 433 MHz.

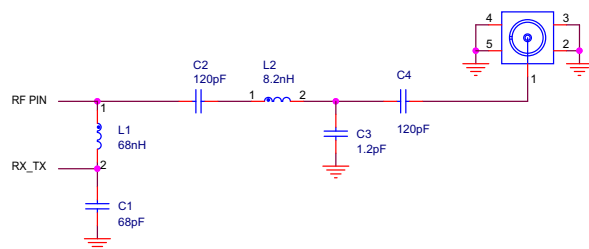


Figure 4. CC13xx RX Only Matching (868/915 MHz)

2.4 CC26xx

For CC26xx, a single-ended configuration is recommended when maximum output power is not needed. For 0 dBm output power using single-ended mode, the current consumption and component count will be lower than for the corresponding differential mode.

Reference designs for both single-ended and differential configurations are available.

1. Go to: <http://www.ti.com/product/CC2640R2F/technicaldocuments>.
2. Scroll down to "Design Files".
3. The designs are named 4XS, 5XD and 7ID. The first number indicate the packet size, X - External bias, I - Internal bias, S - Single-ended, D - Differential.

3 Schematic

3.1 Schematic Overview

Figure 5 shows the different components discussed in the following sub-sections.

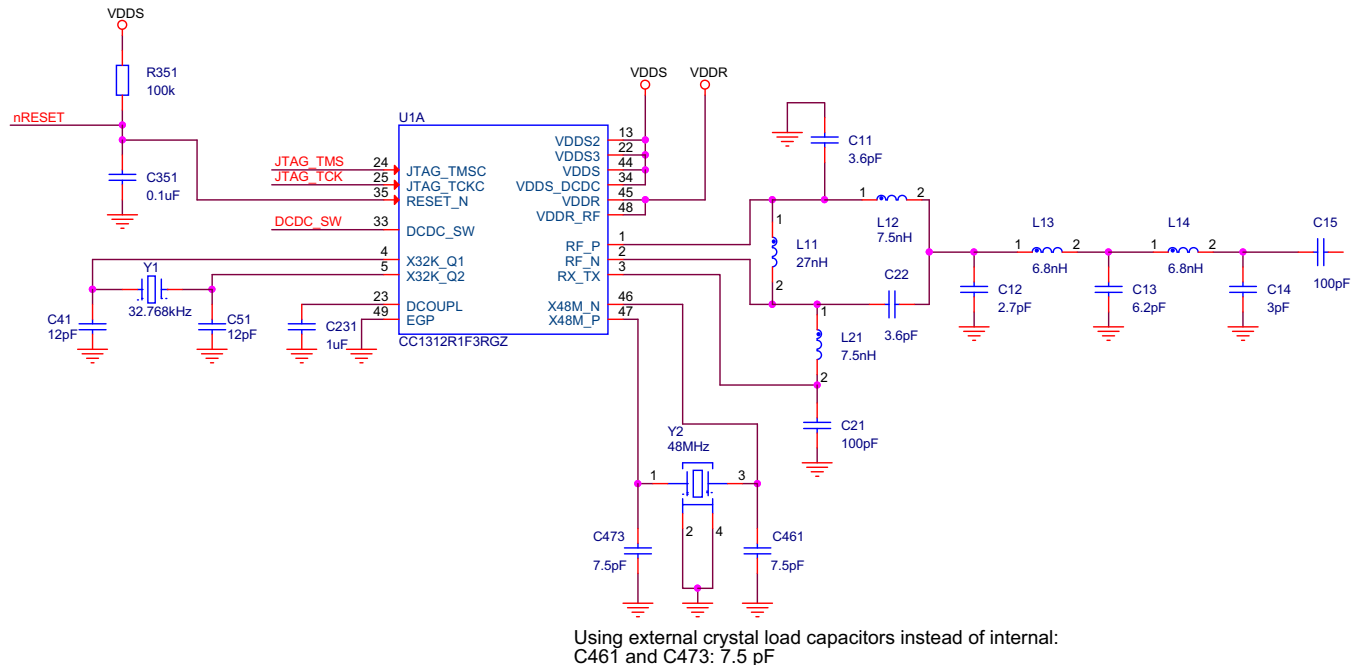


Figure 5. CC1312R 7x7 RF Part Schematic Overview

3.1.1 24/48 MHz Crystal

A 24/48 MHz crystal is required as the frequency reference for the radio.

For CC26x2/CC13x2, there will be spurs at $N \times 48$ MHz offset from the carrier. These spurs are caused by the current going back and forth between the crystal and the XOSC tuning capacitors (which form the oscillator tank together with off-chip capacitances). This current is quite large due to the high Q of the crystal tank and will create an IR drop on the power rails that are shared with the PA and VCO. Setting the XOSC tuning capacitors to zero reduces the spurs by approximately 5 dB for the largest spur compared to the default setting.

The internal capacitor array can be used in most use cases, but it is recommended to use external crystal loading capacitors and setting the internal XOSC tuning capacitors to zero for systems targeting compliance with ARIB STD T-108 and Chinese regulations in 470 – 510 MHz frequency band as well as when using the +20 dBm PA. For information on how to set the internal XOSC tuning capacitors, see [Section 6.4](#).

3.1.2 32.768 kHz Crystal

The 32.768-kHz crystal is optional. The internal low-speed RC oscillator (32-kHz) can be used as a reference if the low-power crystal oscillator is not used. The RC oscillator can be calibrated automatically to provide a sleep timer accurate enough for *Bluetooth*® Low Energy. Using an external crystal has the advantage that it increases sleep clock accuracy and reduces the power consumption for Bluetooth Low Energy (shorter RX windows around connection events). An external crystal is required for time synchronous protocols such as TI 15.4-Stack and WM-Bus.

3.1.3 Balun

A balun is a network that transforms from a balanced (differential) to an unbalanced (single-ended) signal, hence the name balun. The balun has a $\pm 90^\circ$ phase shift implemented by using a low-pass filter and a high-pass filter. The important part is to keep the balun as symmetrical as possible. If only one of the RF pins is used for RF output/input no balun is required. In this case, a filter is required between the chip and the antenna. For details, see [Section 2.3](#).

3.1.4 Filter

An LC filter is placed between the balun and the antenna. The filter has two functions: attenuate harmonics and perform impedance transformation to $50\ \Omega$. The latter is important since measuring equipment such as spectrum analyzers and RF signal generators provide a $50\ \Omega$ load. The word filter balun is sometimes used to describe all the components necessary to implement a balun, filter and to ensure proper impedance matching between the radio and the antenna.

3.1.5 RX_TX Pin

This pin is not present on all CC26x0/CC13x0 and CC26x2/CC13x2 devices. This pin provides ground connection for the input LNA in RX. This is referred to as external bias and improves sensitivity by approximately 1 dB compared to using internal biasing of the LNA.

3.1.6 Decoupling Capacitors

In the reference design, there are several decoupling capacitors. The schematic tells which supply pin the decoupling capacitor is supposed to decouple.

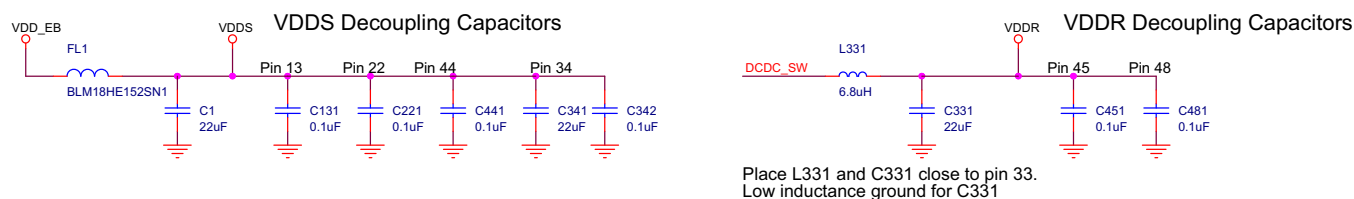


Figure 6. CC1312R 7x7 Decoupling Capacitors

3.1.7 Antenna Components

A pi-match network is recommended between the LC filter and the antenna for antenna impedance matching. For more information, see [Section 5.1](#).

3.1.8 RF Shield

An RF shield is used on some of the TI reference designs to reduce the radiation of spurious signals. Most notably is the 3rd harmonic emission.

3.1.9 I/O Pins Drive Strength

The I/O pins have configurable drive strength and maximum current. All I/O pins support 2 mA and 4 mA, while five pins support up to 8 mA.

Table 2. CC26x0/CC13x0 and CC26x2/CC13x2 Pins With up to 8 mA Drive Strength

7 × 7 QFN (RGZ)	5 × 5 QFN (RHB)	WCSP (YFV)	4 × 4 QFN (RSM)
DIO5	DIO2	DIO2	DIO0
DIO6	DIO3	DIO3	DIO1
DIO7	DIO4	DIO4	DIO2
DIO16	DIO5	DIO5	DIO3
DIO17	DIO6	DIO6	DIO4

3.2 Bootloader Pins

The bootloader communicates with an external device over a 2-pin universal asynchronous receiver/transmitter (UART) or a 4-pin SSI interface. The SSI0 port has the advantage of supporting higher and more flexible data rates, but it also requires more connections to the CC13xx/CC26xx devices. The UART0 has the disadvantage of having slightly lower and possibly less flexible rates. However, the UART0 requires fewer pins and can be easily implemented with any standard UART connection. The serial interface signals are configured to specific DIO's. These pins are fixed and cannot be reconfigured.

Table 3. CC13x0/CC26x0 and CC13x2/CC26x2 Configuration of Signal Interfaces

Signal	Pin Configuration	7 × 7 QFN (RGZ)	5 × 5 QFN (RHB)	4 × 4 QFN (RSM)	2.7 × 2.7 WCSP (YFV)
UART0 RX	Input with pull-up	DIO2 (DIO12 ⁽¹⁾)	DIO1	DIO1	DIO1
UART0 TX	No pull (output when selected)	DIO3 (DIO13 ⁽¹⁾)	DIO0	DIO2	DIO0
SSI0 CLK	Input with pull-up	DIO10	DIO10	DIO8	DIO10
SSI0 FSS	Input with pull-up	DIO11	DIO9	DIO7	DIO9
SSI0 RX	Input with pull-up	DIO9	DIO11	DIO9	DIO11
SSI0 TX	No pull (output when selected)	DIO8	DIO12	DIO0	DIO12

(1) For CC1352x.

3.3 AUX Pins

3.3.1 CC26x2/CC13x2 AUX Pins

There are up to 32 signals (AUXIO0 to AUXIO31) in the sensor controller domain (AUX Domain). These signals can be routed to specific DIO pins given in [Table 4](#). The signals AUXIO19 to AUXIO26 have analog capability, but can also be used as digital I/Os. All the other AUXIO_n signals are digital only.

Table 4. CC13x2/CC26x2 Pin Mapping

DIO	AUX Domain I/O	DIO	AUX Domain I/O	DIO	AUX Domain I/O
DIO30	19	DIO19	30	DIO8	10
DIO29	20	DIO18	31	DIO7	11
DIO28	21	DIO17	1	DIO6	12
DIO27	22	DIO16	2	DIO5	13
DIO26	23	DIO15	3	DIO4	14
DIO25	24	DIO14	4	DIO3	15
DIO24	25	DIO13	5	DIO2	16
DIO23	26	DIO12	6	DIO1	17
DIO22	27	DIO11	7	DIO0	18
DIO21	28	DIO10	8		
DIO20	29	DIO9	9		

3.3.2 CC26x0/CC13x0 AUX Pins

There are up to 16 signals (AUXIO0 to AUXIO15) in the sensor controller domain (AUX). These signals can be routed to specific pins given in [Table 5](#). AUXIO0 to AUXIO7 have analog capability, but can also be used as digital I/Os, while AUXIO8 to AUXIO15 are digital only.

Table 5. CC13x0/CC26x0 Pin Mapping

7 × 7 QFN (RGZ)	5 × 5 QFN (RHB)	WCSP (YFV)	4 × 4 QFN (RSM)	AUX Domain I/O
DIO30	DIO14			0
DIO29	DIO13	DIO13		1
DIO28	DIO12	DIO12		2
DIO27	DIO11	DIO11	DIO9	3
DIO26	DIO9	DIO9	DIO8	4
DIO25	DIO10	DIO10	DIO7	5
DIO24	DIO8	DIO8	DIO6	6
DIO23	DIO7	DIO7	DIO5	7
DIO7	DIO4	DIO4	DIO2	8
DIO6	DIO3	DIO3	DIO1	9
DIO5	DIO2	DIO2	DIO0	10
DIO4	DIO1	DIO1		11
DIO3	DIO0	DIO0		12
DIO2				13
DIO1				14
DIO0				15

3.4 JTAG Pins

The on-chip debug support is done through a dedicated cJTAG (IEEE 1149.7) or JTAG (IEEE 1149.1) interface. The 2-pin cJTAG mode using only TCK and TMS I/O pads is the default configuration after power up. The 4-pin JTAG uses TCK, TMS, TDI, and TDO.

Table 6. CC26x0/CC13x0 and CC26x2/CC13x2 JTAG Pins

Signal	7 × 7 QFN (RGZ)	5 × 5 QFN (RHB)	WCSP (YFV)	4 × 4 QFN (RSM)
TCK	Pin 25	Pin 14	Pin F2	Pin 14
TMS	Pin 24	Pin 13	Pin E4	Pin 13
TDI	DIO17	DIO6	DIO6	DIO4
TDO	DIO16	DIO5	DIO5	DIO3

4 PCB Layout

4.1 Board Stack-Up

Board stack-up is in the reference design zip file (see Design_Name_mechanical.pdf). Most important is the distance from the top layer to the ground layer. Deviating from the recommended board stack-up will change the parasitics and might in some cases lead to a re-design of the filter balun for optimum performance.

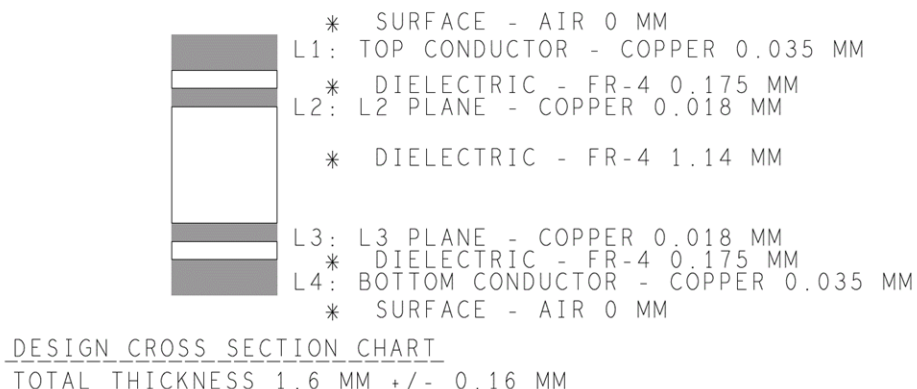


Figure 7. CC1312R Board Stack Up

4.2 Balun

The important part is to keep the balun as symmetrical as possible with regard to the RF ports. Therefore, the trace length from the single ended port to each of the RF pins should be equal to achieve best amplitude and phase balance in the balun. For a good balun PCB layout, see [Figure 8](#). An unbalance in the balun causes higher harmonic level, especially at the 2nd and 4th harmonic. Another effect of having an unsymmetrical balun is reduced output power at the single ended side of the balun. Both component values and component placement is important to achieve best possible symmetry in the balun. Amplitude imbalance should be maximum 1.5 dB and the phase imbalance maximum 10°.

To ensure proper performance it is important to implement the same layout of the balun, match, and filter as in the reference design. Changing the placement of these parts might require tuning on the component values to obtain the desired performance. Tuning requires advanced RF skills and the proper equipment.

There must be an uninterrupted and solid ground plane under all the RF components, stretching from the antenna and all the way back to the ground vias in the chip exposed ground pad (EGP). There must not be any traces under the RF path.

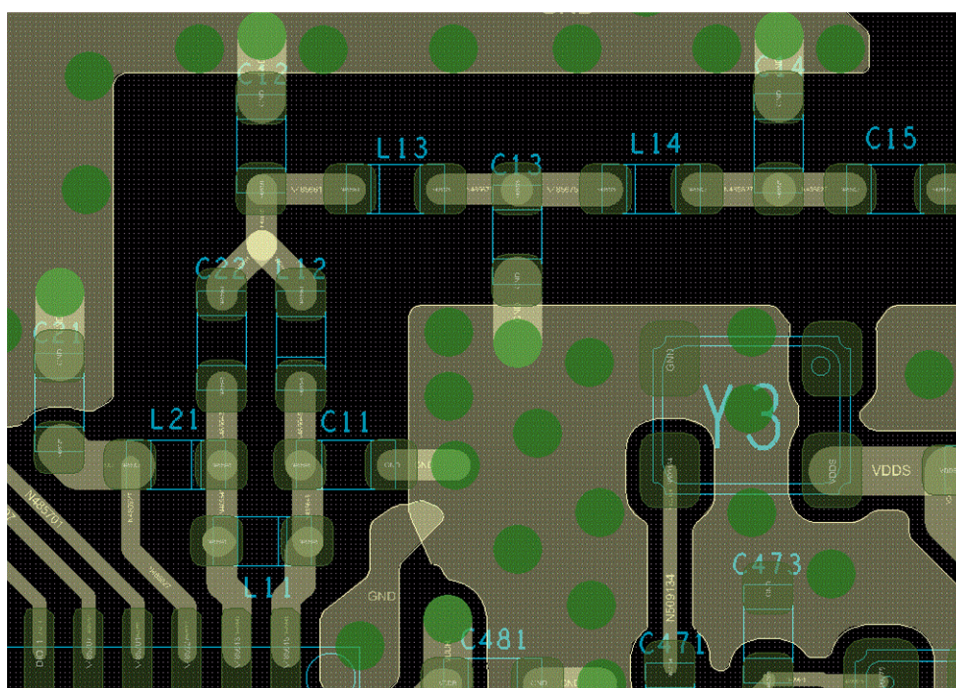


Figure 8. CC1312R Balun and LC Filter PCB Layout

4.3 LC Filter

The LC filter should be laid out so that crosstalk between the shunt components is minimized. [Figure 9](#) shows three different layouts from worse to best. The advantage with the layout to the right is that the parasitic inductance in the PCB track (in black) between the shunt capacitor and the series inductor is in series with the inductor. In the middle figure the parasitic inductance is in series with the shunt capacitor forming a series LC circuit. The placement of C12, L13, C13, L14, and C14 in [Figure 8](#) shows good design practice.

If the design cannot use the reference design as is (for example, use of a different component size) the filter balun will most likely have to be re-tuned. Simulate both the TI reference design and the custom design using an electromagnetic simulator. The two designs should have the same S21/S22.

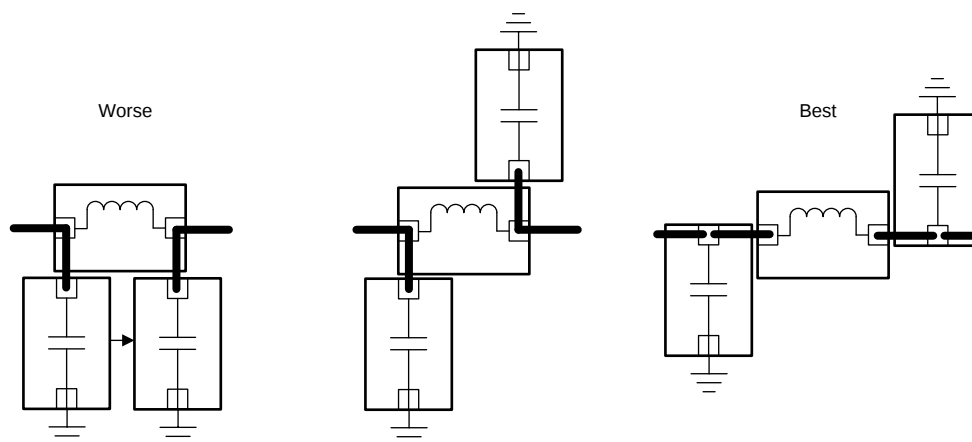


Figure 9. LC Filter PCB Layout Design Guideline

4.4 Decoupling Capacitors

General rules for decoupling capacitors:

- Ensure decoupling capacitors are on same layer as the active component for best results
- Route power into the decoupling capacitor and then into the active component
- Each decoupling capacitor should have a separate via to ground to minimize noise coupling (see [Figure 10](#))
- The decoupling capacitor should be placed close to the pin it is supposed decouple (see [Figure 6](#))
- Ground current return path between decoupling capacitor and chip should be short and direct (low impedance). For details, see [Section 4.5](#).

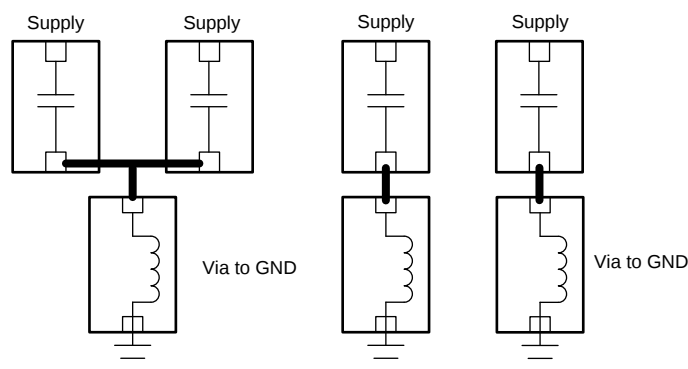


Figure 10. Decoupling Capacitors and VIA to Ground

The figure to the right that uses separate vias to ground, has less noise coupling.

4.5 Current Return Path

There should be a solid ground plane from the capacitor ground pad back to the chip. [Figure 11](#) illustrates this. Failure to follow this may lead to reduced RF performance and higher spurious emission.

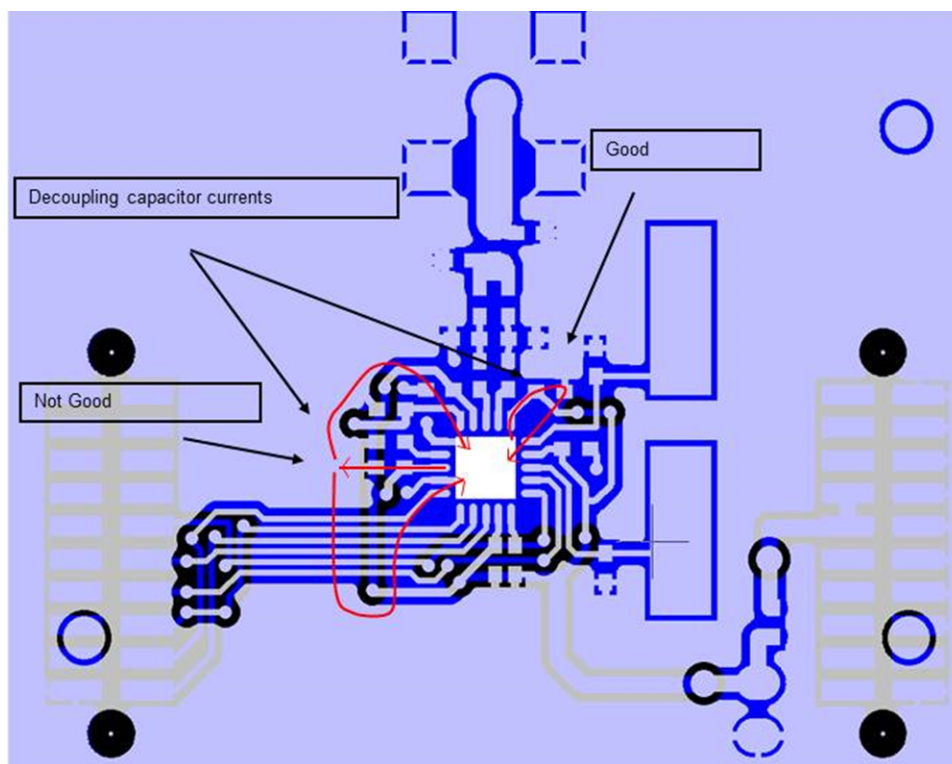


Figure 11. Current Return Path

4.6 DC/DC Regulator

The DCDC components must be placed close to the DCDC_SW pin. The capacitor at the DC/DC regulator output (DCDC_SW pin) must have a short and direct ground connection to the chip (low impedance). Keep a solid ground plane from the capacitor ground pad back to the chip as shown for C331 in [Figure 12](#).

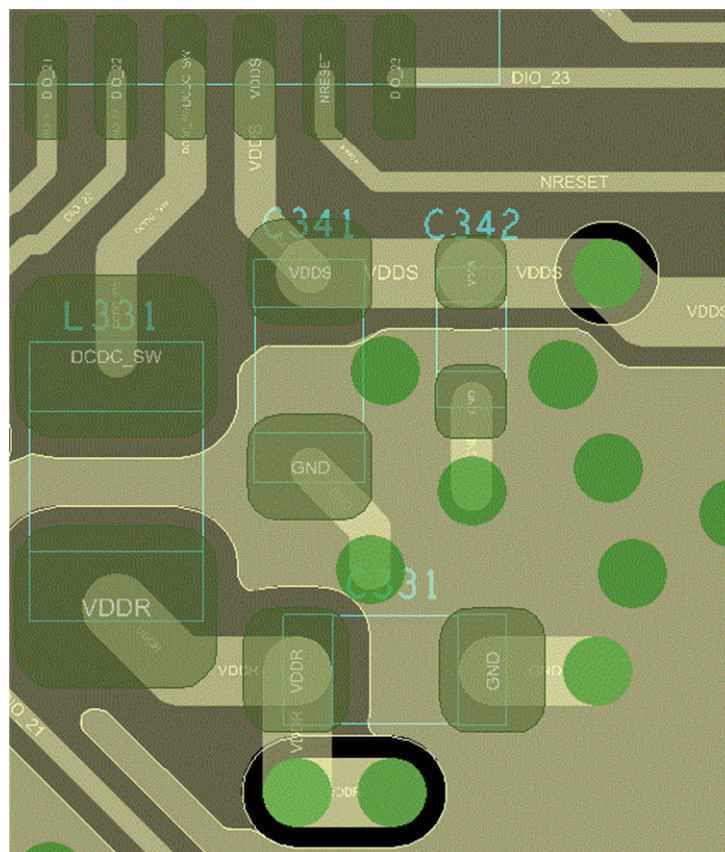


Figure 12. CC1312R DC/DC Regulator PCB Layout

4.7 Antenna Matching Components

A pi-network is recommended for antenna impedance matching. The antenna matching components should be placed as close to the antenna as possible.

4.8 Transmission Lines

Traces in the balun and LC filter are too short to be considered transmission lines, but longer traces, such as from the LC filter, towards the antenna should have a 50 Ω impedance. TXLine is a free tool for PCB trace impedance calculations: [TXLine Transmission Line Calculator](#).

4.9 Electromagnetic Simulation

If the design does not follow the reference design (for example, different filter balun component placement or component size), it is recommended to use Advanced Design System (ADS) or similar to simulate and then compare the impedances and S-parameters of the custom design with the reference design. Changes to the filter balun component values might be required if the custom design deviates too much from the reference design.

5 Antenna

5.1 Single-Band Antenna

The existing antenna documentation available at TI is mainly orientated towards antennas that operate at a single frequency. Two antenna selection guides are available: the [Antenna Selection Quick Guide](#) and a comprehensive [Antenna Selection Guide](#). In addition to the documentation, there is a [CC-Antenna-DK2 and Antenna Measurements Summary](#) available on TI's eStore, as well, with complete documentation. All antenna documentation that is available from TI can be accessed from the [Antenna Selection Quick Guide](#) since it contains hyperlinks to all antenna documentation, antenna measurement reports, and all antenna reference designs.

It is always advised to include an antenna matching network in order to tune and to reduce the mismatch losses of the antenna. For a single-band antenna, the recommendation is to always include a pi-match network prior to the antenna, see [Figure 13](#). Only two of the three footprints/components are required. The impedance of the antenna will determine if footprint/component ANT1 or ANT3 is used. ANT2 will always be used and even if the antenna is perfectly matched, then this can just be set as a 0 Ω resistor.

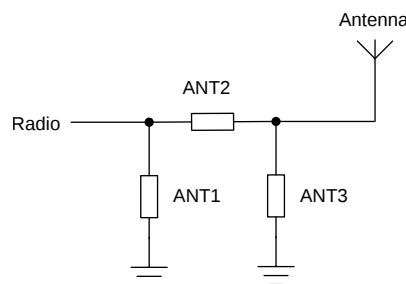


Figure 13. Recommended Antenna PI-Match Network for Single-Band Antennas

5.2 Dual-Band Antenna

The introduction of dual-band operation with advantages of Bluetooth Low Energy combined with long-range advantages of sub-1 GHz sets the need of dual-band antennas. Separate antennas can be used for each of the bands, but physical space is normally limited on most handheld devices that promote usage of dual-band antennas. The most popular dual-band configurations are shown below:

- 863-928 MHz & 2.4 GHz
- 433-450 MHz & 2.4 GHz
- 470-510 MHz & 2.4 GHz

For dual-band operation that contains a low-band and a high-band, the antenna pi-match shown in [Figure 13](#) is not recommended. It is recommended to use an LC, CL match network instead as shown in [Figure 14](#). The LC part is used to match the high-band and the CL part is used for the low-band. Therefore, the LC section will be denoted as L_{HIGH} C_{HIGH} and the CL section as C_{LOW} L_{LOW} in order to identify the components.

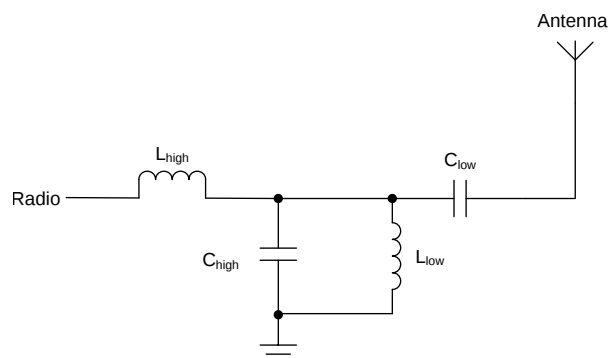


Figure 14. Recommended Antenna Match Network for Dual-Band Antennas

5.2.1 Dual-Band Antenna Match Example: 863-928 MHz and 2.4 GHz

This example is based on LaunchPad-CC1352P1.

- Assemble L_{HIGH} : 0 Ω and C_{LOW} : 0 Ω ; C_{HIGH} : NC and L_{LOW} : NC
- Measure initial impedance with a network analyzer (VNA) at the low-band (868 MHz) and high-band (2440 MHz)
 - 868 MHz: 54 + j30, VSWR: 1.78:1
 - 2.44 GHz: 14 - j32, VSWR: 5.05:1 (This is not required at this stage but included for documentation purposes to note the delta).
- Match the low-band with only the C_{LOW} and L_{LOW} components
 - C_{LOW} : 5.6 pF and L_{LOW} : NC; see [Figure 15](#)

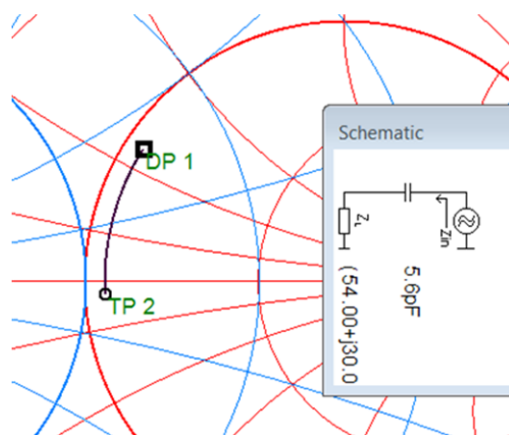


Figure 15. Matching the Low-Band With C_{LOW} : 5.6 pF and L_{LOW} : NC

- Confirm the low-band is matched by measuring the impedances again:
 - 868 MHz: 42 + j2, VSWR: 1.18:1. Good match at the low-band
 - 2.44 GHz: 16+j34, VSWR: 5.38:1
- Match the high-band with only the C_{HIGH} and L_{HIGH} components
 - L_{HIGH} : 2.2 nH and C_{HIGH} : NC; see [Figure 16](#)

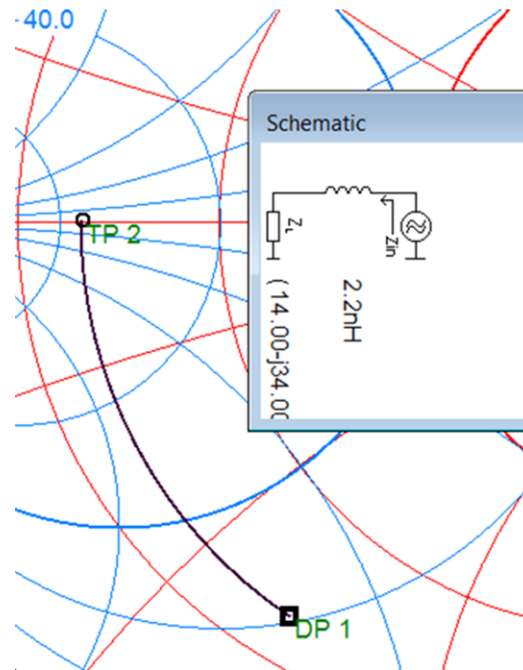


Figure 16. Matching the High-Band With an Ideal Value of L_{HIGH} : 2.2 nH and C_{HIGH} : NC

- L_{HIGH} : 2.2 nH was not sufficient when measured and a value of 3.3 nH was used instead. The antenna match components are based on ideal components with no parasitics. The match is not ideal but the C_{HIGH} component could not be used due to the impedance position in the Smith chart.
- Measure final impedance with a network analyzer (VNA) at the low-band (868 MHz) and high-band (2440 MHz),
 - 868 MHz: $37 + j8$, VSWR: 1.36:1 Good match at the low-band
 - 2.44 GHz: $16 + j8$, VSWR: 3.18:1 Reasonable match at the high-band but would prefer VSWR < 2.00:1; see Figure 17 and Figure 18.

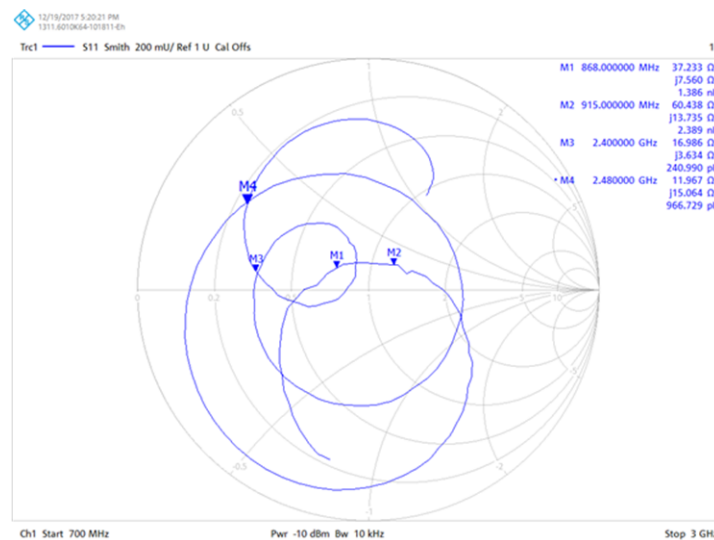


Figure 17. Smith Chart With Final Match Values of L_{HIGH} : 3.3 nH and C_{LOW} : 5.6 pF

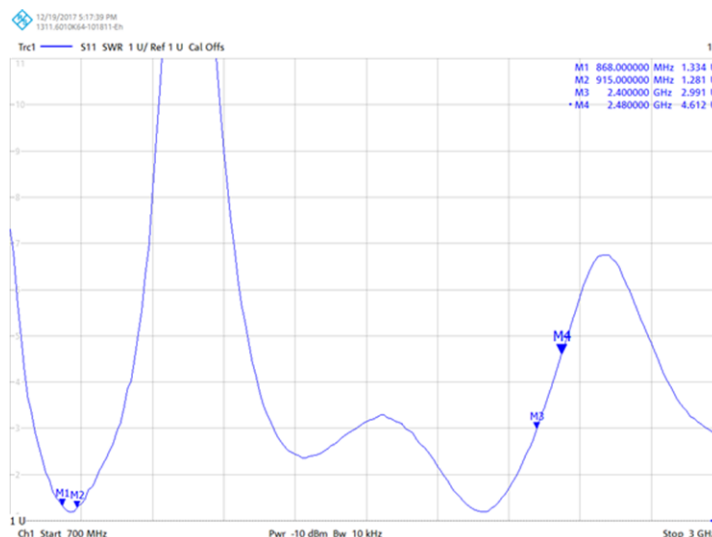


Figure 18. VSWR Chart With Final Match Values of L_{HIGH} : 3.3 nH and C_{LOW} : 5.6 pF

- With the matching components, the antenna match was improved by:
 - 868 MHz: VSWR: 1.78:1 → 1.36:1
 - 2.44 GHz: VSWR: 5.05:1 → 3.18:1

The example shown above used a low-band of 868 MHz but a main requirement of the LaunchPad-CC1352P-1 was for good operation for the complete 863 – 928 MHz band since it was important to cover both ETSI (863-870 MHz) and FCC bands (902-928 MHz). The antenna length on CC1352P1 has a natural resonance of approximately 900 MHz with no matching components.

If the performance at 2.44 GHz is more important than supporting both 868 MHz and 915 MHz ISM bands, then the length of the antenna can be increased so the natural resonance will be around 813 MHz (2440 MHz/3). This would give very good performance at 868 MHz and 2.4 GHz but the 915 MHz band would suffer. A common antenna match for dual-bands is a compromise of performance between the high-band and low-band.

5.2.2 Dual-Band Antenna Match: 433-510 MHz and 2.4 GHz

This example is based on LaunchPad-CC1352P-4.

In order to cover the frequency band 433 – 510 MHz, an external component (LANT) is added to the antenna structure normally used for 863-928 MHz and 2.4 GHz. This is required to keep the antenna relatively small and to maintain a high efficiency. The LANT component extends the length of the antenna structure with the extra inductance added. It is difficult to cover the entire frequency band of 433 – 510 MHz with just one BOM due to the wide bandwidth so the frequency range is divided up into the several regions. An additional antenna structure has also been added that also extends the length of the standard antenna. This makes the 2.4 GHz matching easier since this is more differentiated than just one antenna element structure, see [Figure 19](#).

Value of L_{ANT} component for 433-510 MHz operation:

- 51 nH: 433 MHz
- 39 nH: 470 MHz
- 33 nH: 490 MHz

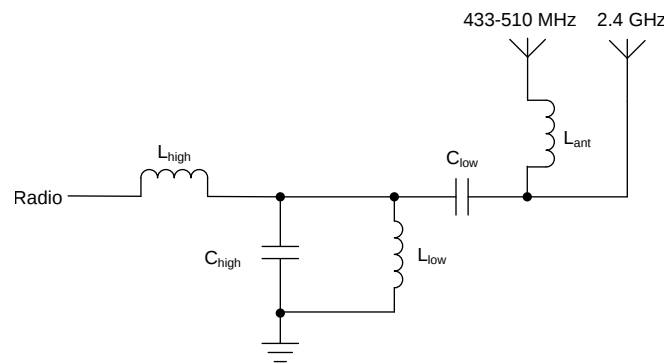


Figure 19. Recommended Antenna Match Network for Dual-Band Antennas (433-510 MHz & 2.4 GHz)

Once the LANT component has been chosen then the matching procedure is similar as shown in the previous example. After the antenna matching process, the final values of the antenna match components can be fixed. As can be seen in [Figure 20](#), the matching of 490 MHz and 2.4 GHz are both below VSWR 1.90 :1, which are good results.

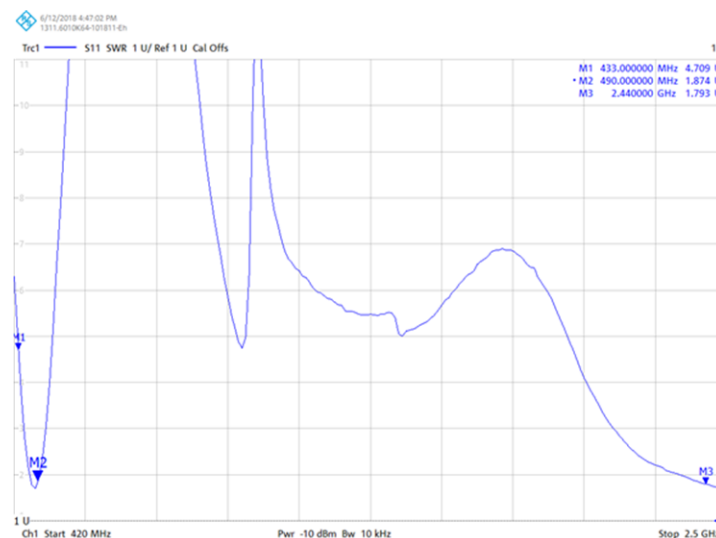


Figure 20. VSWR Chart With Final Match Values of L_{ANT} : 33 nH L_{HIGH} : 3.9 nH and C_{LOW} : 0 Ω

Matching the antenna should be performed in the final casing of the product including all surrounding components such as batteries, displays, and so forth. Casing can affect the antenna's resonance even if the material choice is plastic. The positioning of the antenna or body effects will also affect the antenna's resonance. The antenna is always detuned by a shift downwards in frequency. Therefore, if there are two different environments for the antenna such as handheld and stand-alone on a wooden desk, then it is preferable to have the stand-alone resonance slightly higher so the antenna's bandwidth can be utilized when detuned by body effects/metal objects, and so forth.

6 Crystal Tuning

6.1 CC13xx/CC26xx Crystal Oscillators

The CC13xx/CC26xx devices have two crystal oscillators as shown in Figure 21. The high frequency crystal oscillator (HFXOSC), running at 24 MHz for CC13x0/CC26x0 and 48 MHz for CC13x2/CC26x2, is mandatory to operate the radio. The low frequency crystal oscillator (LFXOSC) is used for RTC timing and only required when accurate RTC timing is necessary, for example for synchronous protocols such as Bluetooth Low Energy.

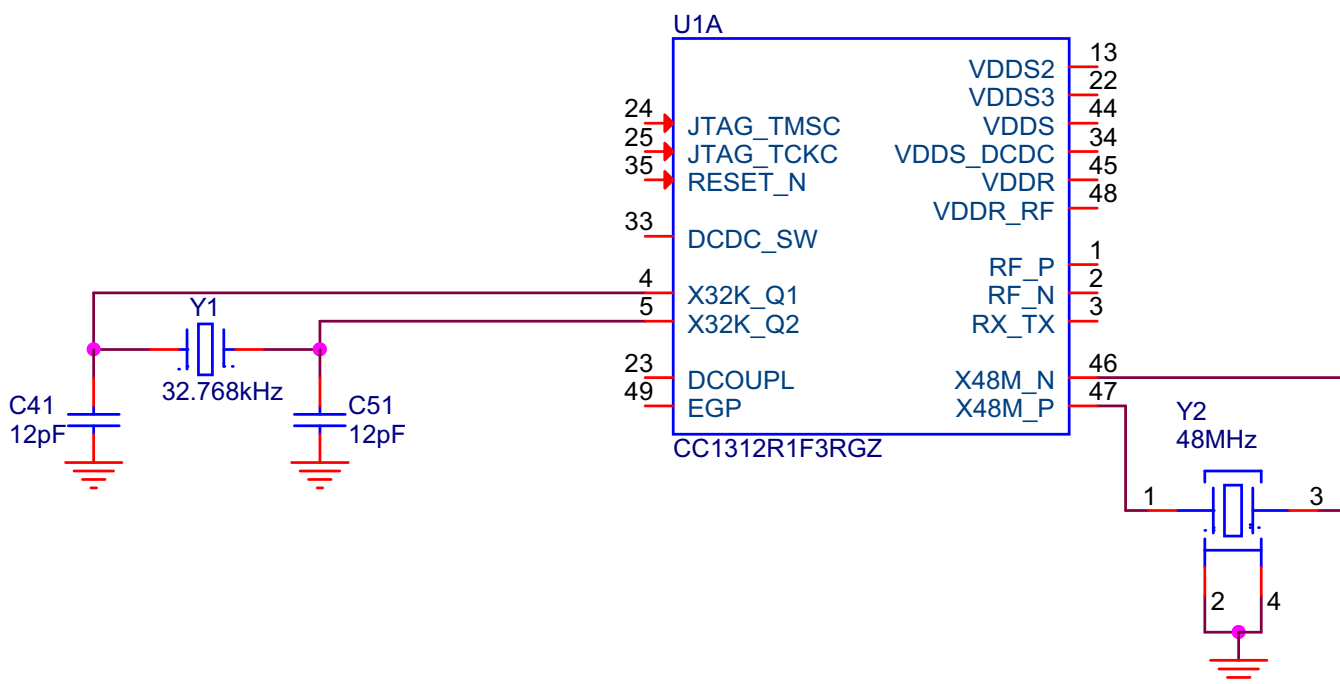


Figure 21. CC1312R With 32 kHz and 48 MHz Crystals

Both crystal oscillators are pierce type oscillators that can be seen in [Figure 22](#). In this type of oscillator, the crystal and the load capacitors form a pi-filter providing a 180° phase shift to the internal amplifier keeping the oscillator locked at the specified frequency. For this frequency to be correct, the load capacitance must be dimensioned properly based on the crystal's capacitive load (CL) parameter.

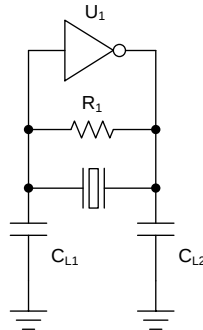


Figure 22. Pierce Type Oscillator

A key difference between the oscillators is that the high frequency oscillator has internal variable load capacitance inside the IC and does in most cases not require external load capacitors. For details on when it is required to use external capacitors instead of the internal variable load capacitance, see [Section 3.1.1](#). The low frequency oscillator on the other hand needs to have external capacitors to operate properly.

6.2 Crystal Selection

When selecting a crystal part, it is important to look at the device-specific CC13xx/CC26xx data sheets that lists requirements for the crystal parameters. All of these requirements must be fulfilled to ensure proper operation of the oscillator(s) and proper operation of the device.

6.3 Tuning the LF Crystal Oscillator

The frequency of the 32-kHz crystal oscillator is set by properly dimensioning the load capacitors relative to the crystal's wanted load capacitance, CL. From the crystal's point of view, the two capacitors are placed in series, which means that the "resistor parallel" equation to calculate the resulting total capacitance must be used. Also keep in mind that the PCB traces and the pads add some parasitic capacitance. [Equation 2](#) shows how to calculate the right load capacitance value.

$$CL = \frac{C1 \times C2}{C1 + C2} + C_{\text{parasitic}} \approx \frac{\text{load capacitor value}}{2} + C_{\text{parasitic}} \quad (2)$$

The last simplification requires that C1 and C2 are equal.

The best way to measure the frequency accuracy of the oscillator is to output the clock signal on an I/O pin. This way the frequency can be measured using a frequency counter without affecting the oscillator. The following Driverlib calls will output the selected 32-kHz clock source in all power states except Shutdown:

```
#include <driverlib/aon_ioc.h>
IOCPortConfigureSet(IOC_IDn, IOC_PORT_AON_CLK32K, IOC_STD_OUTPUT);
AONIOC32kHzOutputEnable();
```

6.4 Tuning the HF Oscillator

The HF oscillator has internal variable load capacitors (cap-array) in the IC and does not require external capacitors to be mounted. There are some exceptions. For details on when it is required to use external capacitors instead of the internal cap-array, see [Section 3.1.1](#).

The load capacitance is set in CCFG.c through the following defines:

```
#ifndef SET_CCFG_MODE_CONF_XOSC_CAP_MOD
// #define SET_CCFG_MODE_CONF_XOSC_CAP_MOD          0x0          // Apply cap-array delta
#define SET_CCFG_MODE_CONF_XOSC_CAP_MOD          0x1          // Don't apply cap-array delta
#endif

#ifndef SET_CCFG_MODE_CONF_XOSC_CAPARRAY_DELTA
#define SET_CCFG_MODE_CONF_XOSC_CAPARRAY_DELTA    0xFF          // Signed 8-
bit value, directly modifying trimmed XOSC cap-array value
#endif
```

The SET_CCFG_MODE_CONF_XOSC_CAP_MOD defines tells the system whether it should use the default value or use an offset from the default value set by SET_CCFG_MODE_CONF_XOSC_CAPARRAY_DELTA. The default cap-array values are 9 pF for CC13x0/CC26x0 QFN, 5 pF for CC2640R2F WCSP, and 6.7 pF for CC13x2/CC26x2.

The cap-array delta value is an offset from the default value that can be either negative or positive. [Table 7](#) shows the resulting total capacitance measured on an evaluation board versus cap-array delta values. Note that the resulting capacitance value includes parasitic capacitances, which is why the lowest setting is not 0 pF. Using a delta value equal to or lower than the most negative value in the table completely disables the internal load capacitor array.

The best way to measure the accuracy of the HF crystal oscillator is to output an unmodulated carrier wave from the radio and measuring the frequency offset from the wanted frequency using a spectrum analyzer. The relative offset of crystal frequency, typically stated in Parts per Million (ppm), is the same as the relative offset of the RF carrier.

For testing purposes cap-array delta values can be adjusted in SmartRF™ Studio. This simplifies tuning greatly by allowing on-the-fly updates of the load capacitance. The optimum value found in SmartRF Studio can then be entered into CCFG in the applicable software project.

Table 7. Cap-Array Delta

Measured Capacitance on Reference Board	CCFG Delta Value for CC13x0/CC26x0 QFN	CCFG Delta Value for CC2640R2F WCSP	CCFG Delta Value for CC13x2/CC26x2 QFN
2,1	< -55	< -28	< -40
2,1	-55	-28	-40
2,2	-54	-27	-39
2,3	-53	-26	-38
2,4	-52	-25	-37
2,5	-51	-24	-36
2,6	-50	-23	-35
2,7	-49	-22	-34
2,7	-48	-21	-33
2,8	-47	-20	-32
2,9	-46	-19	-31
3,0	-45	-18	-30
3,1	-44	-17	-29
3,2	-43	-16	-28
3,3	-42	-15	-27
3,4	-41	-14	-26
3,4	-40	-13	-25
3,6	-38	-12	-24
3,7	-37	-11	-23

Table 7. Cap-Array Delta (continued)

Measured Capacitance on Reference Board	CCFG Delta Value for CC13x0/CC26x0 QFN	CCFG Delta Value for CC2640R2F WCSP	CCFG Delta Value for CC13x2/CC26x2 QFN
3,8	-36	-10	-22
3,9	-35	-9	-21
4,0	-34	-8	-20
4,1	-33	-7	-19
4,3	-32	-6	-18
4,4	-31	-5	-17
4,5	-30	-4	-16
4,6	-29	-3	-15
4,7	-28	-2	-14
4,8	-27	-1	-13
5,0	-26	0	-12
5,1	-25	1	-11
5,2	-24	2	-10
5,3	-23	3	-9
5,5	-21	4	-8
5,6	-20	5	-7
5,8	-19	6	-6
5,9	-18	7	-5
6,1	-17	8	-4
6,2	-16	9	-3
6,4	-15	10	-2
6,5	-14	11	-1
6,7	-13	12	0
6,8	-12	13	1
7,0	-11	14	2
7,1	-10	15	3
7,3	-9	16	4
7,4	-8	17	5
7,6	-7	18	6
7,7	-6	19	7
7,9	-5	21	8
8,2	-4	22	9
8,4	-3	23	10
8,6	-2	24	11
8,8	-1	25	12
9,0	0	26	13
9,2	1	27	14
9,4	2	28	15
9,6	3	29	16
9,8	4	30	17
10,1	5	31	18
10,3	6	32	19
10,5	7	33	20
10,7	8	34	21
10,9	9	35	22
11,1	10	36	23
11,1	> 10	> 36	> 23

7 Integrated Passive Component (IPC)

An Integrated Passive Component (IPC) is a matched-filter balun component specially designed or matched to the RF section. The IPC reduces the component count that saves space and reduces pick-and-place assembly costs. In addition, there is less risk of a poor RF layout with an IPC since the RF crosstalk is minimized. [Table 8](#) lists the available IPC's.

Table 8. Available IPC's

Chip Family	Frequency (MHz)	Vendor	Part Number	Application Report
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	430 - 435	Johanson Technology	0433BM15A0001	SWRA520
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	430 - 435	Johanson Technology	0433BM15A0001E-AEC*1	SWRA520
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	863 - 873	Johanson Technology	0868BM15C0001	SWRA520
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	863 - 873	Johanson Technology	0868BM15C0001E-AEC*1	SWRA520
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	863 - 928	Johanson Technology	0896BM15A0001	SWRA520
CC1120, CC1121, CC1175, CC1200, CC1201	863 - 928	Johanson Technology	0900PC15J0013	SWRA407
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	902 - 928	Johanson Technology	0915BM15A0001	SWRA297
CC1101, CC1111, CC1110, CC110L, CC113L, CC115L, CC430	902 - 928	Johanson Technology	0915BM15A0001E-AEC*1	SWRA297
CC13xx	430-510	Walsin	RFBLN2520090YC3T10	SWRA524
CC13xx	770-928	Murata	LFB18868MBG9E212	SWRA524
CC13xx	770-928	Johanson Technology	0850BM14E0016	SWRA524
CC1352R, CC1352P	863 – 928 2400 - 2480	Murata	LFB21868MDZ5E757	SWRA629
CC1352R, CC1352P	863 – 928 2400 - 2480	Johanson Technology	0900PC15A0036	SWRA629
CC2420	2400 - 2480	Anaren	BD2425N50200A00	SWRA155
CC2430	2400 - 2480	Anaren	BD2425N50200A00	SWRA156
CC2430, CC2480	2400 - 2480	Johanson Technology	2450BM15A0001	
CC2520	2400 - 2480	Johanson Technology	2450BM15B0002	
CC2500, CC2510	2400 - 2480	Johanson Technology	2450BM15B0003	
CC26xx	2400 - 2480	Murata	LFB182G45BG5D920	
CC26xx	2400 - 2480	Johanson Technology	2450BM14G0011	SWRA572
CC26xx	2400 - 2480	Johanson Technology	2450BM14G0011T-AEC*1	SWRA572

8 Optimum Load Impedance

CC13xx/CC26xx supports several front-end configurations, both differential and single-ended operation with either internal or external bias. The different RF front-end configurations are presented in more details in [Section 2](#). TI offers several reference designs for CC13xx/CC26xx showing recommendations for the different RF front-end configuration. Note that the different RF front-end configurations from the different reference designs do not follow the package sizes (7x7 mm, 5x5 mm and 4x4 mm) and can be mixed as wanted.

CC13xx/CC26xx impedance changes with the state of the chip (TX/RX) and the output/input signal level. When operated in receive, the LNA gain is adjusted according to the input signal level and is thus not constant. This results in that the LNA operates with different configuration for the different gain setting. The PA impedance is further different from the receive impedance. It changes with the configured output power level and is not linear. The term output impedance is used for linear amplifiers or amplifiers that can be approximated by a linear equivalent. Output impedance is normally used to design complex conjugate impedance matching between amplifier and load. For linear amplifiers this is sufficient to secure optimum power transfer. This method is thus not valid for the CC13xx/CC26xx series.

CC13xx/CC26xx operations are heavily dependent upon filter-balun impedance up to at least the forth harmonic for sub-1 GHz and up to at least the third harmonic for 2.4 GHz. Matching load impedance only at fundamental frequency could easily result in high current consumption, low output power and high spurious/harmonics.

To get the optimal performance with a CC13xx/CC26xx design, it is highly recommended to follow the reference designs (schematic, layout and stack-up). TI have found the recommended balun and matching circuits through simulations and load- and source-pull measurements over the full operational range. The RF circuits are designed to give best overall TX and RX performance (output power, sensitivity, current consumption, and harmonic and spurious emission).

Note that impedance calculated based on analyzing the data sheet and reference design schematic often deviate from the optimum load impedance given by TI. PCB parasitic and component imperfections generally accounts for these differences. When operating at high frequencies, PCB traces have to be modeled to account for phase shift, skin effect increased resistance, inductive and capacitive effects. Manufacturers of passives normally provide linear LCR models and/or S-parameter models representing their components at higher frequencies. Be aware to check the valid frequency range for the models, and only use them within this range. Simulators often extrapolate the model data without warnings and simulation results become invalid. Remember that valid frequency range is the range up to the highest significant frequency component within your circuit.

There are designs that cannot use the reference design as is (for example, use of a different component size). In this case, it is recommended to simulate both the TI reference design and the customer design in ADS. The two designs should have the same S21/ S22.

CC26xx

- Differential External Bias target load impedance: $45 + j43 \Omega$
- Differential Internal Bias target load impedance: $42 + j21 \Omega$
- Single-ended Internal Bias target load impedance: $38 + j5 \Omega$

CC1310, CC1312

- 863-928 MHz
 - 868 MHz target load impedance: $40 + j15 \Omega$
- 2440 MHz target load impedance: $25 - j10 \Omega$

CC1352R, CC1352P

- 863-928 MHz
 - 898 MHz Tx/Rx target load impedance: $37-j8 \Omega$
 - 898 MHz Rx only optimized target load impedance: $47+j1 \Omega$
- 2450 MHz target load impedance: $33+j11 \Omega$
- 2440 MHz high power PA target load impedance: 200Ω
- 863-928 MHz high power PA target load impedance: 200Ω

9 Power Supply Configuration

9.1 Introduction

The CC13xx/CC26xx devices have three power rails that are exposed on external pins: VDDS, VDDR and DCOUPL. VDDS is the main power source for the wireless microcontroller and must be supplied externally with 1.8 V to 3.8 V. VDDR is an internal power rail that is supplied from the internal DC/DC converter, or the internal Global LDO, but can be powered from an external supply. VDDR is regulated to approximately 1.68 V, or 1.95 V when running in boost mode for maximum output power in sub-1 GHz bands. In boost mode, a minimum VDDS voltage of 2.1 V is required. DCOUPL is supplied internally by either Digital LDO or Micro LDO depending on the power state. This power rail is trimmed to approximately 1.28 V and requires an external decoupling capacitor of 1 μ F.

9.2 DC/DC Converter Mode

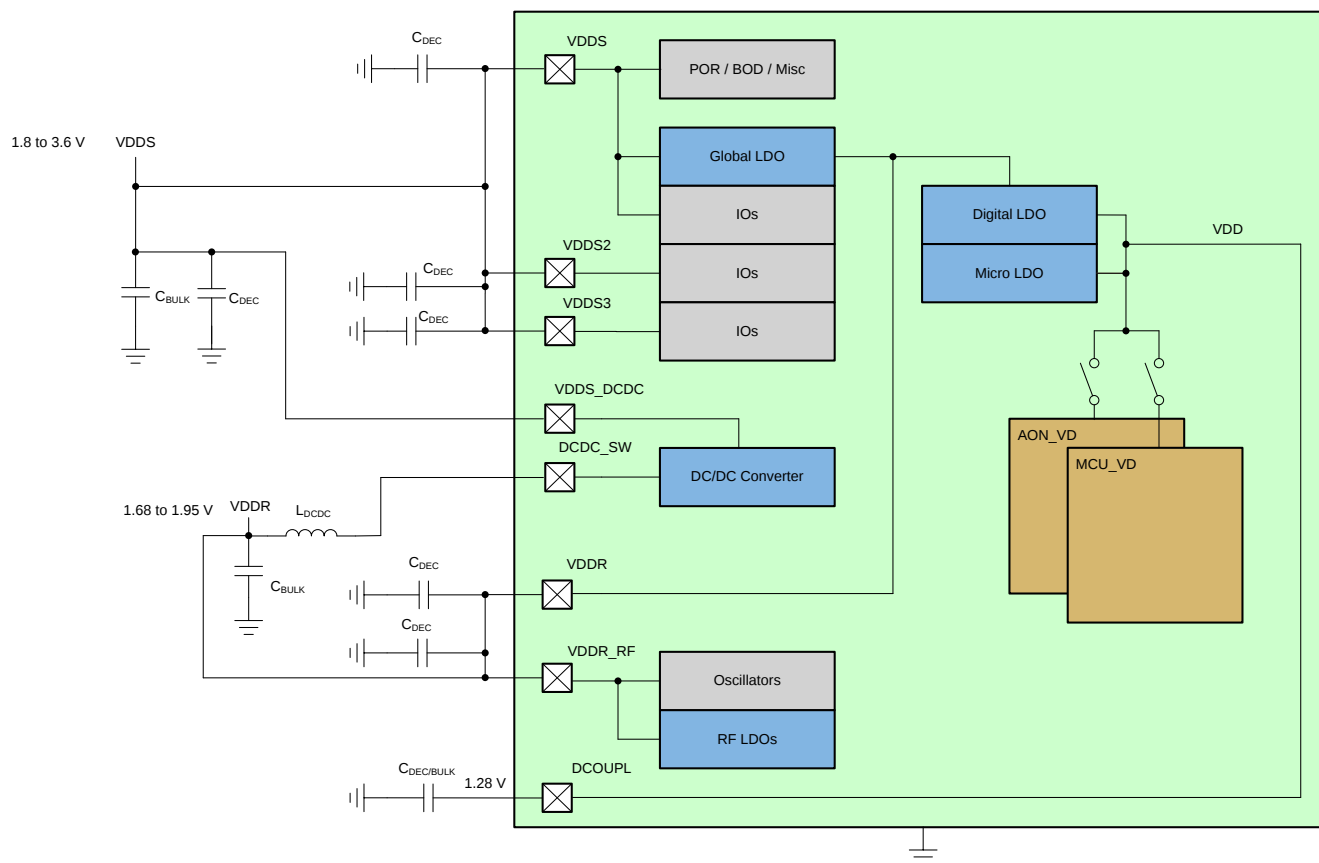


Figure 23. DC/DC Mode

Maximum efficiency is obtained by using the internal DC/DC converter, and it requires an external inductor (LDCDC) and capacitor (CDCDC). The components should be placed as close as possible to the CC13xx/CC26xx device and it is important to have a short current return path for from the CDCDC ground to the pad on the chip (see [Section 4.6](#)). In addition, the bulk capacitor on VDD5 should be placed close to the VDD5_DCDC-pin. The actual value of LDCDC, CDCDC and CBULK vary from device to device. For the actual values, see the device-specific reference design.

When operating in DC/DC mode, the power system dynamically switches between the Global LDO and DC/DC converter depending on the required load to achieve maximum efficiency. If VDD5 drops below 2.0 V, the DC/DC converter will be less efficient than the LDO and the device will run in global LDO mode. For systems operating with VDD5 less than 2.0 V, consider either global LDO or external regulator mode to save component cost and board area.

The following software setup is required in the CCFG to use the DC/DC converter:

```
#ifndef SET_CCFG_MODE_CONF_DCDC_RECHARGE
#define SET_CCFG_MODE_CONF_DCDC_RECHARGE    0x0    // Use the DC/DC during recharge in powerdown
// #define SET_CCFG_MODE_CONF_DCDC_RECHARGE    0x1    // Do not use the DC/DC during recharge in powerdown
#endif

#ifndef SET_CCFG_MODE_CONF_DCDC_ACTIVE
#define SET_CCFG_MODE_CONF_DCDC_ACTIVE        0x0    // Use the DC/DC during active mode
// #define SET_CCFG_MODE_CONF_DCDC_ACTIVE        0x1    // Do not use the DC/DC during active mode
#endif
```

9.3 Global LDO Mode

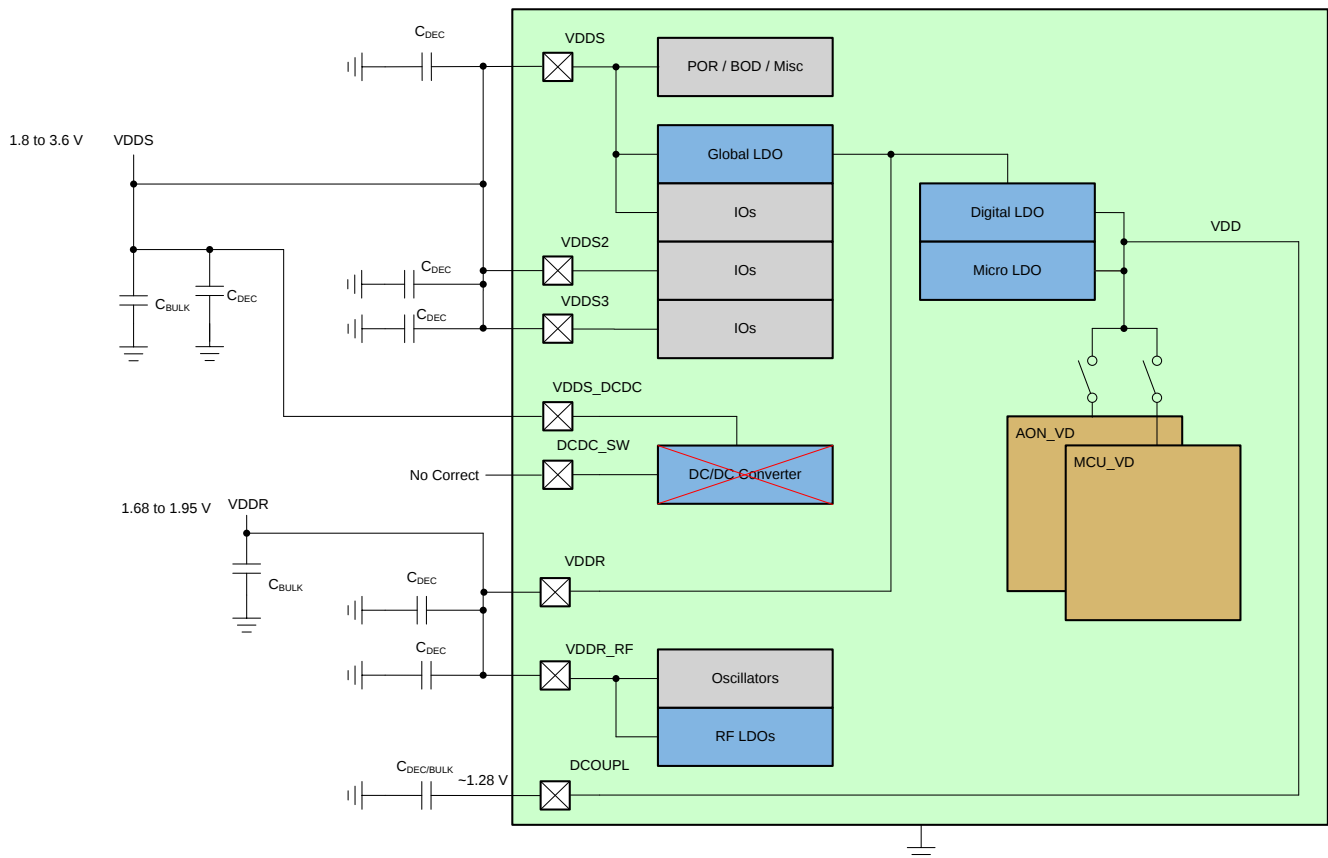


Figure 24. Global LDO Mode

To save cost and PCB area the DC/DC inductor can be removed and VDDR can be supplied from the Global LDO at the cost of higher power consumption. In this mode a bulk capacitor on VDDR is still required and should be placed close to the VDDR pin. The VDDSD_DCDC-pin must be connected to VDDSD and the DCDC_SW should be left floating to avoid short circuiting VDDSD if the DC/DC converter is mistakenly enabled from software. The VDDSD bulk capacitor does not need to be close to the VDDSD_DCDC pin and should rather be placed close to the VDDSD pin.

The following software setup is required in the CCFG to disable the DC/DC converter and supply VDDR from Global LDO:

```
#ifndef SET_CCFCG_MODE_CONF_DCDC_RECHARGE
// #define SET_CCFCG_MODE_CONF_DCDC_RECHARGE 0x0 // Use the DC/DC during recharge in
powerdown
#define SET_CCFCG_MODE_CONF_DCDC_RECHARGE 0x1 // Do not use the DC/DC during recharge in
powerdown
#endif

#ifndef SET_CCFCG_MODE_CONF_DCDC_ACTIVE
// #define SET_CCFCG_MODE_CONF_DCDC_ACTIVE 0x0 // Use the DC/DC during active mode
#define SET_CCFCG_MODE_CONF_DCDC_ACTIVE 0x1 // Do not use the DC/DC during active mode
#endif
```

9.4 External Regulator Mode

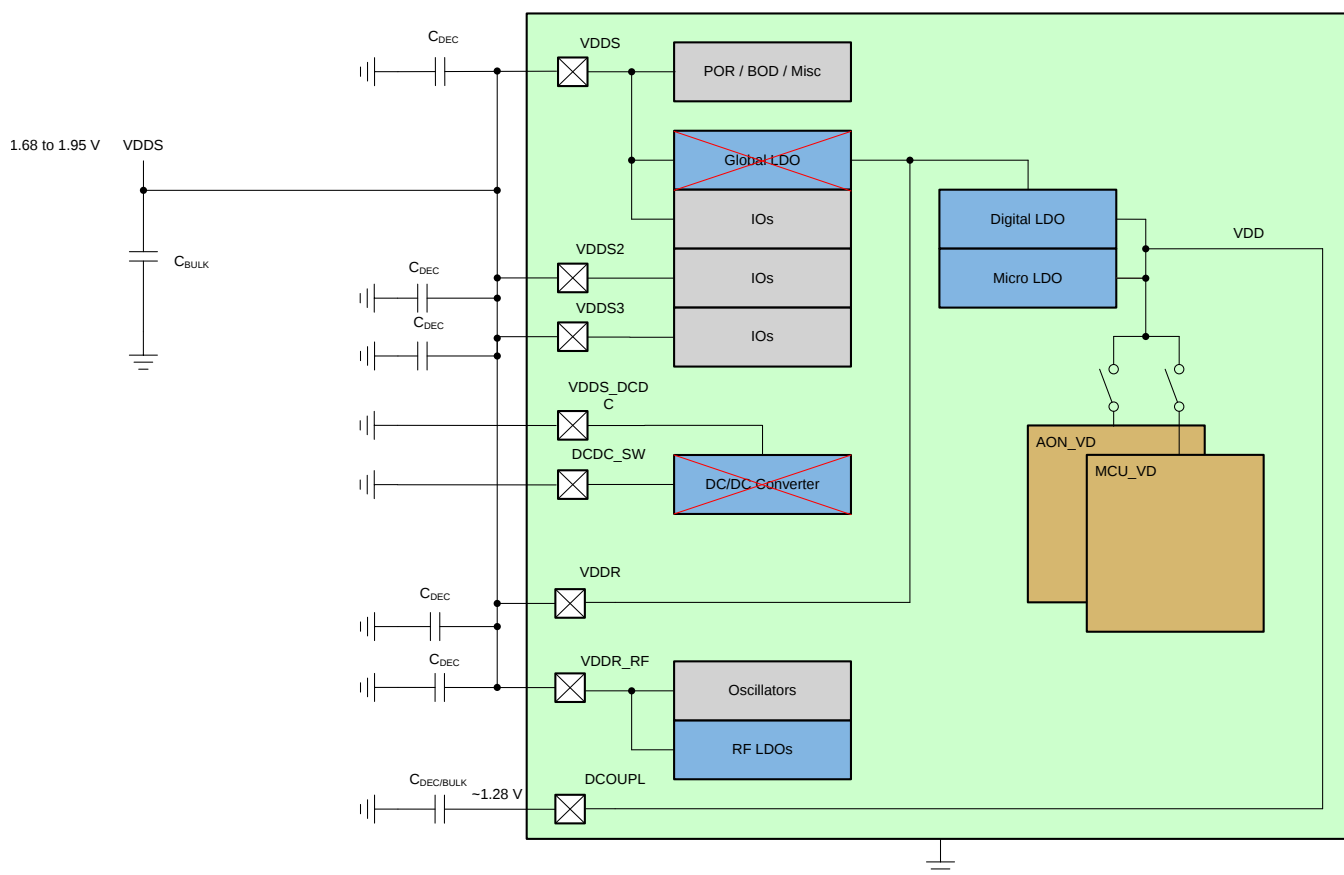


Figure 25. External Regulator Mode

In external regulator mode, neither the Global LDO nor the DC/DC is active and both VDD5 and VDDR must be powered from the same rail. The regulators are disabled by connecting VDD5_DCDC to ground. Note that the maximum voltage level on the external regulator is limited by VDDR and should not exceed the absolute maximum rating defined in the device-specific data sheet. To achieve maximum output power for the sub-1 GHz PA, the supply voltage should be set to 1.95 V.

NOTE: External Regulator Mode is only supported on CC26x0 devices.

10 Board Bring-Up

Before starting to develop software or doing range testing, it is recommended to do conducted measurements to verify that the board has the expected performance. Typically, the sensitivity, output power, harmonics, and current consumption should be measured to verify the hardware design.

The required measurements depend on the type of board and application. If it is a design with 10 m range requirement the checkout does not need to be as detailed as for a design with a range extender. For the latter, and other designs that require high performance, having access to a spectrum analyzer and a signal generator with the option to send RF packets is highly recommended.

Different measurement methods are discussed in the following sections. It is up to the reader to select the methods applicable for their board.

10.1 Power On

When powering on the board for the first time, check that the voltages on the following pins are as expected.

CC13xx and CC26xx

- VDDR = 1.68 V for CCFG_FORCE_VDDR_HH = 0
- VDDR = 1.95 V for CCFG_FORCE_VDDR_HH = 1
- DCOUPL = 1.27 V

Do NOT measure directly on the X24M_P and X24M_N nor X48M_P and X48M_N pins since this could brick the device.

10.2 RF Test: SmartRF Studio

In order to use SmartRF Studio for testing, the board needs a connector that enables a debugger to be connected directly to the RF chip:

- For the CC13xx and CC26xx, an XDS100v3, XDS110 or XDS200 should be used.

The required pins in cJTAG-mode are VDDS, GND, RESET, TCK and TMS.

1. Connect a debugger to the board. Open SmartRF Studio and verify that the device is visible in the list of connected devices.
2. Place two good known boards with 2 m distance. In this context “good known boards” are EM’s or LaunchPads from TI. Use a predefined PHY setting in SmartRF Studio that is a closest match to the PHY that will be used in the final product
3. Set one board to PacketRX and the other to PacketTX and transmit 100 packets. Confirm that the packets are received and note the RSSI for the received packets.
4. Replace the board used in TX with the device under test (DUT). Repeat the test described in 3.
5. Replace the board used in RX with the DUT. Replace the board used in TX with a good known board. Repeat the test described in 3.
6. If possible, the measurements should be done with a good known antenna first and then repeated with the antenna that is going to be used in the final design later. A poorly tuned antenna could cause a significant loss in sensitivity/output power.
7. If the results are satisfactory, change the settings from the predefined setting to the RF settings planned to be used in the final product. Repeat the tests described in 3 to 5 with the wanted RF settings.

If the RSSI deviates from the reference, the schematic and layout should be reviewed. Note that if the network between the RF ports and the antenna on the customer board is different from the TI evaluation board, the losses due to SAW filters and switches must be taken into consideration.

10.3 RF Test: Conducted Measurements

For high performance designs it is highly recommended to perform conducted measurements to verify the performance before setting up an RF link.

10.3.1 Sensitivity

1. Disconnect the antenna and perform conducted measurements at the SMA connector or solder a semi rigid coax cable at the 50 Ω point.
2. Configure the board under test and use the PacketRX option in SmartRF Studio similar to the test described in [Section 10.2](#). In PacketRX mode, you can set an expected packet count.
3. Preferred: Use a signal generator that is capable of transmitting data packets. Remember to set up the sync word and CRC correctly.
4. If a signal generator is not available, use an EM/LaunchPad as a transmitter. Use coax cables and attenuation between the EM/LaunchPad SMA connector and the 50 Ω point on the custom board.

NOTE: It is difficult to get an accurate number using this method since the exact values of output power and attenuation are normally not known. Some energy will also travel over the air from the EM to the DUT. In addition, background noise could impact the results. To get more accurate results, the receiver should be placed in a shielded box.

5. SmartRF Studio will calculate the packet error rate (PER) and bit error rate (BER).

If the wanted RF settings are different from the predefined setting, PER vs level should be run in addition. The input power level should be increased in 1- 2 dB steps from the sensitivity limit to around 0 dBm. For each power level, transmit at least 100 packets and record the PER. If the AGC settings are not optimal it is common that the PER for some of the steps will be above 0 (residual PER) and if that is the case the AGC settings have to be reviewed.

If the conducted sensitivity is poor:

- Are the settings the same as the recommended values from SmartRF Studio? If the sensitivity is good when using SmartRF Studio and not with the settings used for the project the settings have to be reviewed.
- What is the frequency difference between the DUT and the signal source? Frequency offset can be measured by transmitting an un-modulated continuous wave
- Is the schematic, including all component values, in accordance with the reference design?
- Is the layout in accordance with the reference design?

10.3.2 Output Power

1. Disconnect the antenna and perform conducted measurements at the SMA connector or solder a semi-rigid coax cable at the 50 Ω point.
2. Preferred: Use a spectrum analyzer (SA). Use 1 MHz RBW for measuring output power.
3. If an SA is not available use an EM or Launchpad with a SMA connection point. Use coax cables and attenuation between the EM/LaunchPad SMA connector and the 50 Ω point on the custom board. Use SmartRF Studio and set the EM/Launchpad in continuous RX and read the RSSI. Note that the RSSI has a given tolerance so the measurement will not be as accurate as the preferred method.

10.4 Software Bring-Up

For CC13xx:

Basic examples for RF and other drivers can be found under TI Drivers under software -> Examples -> Development Tools -> <Development board in question> at <http://dev.ti.com/tirex/#/>. Before starting to write own software it is recommended to run the RF examples that are closest to the wanted application unmodified and verify that they work. Then, if required, change the RF settings to the wanted data rate, and so forth.

For CC26xx and Bluetooth Low Energy:

For more information, see [Initial Board Bring Up](#) on recommended software images to run initially.

Basic examples for RF and other drivers can be found under TI Drivers under software -> Examples -> Development Tools -> <Development board in question> at <http://dev.ti.com/tirex/#/>.

10.5 Hardware Troubleshooting

This section covers some of the common causes for poor performance.

10.5.1 No Link: RF Settings

To get a link between two RF chips the two RF chips have to operate on the same frequency and with the same RF settings. This means that the two have to use the same data rate, deviation and modulation format. A common mistake is that the sync word has been set differently on the two devices, they have to be equal.

10.5.2 No Link: Frequency Offset

For narrow band systems a too large frequency offset between the TX and RX devices could result in no link or a very poor link.

The minimum required RX bandwidth to ensure reception is given by:

$$\text{RX BW} = \text{Signal Bandwidth} + 4 \cdot \text{ppm Crystal} \cdot \text{RF Frequency of Operation} \quad (3)$$

For FSK the signal bandwidth can be approximated as data rate + 2*frequency deviation (Carson's rule).

For CC13x0: For low data rates, the bit repetition patch [CC13x0 Low Data Rate Operation](#) should be used. If this patch is not used, the frequency offset tolerance could be under 10 ppm, which could cause loss of link with a normal crystal tolerance.

10.5.3 Poor Link: Antenna

An antenna needs a matching network in order to tune and reduce the mismatch losses of the antenna. If the antenna is not tuned, energy will be lost both in TX and RX and the link budget will be lower. For more details, see [Section 5](#).

10.5.4 Bluetooth Low Energy: Device Does Advertising But Can Not Connect

If using the 32 kHz crystal oscillator as RTC source:

- Incorrect load capacitors for the 32.768 kHz crystal – causes frequency offset
- 32 kHz crystal does not start up (incorrect load capacitors, crystal missing, soldering issues) – the device defaults to run the RTC from the 48 MHz RC oscillator at 31.25 kHz. For more information, see the *PRCM* chapter in the [CC13x0, CC26x0 SimpleLink™ Wireless MCU Technical Reference Manual](#) and the [C13x2, CC26x2 SimpleLink™ Wireless MCU Technical Reference Manual](#).

If using the 32 kHz RC oscillator as RTC source:

- Calibration is not configured correctly. For more information, see the Bluetooth Low Energy Stack User's Guide that is provided with the SDK.

Incorrect RTC frequency will lead to the device missing the connection events and thus breaking the link with the central device.

To debug this problem, the 32 kHz clock can be output on an I/O pin and measured with a frequency counter. For more information on how to do this, see the *I/O* chapter in the [CC13x0, CC26x0 SimpleLink™ Wireless MCU Technical Reference Manual](#) and the [C13x2, CC26x2 SimpleLink™ Wireless MCU Technical Reference Manual](#). By outputting the clock on a pin, you will always measure the `_selected_` RTC clock source, as well as be able to measure without affecting the clock source (which probing the crystal for example will do).

If using a 32.768 kHz crystal make sure the crystal part is within the requirements outlined in the device-specific CC13xx/CC26xx data sheets. Also make sure that the load capacitors are dimensioned properly as shown in [Section 6.3](#).

Verify that the BLE-Stack has been configured with the correct Sleep Clock Accuracy. The default setting is 40 ppm and can be adjusted with the `HCI_EXT_SetSCACmd` API, see `hci.h` or the TI Vendor Specific API Guide included in the SDK.

10.5.5 Poor Sensitivity: DCDC Layout

It is highly recommended to follow the reference design when it comes to the components connected to the DCDC_SW pin. The shunt capacitor following the series inductor from the DCDC_SW pin has to have a short return path to chip ground from the ground pad (see [Section 4.6](#)). A poor DCDC layout could cause more than 5 dB loss in sensitivity. To check if the sensitivity is limited by the DCDC, turn off the DCDC in the CCFG.c file.

10.5.6 High Sleep Power Consumption

- Note that the chip is not going into the lowest power modes when a debugger is connected
- Software: Use the pinStandby or pinShutdown examples in the relevant SDK
- When measuring current draw on a Launchpad, remove all jumpers.
- Ensure that every IC on the board is powered down.
- If the application is configured to use the 32 kHz crystal (set in CCFG.c), check that this is connected and that the oscillator is running.

11 References

- [TXLine Transmission Line Calculator](#)
- Texas Instruments: [Antenna Selection Quick Guide](#)
- Texas Instruments: [Antenna Selection Guide](#)
- [CC-Antenna-DK2](#)
- Texas Instruments: [CC-Antenna-DK2 and Antenna Measurements Summary](#)
- Texas Instruments: [CC13x0 Low Data Rate Operation](#)
- Texas Instruments: [Monopole PCB Antenna with Single or Dual Band Option](#)
- Texas Instruments: [LAUNCHXL-CC1310 Design Files](#)
- Texas Instruments: [SimpleLink Sub-1 GHz CC1312R Wireless \(MCU\) LaunchPad Dev Kit 868MHz/915MHz App](#)
- Texas Instruments: [2.4-GHz Inverted F Antenna](#)
- Texas Instruments: [LAUNCHXL-CC2640R2 Design Files](#)
- Texas Instruments: [CC26x2R LaunchPad Design Files](#)
- Texas Instruments: [Miniature Helical PCB Antenna for 868 MHz or 915/920 MHz](#)
- Texas Instruments: [LAUNCHXL-CC1350 Design Files](#)
- Texas Instruments: [Monopole PCB Antenna with Single or Dual Band Option](#)
- Texas Instruments: [2.4-GHz Inverted F Antenna](#)
- Texas Instruments: [CC1352R LaunchPad Design Files](#)
- Texas Instruments: [LAUNCHXL-CC1352P-2 Design Files](#)
- Texas Instruments: [LAUNCHXL-CC1352P-4 Design Files](#)
- Texas Instruments: [CC1350STK Design Files](#)
- Texas Instruments: [CC1125 BoosterPack™ for 868/915 MHz BOOSTXL-CC1125](#)
- Texas Instruments: [Matched Integrated Passive Component for 868 / 915 MHz operation with the CC112x, CC117x & CC12xx high performance radio series](#)
- Texas Instruments: [Johanson Technology, Inc. Highly temperature-stable Impedance Matched RF Front End Differential Balun-Band Pass Filter Integrated Ceramic Component](#)
- Texas Instruments: [CC1310 Integrated Passive Component for 779-928 MHz](#)
- Texas Instruments: [Matched Filter Balun for CC1352 and CC1352P](#)
- Texas Instruments: [Anaren 0404 \(BD2425N50200A00\) balun optimized for Texas Instruments CC2420 Transceiver](#)
- Texas Instruments: [Anaren 0404 \(BD2425N50200A00\) balun optimized for Texas Instruments CC2430 Transceiver](#)

References

www.ti.com

- Texas Instruments: [Johanson Balun for the CC26xx Device Family](#)
- Texas Instruments: [CC13x0, CC26x0 SimpleLink™ Wireless MCU Technical Reference Manual](#)
- Texas Instruments: [C13x2, CC26x2 SimpleLink™ Wireless MCU Technical Reference Manual](#)

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from A Revision (February 2019) to B Revision	Page
• Update was made in Section 3.2	12

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated