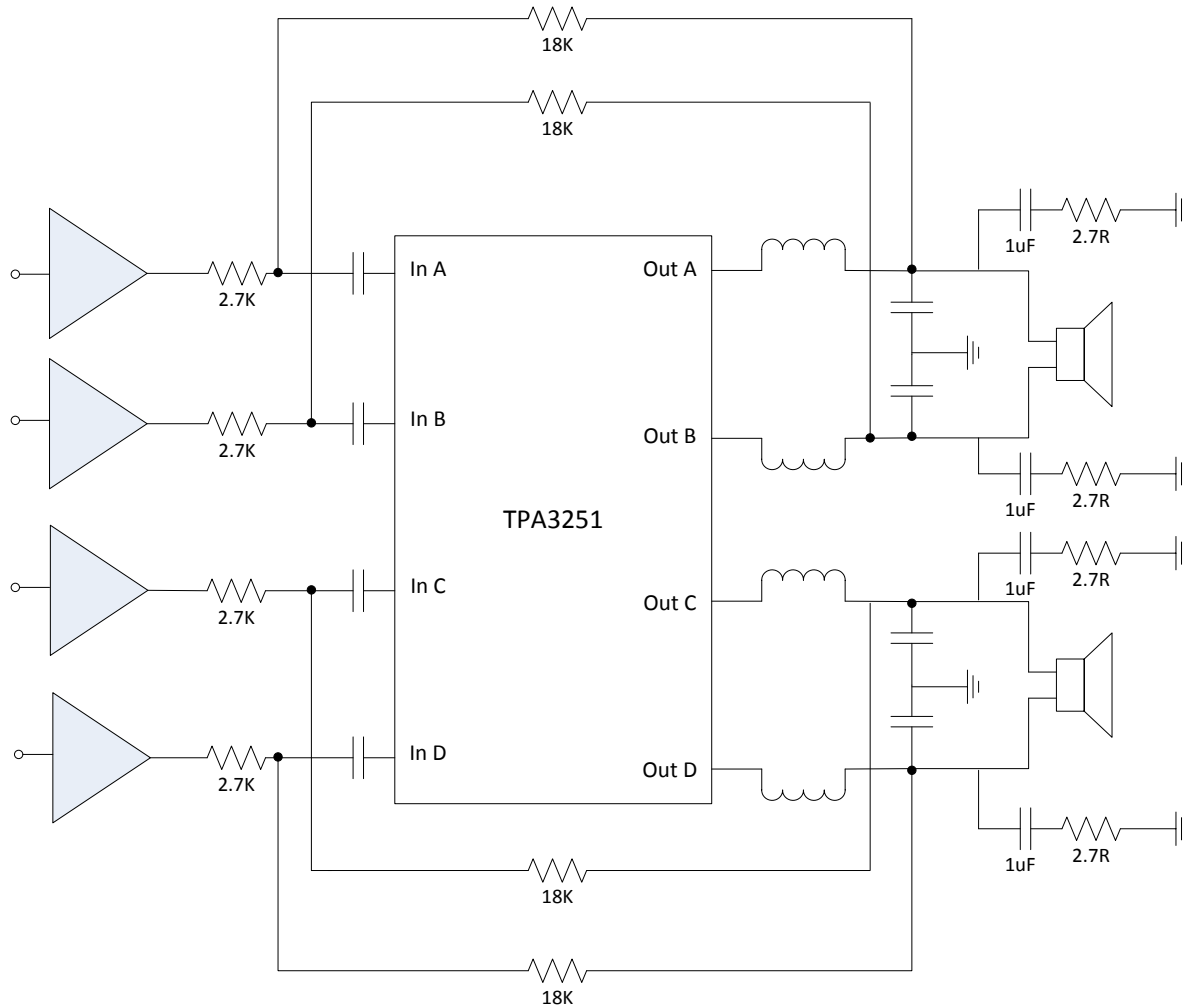



Intro to PFFB

TPA3251

PFFB Implementation (TPA3251)



PFFB Implementation (TPA3251)

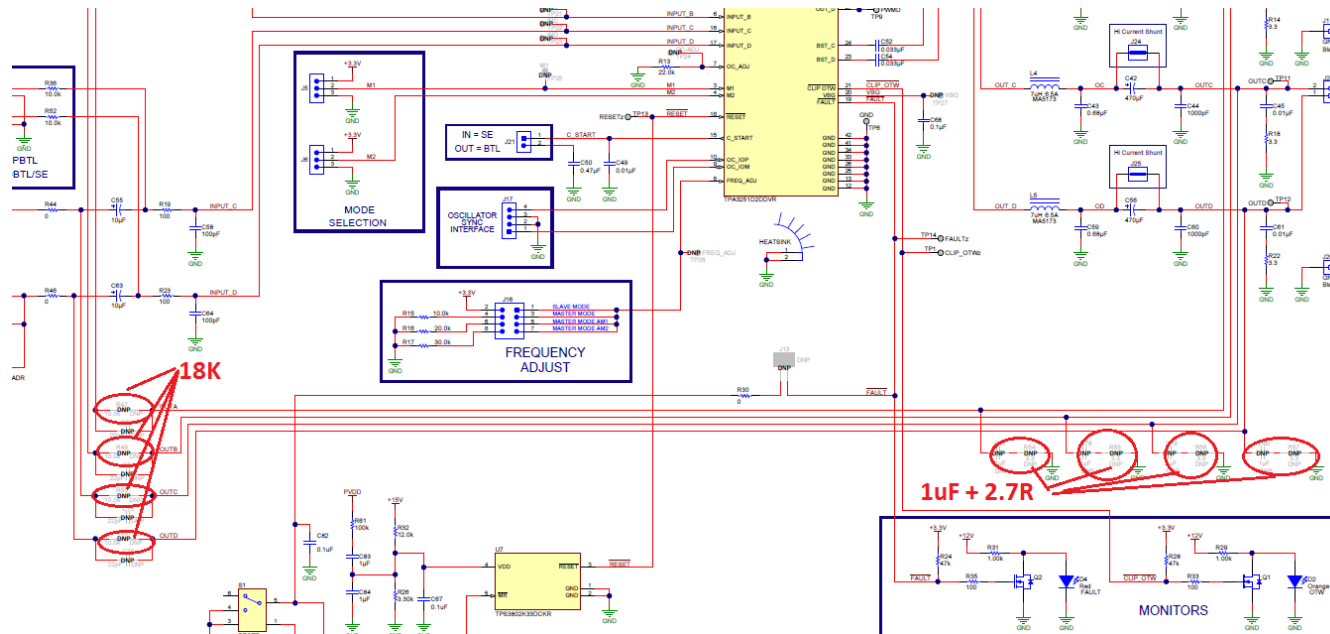

The components are as follows:

- Input Resistors R4 R12 R44 R46 = 2.7K Ω
- Feedback Resistors R47 R49 R50 R51 = 18K Ω
- Zobel Resistors R54 R55 R56 R57 = 2.7 Ω
- Zobel Capacitors C77 C78 C79 C80 = 1 μ F
- Op-Amp Feedback Pole C18 C23 C57 C65 = 330pF

Gain Parameters

$$A_f = \frac{A_0}{(1 + A_0\beta)}$$

$$A_0 = 20 \text{ dB} = 10 \quad \beta = \frac{2.7\text{k}}{(2.7\text{k} + 18\text{k})} = 0.13$$

$$A_f = \frac{10}{(1 + (10 \times 0.13))} = 4.35 = 12.8 \text{ dB}$$

| Gain | TPA3251 (PVDD = 36 V, Fpwm = 600 kHz) | TPA3255 (PVDD = 51 V, Fpwm = 450 kHz) |
|-------------------------|---|---|
| Measured Gain PFFB | 11 | 12.2 |
| Ideal Gain Compensation | 9 | 9.3 |
| Restored System Gain | 20 | 21.5 |

| Feedback Parameters | TPA3251 (PVDD = 36 V, Fpwm = 600 kHz) | TPA3255 (PVDD = 51 V, Fpwm = 450 kHz) |
|-------------------------|---|---|
| Gain Ao (dB) | 20 | 21.5 |
| Feedback Factor β | 0.13 | 0.119 |
| PFFB Gain Af (dB) | 12.8 | 13.8 |
| Negative Feedback (dB) | 7.2 | 7.7 |

Stability

- Stability is measured by % overshoot

$$\text{Overshoot}(\%) = \left(\frac{(V_{\text{peak}}) - V_{\text{ideal}}}{V_{\text{ideal}}} \right) \times 100$$

