


Tapped Inductor Bandpass Filter Design

High Speed Signal Path Applications

7/21/2009 v1.6




Tapped Inductor BP Filter

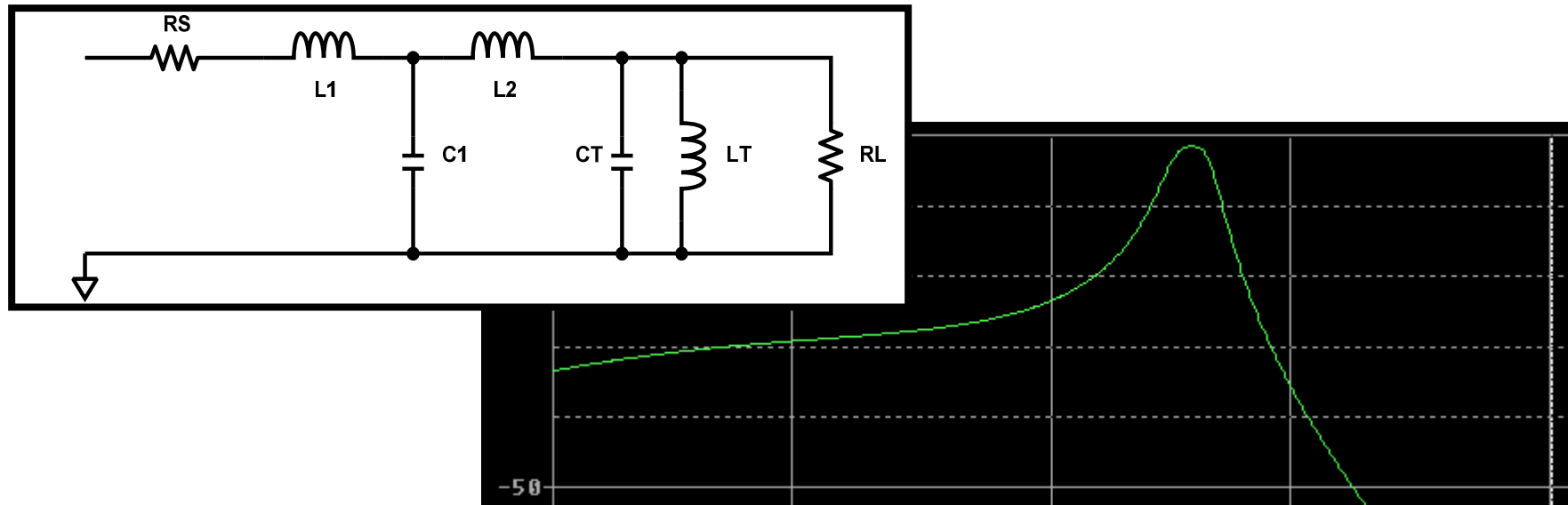

- **1st order (6 dB/oct) LOW frequency roll-off**
 - Shunt L_T
- **4th order (24 dB/oct) HIGH frequency roll-off**
 - Series L_1, L_2 – Shunt C_1, C_T
- **Called “Tapped Inductor” because filter uses a series-L T-match impedance transform**

Tapped Inductor BP Filter

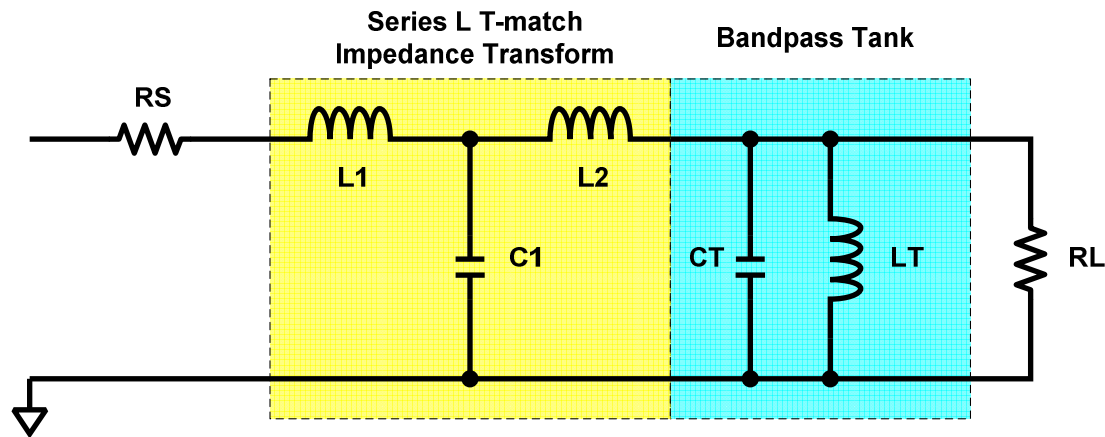


- Tank provides 1st order Bandpass profile
- Impedance transform matches R_L to R_S at center frequency and increases high frequency roll-off to 4th order

Pros / Cons

- Why is this architecture good?

 
- Avoids capacitors in series branches which are very susceptible to shunt parasitics
- Provides best harmonic tone rejection with lowest possible filter complexity
- Good noise rejection despite shallow roll-off at low frequencies
- Relatively easy to design filters up to 300 MHz with 3dB Q~5 ($Q = F_0/BW$)
- Design procedure provides flexible matching of R_L to R_S



- Drawbacks?

- Shallow low frequency roll-off may limit noise performance
- For large R_S , R_L , and large Q's \rightarrow C1 becomes prohibitively small
- Wider passband requires shallower stopband (tradeoff)

Theory

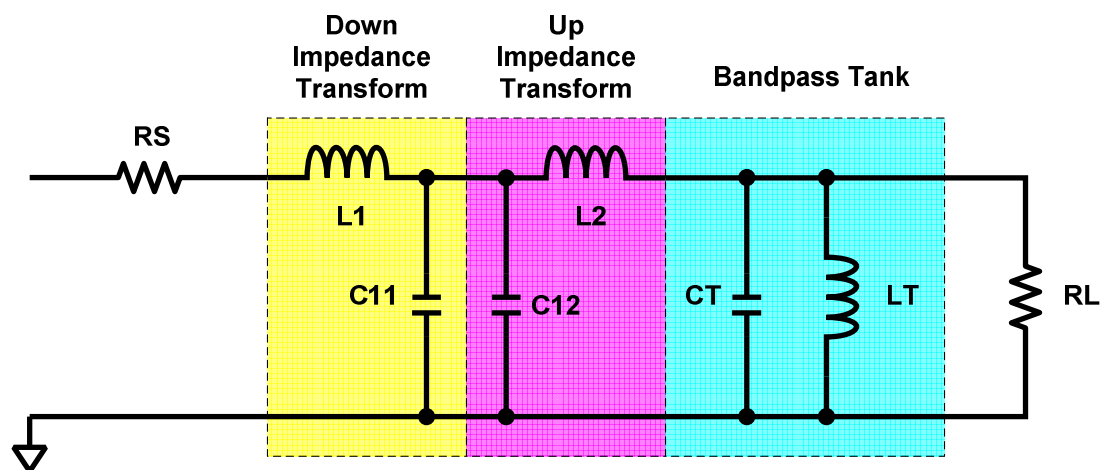


- Filter can be broken into parts for analysis
 - Bandpass Tank
 - T-match split into Up/Down impedance transforms
 - Each section characterized by ω_0 and Q
 - Design procedure works from load up to source

Theory: Filter Loss and Impedance Matching

- Impedance Matching

 - Power transfer maximized and reflections minimized when $R_S = R_{in}$
- R_{in} is equivalent resistance looking into T-match




- Filter Loss

- Related to R_S , R_L , and Q 's used in design
- Certain configurations can cause voltage gain

Theory: Bandpass Tank

- LC Bandpass Tank

 - Impedance should equal R_L at center frequency due to parallel cancellation of L_T and C_T
- Sets the center frequency and influences the BW



- Design procedure

- Choose filter center frequency F_0
- Choose suitable Q_T
- Choose R_S and R_L based on source/driver requirements and passband loss
- Solve for C_T using Q equation
- Solve for L_T using F_0 equation

$$Q_T = 2\pi f_0 \cdot R_L C_T$$

$$f_0 = \frac{1}{2\pi\sqrt{L_T C_T}}$$


Theory: Up Impedance Transform

- Up Impedance Transform

- When properly designed, impedance looking into network will be real and $> R_L$ at center frequency
- Q_U must be high enough to isolate C_{12} from the tank to preserve the tank center frequency

- Design procedure

 - Choose desired Q_U
- Solve for L_2 using Q equation
- Solve for L_2'
- Solve for C_{12} using F_0 equation
- Solve for R_{in}'



$$Q_U = 2\pi f_0 \frac{L_2}{R_L}$$

$$L_2' = L_2 \left(\frac{1 + Q_U^2}{Q_U^2} \right)$$


$$f_0 = \frac{1}{2\pi \sqrt{L_2' C_{12}}}$$

$$R_{in}' = R_L (1 + Q_U^2)$$

Theory: Down Impedance Transform

- **Down Impedance Transform**

 - When properly designed, impedance looking into network will be real and $R_{in} < R_{in}'$ at center frequency



- **Design procedure**

- Choose desired Q_D
- Solve for C_{11} using Q equation and R_{in}' from Up Transform design procedure
- Solve for C_{11}'
- Solve for L_1 using F_0 equation
- Solve for R_{in}

$$Q_D = 2\pi f_0 \cdot R_{in}' C_{11}$$

$$C_{11}' = C_{11} \left(\frac{Q_D^2}{1 + Q_D^2} \right)$$

$$f_0 = \frac{1}{2\pi \sqrt{L_1 C_{11}'}}$$

$$R_{in} = R_{in}' \left(\frac{1}{1 + Q_D^2} \right)$$

Theory: Effect of Q

- **Effect of Q**
 - After load/source/frequency are set, Q's are the only design knobs
 - Closely related to Bandwidth of filter
 - Higher Q typically results in less loss and a narrower filter but makes filter more sensitive and harder to tune on the actual board
- **Choosing Q_T**
 - Intuitive trend is $Q_T \sim F_o/BW$ but the results are not simple
- **Choosing Q_U**
 - Set > 3 to prevent ripples in passband
- **Choosing Q_D**
 - Use equation for impedance matching:
 - OR Set $Q_U < Q_D < 12$ for relaxed component values and possible voltage gain increase

$$\frac{R_L}{R_S} = \frac{1 + Q_U^2}{1 + Q_D^2}$$

Theory: Tips

- For $R_L=4R_S \rightarrow Q_T=5, Q_D=2.34, Q_U=5$
 - Impedance matched, Gain ~ 0 dB
- For $R_L=4R_S \rightarrow Q_T=6, Q_D=3, Q_U=10$
 - Gain > 0 dB
- For $R_L=R_S \rightarrow Q_T=6, Q_D=3, Q_U=3$
 - Loss ~ 6 dB
 - Can't increase Q_U much because R_{in} becomes too small (Avoid)
- Setting low Q_D or Q_U for wide BW can cause deep ripples in passband due to poor impedance transform.
- Increased gain can occur when $R_L > 2R_S$. Set $Q_D > 1.5Q_U$ only under this condition.
- Very large R_L can cause prohibitively small C_1 and large L1, L2

Theory: Tips

- Large Q_T allows for narrower and flatter bandpass but the quality is very sensitive to $(C_{11}+C_{12})$. Variations cause significant misshaping. Difficult to tune frequency.
- Small Q_T allows for easier tuning without misshaping by changing C_T OR $(C_{11}+C_{12})$. Easier to tune with C_T because it is usually much bigger.
- True bandwidth depends on both the tank and T-network.
- Filter voltage gain at center frequency:

$$\left. \frac{V_{out}}{V_{in}} \right|_{f=f_0} \sim 20 \log \left(\frac{R_{in}}{R_S + R_{in}} \right) + 10 \log \left(\frac{R'_{in}}{R_S} \right) + 10 \log \left(\frac{R_L}{R'_{in}} \right) \quad R_{in} = \left(\frac{1 + Q_U^2}{1 + Q_D^2} \right) R_L$$

- For gain > 0 dB: $R_L/R_S > 1$ and $R_S \ll R_{in}$
- An impedance matched filter ($R_{in} = R_S$) has ~0 dB gain for $R_L = 4R_S$


Theory: Tips

• Voltage output Amplifier

- Filter impedance Xform modeled as Transformer with coil ratio of 1:n (therefore an impedance ration of 1:n²)


$$\left. \frac{V_{out}}{V_{in}} \right|_{f=f_0} = \frac{n \cdot R_L}{R_L + n^2 \cdot R_S} \quad n^2 = \frac{1 + Q_U^2}{1 + Q_D^2}$$

 - If $R_L = 4 \cdot R_S$, $n=2$, then $G_V=1$
 - Impedance is also matched because $R_S = R_L/n^2$
 - For a R_S, R_L voltage divider, $G_V=0.8$ (-2dB)
 - The LC network achieves a voltage gain of 2dB



• Current output Amplifier

 - No series R loss, $G_V = n$
- Amplifier requires large R_S, R_L for large amplifier gain
- If $R_L = R_S$, $n=1$, then $G_V=1$
 - Impedance is matched, $Q_U = Q_D$
- If $R_L = R_S$, $n=2$, then $G_V=2$
 - Impedance not matched, risk more ripple in passband




Theory: Tips

- Reducing QD and QU proportionally while maintaining an impedance match widens bandwidth of filter and impedance match


filter profile

Input Impedance
(25 ohm match)


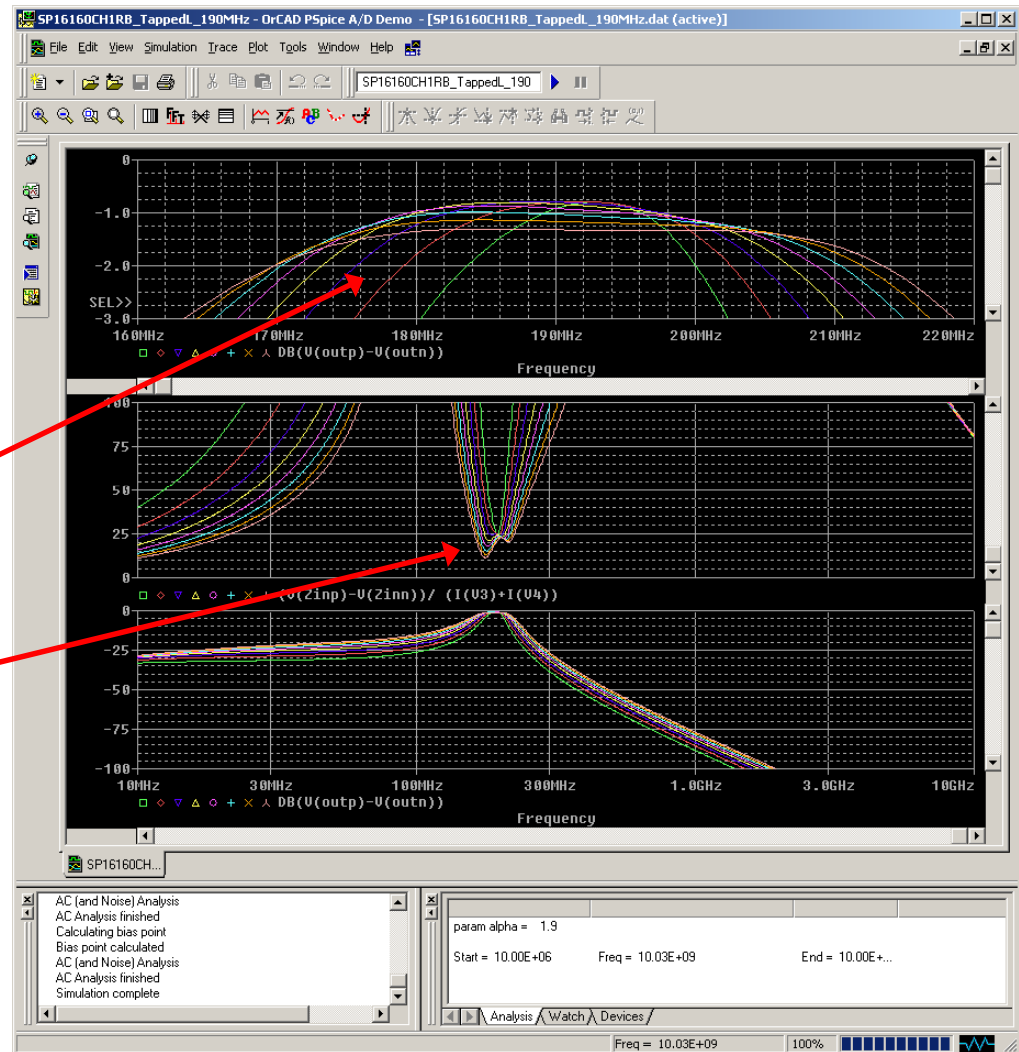


 Example

- $F_0=190\text{MHz}$, 30MHz -1dB Bandpass Filter
- $R_S=50$, $R_L=150$




	A	B	C	D	E
1					
2	Filter Characteristics				
3	Wo	BW	Q		
4	1.90E+08	3.00E+07	6.333333333		
5					
6	Source/Load				
7	RS	RL			
8	50	150			
9					
10	Tuned Tank				
11	QT	L3	C3		
12	6	2.09E-08	3.35E-11		
13					
14	Upward Impedance Xform				
15	Q2	Rin'	L2'	L2	C12
16	3	1500	4.18774E-07	3.77E-07	1.68E-12
17					
18	Downward Impedance Xform				
19	Q1	Rin	C11'	L1	C11
20	7	30	3.83039E-12	1.83E-07	3.91E-12

 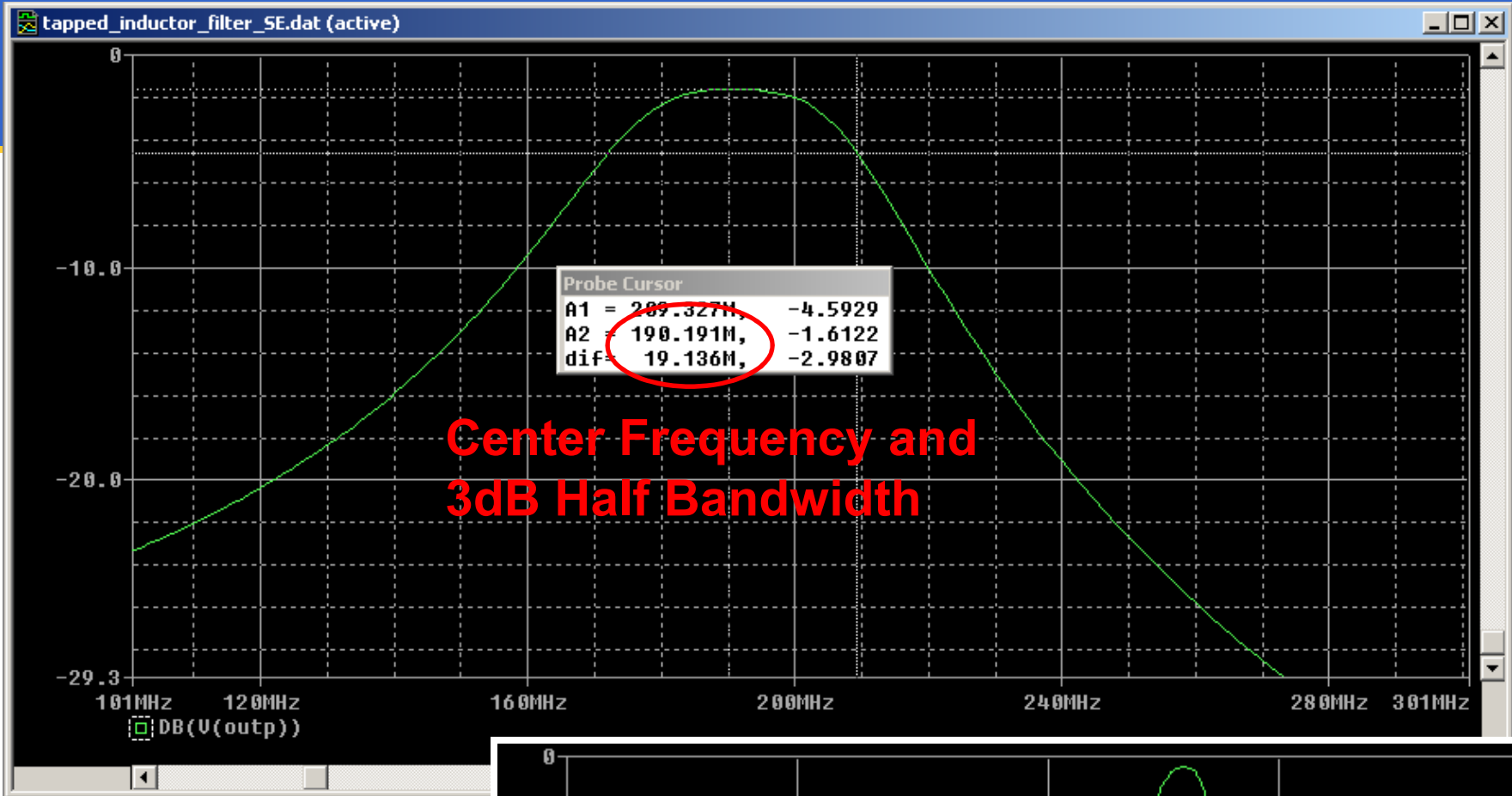

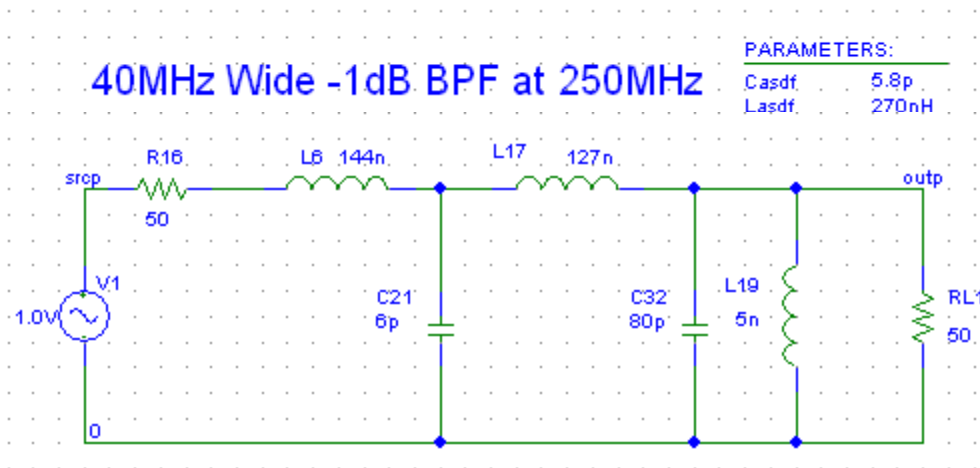
Example

- $F_0=250\text{MHz}$, 40MHz -1dB Bandpass Filter
- $R_S=50$, $R_L=50$




	A	B	C	D	E
1					
2	Filter Characteristics				
3	Wo	BW	Q		
4	2.50E+08	4.00E+07	6.25		
5					
6	Source/Load				
7	RS	RL			
8	50	50			
9					
10	Tuned Tank				
11	QT	L3	C3		
12	6.25	5.09E-09	7.96E-11		
13					
14	Upward Impedance Xform				
15	QU	Rin'	L2'	L2	C12
16	4	850	1.35264E-07	1.27E-07	3.00E-12
17					
18	Downward Impedance Xform				
19	QD	Rin	C11'	L1	C11
20	4	50	2.81927E-12	1.44E-07	3.00E-12
21					

Example

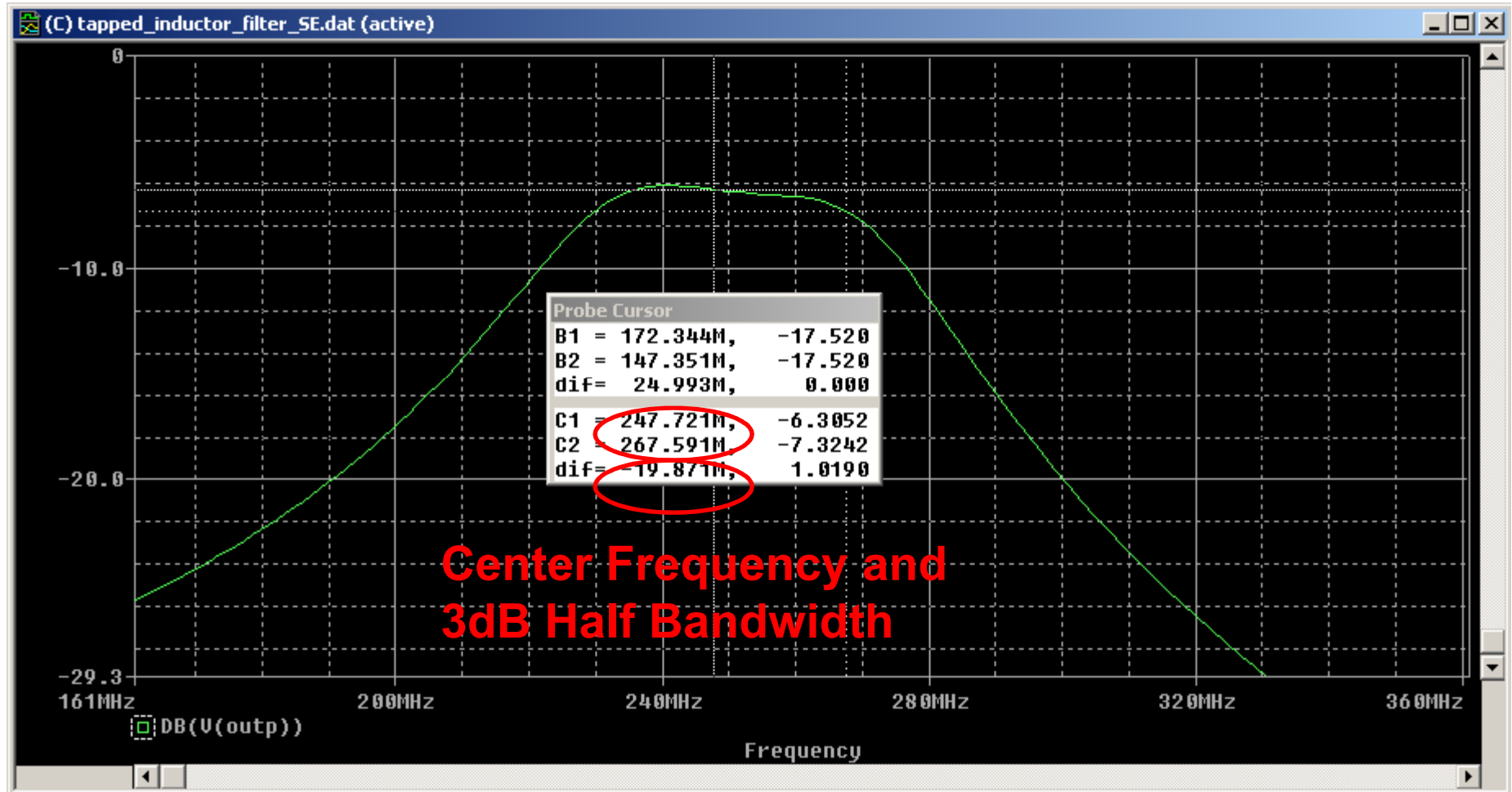


Architecture Example

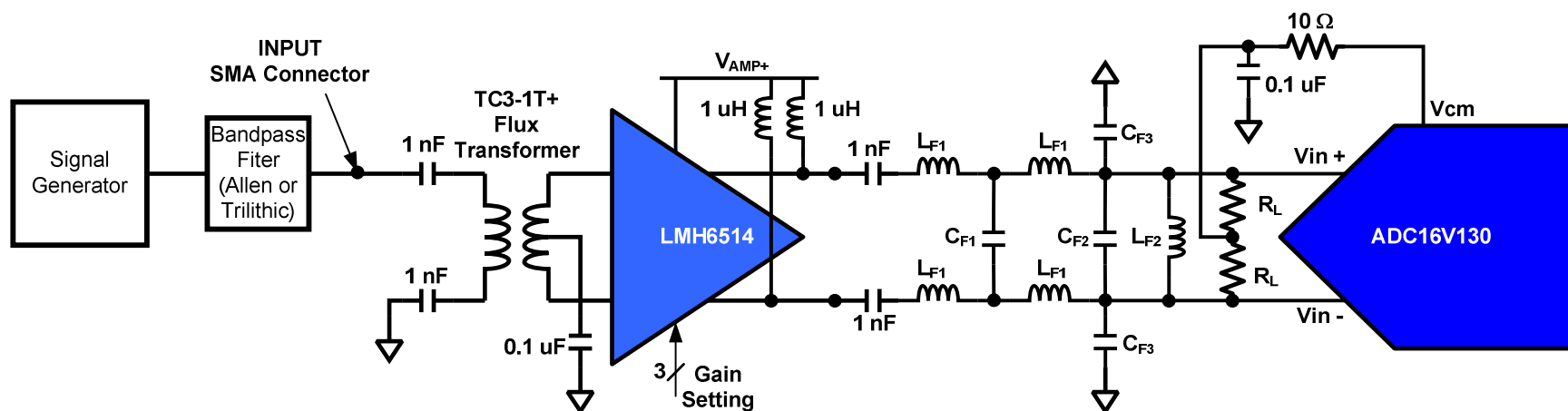

- **Differential implementation**
- **Additional large series caps for AC coupling**
- **ADC sets input common mode through load resistors**
- **Tank caps separated into common mode and differential loads for better charge kickback suppression from ADC**

Practical Issues

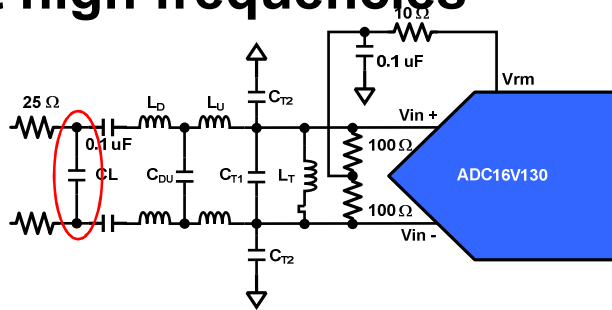
- Input impedance matching good in bandwidth, but has peaking at certain frequencies
- Insert a small cap (CL) after the series output R's of DVGA to reduce impedance resonance at high frequencies



Solid filter profile


Impedance resonances
(swept CL, green: CL=0.1pF)

Peaking due to bond wire inductance

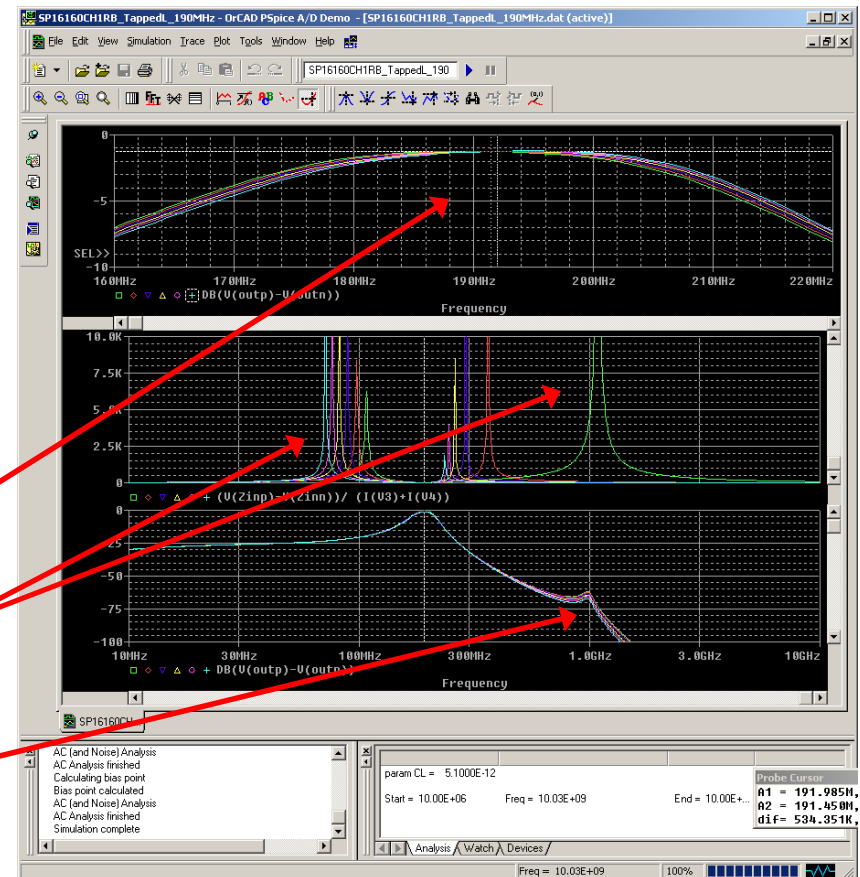

Practical Issues

- **Charge kickback from ADC resonates with bond wire inductance and LC tank (observed in simple model simulation)**
 - Lower tank Q decays faster but bigger initial spike
 - Higher tank Q decays slower but smaller initial spike
- **Differential and CM error depends on whether sampling instant lands on maximum or minimum of kickback ringing**
 - Can create seemingly illogical SFDR variations across signal frequency, amplitude, sampling rate, common-mode capacitance, etc.

 

Sampling Instant for ADC16DV160

References

- T.H. Lee, “The Design of CMOS Radio-Frequency Integrated Circuits,” Cambridge University Press, 2004, pp. 92-99. (Impedance matching)

