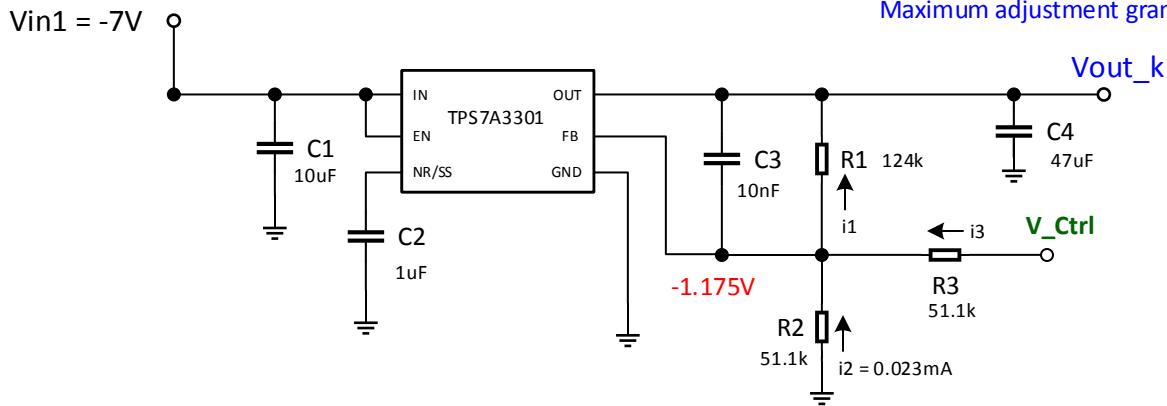


DAC+OpAmp-Controlled, adjustable Vout, Negative-Voltage LDO circuit concept

Four independent Vouts, each adjustable between [-6.2, -1.8]V. Each: 120mA max. Maximum adjustment granularity: 0.02V.



- 1.) If $V_{Ctrl} = -1.175V$, then $i3 = 0$ and $i1 = i2$.
- 2.) Select $R1 = 122.826\text{ k}\Omega$ so that V_{out_k} is mid-range when $i3=0$ (approx. $-4V$). Nearest Standard Value: $124\text{ k}\Omega$, making $V_{out_k} = -4.027V$
- 3.) To get $V_{out_k} = -6.2V$, $i3 = i1 - i2 = [(-1.175+6.2)/124] - 0.023 = +0.017524\text{ mA}$. Thus, V_{Ctrl} would have to be $-0.2795V$
- 4.) To get $V_{out_k} = -1.8V$, $i3 = i1 - i2 = [(-1.175+1.8)/124] - 0.023 = -0.01796\text{ mA}$. Thus, V_{Ctrl} would have to be $-2.093V$.

