

ADS8860 + TLE214x

Art Kay

11/18/2022


TACQ and accuracy target

$$t_{acq} = \frac{1}{500 \text{ kHz}} \cdot 300 \text{ ns} = 1.7 \text{ } \mu\text{s}$$

$$\frac{5 \text{ V}}{2^{16}} = 76.294 \text{ } \mu\text{V} \quad 1 \text{ LSB}$$


$$\frac{5 \text{ V}}{2^{16}} \cdot .5 = 38.147 \text{ } \mu\text{V} \quad \frac{1}{2} \text{ LSB}$$

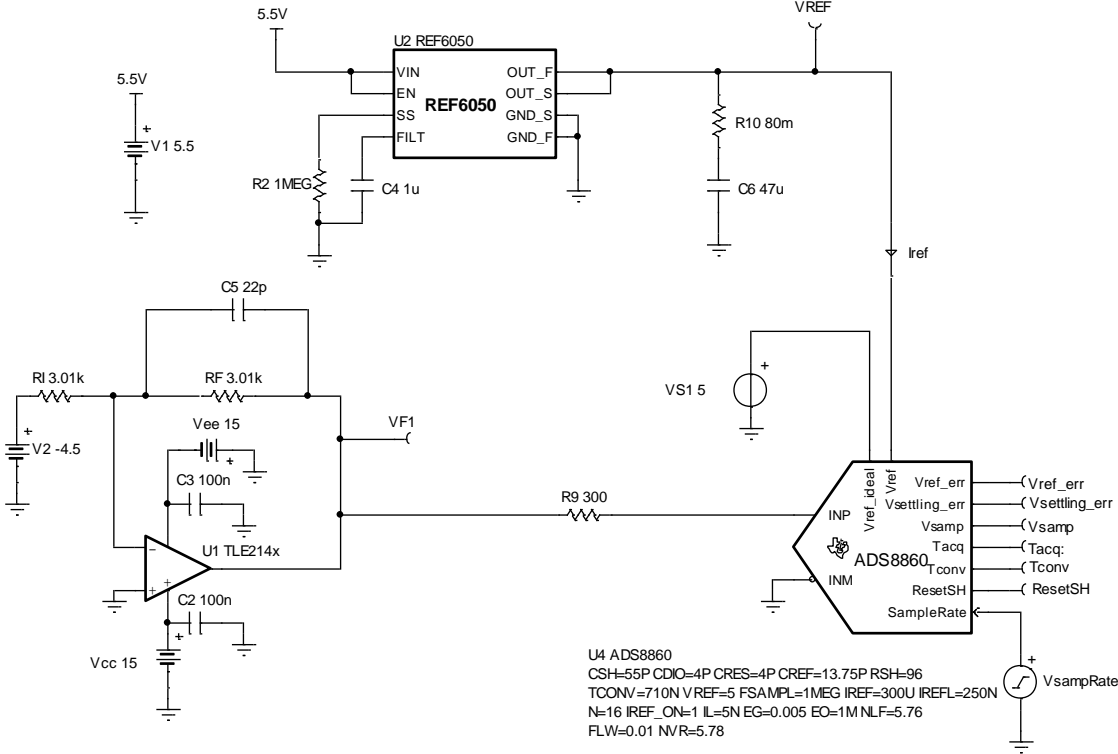Measurement of OPA211 and OPA188: With Filter




This is the circuit I simulated

Simulation results

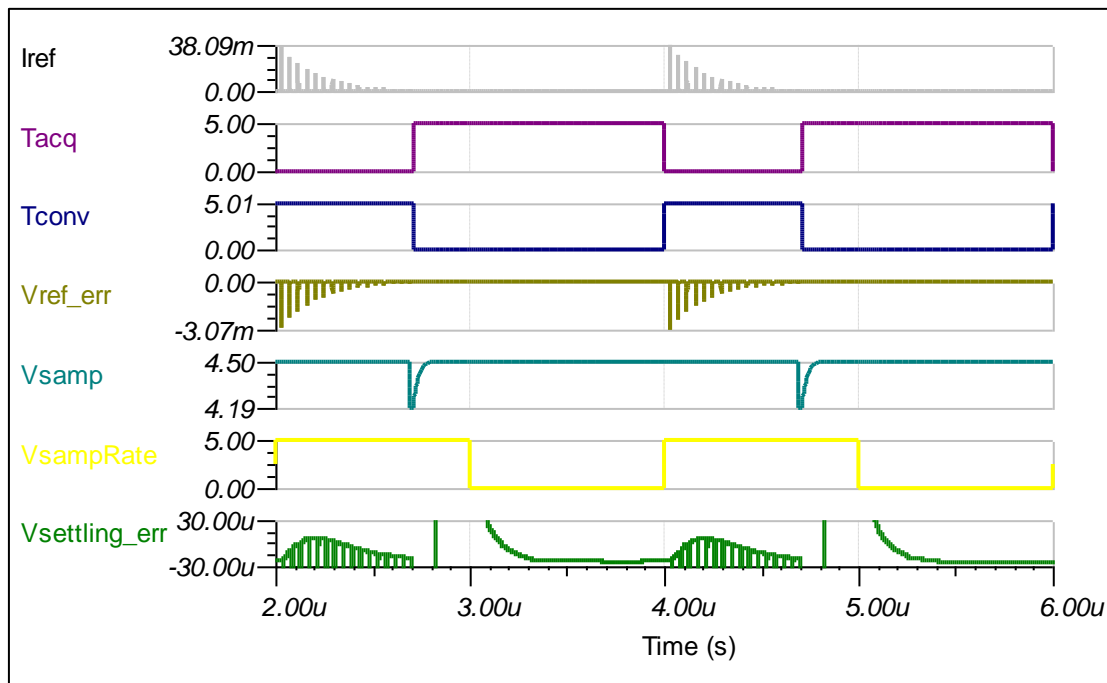

Here is the transient simulation result with $f_s = 500\text{kHz}$. The key curve to look at is the bottom “settling_error” curve. This error settles out to less than 30uV

Optional RC filter

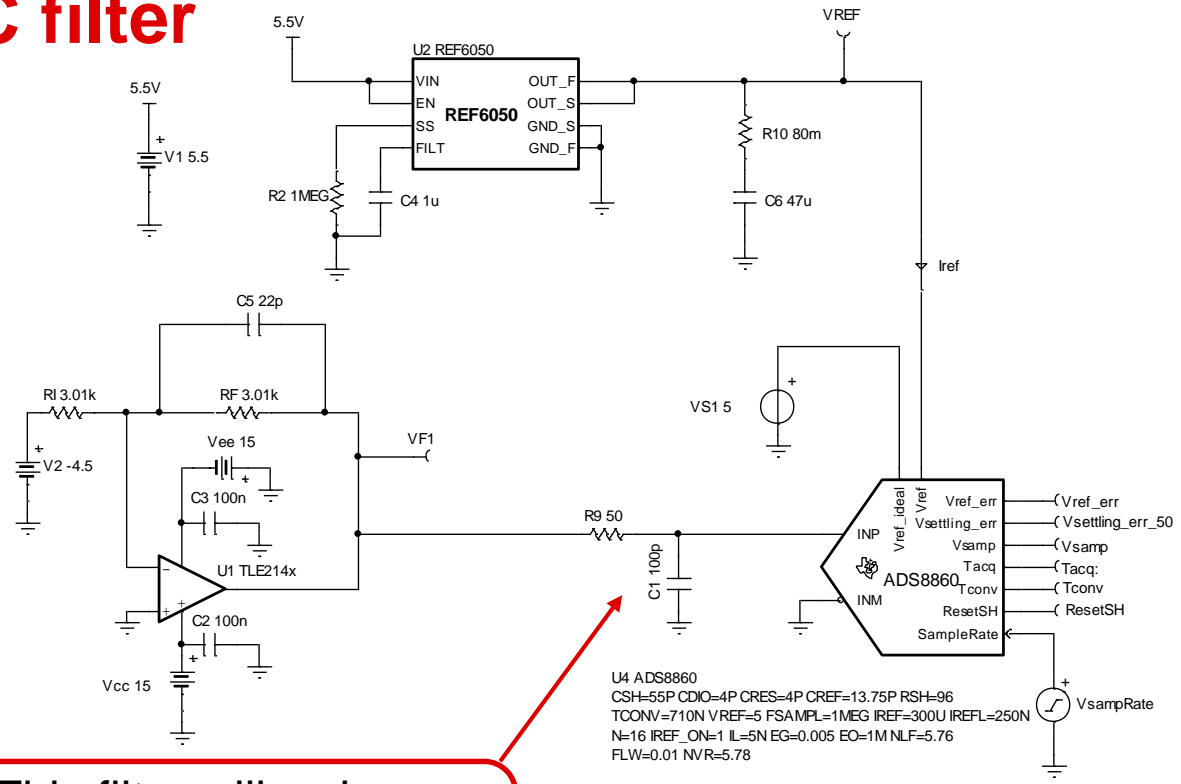

This filter will reduce noise and generally gives better settling

Settling 300 ohm vs 50 ohm x 100pF

