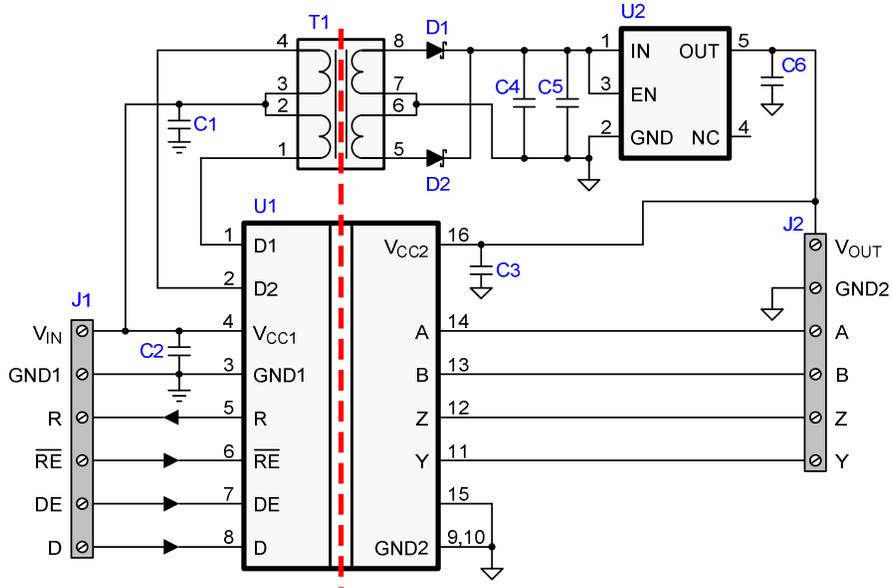


## Circuit Function and Benefits

This circuit provides an isolated, 20 Mbps, 3.3 V to 3.3 V RS-485 interface using the ISO35T, isolated RS-485 transceiver and the TPS76333 high-accuracy linear regulator. This circuit achieves signal and power isolation and at the same time decreases board space and power consumption.



**Figure 1: Isolated, full-duplex, 1 Mbps, 3.3 V to 3.3 V RS-485 Interface**


## Circuit Description

The ISO35T is an isolated differential line transceiver with integrated transformer driver that provides the primary voltage for an isolation transformer. The device is ideal for long transmission lines because the ground loop is broken to allow the device to operate with a much larger common-mode voltage range. The symmetrical isolation barrier of each device is tested to provide 2500 Vrms of isolation between the line transceiver and the logic-level interface.

The galvanically isolated differential bus transceiver is designed for full-duplex data communication on multipoint bus-transmission lines. The transceiver combines a galvanically isolated differential line driver and differential input line receiver.

Any cabled I/O can be subjected to electrical noise transients from various sources. These noise transients can cause damage to the transceiver and/or near-by sensitive circuitry if they are of sufficient magnitude and duration. The ISO35T can significantly reduce the risk of data corruption and damage to expensive control circuits.

The integrated transformer driver consists of an oscillator followed by a flip-flop stage generating two, complementary, 50% duty-cycle square waves. These two signals drive the ground-referenced N-channel power switches. Internal circuitry ensures break-before-make action between the two switches.

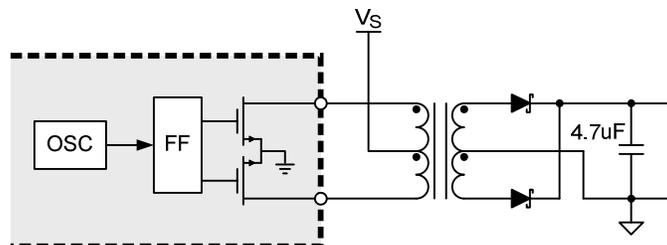

**Figure 2: Simplified transformer driver**

A pair of Schottky diodes and a bulk capacitor build a full-wave rectifier providing the input voltage for the TPS76333 linear voltage regulator.

This low-dropout (LDO) voltage regulator offers the benefits of low-dropout voltage, low-power operation, and miniaturized packaging. The regulator features low dropout voltages and quiescent currents compared to conventional LDO regulators. Offered in a 5-terminal, small outline integrated-circuit SOT-23 package, the TPS76333 is ideal for cost-sensitive designs and for applications where board space is at a premium.

A combination of new circuit design and process innovation has enabled the usual PNP pass transistor to be replaced by a PMOS pass element. Because the PMOS pass element behaves as a low-value resistor, the dropout voltage is very low (typically 300 mV at 150 mA of load current) and is directly proportional to the load current. Since the PMOS pass element is a voltage-driven device, the quiescent current is very low (140  $\mu$ A maximum) and is stable over the entire range of output load current (0 mA to 150 mA).

The TPS76333 also features a logic-enabled sleep mode to shut down the regulator, reducing quiescent current to 1  $\mu$ A maximum at  $T_J = 25^\circ\text{C}$ . The TPS76333 output provides a regulated 3.3 V power supply to the ISO35T bus-side circuitry ( $V_{cc2}$ ) as shown in Figure 1.

Although not required, a 0.047  $\mu$ F or larger ceramic bypass input capacitor, connected between IN and GND and located close to the TPS763xx, is recommended to improve transient response and noise rejection. A higher-value electrolytic input capacitor may be necessary if large, fast-rise-time load transients are anticipated and the device is located several inches from the power source.

Like all low dropout regulators, the TPS76333 requires an output capacitor connected between OUT and GND to stabilize the internal loop control. The minimum recommended capacitance value is 4.7  $\mu$ F and the ESR (equivalent series resistance) must be between 0.3  $\Omega$  and 10  $\Omega$ . Capacitor values 4.7  $\mu$ F or larger are acceptable, provided the ESR is less than 10  $\Omega$ . Solid tantalum electrolytic, aluminum electrolytic, and multilayer ceramic capacitors are all suitable, provided they meet the requirements described above. Most of the commercially available 4.7  $\mu$ F surface-mount solid tantalum capacitors, including devices from Sprague, Kemet, and Nichico, meet the ESR requirements stated above.

### Common Variations


Powering the ISO35T requires a 1CT : 1.5CT transformer (T1) to assure sufficient headroom for the TPS76333 LDO to provide a regulated 3.3 V output. The external transformer used with the ISO35T must have a center-tapped primary winding. The turns-ratio of the transformer must provide the minimum required output voltage at the maximum anticipated load current with the minimum input voltage. Table 1 lists suitable transformers for the circuit in Figure 1.

**Table 1. Recommended Isolation Transformers**

Manufacturer	1:1.5 Transformer
Coilcraft	DA2303-AL
Murata	782485/55C


## Circuit Performance

Figure 3 shows a low frequency sweep for measuring the radiated emissions to demonstrate compliance with the EN55022 standard, which specifies the limits and methods of measurement of radio disturbance characteristics of information technology equipment.

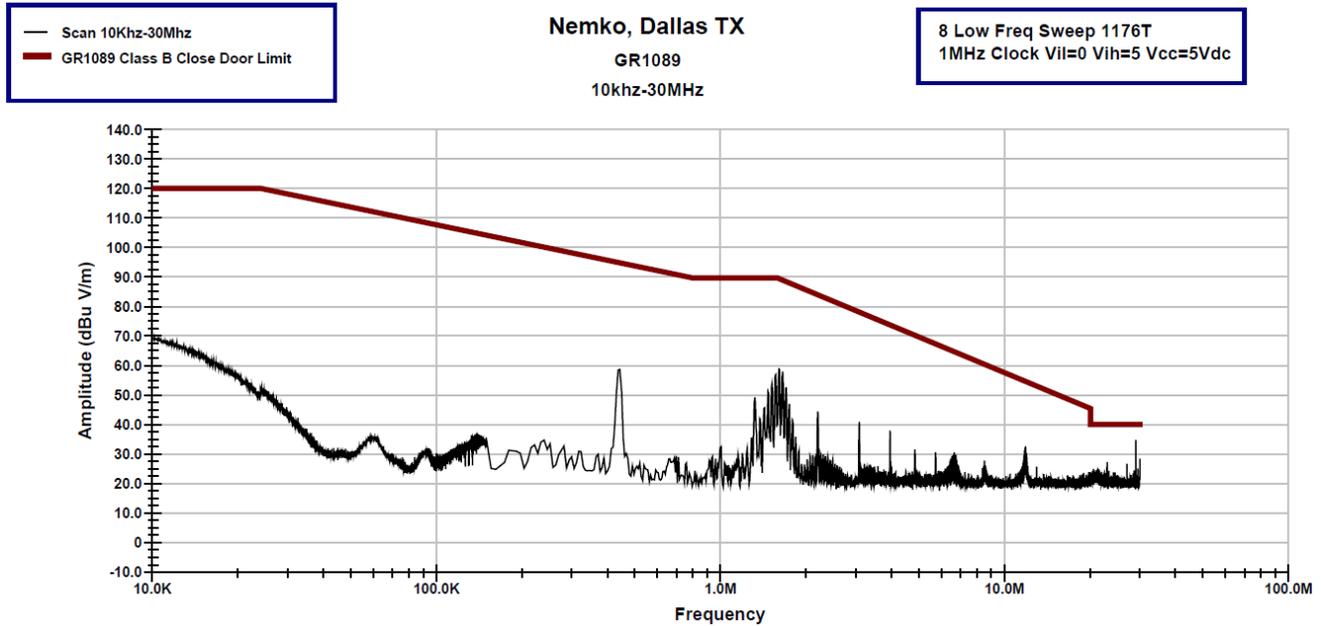

**Figure 3: Radiated emissions (dBuV/m) from 10 kHz to 30 MHz**


Figure 4 shows the circuit's efficiency over the load current. While load currents in the lower 20 mA can be expected for low data rates and no common-mode voltage, higher load currents around 100 mA will be required for high data rates and high common-mode voltages.

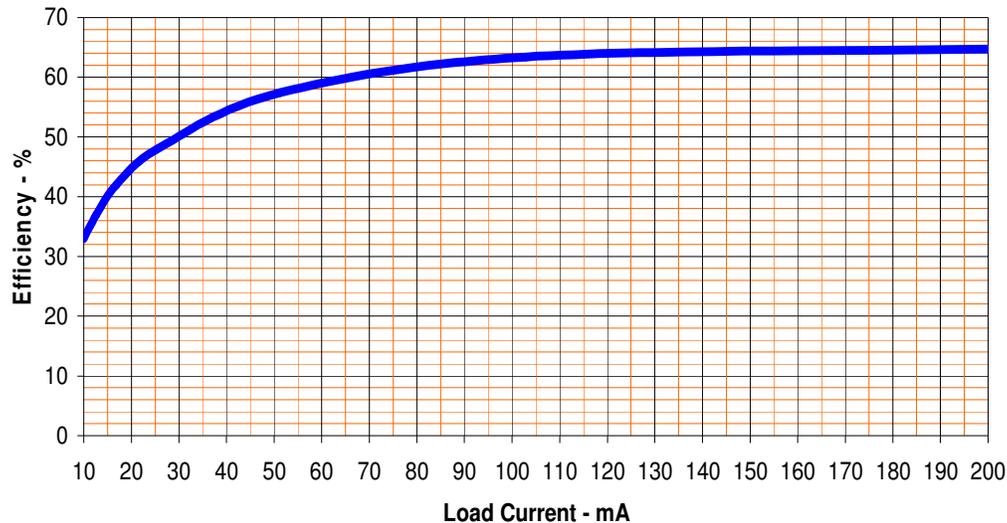

**Figure 4: Efficiency over load current**

## Circuit Layout & BOM

Figure 5 shows the silk-screen as well as the top and bottom layers of the 2-layer board, with the actual dc-dc converter capturing an area of 20 mm x 14 mm only.

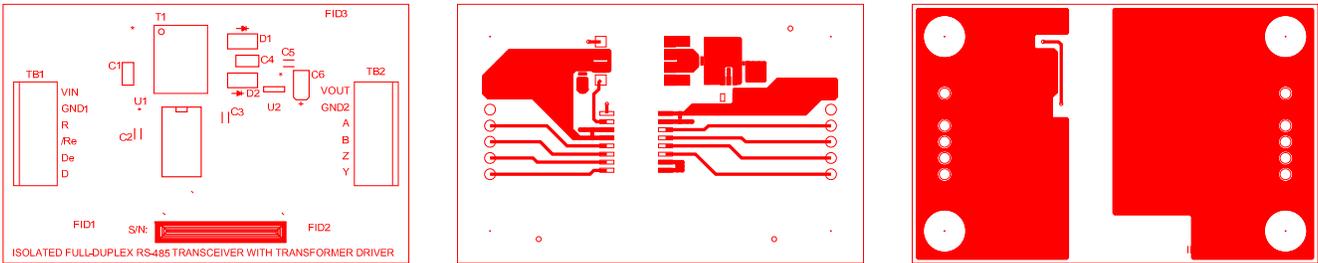

**Figure 5: Board layout: Silk screen (left), top-layer (middle), bottom-layer (right)**

Figure 6 shows an picture of the actual board.



**Figure 6: Reference design board: Top View**

Table 2 shows the final bill of material:

**Table 2. Bill of Material**

Designator	Part No.	Manufacturer	Value	Package/Size
U1	ISO35T	TI	Full-Duplex XCVR	DW-16
U2	TPS76333	TI	3.3V LDO	DBV-5
D1, D2	MBR0520L	Fairchild	0.4 W Schottky	SOD123
C2, C3, C5	C0402C104K4RACTU	KEMET	0.1uF/16V/X7R (Ceramic)	0402 (1 x 0.5 mm <sup>2</sup> )
C1, C4	GRM21BR61C106KE15L	Murata	10uF/16V/X5R (Ceramic)	0805 (2 x 1.25 mm <sup>2</sup> )
C6	T491A475K016AT	KEMET	4.7uF/16V (Tantalum)	3.2 x 1.6 mm <sup>2</sup>
T1	DA2303-AL	Coilcraft	1:1.5	10 x 12 mm <sup>2</sup>
J1, J2	MPT 0,5 / 6-2,54	Phoenix-Contact	6-Position Terminal Block	6.2 x 15.7 mm <sup>2</sup>