

# ***Making the Most of a Low-Power, High-Speed Operational Amplifier***

*Xavier Ramus*
*High-Speed Products*

## **ABSTRACT**

High-speed, high-performance operational amplifiers tend to be associated with high power dissipation. This application note compares the relative performance of several low-power, high-speed operational amplifiers and describes trade-offs to balance performance with low quiescent power dissipation.

## **Contents**

1	Introduction .....	2
2	Bandwidth Performance Comparison .....	2
3	Harmonic Distortion Comparison .....	4
4	Low-Power Filtering .....	8
5	Multiplying DAC Transimpedance Amplifier .....	10
6	Conclusion .....	12

## **List of Figures**

1	OPA890 Open-Loop Gain and Phase Performance .....	2
2	Video Summing Amplifier Circuit.....	3
3	VFA Loop Gain (Typical Performance) .....	4
4	CFA Loop Gain (Typical Performance) .....	4
5	OPA2889 Low-Frequency Harmonic Distortion (Gain of $-1V/V$ ) .....	5
6	OPA683 Low-Frequency Harmonic Distortion (Gain of $-1V/V$ ).....	5
7	OPA683 Open-Loop Transimpedance Gain Performance .....	6
8	OPA2889 Open-Loop Gain Performance.....	6
9	OPA847 Low-Frequency Harmonic Distortion (Gain of $-10V/V$ ) .....	7
10	OPA683 Low-Frequency Harmonic Distortion (Gain of $-10V/V$ ) .....	7
11	MFB Filter Topology Using the OPA2889 .....	8
12	MFB Filter Frequency Response .....	8
13	Single-Supply Sallen-Key Filter Implementation .....	9
14	Butterworth Low-Pass Filter Frequency Response .....	10
15	Multiplying DAC Transimpedance Driver .....	10
16	Multiplying DAC Frequency Response Using the OPA890 as Output Stage.....	11

## 1 Introduction


Achieving undeniably portable instrumentation requires the use of a low power dissipation operational amplifier. It is extremely difficult to balance various low-power application circuits while maintaining high system performance. This difficulty is partly the result of the ac performance degradation, such as slew rate and bandwidth, as the amplifier quiescent current is reduced. In this application report, we first start with bandwidth performance comparison, then move to harmonic distortion, and see what actual losses we must address with low quiescent current devices. This document concludes with the analysis of several application circuits as well as reviewing the advantages of each amplifier topology for each application.

## 2 Bandwidth Performance Comparison

A useful practice for voltage-feedback amplifiers (VFAs) is to do a side-by-side comparison of the gain bandwidth product (GBP) and the quiescent current for a given op amp.

Note that for different op amp architectures such as the current-feedback amplifier (CFA), this approach does not work because a CFA does not have a GBP. Instead, the bandwidth of the highest gain shown in the product data sheet is used to mirror the GBP definition of the VFA.

The method used to derive the GBP from the data sheet is provided below for a high-speed VFA. It is extremely rare to have the unity-gain bandwidth be equal to the gain bandwidth product. This rarity is as much the result of the practice of not having overcompensated amplifiers as it is the effects of package parasitics that extend the unity-gain bandwidth. For high-speed amplifiers, you must measure the GBP at gain of 40dB or greater in the open-loop gain graph. The example performance graph shown in [Figure 1](#) is taken from the [OPA890](#) data sheet.

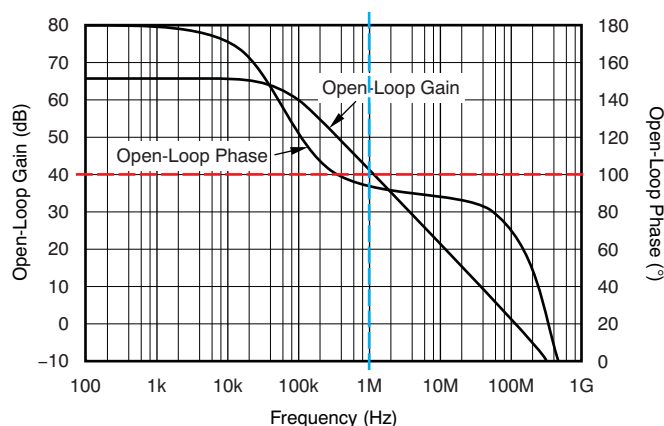

**Figure 1. OPA890 Open-Loop Gain and Phase Performance**

In [Figure 1](#), at the intersection of the red line and the blue line, you measure the GBP; in the case of the OPA890, this measurement results in a bandwidth of 1.3MHz for a 100V/V gain (40dB), or 130MHz GBP. This number is consistent with the number reported in the  $\pm 5V$  electrical specifications table of the device data sheet.

Table 1 summarizes the bandwidth and quiescent current information for various low-power, high-speed VFAs and CFAs.

Table 1. VFA and CFA Comparison

VFA Device	Gain Bandwidth Product (MHz)	Quiescent Current (mA)	
<a href="#">OPA890</a>	130	1.1	
<a href="#">OPA2889</a>	75	0.46	
<a href="#">THS4281</a>	38	0.8	
CFA Device	Bandwidth (MHz)	Gain <sup>(1)</sup> (V/V)	Quiescent Current (mA)
<a href="#">OPA684</a>	71	100	1.7
<a href="#">OPA683</a>	35	100	0.94

<sup>(1)</sup> Highest gain recommended for this device.

By comparing the OPA890 with the OPA683, we can see the clear advantage of using a current-feedback amplifier for high-gain applications. If we tried to use the OPA890 in a 100V/V application, we would achieve a 1.3MHz, -3dB bandwidth. This performance pales in comparison with the 35MHz bandwidth of the OPA683, or for slightly more quiescent power dissipation, the 71MHz bandwidth of the OPA684.

Note that all of these devices are capable of operating on a +3V supply; at this low supply voltage, though, only the THS4281 has the full output voltage swing because it is a rail-to-rail input/output (RRIO) op amp.

The application described in Figure 2 takes advantage of the low-power CFA OPA684 for a video summing amplifier. In this configuration, the OPA684 provides greater than 120MHz bandwidth. If a VFA (such as the OPA890) were used instead, the maximum bandwidth would be limited to 15.5MHz as a result of the gain bandwidth product dependency for the VFA architecture. To achieve the same bandwidth as the OPA684, a 1GHz GBP VFA would be required. Although such devices are readily available, the quiescent current would have to be increased tenfold.

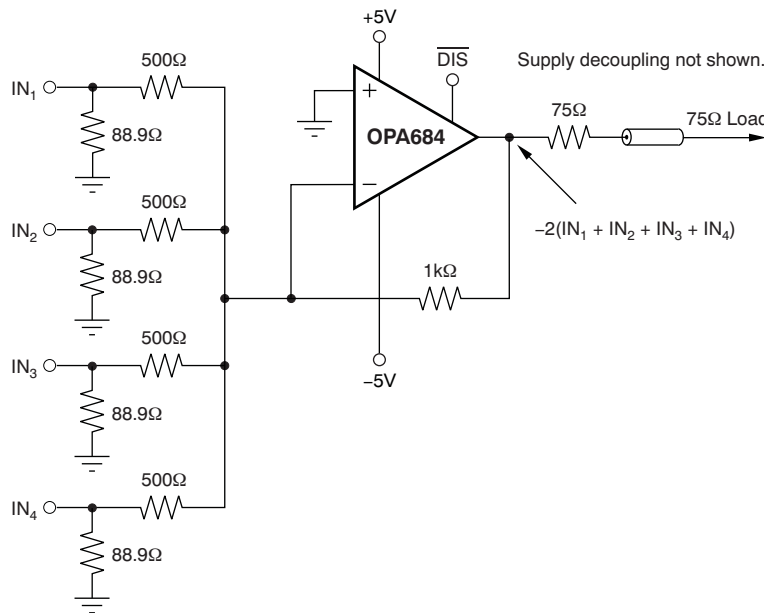



Figure 2. Video Summing Amplifier Circuit

Figure 2 shows a typical inverting summing application where four sources are summed through 500Ω gain resistors while also including an 88.9Ω terminating impedance, to present a 75Ω input impedance to each source. The gain for each channel is -2V/V to the output pin and -1V/V to the matched load. For the


OPA684, the extremely low inverting input impedance ensures non-interactive summing for all of the channels. The amplifier bandwidth is largely independent of variations in the gain setting elements, and instead depends primarily on the feedback resistor value. This type of circuit may be used to sum numerous signals together or, where the earlier stages can be disabled, to allow multiple channels to be brought together with only the active channel passing on to the output.

### 3 Harmonic Distortion Comparison

Harmonic distortion for both VFAs and CFAs depends on the loop gain. For a VFA, the loop gain is the difference between the noise gain of the closed-loop amplifier and the open-loop gain; for a CFA, it is the difference between the compensation element and the open-loop transimpedance gain. [Figure 3](#) shows the loop gain performance for a VFA, while [Figure 4](#) illustrates the loop gain performance for a CFA.

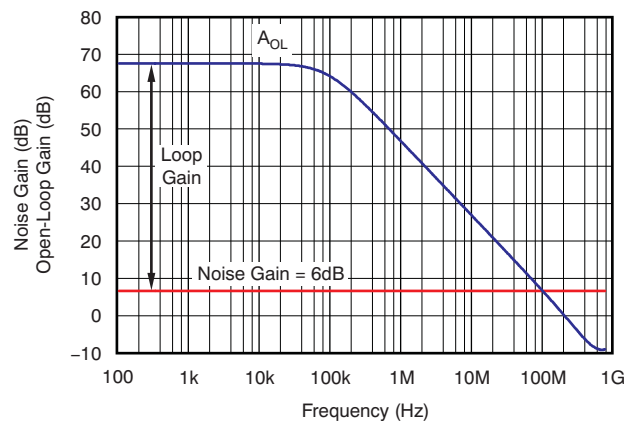

**Figure 3. VFA Loop Gain (Typical Performance)**

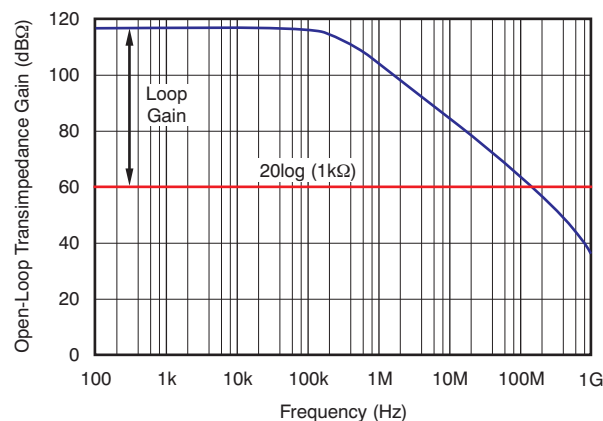

**Figure 4. CFA Loop Gain (Typical Performance)**

By comparing [Figure 3](#) and [Figure 4](#), we can see that a CFA has less loop gain than a VFA for low-gain operation if comparing dB to dBΩ directly. This characteristic indicates that a CFA may maintain better distortion at higher gains than does a VFA if only the gain resistor is changed. Conversely, at low gains, the VFA achieves much better distortion than the CFA if the gain is adjusted using only the gain resistor. Note that for both architectures, loop gain varies with frequency. The CFA maintains a higher loop gain with higher frequency than does a VFA.

To the first order, the loop-gain of a CFA depends on the feedback resistor. To the second order, it depends on the noise gain and the inverting input resistance, as can be seen in the following equation.


$$R_{\text{COMP}} = R_F + r_i \times \text{NG}$$

With:


- $R_{\text{COMP}}$ : Total compensation of a CFA
- $R_F$ : Feedback resistor
- $r_i$ : Inverting input resistance
- NG: Noise Gain

As the NG increases,  $R_F$  can be reduced to optimize the bandwidth.

As an example, the relationship between distortion and the amplifier architecture for low gain performance is shown in the harmonic distortion graphs for the [OPA2889](#) and [OPA683](#). These plots, tested under the same conditions to 1MHz, are shown in [Figure 5](#) and [Figure 6](#), respectively.

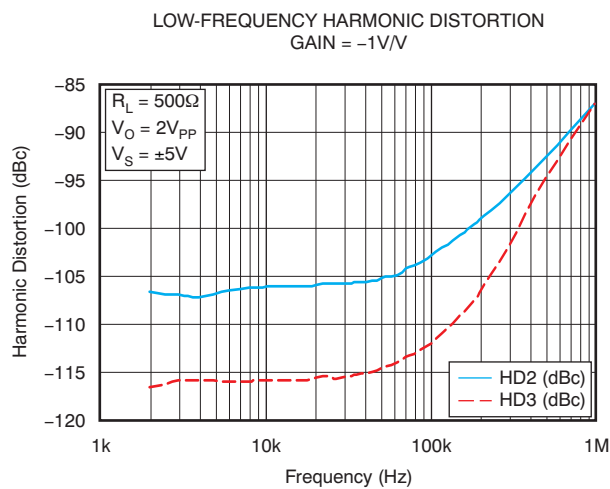

**Figure 5. OPA2889 Low-Frequency Harmonic Distortion (Gain of  $-1V/V$ )**

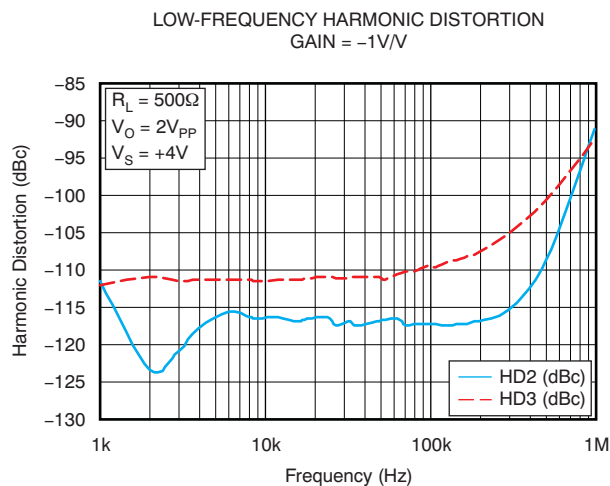

**Figure 6. OPA683 Low-Frequency Harmonic Distortion (Gain of  $-1V/V$ )**

Note that as the open-loop gain for a VFA and the open-loop transimpedance gain for a CFA decrease, the harmonic distortion deteriorates.

The open-loop transimpedance gain of the OPA683 is shown in Figure 7. Here, the roll-off frequency of the open-loop transimpedance gain matches the increase in distortion in Figure 6. The same relation between roll-off of the open-loop gain and corner frequency at which the distortion increases can be observed for the OPA2889, as Figure 8 illustrates.

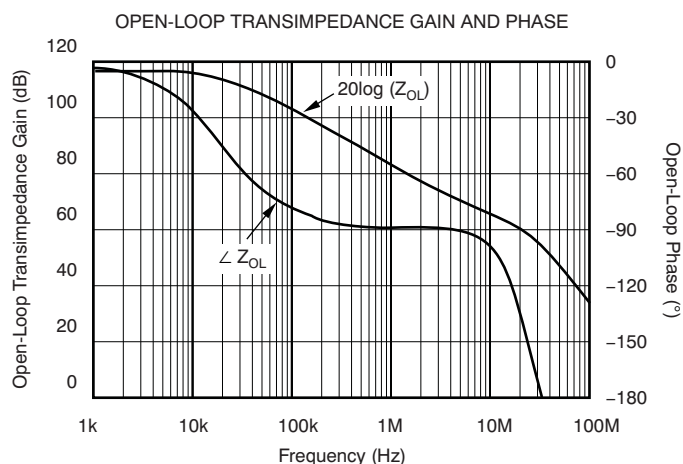


Figure 7. OPA683 Open-Loop Transimpedance Gain Performance

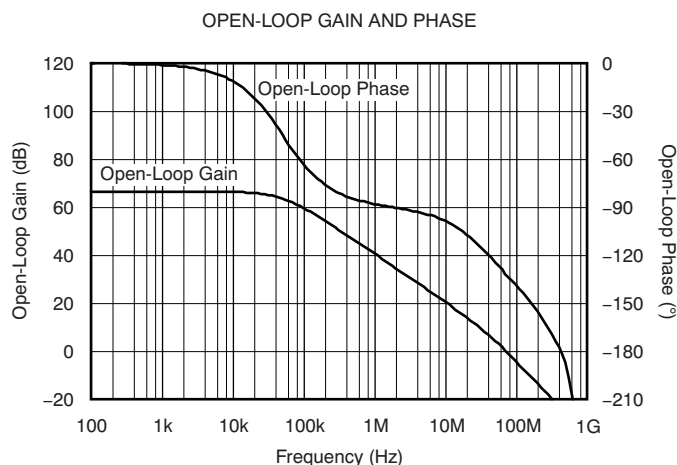


Figure 8. OPA2889 Open-Loop Gain Performance

Keeping in mind that CFAs do have an advantage for high-gain circuits, how does the OPA683 compare to a high-bandwidth, decompensated VFA? Figure 9 and Figure 10, respectively, compare the OPA847 to the OPA683.

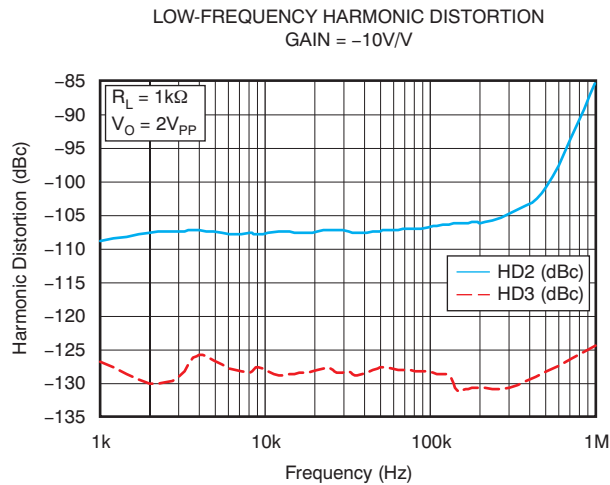


Figure 9. OPA847 Low-Frequency Harmonic Distortion (Gain of -10V/V)

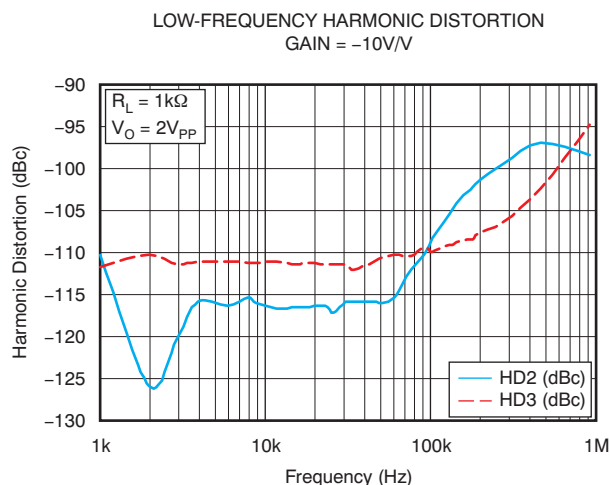


Figure 10. OPA683 Low-Frequency Harmonic Distortion (Gain of -10V/V)

Recall that at a gain of 100V/V, the OPA683 continues to have a bandwidth of 35MHz. The OPA847, with a GBP of 3900MHz, would achieve 39MHz for the same gain. Distortion, as shown in Figure 9, is very close at 100kHz to that of the OPA683; but the OPA847 requires 18.1mA to achieve this level of performance, whereas the OPA683 requires only 0.94mA.

Why then would we use the OPA847?

This amplifier, with its much higher quiescent current, also offers many specifications that the OPA683 cannot achieve—such as very low noise and (for a high-speed amplifier) relatively good dc precision. On the other hand, the OPA683 has more drive capability.

All in all, the final application dictates the amplifier requirements; but low-power devices should not necessarily be excluded in favor of higher dissipation amplifiers when they have adequate performance for the end application.

## 4 Low-Power Filtering

There are several common filtering architectures, among which two active-filter approaches are prominent: the multiple-feedback filter and the Sallen-Key filter.

### 4.1 MFB Filters

The *multiple-feedback filter* (MFB) is also called an infinite gain filter because the operational amplifier operates as an integrator. A typical fully-differential MFB filter is shown in Figure 11 with a 2MHz Butterworth filter frequency response shown in Figure 12.

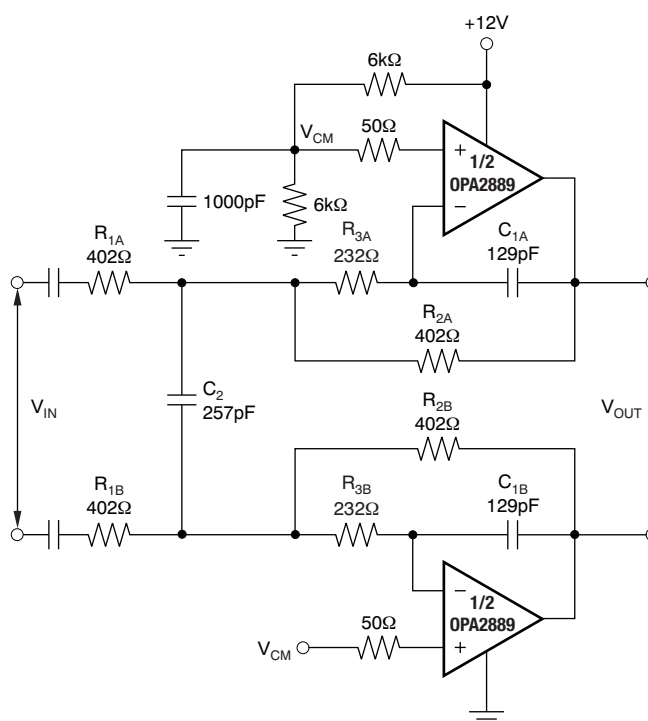


Figure 11. MFB Filter Topology Using the OPA2889

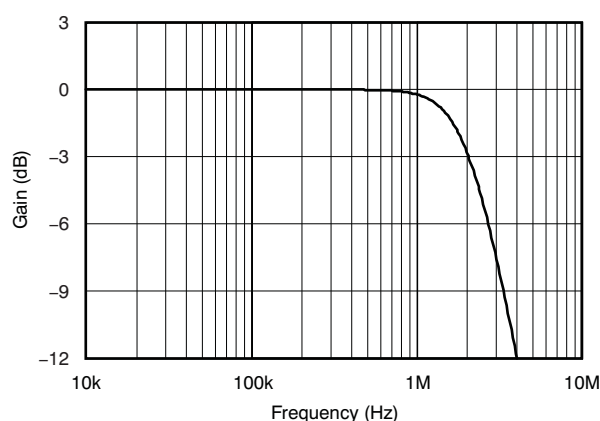


Figure 12. MFB Filter Frequency Response

In the circuit shown in Figure 11, the noninverting inputs are used to set the common-mode voltage ( $V_{CM}$ ) at the output of the differential circuit. In this case, it is generated by two 6k $\Omega$  resistors that set the reference at the mid-supply, and bypassed by a 1nF capacitor. This capacitor eliminates the high-frequency noise contribution of the 6k $\Omega$  resistors. A 50 $\Omega$  series resistance on the noninverting input



helps isolate any LC parasitic elements and avoids potential oscillations. The common-mode gain for each of the amplifier is 1V/V. Consequently, a unity-gain stable amplifier is required. A non-unity-gain stable amplifier may be used in this application to provide better distortion, if necessary, at the expense of additional components in order to provide the adequate noise gain shaping to the common-mode gain of the amplifier.


Note that because of the capacitance across the feedback path, a VFA is required for this filter. CFA use is not recommended with this filter architecture. The filter design here is a Butterworth filter and has been implemented using the following component ratios:

- $f_o = \frac{1}{2\pi RC}$
- $R_1 = R_2 = 0.65 \cdot R$
- $R_3 = 0.375 \cdot R$
- $C_1 = C$
- $C_2 = 2 \cdot C$

One advantage of this type of filter is the independent setting of characteristic pulsation and the quality coefficient  $\omega_o$  and Q. This topology is normally used in filters that have high Qs and require a high gain.

## 4.2 Sallen-Key Filters

A Sallen-Key topology is normally used to set the gain independently of the filter. In a unity-gain configuration, this filter is usually applied in filters with high-gain accuracy and low Q. A typical Sallen-Key filter circuit, as Figure 13 illustrates, shows a single-supply, low-pass filter with a 4V/V gain. The dc noise gain is set to 1V/V because of the series capacitor in the gain. With this dc isolation for the gain, the bias can be easily set by a resistor divider at the filter input. This technique is accomplished here with two 12.5k $\Omega$  resistors. The filter resistors and capacitors have been adjusted to provide a Butterworth (Q = 0.707) response with a  $\omega_o = 2\pi \cdot 5\text{MHz}$ . This approach gives a flat passband response with a -3dB cutoff at 5MHz.

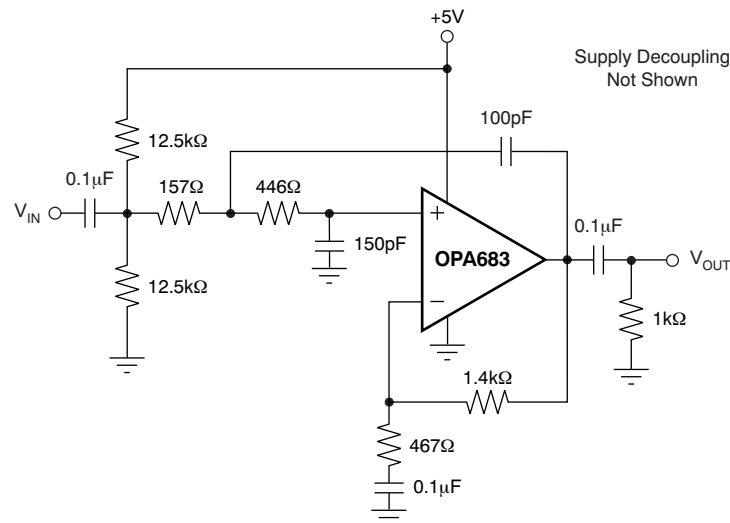

**Figure 13. Single-Supply Sallen-Key Filter Implementation**

The OPA683 provides an exceptionally capable gain block for implementing Sallen-Key-type filters. Typically, the bandwidth interaction with gain settings for low-power amplifiers constrain these filters to using unity-gain amplifiers. Because the OPA683 holds very high bandwidth to high gains, however, applications that provide signal gain as well as the desired filter shape are easily implemented.

Figure 14 shows an example of a 5MHz, second-order, low-pass filter where the amplifier provides a voltage gain of 4V/V. This single-supply implementation (applicable to single +12V operation as well) consumes only 5.1mW quiescent power.

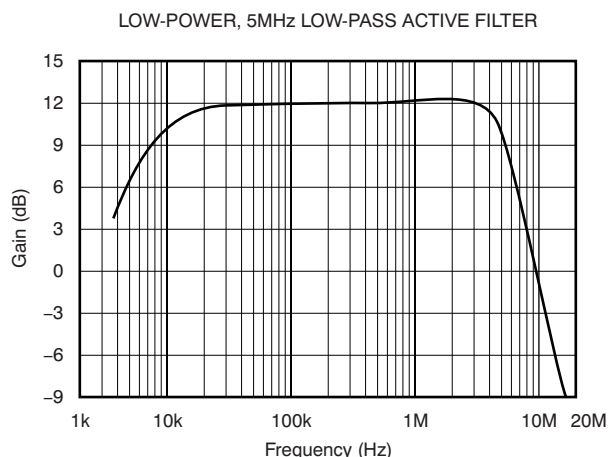


Figure 14. Butterworth Low-Pass Filter Frequency Response

## 5 Multiplying DAC Transimpedance Amplifier

Multiplying digital-to-analog converters (DACs), such as the [DAC7822](#), can make good use of the low-power, high slew rate VFA. A typical circuit, shown in [Figure 15](#), shows the OPA890 used as the output transimpedance driver. Note that a CFA can be used in transimpedance applications; however, because the feedback element is also the compensation element, a CFA would generally provide very little flexibility in a design where bandwidth is important. Additionally, in a VFA transimpedance application, a feedback capacitance controls the frequency response peaking and achieves unconditional stability. Such a technique is not recommended for CFAs because it may lead to instability under the best case conditions.

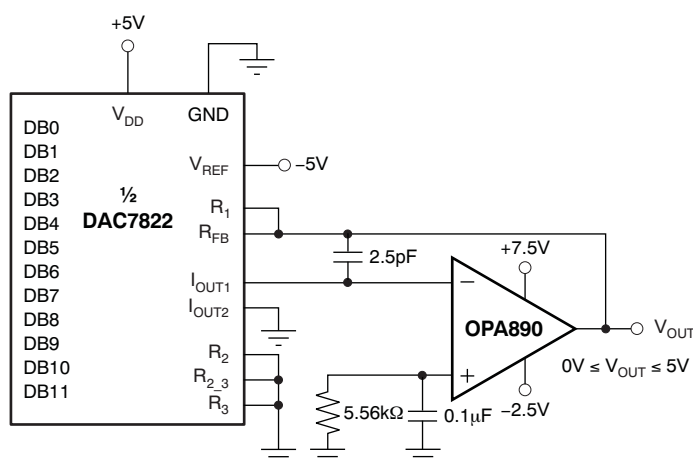


Figure 15. Multiplying DAC Transimpedance Driver

In the schematic illustrated in [Figure 15](#), the transimpedance gain is set by a resistor internal to the DAC7822. The 2.5pF capacitance was selected to achieve a flat frequency response. On the inverting node, a 5.56kΩ resistor is used to minimize dc offset error. A 0.1μF capacitor was placed in parallel to this resistance to minimize the noise contribution for frequency above 300Hz.

Note that in order to achieve maximum amplitude, the supply voltages were set at +7.5V and -2.5V for the amplifier, allowing the output voltage to swing between 0V and 5V. Figure 16 shows the frequency response of this circuit.

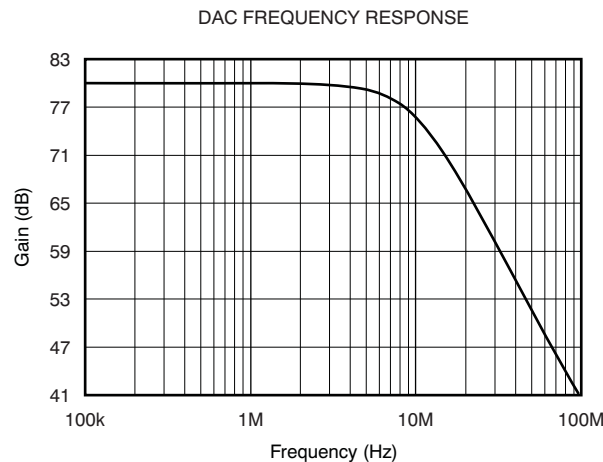


Figure 16. Multiplying DAC Frequency Response Using the OPA890 as Output Stage

Now look more closely at the interaction of the OPA890 with the DAC7822. We can see that the output impedance out of the DAC7822 is not high impedance, but varies between 4.5kΩ and 22.1kΩ (excluding code 000h) for a 10kΩ nominal  $V_{REF}$  input resistance. The  $I_{OUT}$  resistance changes are directly related to the code change. This relatively low impedance has multiple effects when an operational amplifier is used.

Some of the effects that apply to all amplifier technologies are:

- the noise gain of the amplifier changes for each code;
- the output offset voltage of the amplifier changes for each code because of the input offset voltage;
- the input offset current cannot be cancelled. The effects of the input bias current can be reduced, but not eliminated, by selecting a CMOS amplifier instead of a bipolar amplifier, thus affecting the total output offset voltage of the amplifier with each code.
- The noninverting pin of the amplifier must be tied to ground and cannot be used to create a dc offset to center the output voltage to any desired value.

The following analysis excludes the input offset current. The total output offset voltage variations, as a result of the code changing internally to the DAC, can be expressed as:

$$\Delta V_{OSO} = +\Delta NG \cdot \{ [(R_F \parallel R_{OUT1}) - R_S] + V_{OS} \}$$

where:

$$4.5k\Omega \leq R_{OUT1} \leq 22.1k\Omega$$

$$R_F = 10k\Omega$$

Using this value, the variation of the parallel combination of  $R_F$  and  $R_{OUT1}$  can be constrained to:

$$4.19k\Omega \leq (R_F \parallel R_{OUT1}) \leq 6.88k\Omega$$

In order to optimize the bias current cancellation,  $R_S$  is selected to be the average of those limiting numbers, or:

$$R_S = \frac{(6.88k\Omega + 4.19k\Omega)}{2} = 5.56k\Omega$$

Looking at the variation for each code, the total error (when including all codes) is ~3.9 LSB for the OPA890.

Notice that most of the error occurs at the first few codes (0, 1, 2). Excluding these codes from the analysis then yields the result shown in [Table 2](#).

**Table 2. DC Accuracy vs Code**

<b>Codes</b>	<b>Total Error Because of <math>V_{OS}</math> and <math>I_B</math></b>
All codes	3.9 LSB
Excluding code 0	2.5 LSB
Excluding code 0 and 1	2 LSB
Excluding code 0, 1 and 2	1.83 LSB

Note that 1LSB = 1.221mV in the circuit shown in [Figure 13](#).

Eliminating a few codes increases the resolution of this high-speed, low-power, multiplying DAC transimpedance amplifier solution.

## 6 Conclusion

Relatively high bandwidth and high slew rate devices are now available with low power dissipation. This report has discussed the some of the trade-offs between various architectures as well as offered a better understanding of the specification, along with suggestions and solutions for low-power applications.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated