





With a Single-Ended Input:  
 Output = (Gain INA322) · (Input Amplitude)  
 Output = (5V/V) · (100mVpp) = 0.5Vpp

