

Miller Effect

Notice Miller Capacitance is defined as


$$C_M = C_i (1 + A_v)$$

Annotations for the equation above:


- C_M : Miller Cap
- C_i : Capacitor of amplifier
- $(1 + A_v)$: Miller Effect
- A_v : Amplifier Gain

Let's derive this through example


Example Common Source Amplifier

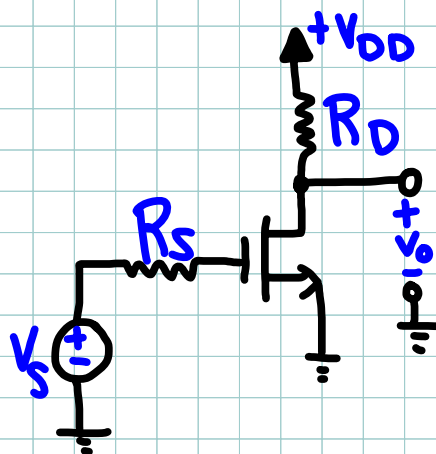

AC Model

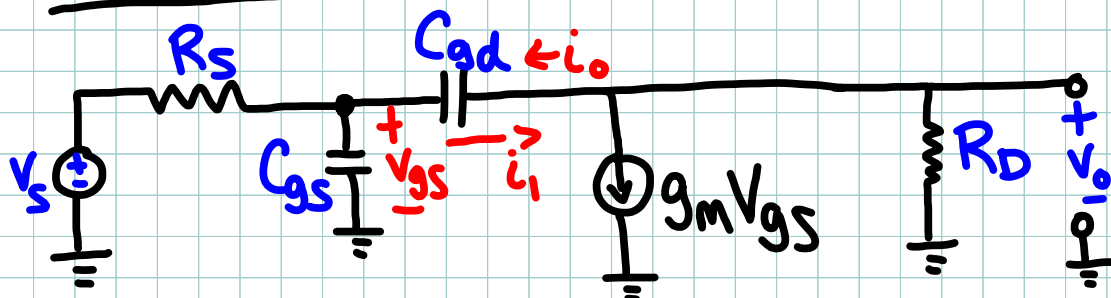

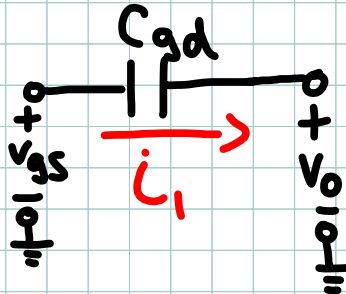Let's Look at current i_1 , flowing through C_{gd} .



$$i_1 = \frac{V_{gs} - V_o}{\left(\frac{1}{sC_{gd}}\right)}$$

$$i_1 = sC_{gd}(V_{gs} - V_o)$$

Let's solve for V_{out} and plug it's result back in.

For low frequencies C_{gd} is an open
Therefore


$$V_o = -g_m V_{gs} R_D$$

$$i_1 = sC_{gd}(V_{gs} - V_o) = sC_{gd}(V_{gs} + g_m R_D V_{gs})$$

$$i_1 = V_{gs} [1 + g_m R_D] sC_{gd}$$

$$C_M = C_{gd} [1 + g_m R_D]$$

Let's look at current i_o

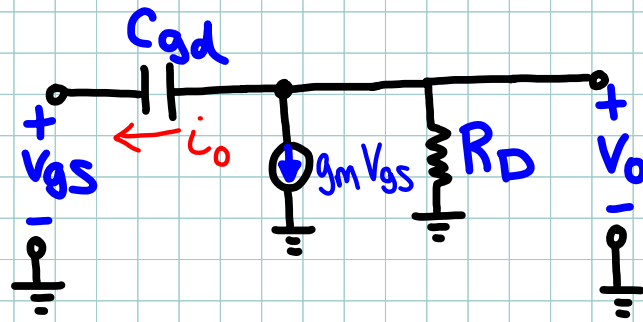

$$i_o = (V_o - V_{gs}) s C_{gd}$$

$$V_o = -g_m V_{gs} R_D$$

or $V_{gs} = -\frac{V_o}{g_m R_D}$



$$\therefore i_o = \left(V_o + \frac{V_o}{g_m R_D} \right) s C_{gd}$$

$\uparrow$
 $A = g_m R_D$

A is very large

$$\therefore i_o \approx V_o s C_{gd}$$

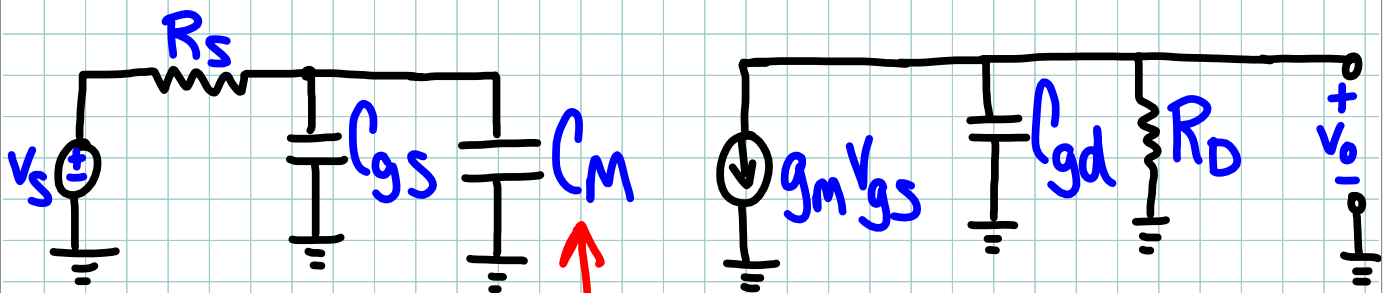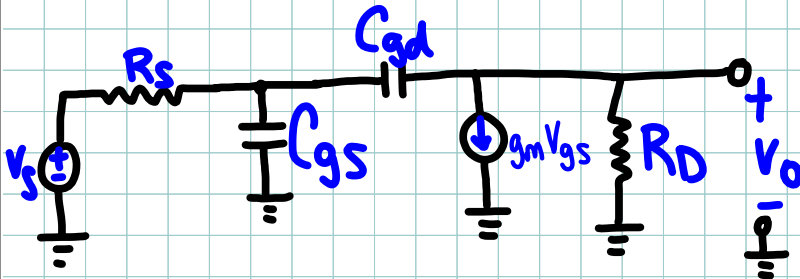Therefore The following two circuits are equivalent.



$$C_M = C_{gd} [1 + g_m R_L]$$