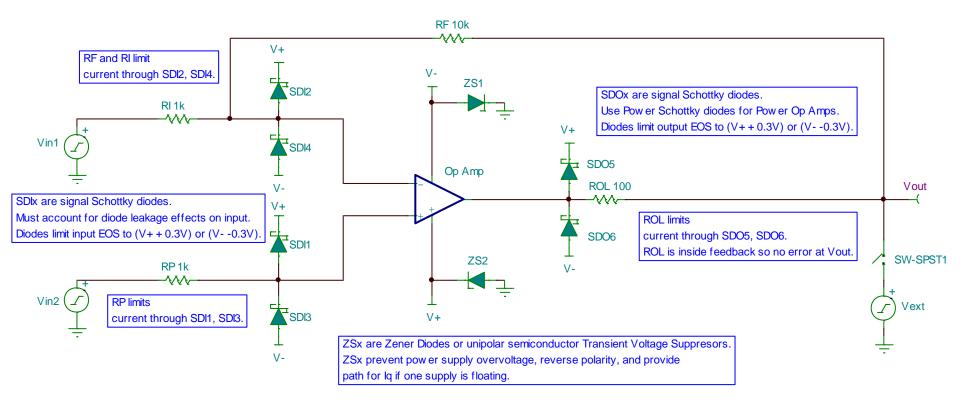
# Avoid Electrical Overstress (EOS) Dual Supply Power Op Amp Apps

Tim Green
Senior Analog Applications Engineer
Precision Analog Linear Applications



### **Complete External EOS Protection**

#### **Complete EOS Protection using External Devices**






## **EOS Iq Protection using Zeners or Unipolar Semiconductor Transient Voltage Suppressors**

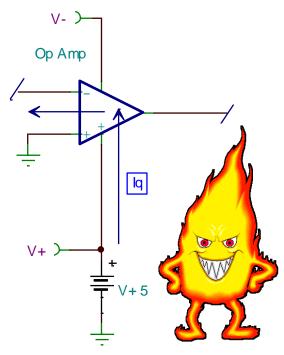
**Iq with Open Supply** 

V- high impedance or effectively an open. Iq finds a path through reverse biased input stage junctions and out +input.



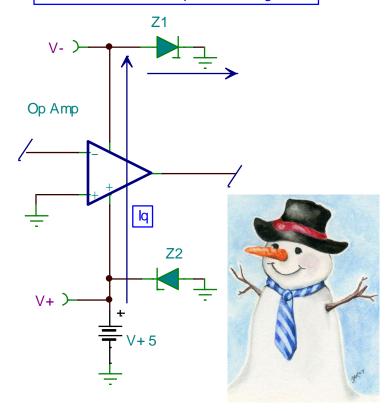**Iq without Supply Zeners** 

- V- high impedance BUT Z1 is forward bias.
- V- now is +0.6V and Iq flows through Z1




**Iq with Supply Zeners** 




### **OPA364 Internal ESD Structures**
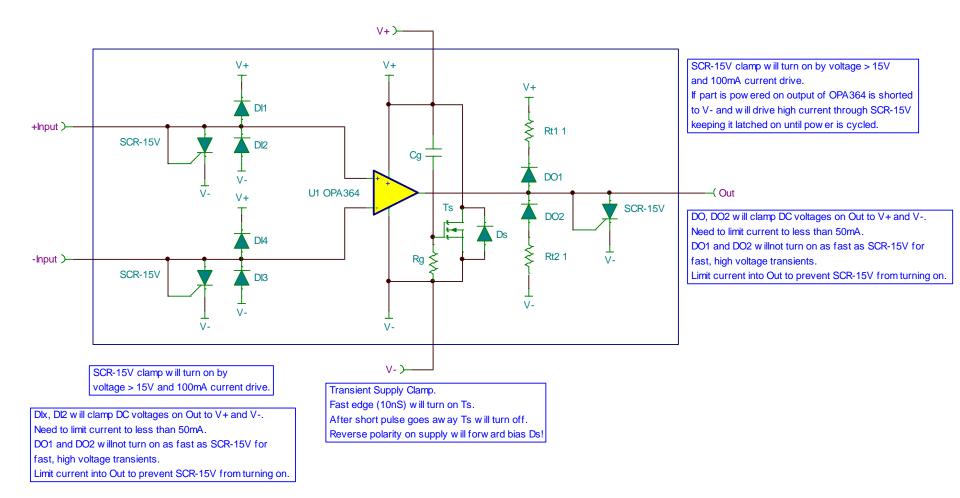
#### **OPA364 Equivalent Schematic with ESD Cells**






# Power Op Amp Output Snubber

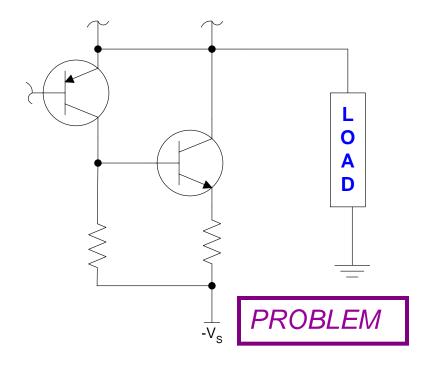

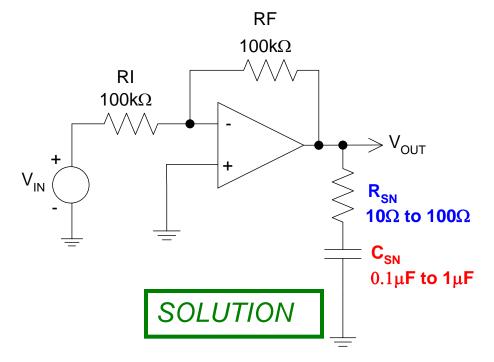- √ fosc > fGBW
- √ oscillates unloaded? -- no
- √ oscillates with V<sub>IN</sub>=0? -- no



Some Op Amps use composite output stages, usually on the negative output, that contain local feedback paths. Under reactive loads these output stages can oscillate.

The Output R-C Snubber Network lowers the high frequency gain of the output stage preventing unwanted oscillations under reactive loads.