

### Created by Dr. John Brown Prepared by Thomas Kuehl & Laura Groskie Texas Instruments – Tucson, AZ




### Presentation Outline

- Biopotentials
- Electrocardiogram, ECG
- ECG characteristics
- ECG electrodes and connections
- The DAS/ECG board electrical functions and capabilities
- AC and DC applications for the DAS/ECG board




# **Biopotentials – Muscle Cell**

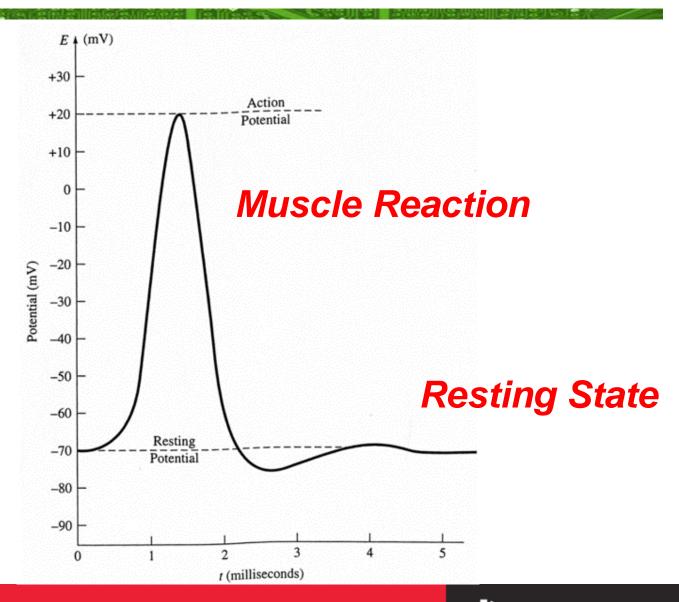



Biopotentials from Cells Electrical Signals From the Body

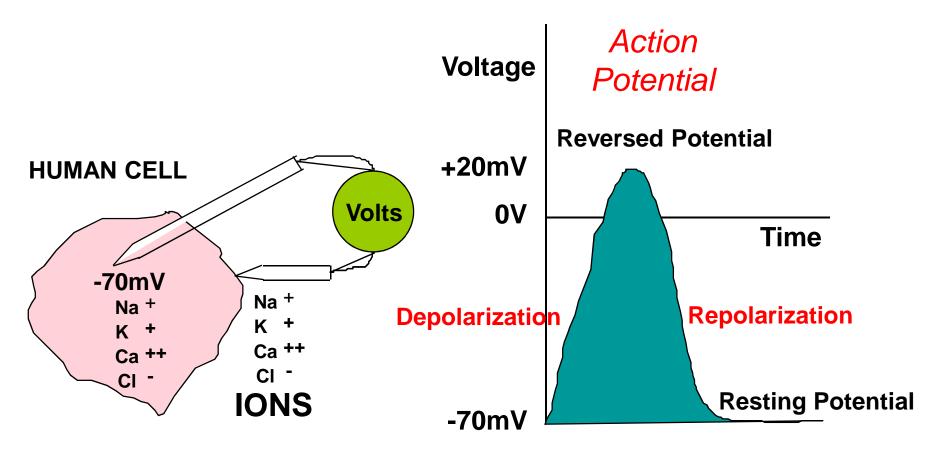
### **EVERY CELL IS LIKE A LITTLE BATTERY**





# **Biopotentials from Cells**


Electrical Signals From the Heart

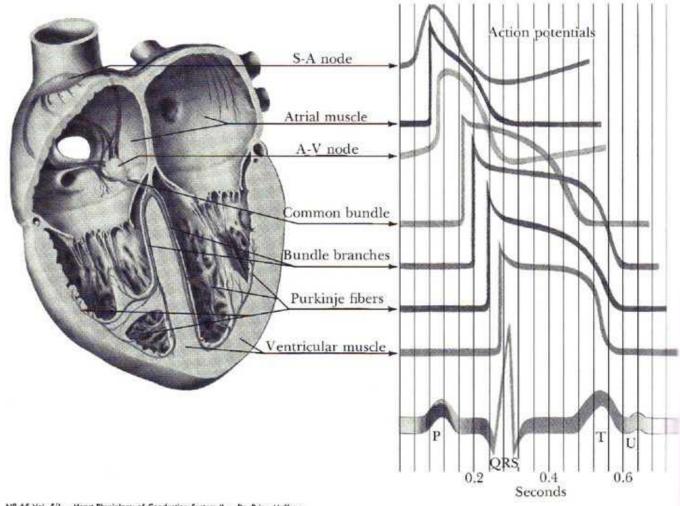

N8-65 Vol. 5/1 - Heart Physiology of Conduction System II - Dr. Brian Hoffman

Technology for Innovators<sup>™</sup>
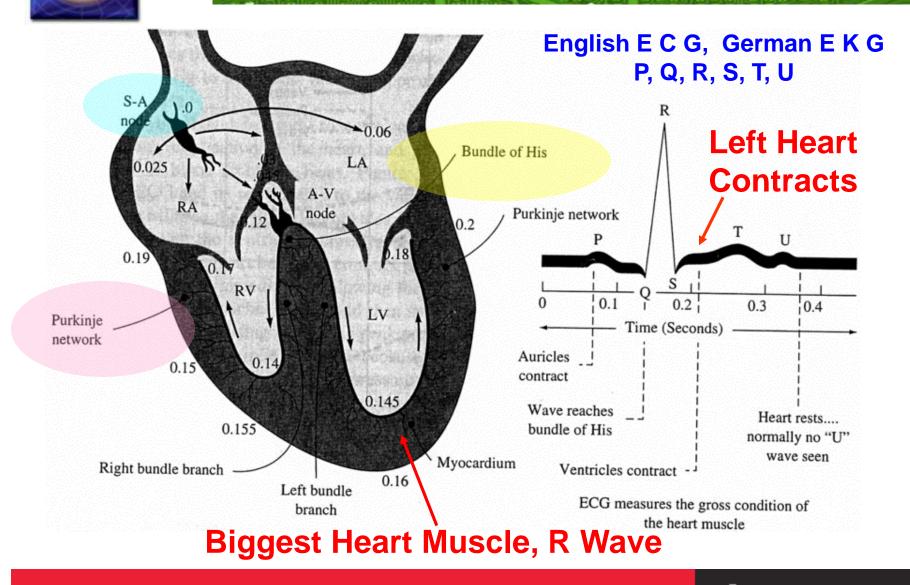
### Cardiac Conduction System of the Heart ECG Waveforms



lech Da


Technology for Innovators<sup>™</sup>

**U** TEXAS INSTRUMENTS




### **Biopotentials from Cells - Electrodes**

### **IONS to ELECTRONS CONVERTER**

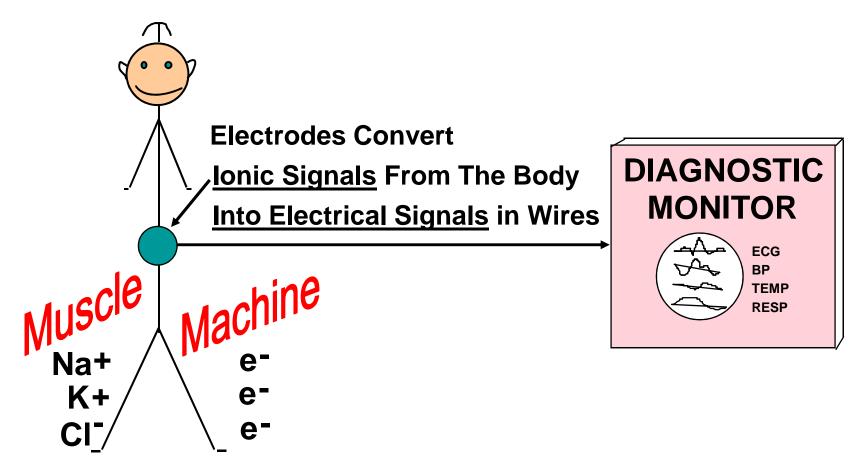




### **Basic ECG electrode connections**

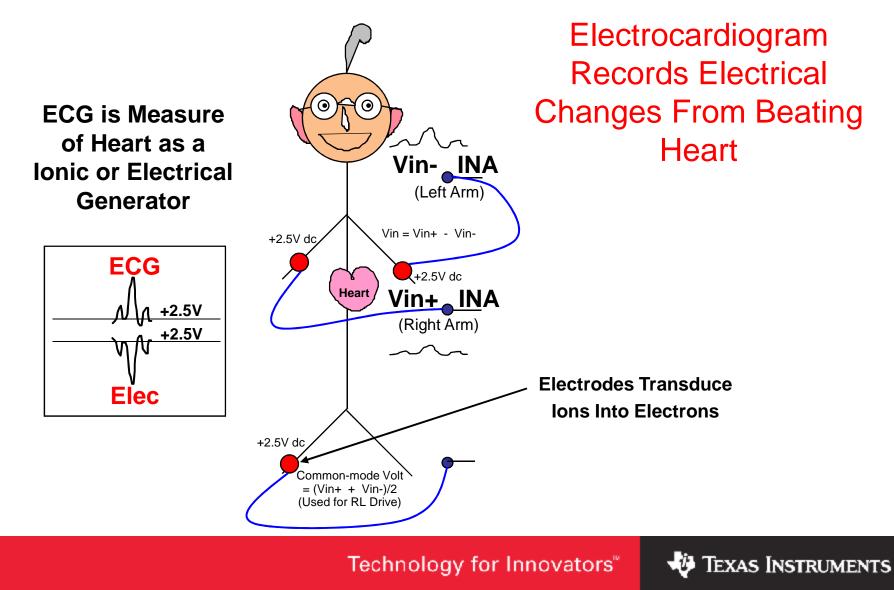




### ECG Einthoven Triangle, 1907

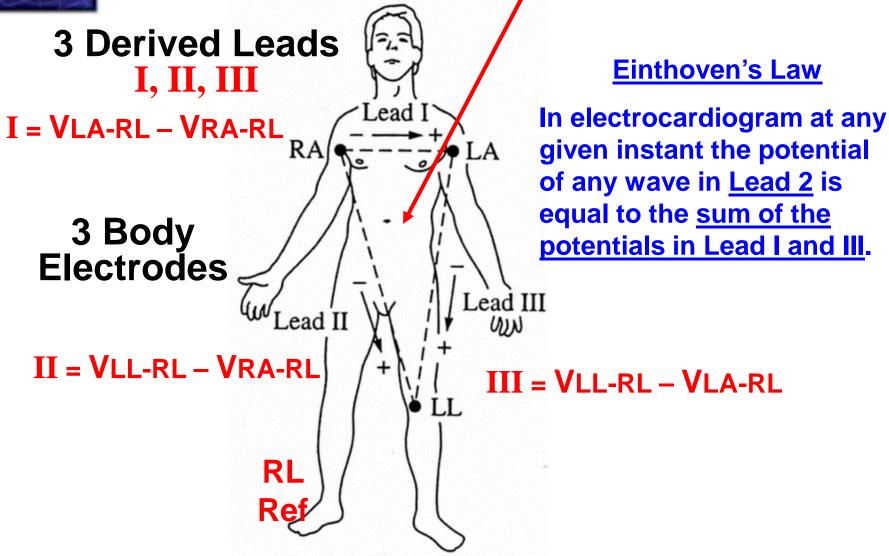




### ECG Electrode – Electrical Model

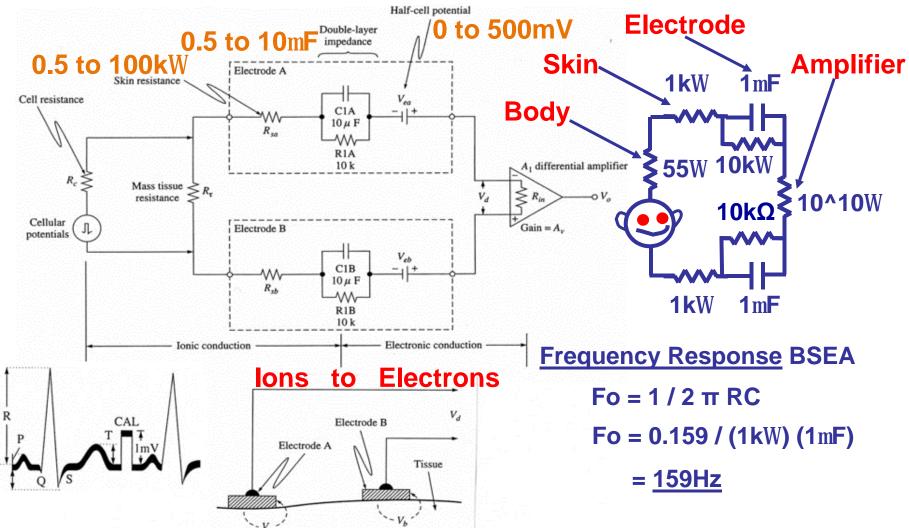


Technology for Innovators"

🏘 Texas Instruments

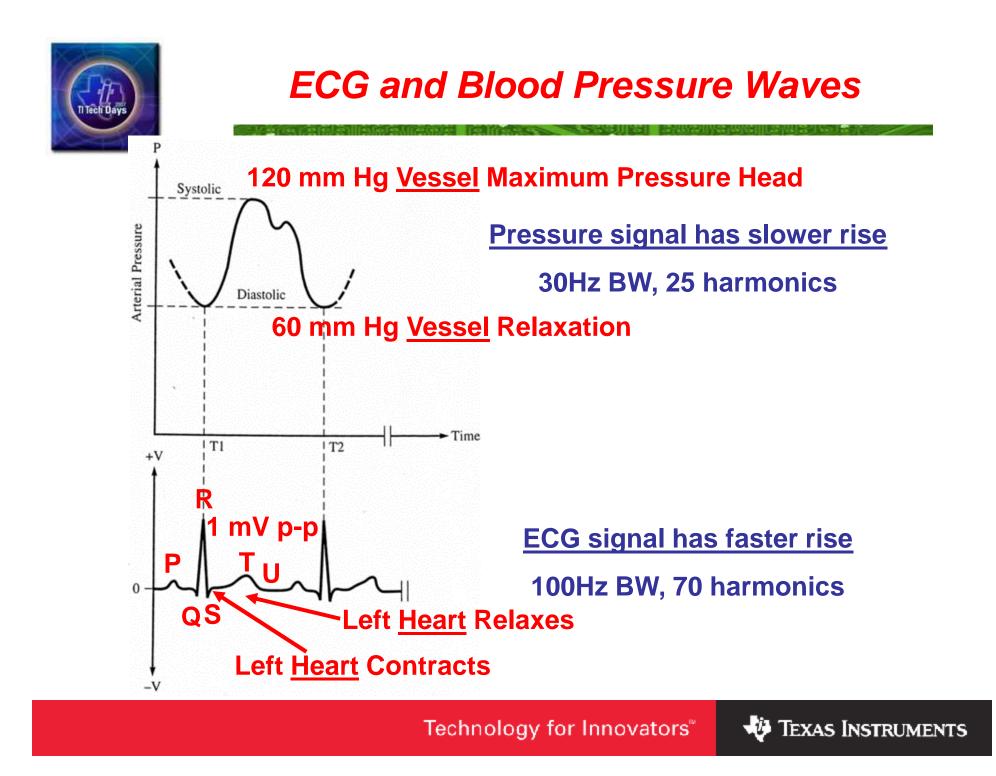



**Actual ECG - Normal** 

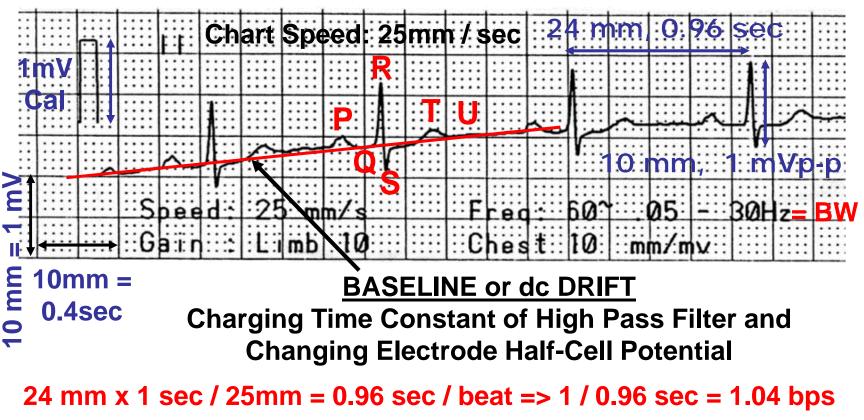



# **62 bpm**

at rest


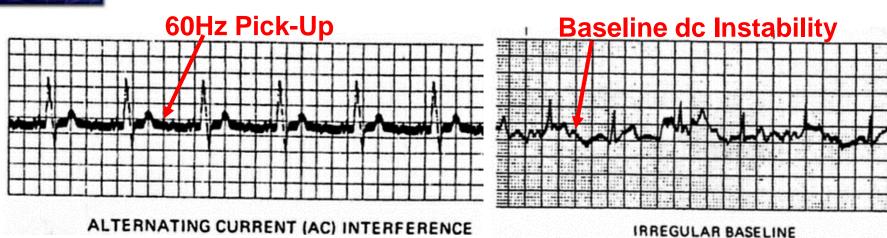
### **ECG Irregular Tracings Due to Artifacts**



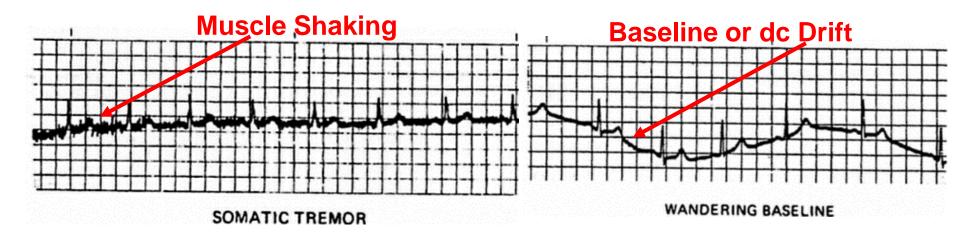


Technology for Innovators<sup>™</sup>

🛷 Texas Instruments



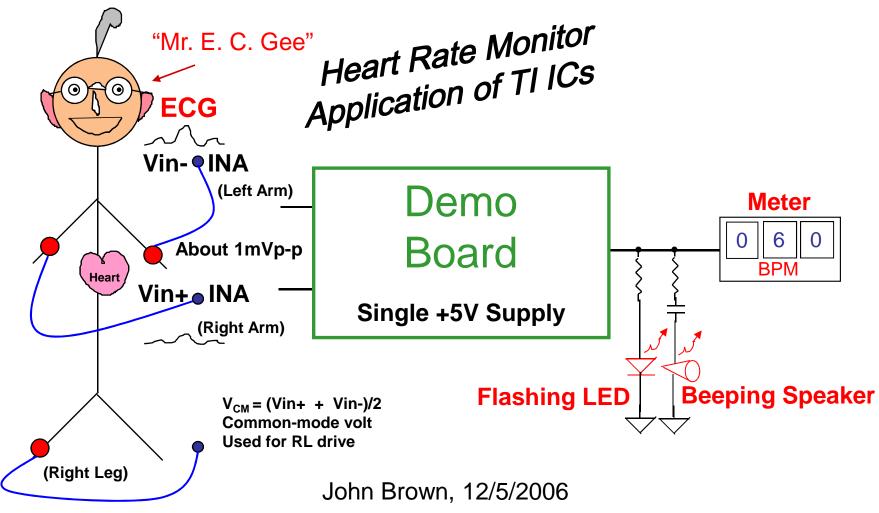
Can Also Be Used As Precision Low-Level Data Acquisition System Front-End



Technology for Innovators"


Texas Instruments



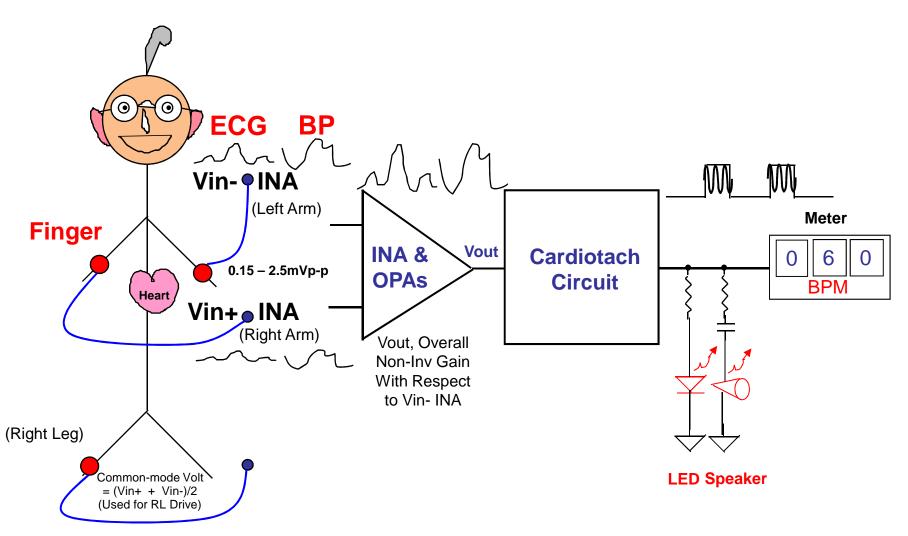


Technology for Innovators"


♣ Texas Instruments

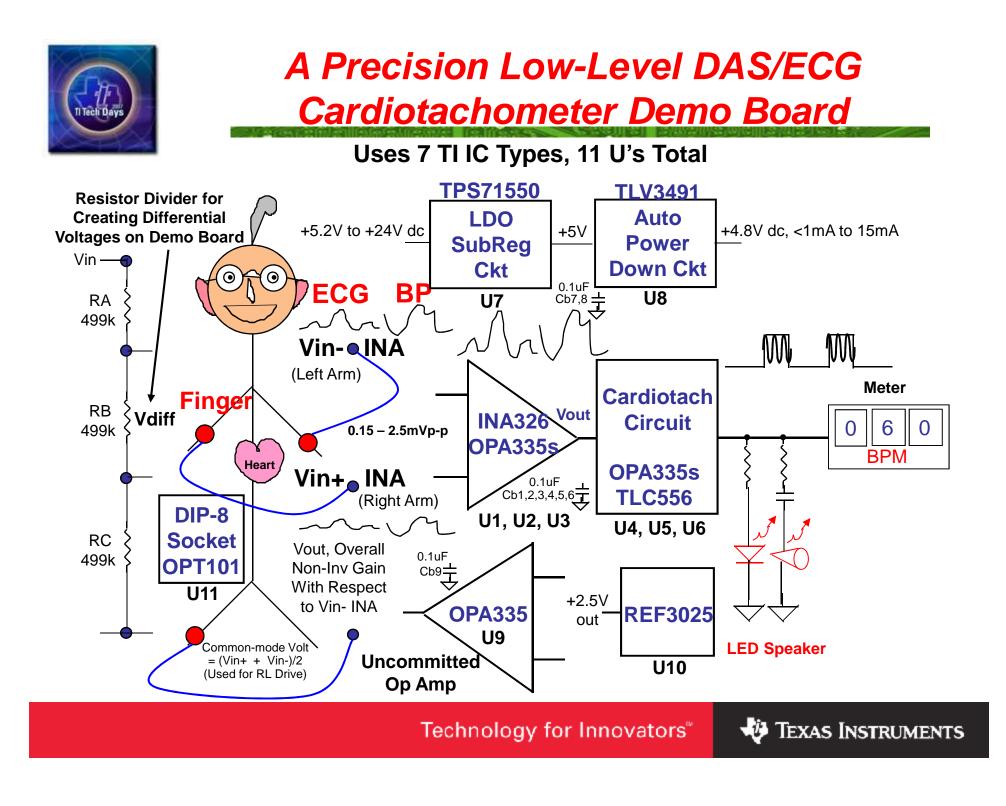



AC-coupled input stage

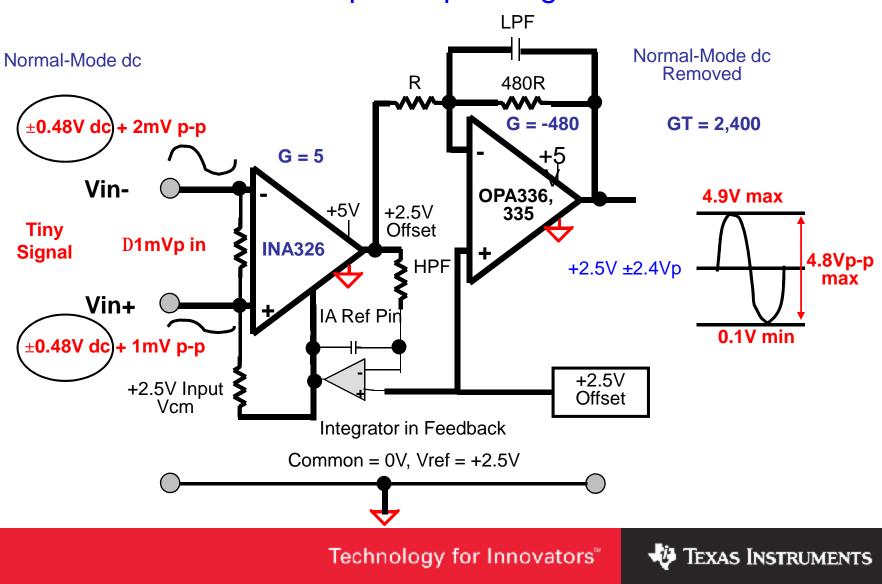

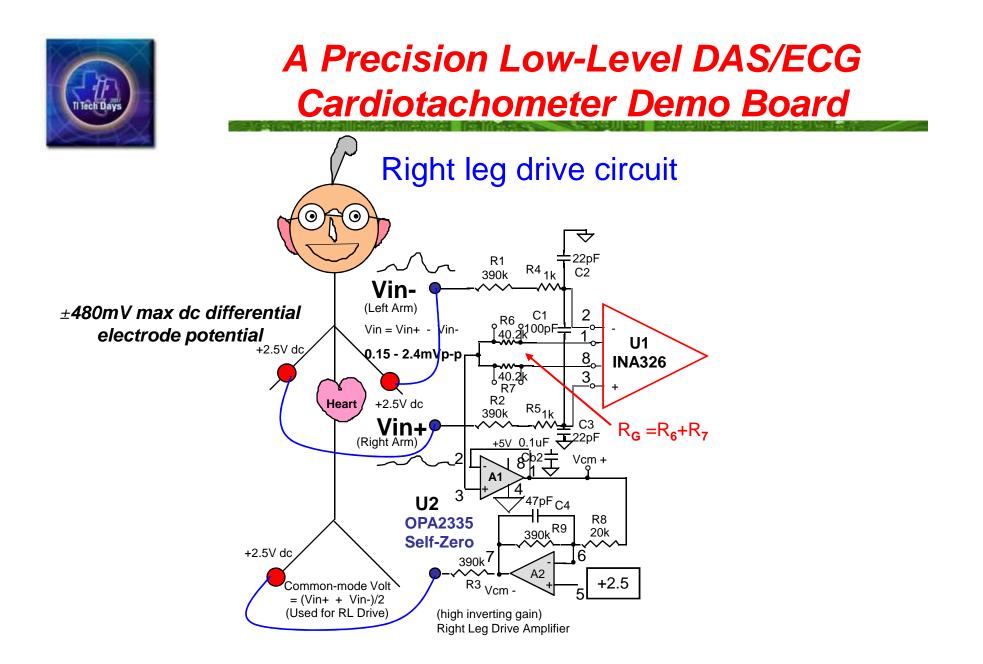


Technology for Innovators<sup>™</sup>

🏘 Texas Instruments



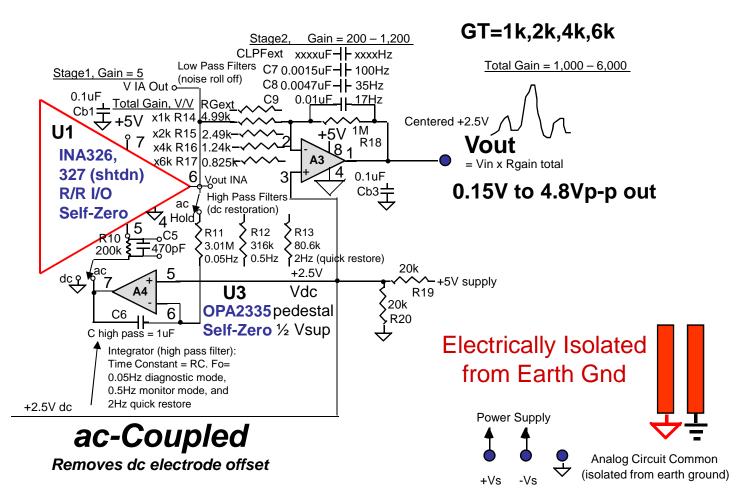
CMOS +5V SINGLE SUPPLY, INA326/7 & OPA2335



Technology for Innovators<sup>™</sup>



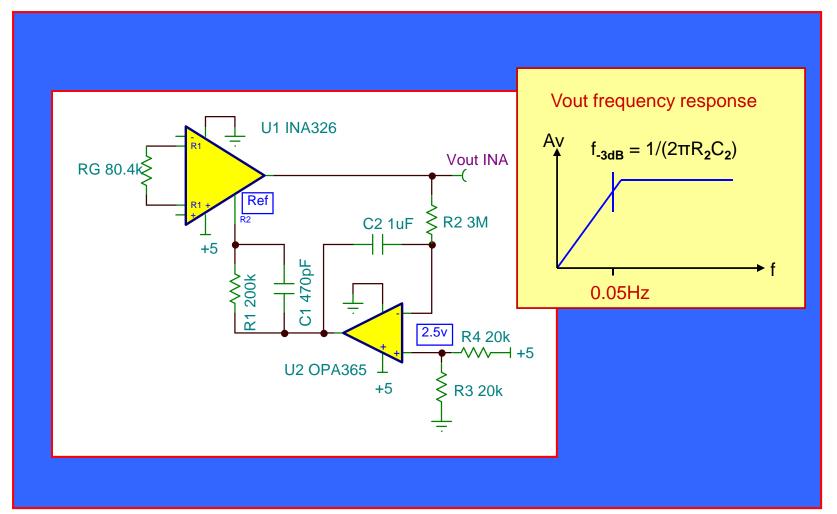
#### DC restorer - removes electrode offset



Technology for Innovators<sup>™</sup>

**W** Texas Instruments




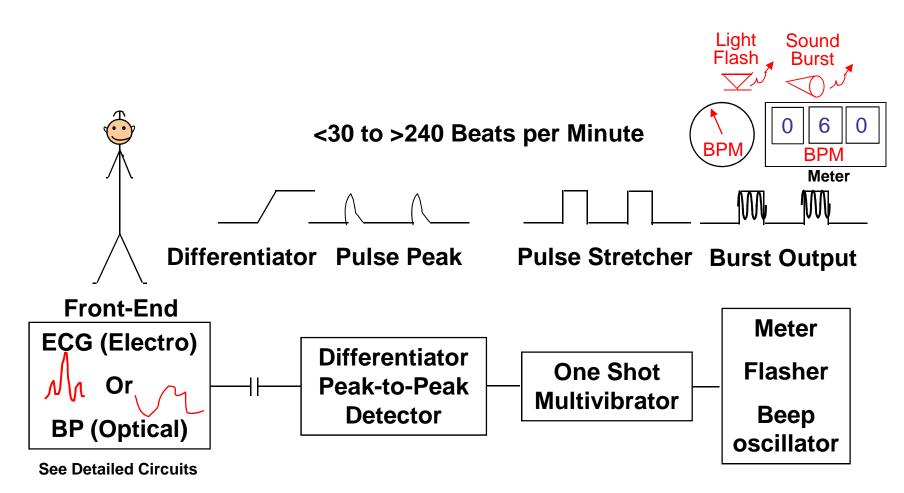




+5V Single Supply

#### Front-End

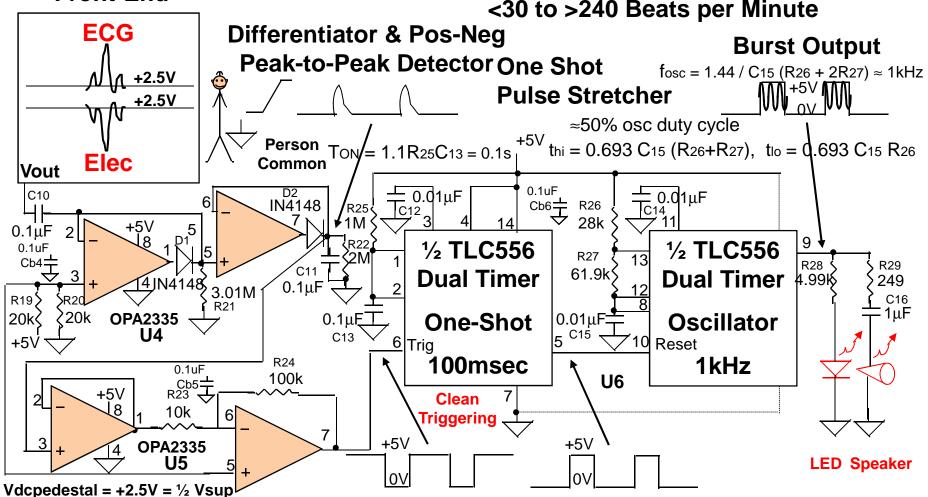


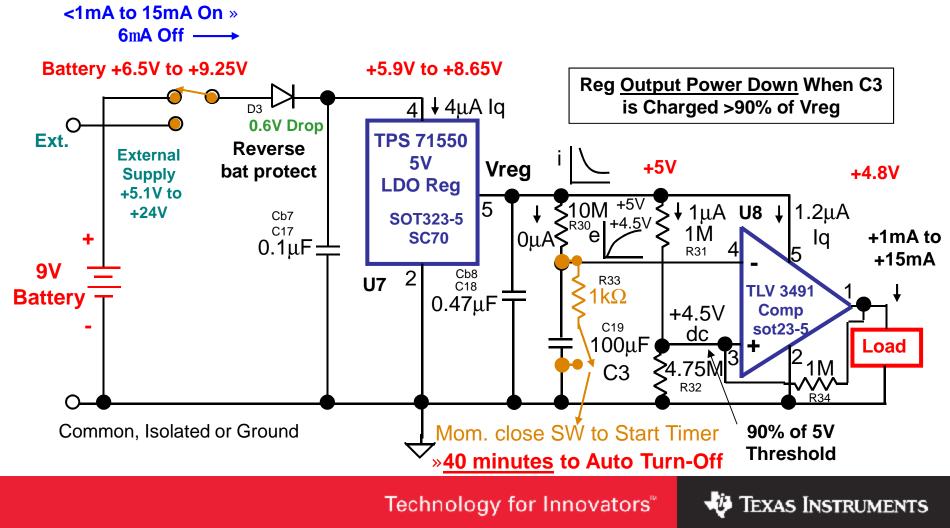
#### Battery, Power Sub-Regulator and Auto Power Down Circuit






#### "Pin-Plug and Play" features

- Wires to pin-sockets, no soldering, plus plug selectable gain & BW
- Self contained ICs, resistors, capacitors, LED, speaker, switches
- Battery operated (+9V included) or external supply up to 24V max with auto-sleep
- Adjustable gain & BW (Separate LPF & HPF), differential or singleended inputs, ac or dc coupled
- Breadboard area for additional circuits


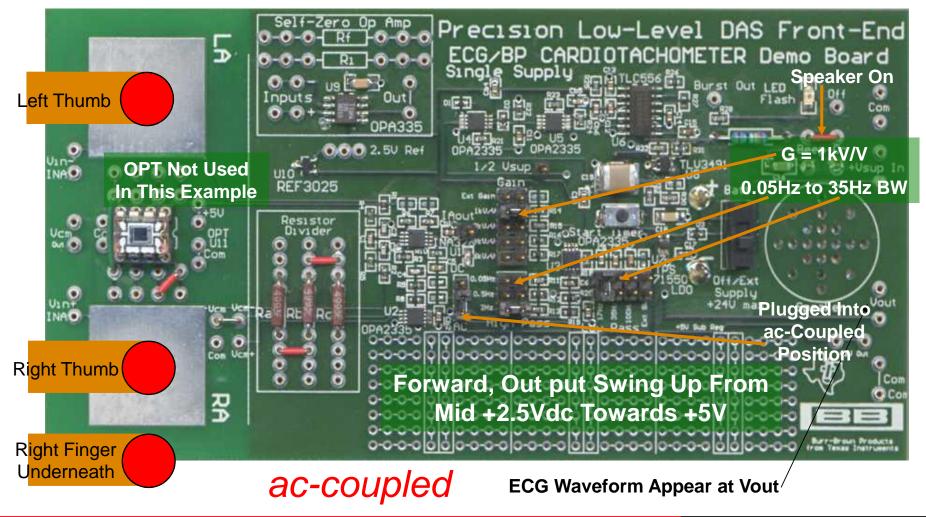
#### Can Hold Right Side of Board Against Table to Steady Skin-Electrode Contact




Technology for Innovators"


**TEXAS INSTRUMENTS** 

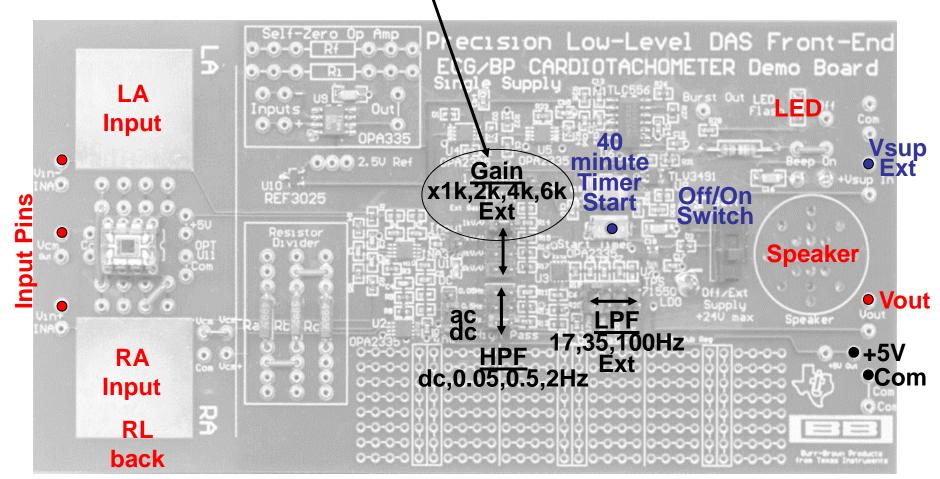
- (7)



Gain Control, Selected By Changing Shorting Bar Position



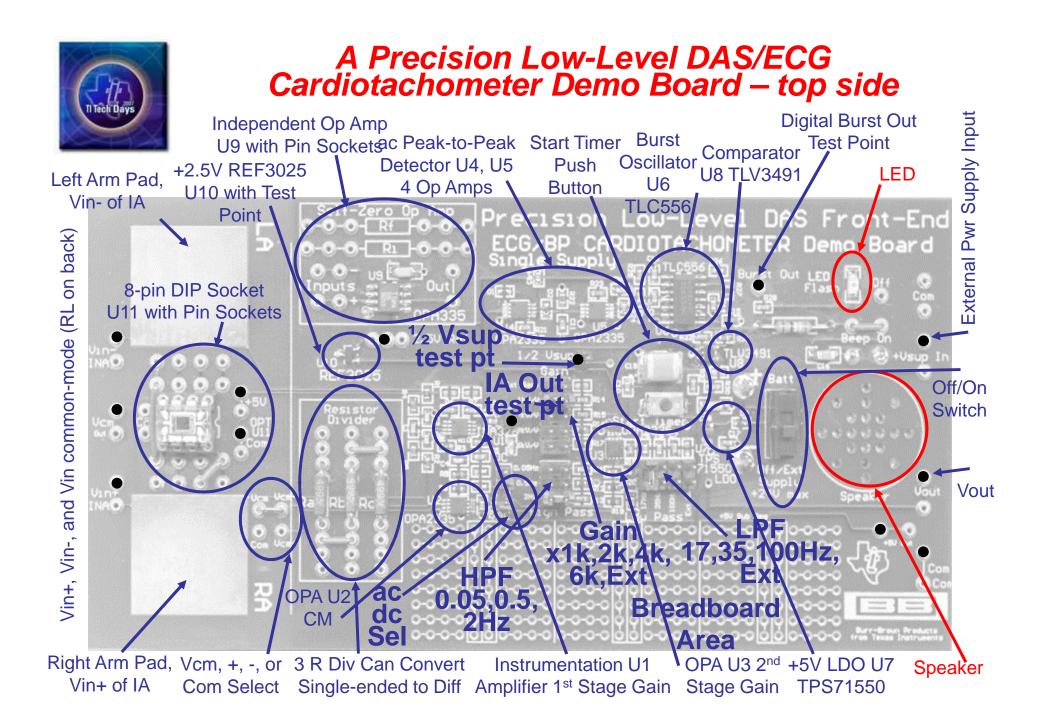

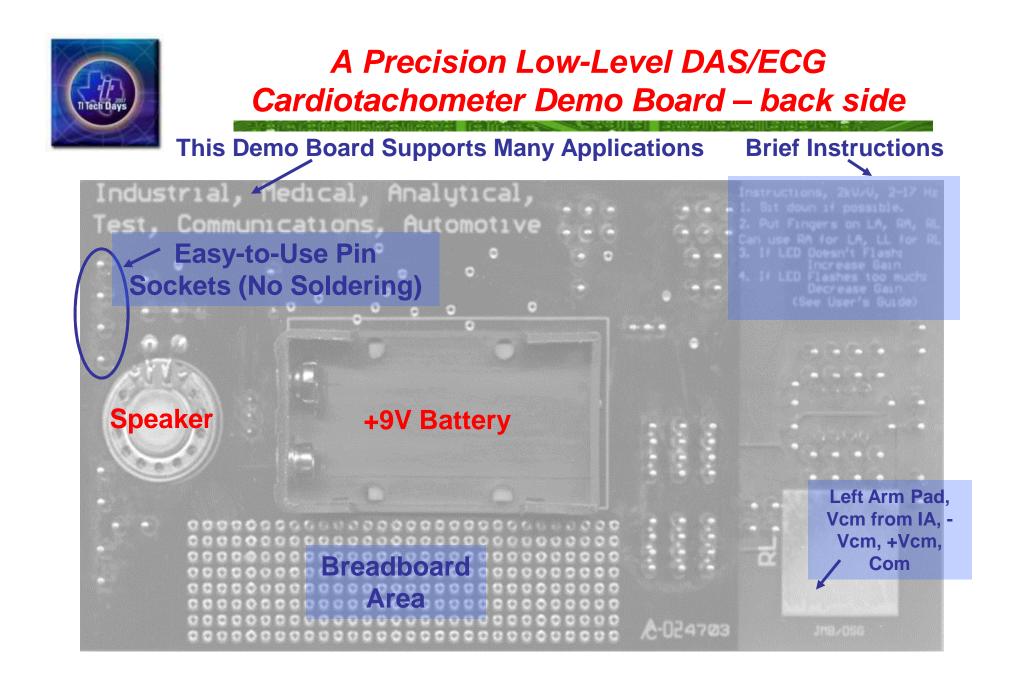


Technology for Innovators"

🐶 Texas Instruments



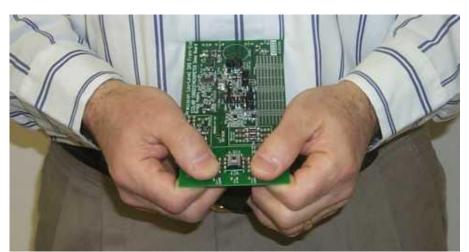
### Low-Level DAS / ECG Cardiotachometer Demo Board - <u>Standing</u>





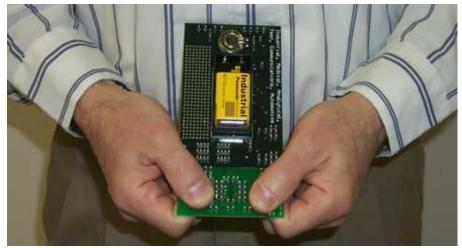Gently Hold Electrode Pad Areas (relax fingers), Standing can be ok. Sit Down if Possible





💠 Texas Instruments


Technology for Innovators<sup>™</sup>


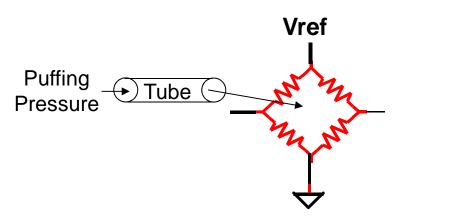
# Additional Applications

- Industrial pressure, temperature flow and humidity and general sensor signal conditioning
- Medical diagnostic and biophysical monitoring
- Analytical and scientific instrumentation
- Communications sensor and signal amplification
- Automotive sensors






# **Pressure Bridge Application**

# **Quickly Puffing on Tube**

# ac-Coupled


Technology for Innovators®


**V** Texas Instruments

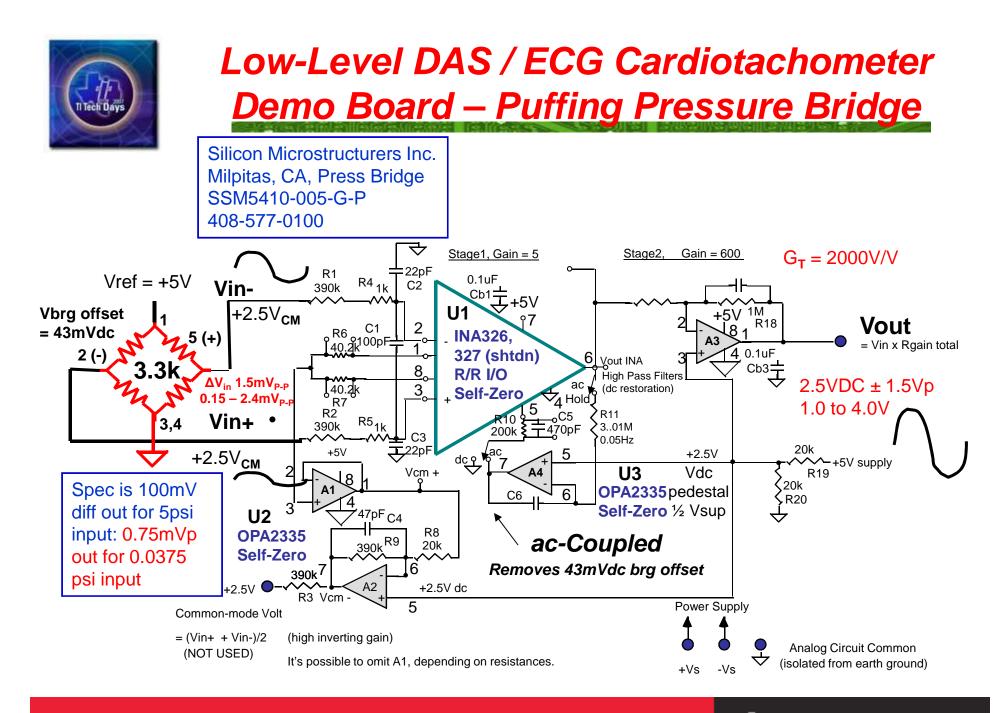


Technology for Innovators"

Texas Instruments

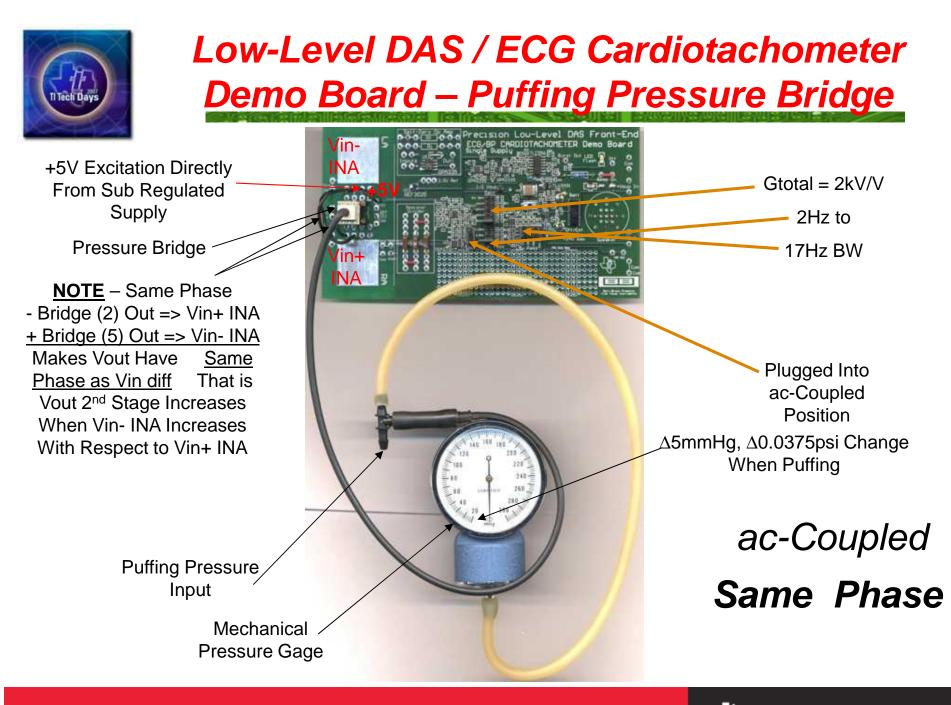

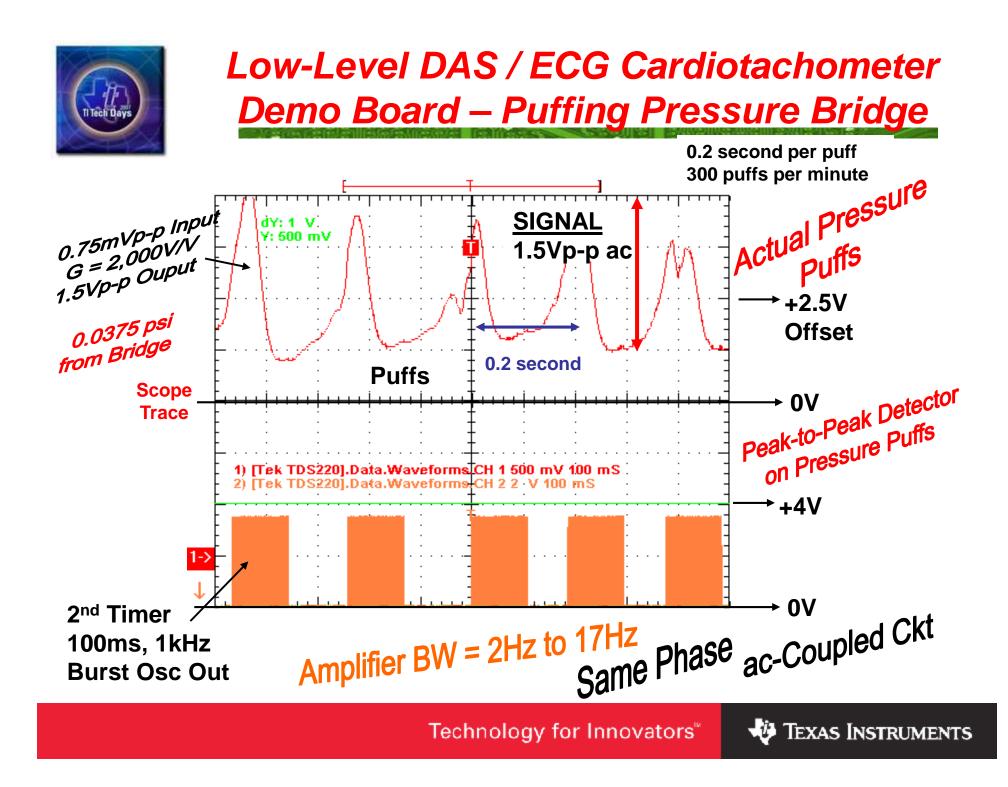



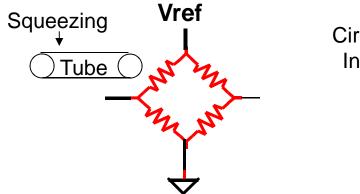

Circuit Uses OPA336s Instead of OPA335s

Texas Instruments

### **Pressure Bridge Application**


# **Slowly Squeezing on Tube**

dc-Coupled



### dc-coupled
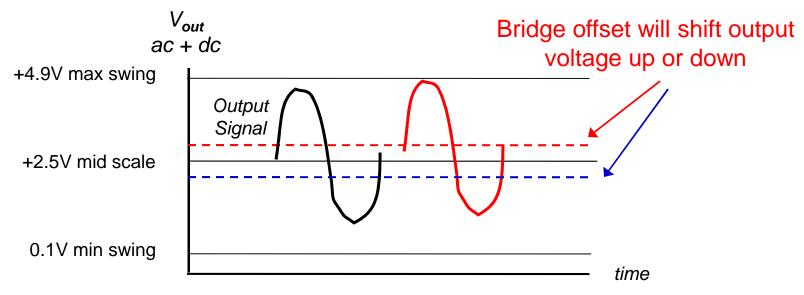
### dc bridge offset (Normal-Mode voltage) is not removed




In single supply circuits, a mid-scale offset is used with the amplifiers to assure linear operation.

Technology for Innovators®

**TEXAS INSTRUMENTS** 


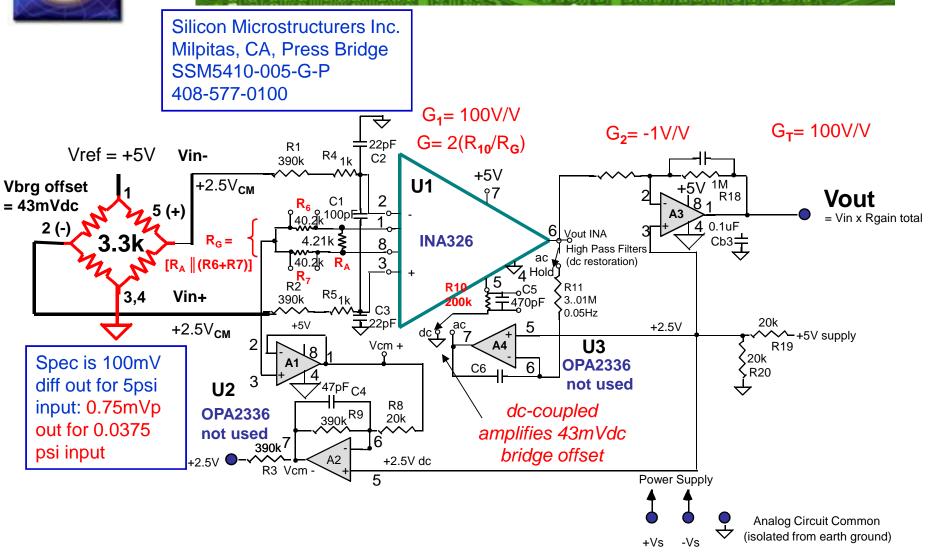
### Low-Level DAS / ECG Cardiotachometer Demo Board – Squeezing Pressure Bridge



Technology for Innovators"

TEXAS INSTRUMENTS



### Low-Level DAS / ECG Cardiotachometer Demo Board – Squeezing Pressure Bridge


#2, +2.5V Excitation Buffered Through Op amp Or

#1, +5V Excitation Directly From Sub Regulated Supply

<u>NOTE</u> – Opposite Phase + Bridge (5) Out => Vin+ INA - Bridge (2) Out => Vin- INA Makes Vout Have <u>Opposite</u> <u>Phase as Vin diff</u> That is Vout 2nd Stage Decreases When Vin+ INA Increases With Respect to Vin- INA

Pressure Bridge

Pressure Tubing T-Connection

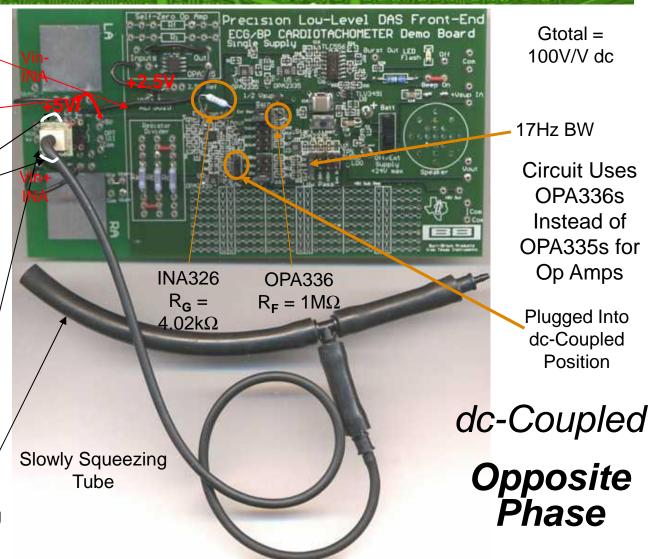



Technology for Innovators"

🤣 Texas Instruments


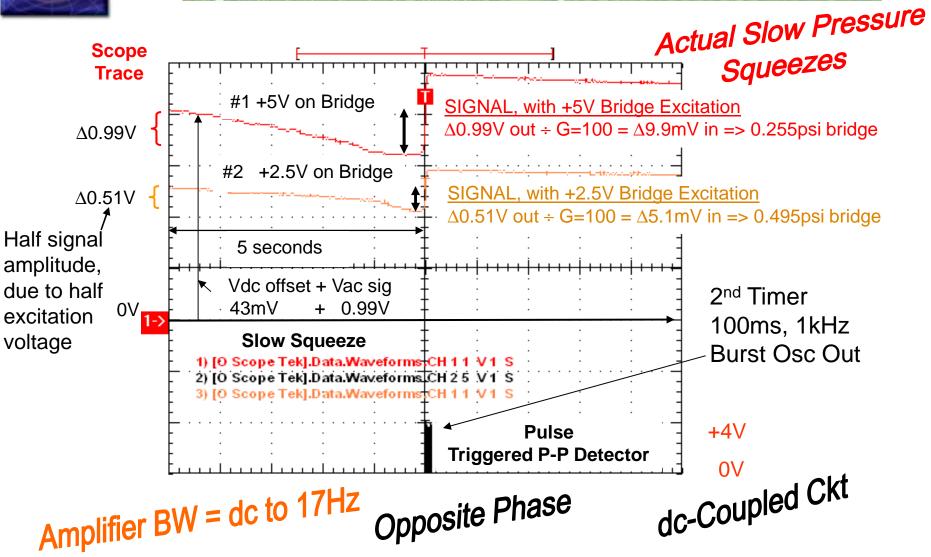
### Low-Level DAS / ECG Cardiotachometer Demo Board – Squeezing Pressure Bridge




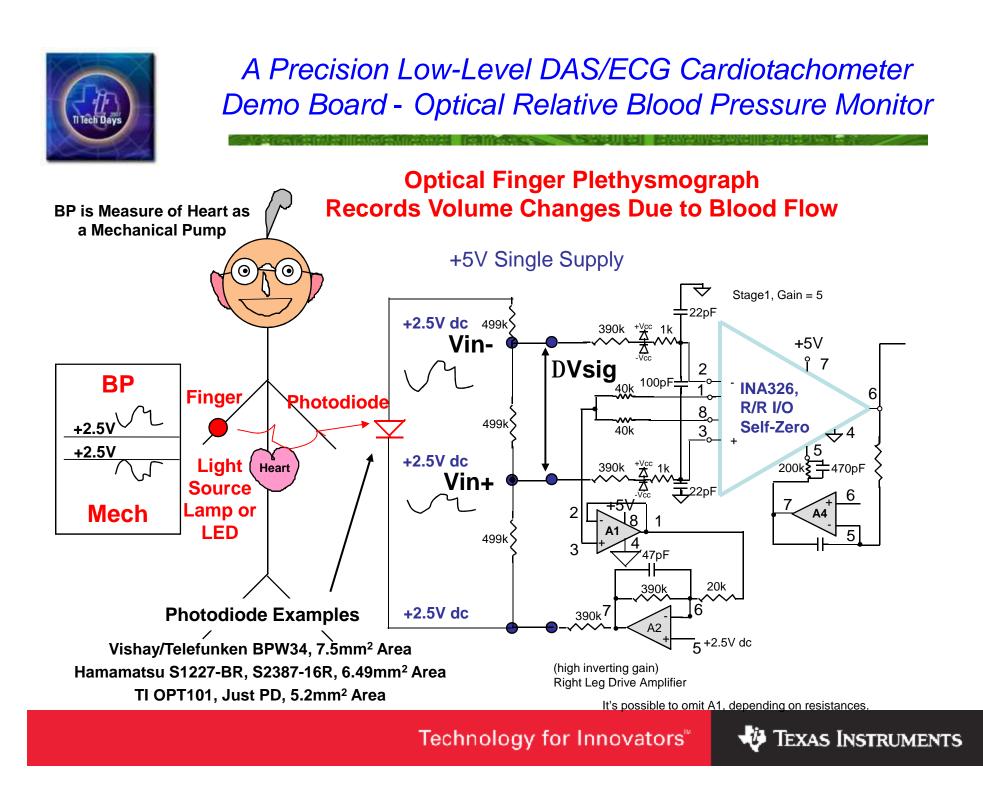



A Precision Low-Level DAS/ECG Cardiotachometer Demo Board - Optical Relative Blood Pressure Monitor

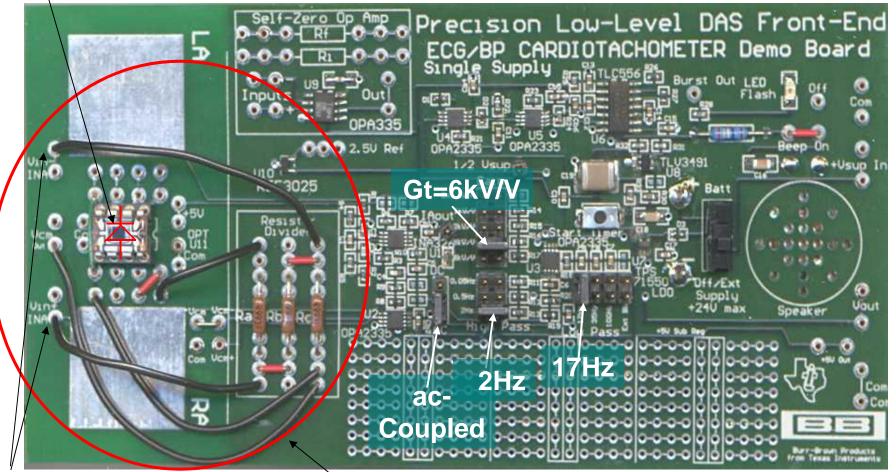Photodiode Inside OPT101 (Can Use Separate Photodiode)




Differential Input Voltage

OPT101 Photodiode Connected to 3-R Divider to Create Differential Input Voltage

Technology for Innovators<sup>™</sup>

🤣 Texas Instruments

ac-Coupled

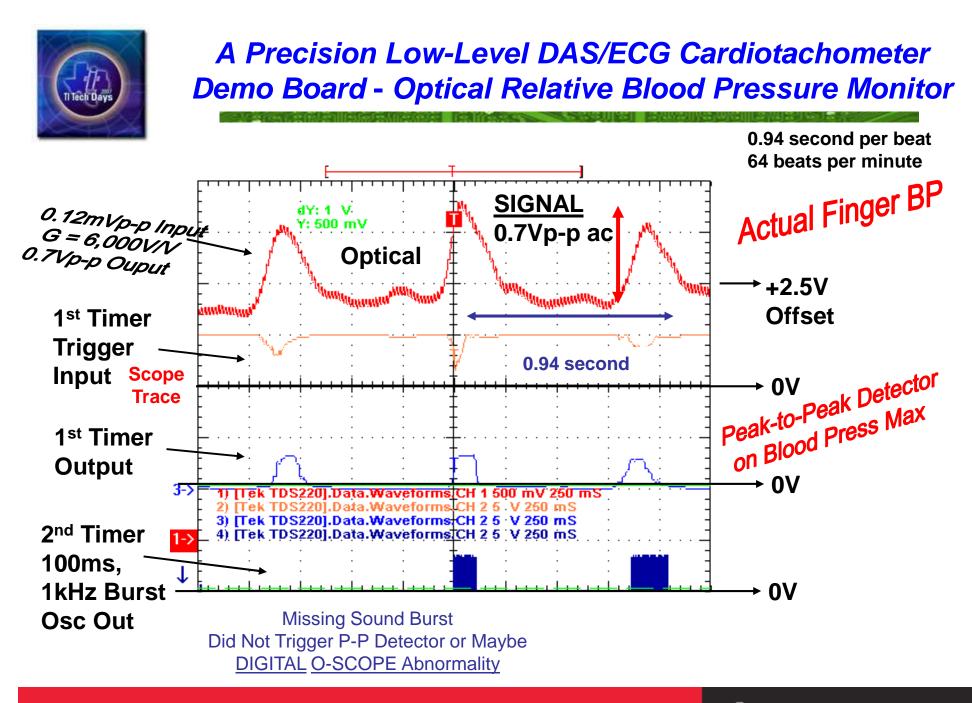



The low-level DAS/ECG demo board:

- Provides a useful platform for low signal level circuit development.
- Is useful as a portable, self-contained cardiotachometer.
- Demonstrates the ability of very small amplitude signals to be amplified in the presence of large common-mode signals.
- Provides either AC or DC coupling, but very large gain may be difficult to use for DC due to offset.
- Accommodates a variety of medical and non-medical sensors and applications.