

**Design Review: A 300W,
300KHz Current-Mode
Half-Bridge Converter
with Multiple Outputs
Using Coupled Inductors**
by Roger Adair

TOPIC 6

Design Review: A 300W, 300KHz Current-Mode Half-bridge Power Supply with Multiple Outputs using Coupled Inductors

Table of Contents

Introduction

Specifications

Topology; half bridge with current mode control.

Advantages and disadvantages.

Stability of half bridge converter using current mode control.

Solution of stability problem.

PWM control stage and gate driver circuit.

Power stage and transformer design.

Current mode control and slope compensation.

Coupled inductor design.

Feedback loop.

References.

Introduction

This paper gives a practical example of the design of an off-line switching power supply. The half-bridge topology is used with current mode control. Until recently this was considered an unstable combination, but a simple compensation circuit is now available and is described in this paper. This power supply has two outputs and uses a coupled inductor. Using a coupled inductor with a current mode controlled buck type topology is especially helpful, as will be explained later.

Specifications

Topology: Half Bridge

Mode: Current Mode

Output: 5V \pm 1%, 10 to 50A, ripple v = 100mV pp max
15V \pm 5%, 1A to 4A, ripple v = 200mV pp max

Frequency: 300KHz (600KHz oscillator)

Efficiency: 75%

Input: 110/220VAC

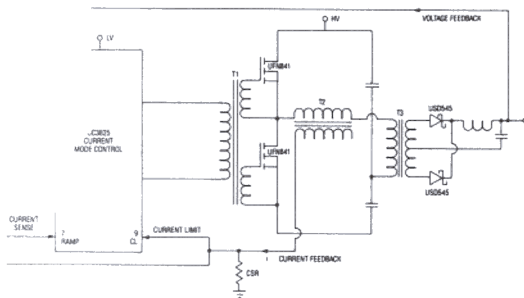


Figure 1. Simplified Schematic Showing Voltage Feedback and Current Mode Pat

Topology — Half Bridge with Current Mode Control

Advantages of Half Bridge:

1. Voltage rating of switching devices is one-half that required by Flyback or Forward converter.
2. Output filter inductor helps capacitor (compared to flyback)
3. More efficient use of transformer core and copper.
4. Leakage inductance energy is returned to the input capacitor instead of being dissipated in resistive snubbers.

Advantages of Current Mode:

1. Removes one pole of half bridge's 2 poles.
 - a. Easier to compensate.
 - b. Better large signal performance from error amplifier.
2. Gives input voltage feed forward. (Good output regulation for input line changes.)

The Stability Problem of the Half Bridge Topology Using Current Mode Control (Refer to Figure 3)

Assume that Q2 closes with a longer pulse width than Q1. Current mode control keeps the peak current equal, so the amount of charge transferred from C2 is more when Q2 is closed. As a result the voltage at node 2 will decrease. The next time Q2 closes the voltage across the primary will be less so the current ramp will have a slower slope. The peak current will be kept the same, so the pulse width will be wider. This means that the node 2 voltage decreases even further, and eventually reaches zero. It is this stability problem that has prevented the widespread use of the half-bridge topology with current mode control. Fortunately there is a simple solution to this problem, using an auxiliary transformer winding made of small diameter wire with the same number of turns as the primary winding, and two small high voltage diodes. The credit belongs to an unknown engineer who attended one of our seminars in 1984.

Operation of the Correction Circuit

Assume that node 2 is low by 1 volt, at 49.5V. When Q1 closes, the primary voltage is $V_{CC} - V_{node 2} = 100V - 49.5V = 50.5V$. The auxiliary winding also has 50.5V across it, by transformer action, with the polarity as shown. Diode D1 will hold node 3 at approx. 0 volts. The other end of the aux. winding, node 2, will try to go to +50 volts. However, as node 2 voltage approaches 50 volts (from its original value of 49V) the voltage across the primary will also approach 50 volts.

If Q2 closes when node 2 is low, no corrective action takes place. Corrective action takes place when the other half of the cycle occurs, ie, when Q1 closes again. If node 2 is high, corrective action occurs when Q2 is closed.

PWM Controller

The PWM controller used is the UC3825, a high speed 1MHz chip with voltage or current mode capability, dual high current 1.5A totem pole outputs, 50ns propagation for shutdown during fault conditions, and other desirable features. It is somewhat similar to the UC3525A and UC3526A, with the addition of much faster speed and current mode capability.

Control and Gate Drive Circuits (See Figure 2)

The MOSFET gate drive circuit consists of the dual totem pole outputs of the UC3825 driving a small toroidal transformer with two secondaries having opposite polarity outputs. There are several advantages to this type of drive; first, no coupling capacitors are needed because of the balanced drive, and second, during off time both ends of the primary are grounded, preventing transients from turning on the MOSFETs.

 


Figure 3.

Power Stage

This part of the design selects the power MOSFETs and calculates the amount of heat sinking needed.

$$I_{pri} = \frac{P_o}{V_{in} \times \text{Eff.} \times \text{D.F.}} = \frac{300W}{100V \times 0.75 \times 0.9} = 4.45A,$$

(where D.F. is the Duty Factor)

I_{pri} is time shared by the two MOSFETs

$I_{pri} = 4.45A$ plus 10% safety margin = 4.9A

$V_{PRI(max)} = 385V$

From the TO-220 MOSFET selection guide in the catalog, the UFN841 is rated at 450V, and 5.0A continuous at 100°C case. Since each of the MOSFETs will carry the 4.9A for less than half of a cycle, the current rating is OK.

 


Figure 4.

The junction temperature rise due to dissipation in $R_{DS(ON)}$ during ON time should be decided (55°C) and the amount of heat sinking needed should be decided, 55°C. The fact that the $R_{DS(ON)}$ increases with temperature has to be factored into the calculations. From the data sheet curve that factor is 1.5 at 80°C.

$$P_D = I^2 R_{DS(ON)} \times \text{D.F.} = 4.9^2 \times (0.80 \times 1.5) \times 0.45 = 12.9W \text{ average}$$

where $R_{DS(ON)}$ is at T_j of 80°C (55°C rise)

$$R\theta_{JA} = \frac{\Delta T_j}{P_D} = \frac{55^\circ C}{12.9W} = 4.3^\circ C/W$$

Two heatsinks 2" x 2.3" piggybacked will have a thermal resistance of 3°C/W. The TO-220 will add 1°C/W for a total of 4°C/W, just under the value required.

Power Transformer Design

First the approximate value of flux is determined. It is expected that at 300KHz it will be core loss limited. The allowable temperature rise of the transformer is decided, 40°C. The core and copper loss are made equal as a first approximation. It is planned to use the Ferroxcube ETD series of cores.

$$\text{Temperature rise due to core loss} = \frac{40^\circ C}{2} = 20^\circ C$$

$R\theta$ of ETD-34 (smallest ETD) = 19°C/W

$$P = \frac{20^\circ}{19^\circ C/W} = 1.05W$$

$$\frac{P}{Vol} = \frac{1.05W}{7.64cm^3} = 140 \text{ mw/cm}^3$$

For 3C6A core loss curve at 140mw/cm³

B_{max} (at 300KHz) = 600GAUSS

$$\Delta B = 2B_{max} = 2 \times 600G = 1200G \text{ pk to pk} \\ = 0.12 \text{ Tesla}$$

Now the core size can be selected, using the area product method. (Refer to Section M5 for a similar method.)

$$\text{Area product } AP = A_w A_e = \frac{11.1 P_{in} 1.143}{K \Delta B F} \text{ cm}^4 \\ = \frac{11.1 \times 300W / 0.75 1.143}{(1 \times 0.3 \times 0.41) \times 0.12T \times 300KHz} = 1.03cm^4$$

$$\text{For ETD-34, } AP = A_e A_w = 0.971cm^2 \times 1.22cm^2 \\ = 1.18cm^4$$

Minimum number of primary turns to support the primary voltage at the frequency selected.

$$N_{pri} = \frac{V_{pri(min)} \times 10^4}{2F \Delta B A_e} \\ = \frac{100V \times 10^4}{2 \times 300K \times 0.12T \times 0.971cm^2} = 14.2 \text{ turns minimum}$$

Turns ratio: Primary to 5 volt secondary

$$N = \frac{N_p}{N_s} = \frac{k [V_{in(min)} - V_{(on)}] \text{ D.F.}}{V_o + V_f}$$

where k is allowance for inaccuracies, IR drops and delays.

$$= \frac{0.9(100-3.2)0.9}{5 + 0.55} = 14.1$$

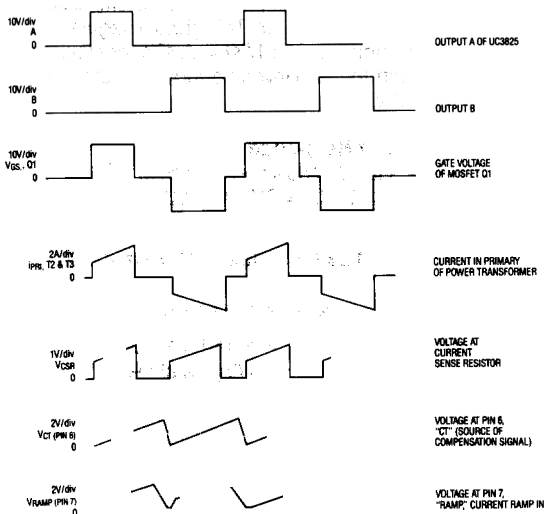


Figure 5.

Since 5V and 15V are required, the secondary turns ratio needed is approximately 3 to 1 (Approx. because of rectifier drops). The primary will have 14 turns, and the 5V secondary will have 1 turn (C.T.), in order to minimize copper volume and loss and window area needed. The 15V secondary will have 3 turns (C.T.) and an output of 15.5 volts.

Primary (See Sections M5 and M2)

$$I_p(\max) = I_{in}(\max) / K_t = \frac{P_{in}(\max)}{V_{in}(\min) \times K_t} = \frac{300/.75}{100 \times 1} = 4.0A$$

$$J_{\max} = 450 (AP)^{-0.125} = 450 \times 1.18^{-0.125} = 450 \times 0.98 = 440A/cm^2$$

$$A_{xp} = I_p(\max) / J_{\max} = 4.0/440 = .009 \text{ cm}^2 = \#17\text{AWG}$$

Depth of penetration at 300KHz = .013 cm, diameter of #17 is 0.115 cm

Use 20 x #32 in parallel. (Twisted.) See Section M2 for eddy current loss curves. Wind in two banks, one bank on each side of the secondary windings. This is termed interleaving. It reduces leakage inductance by a factor of 3.

5V Secondary

$$I_s(\max) = I_o(\max) / 1.414 = 50A / 1.414 = 35A$$

$$A_x(\text{sec}) = I_s(\max) / J_{\max} = 35 / 440 = 0.079\text{cm}^2$$

Use copper strap 10 mils x 0.8" = .008 sq in = 0.052cm²

Area OK since strap is better than wires.

Check eddy current loss factor; $D_{pen} = 7.5/f (1/2) = 7.5 (300K) 1/2 = .013\text{cm} = 5 \text{ mils}$. Strap is 10 mils thick. Primary is interleaved around secondary so depth is 5 mils in from each side for a total of 10 mils.

15V Secondary

$$I_s(\max) = I_o(\max) / 1.414 = 4A / 1.414 = 2.82A$$

$$A_x = I_s(\max) / J_{\max} = 2.82 / 440 = .0064\text{cm}^2$$

Use copper foil 3 mils thick x 0.3 inches wide.

Losses and Temperature Rise of Transformer

$$P_w = 2 I_p^2 N_p^2 l R = 2 \times 4^2 \times 14 \times 6.0 \times .00028 = 0.66 \text{ watts (pri \& sec)}$$

For 3C6A, loss = 1.05W

$$P_t = P_w + 0.66 + 1.05 = 1.71W$$

For ETD-34, $R_{\theta} = 19^\circ\text{C/W}$

$$\Delta T = P_t \times R_{\theta} = 1.71W \times 19^\circ\text{C/W} = 32.5^\circ\text{C rise (less than } 40^\circ\text{C is OK)}$$

Current Sense and Slope Compensation

Known circuit values:

$$\text{Power transformer turns ratio} = 14$$

$$\text{Current sense transformer turns ratio} = 50$$

$$\text{Maximum primary current} = 4.0A$$

$$\text{Voltage threshold at current limit pin of UC3825, } 1.0V$$

$$T_{ON} \text{ of UC3825 at } 600\text{KHz} = 1/600\text{K} - 0.1\mu\text{s deadtime} = 1.57\mu\text{s}$$

For current sense circuit:

$$I_{SEC} = \frac{I_{pri}}{N} = \frac{4.0A}{50} = 0.080A$$

Using margin of 20%

$$R_{CSR} = \frac{V_{th}}{1.2 I_{SEC}} = \frac{1.0V}{0.08 \times 1.2} = 10 \text{ ohms}$$

Slope compensation, from current slope of 5V output inductor, to ramp input (Pin 7) of UC3825, and from CT (Pin 6)

$$di/dt(\text{sec}) = V_{sec}/L = 5.7V/0.5\mu\text{H} = 11.4A/\mu\text{s}$$

$$di/dt(\text{pri}) = \frac{11.4A/\mu\text{s}}{14} = 0.81A/\mu\text{s}$$

$$V_{\text{slope at CSR}} = \frac{di/dt(\text{pri})}{50} \times R_{CSR} = \frac{0.81 \times 10}{50} = 0.16V/\mu\text{s}$$

$$V_{osc} \text{ slope at pin 6} = 1.8V/1.57\mu\text{s} = 1.15V/\mu\text{s}$$

$$R_{\text{comp}} = \frac{R_{in} \times V_{osc} \text{ slope}}{V_{\text{slope}} \times k} = \frac{R_{in} \times 1.15}{0.16 \times .75} = R_{in} \times 9.6$$

where k = ratio of slope compensation introduced, to inductor slope, value usually between 0.5 and 1.0.

Current Sense Transformer

The transformer should not saturate. Circuit energy is $1/2 L i^2$

For the 846T250 core, primary inductance of 1 turn, L_{pri}

$$= A_L N_p^2 / N^2 = 1650\text{mh} \times 1^2 / 1000^2 = 1.65\mu\text{H},$$

$$W = 1/2 L i^2 = 1/2 \times 1.65\mu\text{H} \times 13.2\mu\text{J}$$

Maximum core energy storage:

$$W = \frac{B^2 A_e l_e \times 10^{-8} \text{ (cm)}}{2\mu_e} = \frac{2500^2 \times .259 \times 5.42 \times 10^{-8}}{2 \times 2700} = 16\mu\text{J}$$

Coupled Filter Inductor Design

If both inductor coils are wound on a common core, then several benefits are obtained, eg, good dynamic cross-regulation, current limiting to prevent core saturation, and low cost and smaller size. Two design constraints need to be observed. First, use the same turns ratio for the inductor windings as the secondary windings of the transformer. Second, use a winding arrangement that gives approximately 2% or more leakage inductance. (These two points will minimize circulating ripple currents and make matching rectifier V_f 's unnecessary.)

Coupled inductors are especially useful when current mode control is being used. Separate inductor-capacitor filters for each output each have a tendency to series resonate at their own frequencies, since current mode makes the output look like a high impedance. This adds large gain and phase shifts at these different frequencies, all usually within the loop closing frequency, and thus causing unaccustomed problems. Coupled inductors minimize this effect.

Other factors should be considered when using coupled inductors, such as ripple current, leakage inductance and wiring inductance. Refer to Section M7 for a more complete discussion.

Closing the Loop

The oscillator frequency is 600KHz. Theory suggest that we close the loop at 0db at a frequency no higher than $f_{odb} = f_{sw}/2\pi D = 600\text{KHz}/2\pi \cdot 0.9 = 106\text{KHz}$, where D = maximum duty factor.

For current mode operation of a buck type converter the inductor does not appear in the forward signal path. Instead there is a pole consisting of the output filter capacitor and the effective output load resistance. This resistance changes as the load current changes: $R_o = V_o / I_o$.

The output filter capacitor and its ESR constitute a zero in the forward path. For electrolytic capacitors, whose capacitance is usually much larger than necessary in order to get a low enough ESR to meet the ripple voltage spec, the frequency of this zero is fairly low, and in many cases, it is used to get enough phase margin to close the loop. In the design discussed here, polypropylene film capacitors are used; their zero is above a megahertz and thus does not enter into loop closure.

The approach taken here is to reduce the gain of the error amplifier with a slope of -20db/decade through 0db to a negative gain equal to the (positive) gain of the control to output response at 106KHz. The error amplifier is then flattened out at the lowest output pole frequency by adding a zero in the EA compensation network. Refer to Figure 6.

In designing the network around the error amplifier, we wish to use low values of resistance for low noise pickup, but not so low as to load down the output of the EA. For this case

47K is used in the feedback path, in series with 0.002uf, and 47K in series with the input. This gives a negative gain of $10x = -20\text{db}$, and a zero at 17KHz. A 47K resistor is also put in series with the non-inverting input to help negate input current offset.

Control to Output Response

The main output is 5V at 50A max., 5A min.

$$R_o = 5\text{V}/50\text{A} = 0.1\Omega, R_o = 5\text{V}/5\text{A} = 1\Omega$$

The output filter capacitor is $15\mu\text{F}$.

$$R_p = 1/2\pi R_o C = 1/2\pi \cdot 0.1 \times 15\mu = 110\text{KHz at } 50\text{A}, 11\text{KHz at } 5\text{A}$$

$$k = \text{Max } I_L / \text{max } V_C = 50\text{A}/1.0\text{V} = 50\text{A/V}$$

$$V_o / V_C = K R_o = 50 \times 0.1 = 5 \text{ (14db) at } 50\text{A} \\ = 50 \times 1 = 50 \text{ (34db) at } 5\text{A}$$

 


Figure 6.

Bibliography

- Current mode control, SEM 400 Topic 1, and Application Note U-97
- MOSFET Gate Drive, Addenda, Section D2 or Application Note U-98
- Transformers, Addenda, Section M5
- Inductors, Addenda, Section M6
- Coupled Inductors, Addenda, Section M7
- Feedback Loop, Addenda, Section C1
- Snubbing, Application Note U-85
- Eddy Current Losses, Addenda, Section M-2

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, license, warranty or endorsement thereof.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Resale of TI's products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Also see: [Standard Terms and Conditions of Sale for Semiconductor Products](http://www.ti.com/sc/docs/stdterms.htm). www.ti.com/sc/docs/stdterms.htm

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265