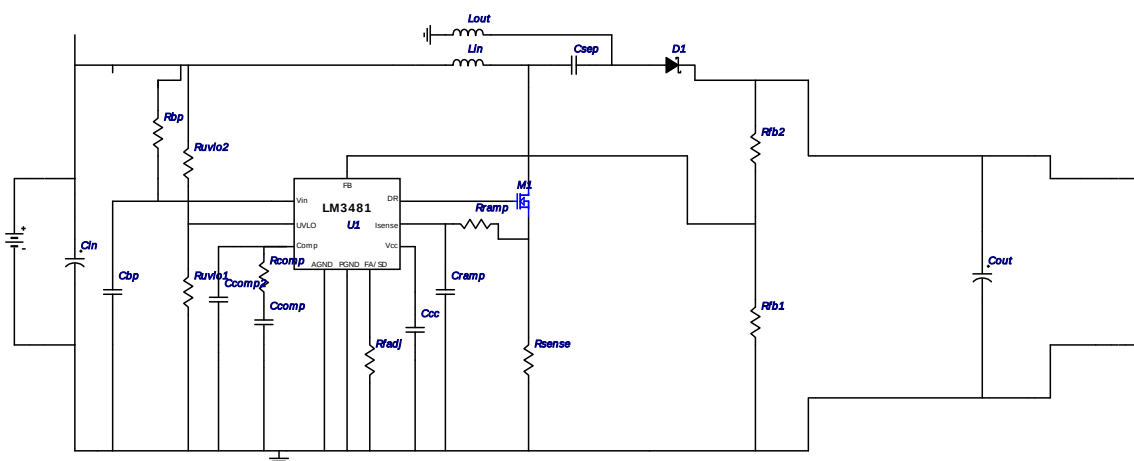



WEBENCH® Design Report

Design : 1043996/35 LM3481MM
LM3481MM 4.5V-25.0V to 5.4V @ 1.0A



Electrical BOM

#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
1.	Cbp	Kemet	C0603C104K5RACTU Series= X7R	1	\$0.01	Cap= 100.0 nF VDC= 50.0 V IRMS= 0.0 A	0603 10mm2
2.	Ccc	MuRata	GRM155R61A224KE19D Series= X5R	1	\$0.01	Cap= 220.0 nF VDC= 10.0 V IRMS= 0.0 A	0402 8mm2
3.	Ccomp	MuRata	GRM155R61A563KA01D Series= X5R	1	\$0.01	Cap= 56.0 nF VDC= 10.0 V IRMS= 0.0 A	0402 8mm2
4.	Ccomp2	MuRata	GRM1885C1H751JA01D Series= C0G/NP0	1	\$0.02	Cap= 750.0 pF VDC= 50.0 V IRMS= 0.0 A	0603 10mm2
5.	Cin	Nippon Chemi-Con	EMVY350ADA680MF80G Series= MVY	1	\$0.13	Cap= 68.0 µF ESR= 340.0 mOhm VDC= 35.0 V IRMS= 280.0 mA	 CAPSMT_62_F80 74mm2
6.	Cout	Nippon Chemi-Con	APXE100ARA121MF61G Series= PXE	1	\$0.48	Cap= 120.0 µF ESR= 25.0 mOhm VDC= 10.0 V IRMS= 2.53 A	 CAPSMT_62_F61 74mm2
7.	Cramp	Yageo America	CC0805KRX7R9BB821 Series= X7R	1	\$0.01	Cap= 820.0 pF VDC= 50.0 V IRMS= 0.0 A	 0805 13mm2
8.	Csep	TDK	C4532X7R1H475M Series= X7R	1	\$0.35	Cap= 4.7 µF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 2.9 A	 1812 39mm2
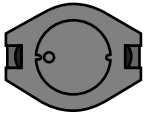
#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
9.	D1	Diodes Inc.	B260A-13-F	1	\$0.11	VF@Io= 700.0 mV VRRM= 60.0 V	 SMA 37mm2
10.	Lin	Würth Elektronik eiSos	744071150	1	\$1.10	L= 15.0 µH DCR= 46.0 mOhm	 IND_WE-TPC 23mm2
11.	Lout	Bourns	SDR1005-470KL	1	\$0.28	L= 47.0 µH DCR= 190.0 mOhm	 SDR1005 176mm2
12.	M1	Vishay-Siliconix	SI4446DY	1	\$0.26	VdsMax= 40.0 V IdsMax= 3.9 Amps	 SOIC-8 55mm2
13.	Rbp	Vishay-Dale	CRCW040220R0FKED Series= CRCW..e3	1	\$0.01	Res= 20.0 Ohm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
14.	Rcomp	Vishay-Dale	CRCW04022K61FKED Series= CRCW..e3	1	\$0.01	Res= 2.61 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
15.	Rfadj	Vishay-Dale	CRCW040247K5FKED Series= CRCW..e3	1	\$0.01	Res= 47.5 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
16.	Rfb1	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	1	\$0.01	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
17.	Rfb2	Vishay-Dale	CRCW040232K4FKED Series= CRCW..e3	1	\$0.01	Res= 32.4 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
18.	Rramp	Vishay-Dale	CRCW0805100RFKEA Series= CRCW..e3	1	\$0.01	Res= 100.0 Ohm Power= 125.0 mW Tolerance= 1.0%	 0805 13mm2
19.	Rsense	Stackpole Electronics Inc	CSR1206FK25L0 Series= ?	1	\$0.10	Res= 25.0 mOhm Power= 500.0 mW Tolerance= 1.0%	 1206 19mm2
20.	Rvlo1	Vishay-Dale	CRCW040268K1FKED Series= CRCW..e3	1	\$0.01	Res= 68.1 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
21.	Rvlo2	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	1	\$0.01	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
22.	U1	Texas Instruments	LM3481MM	1	\$0.90	Switcher	 MUA08A 34mm2

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	3.486 m A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	1.218 A	Current	Output capacitor RMS ripple current
3.	Csep IRMS	1.223 A	Current	SEPIC capacitor RMS ripple current
4.	D1 Irms	1.571 A	Current	D1 Irms
5.	IC Ipk	8.24 m A	Current	Peak switch current in IC
6.	Iin Avg	1.549 A	Current	Average input current
7.	Iin Ipk	1.693 A	Current	Iin peak current
8.	Iin Ipp	415.571 m A	Current	Peak-to-peak input inductor ripple current
9.	Iin Irms	1.499 A	Current	Iin ripple current
10.	Lout Ipk	1.064 A	Current	Lout peak current
11.	Lout Ipp	133.415 m A	Current	Peak-to-peak output inductor ripple current
12.	Lout Irms	1.003 A	Current	Lout ripple current
13.	M1 Irms	1.947 A	Current	M1 MOSFET Irms
14.	BOM Count	22.0	General	Total Design BOM count
15.	FootPrint	645.0 mm2	General	Total Foot Print Area of BOM components
16.	Frequency	405.0 k Hz	General	Switching frequency
17.	IC Tolerance	19.0 m V	General	IC Feedback Tolerance
18.	Mode	CCM	General	Conduction Mode

#	Name	Value	Category	Description
19.	Total BOM	\$3.85	General	Total BOM Cost
20.	D1 Tj	47.625 degC	Op_Point	D1 junction temperature
21.	SEPIC Resonance Freq	12.565 k Hz	Op_Point	SEPIC Resonance Frequency
22.	V SEPIC damping factor	128.314 m	Op_Point	V SEPIC damping factor
23.	Vin p-p	4.037 m V	Op_Point	Peak-to-peak input voltage
24.	Vsep p-p	314.979 m V	Op_Point	Peak-to-peak sepic voltage
25.	Cross Freq	6.151 k Hz	Op_point	Bode plot crossover frequency
26.	Duty Cycle	60.5 %	Op_point	Duty cycle
27.	Efficiency	77.49 %	Op_point	Steady state efficiency
28.	Gain Marg	10.152 db	Op_point	Bode Plot Gain Margin
29.	IC Tj	71.2 degC	Op_point	IC junction temperature
30.	IOUT_OP	1.0 A	Op_point	Iout operating point
31.	M1 TJOP	63.421 degC	Op_point	M1 MOSFET junction temperature
32.	Phase Marg	57.901 deg	Op_point	Bode Plot Phase Margin
33.	Phase Shift	59.258 deg	Op_point	Bode Plot Phase Shift
34.	VIN_OP	4.5 V	Op_point	Vin operating point
35.	Vout p-p	70.611 m V	Op_point	Peak-to-peak output ripple voltage
36.	Cin Pd	4.131 μ W	Power	Input capacitor power dissipation
37.	Cout Pd	37.074 m W	Power	Output capacitor power dissipation
38.	Csep Pd	4.484 m W	Power	SEPIC capacitor power dissipation
39.	D1 Pd	704.99 m W	Power	Diode power dissipation
40.	D1 PdCond	700.0 m W	Power	Diode conduction losses
41.	D1 PdSw	4.99 m W	Power	Diode switching losses
42.	IC Pd	206.0 m W	Power	IC power dissipation
43.	Lin Pd	104.851 m W	Power	Lin power dissipation
44.	Lout Pd	191.455 m W	Power	Lout power dissipation
45.	M1 Pd	371.439 m W	Power	M1 MOSFET total power dissipation
46.	M1 PdCond	237.761 m W	Power	M1 MOSFET conduction losses
47.	M1 PdSw	133.679 m W	Power	M1 MOSFET switching losses
48.	Rsense Pd	94.797 m W	Power	LED Current Rsns Power Dissipation
49.	Total Pd	1.569 W	Power	Total Power Dissipation

Design Inputs

#	Name	Value	Description
1.	Iout	1.0 A	Maximum Output Current
2.	Iout1	1.0 Amps	Output Current #1
3.	VinMax	25.0 V	Maximum input voltage
4.	VinMin	4.5 V	Minimum input voltage
5.	Vout	5.4 V	Output Voltage
6.	Vout1	5.4 Volt	Output Voltage #1
7.	base_pn	LM3481	National Based Product Number
8.	Ta	30.0 degC	Ambient temperature

Design Assistance

1. **LM3481** Product Folder : <http://www.ti.com/product/LM3481> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).