
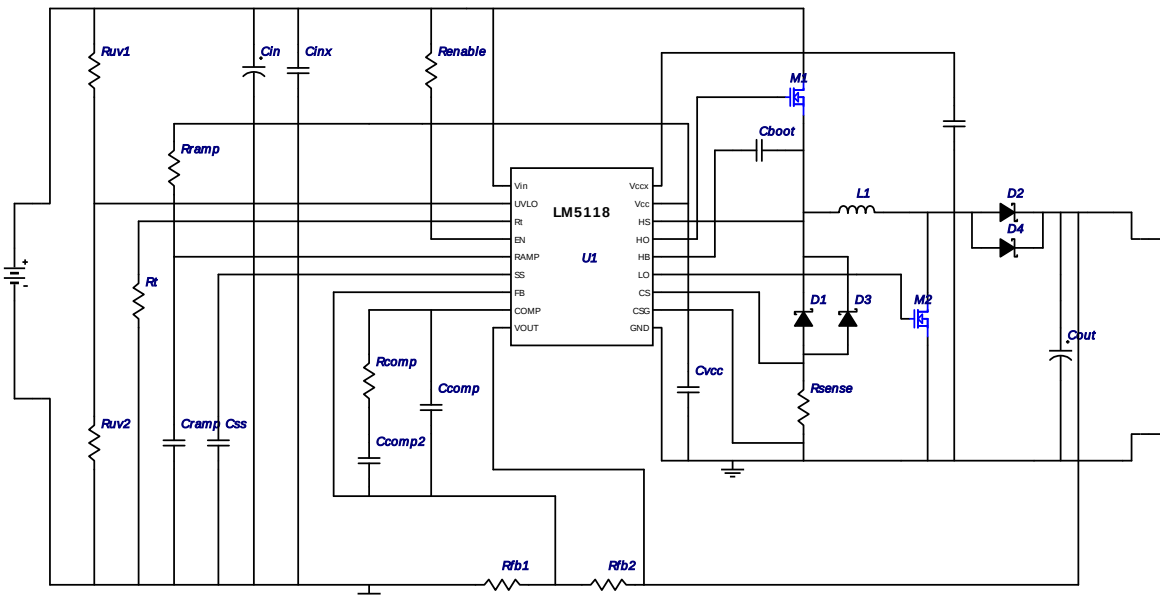
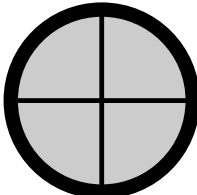



WEBENCH® Design Report

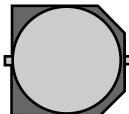Design : 3595001/19 LM5118MH/NOPB
LM5118MH/NOPB 23.0V-34.0V to 28.0V @ 5.0A



Electrical BOM

#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
1.	Cboot	MuRata	GRM21BR71E104KA01L Series= X7R	1	\$0.01	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	 0805 13mm2
2.	Ccomp	Yageo America	CC0805KRX7R9BB271 Series= X7R	1	\$0.01	Cap= 270.0 pF VDC= 50.0 V IRMS= 0.0 A	 0805 13mm2
3.	Ccomp2	Yageo America	CC0805KRX7R9BB272 Series= X7R	1	\$0.01	Cap= 2.7 nF VDC= 50.0 V IRMS= 0.0 A	 0805 13mm2
4.	Cin	Panasonic	EEUED2D221 Series= 286	3	\$1.28	Cap= 220.0 µF ESR= 110.775 mOhm VDC= 200.0 V IRMS= 2.0 A	 CAPPR7.5-18X31.5 400mm2
5.	Cinx	Kemet	C0805C104K5RACTU Series= X7R	1	\$0.01	Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A	 0805 13mm2
6.	Cout	Panasonic	EEE-FC1H470P Series= FC	14	\$0.24	Cap= 47.0 µF ESR= 300.0 mOhm VDC= 50.0 V IRMS= 500.0 mA	 SM_RADIAL_G 172mm2
7.	Cramp	Yageo America	CC0805KRX7R9BB272 Series= X7R	1	\$0.01	Cap= 2.7 nF VDC= 50.0 V IRMS= 0.0 A	 0805 13mm2
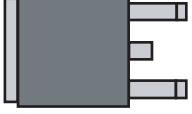
#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
8.	Css	Yageo America	CC0805KRX7R9BB223 Series= X7R	1	\$0.01	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	 0805 13mm2
9.	Cvcc	MuRata	GRM155R61A105KE15D Series= X5R	1	\$0.01	Cap= 1.0 µF VDC= 10.0 V IRMS= 0.0 A	 0402 8mm2
10.	D1	Vishay-Semiconductor	MBRB745PBF	1	\$0.67	VF@Io= 700.0 mV VRRM= 45.0 V	 DDPAK 210mm2
11.	D2	Vishay-Semiconductor	MBRB745PBF	1	\$0.67	VF@Io= 700.0 mV VRRM= 45.0 V	 DDPAK 210mm2
12.	D3	Vishay-Semiconductor	MBRB745PBF	1	\$0.67	VF@Io= 700.0 mV VRRM= 45.0 V	 DDPAK 210mm2
13.	D4	Vishay-Semiconductor	MBRB745PBF	1	\$0.67	VF@Io= 700.0 mV VRRM= 45.0 V	 DDPAK 210mm2
14.	L1	CUSTOM	CUSTOM	1	\$0.00	L= 50.664 µH DCR= 28.0 mOhm	CUSTOM 0mm2
15.	M1	NXP Semiconductor	PSMN5R5-60YS	1	\$0.63	VdsMax= 60.0 V IdsMax= 74.0 Amps	 LPAK 56mm2
16.	M2	AOS	AON7242	1	\$0.49	VdsMax= 40.0 V IdsMax= 30.0 Amps	 TRANS_AOS_DFN3.3X3.3 28mm2
17.	Rcomp	Vishay-Dale	CRCW040286K6FKED Series= CRCW..e3	1	\$0.01	Res= 86.6 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
18.	Renable	Vishay-Dale	CRCW04021M00FKED Series= CRCW..e3	1	\$0.01	Res= 1000.0 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
19.	Rfb1	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	1	\$0.01	Res= 1,000 Ohm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
20.	Rfb2	Vishay-Dale	CRCW040221K5FKED Series= CRCW..e3	1	\$0.01	Res= 21.5 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
21.	Rramp	Vishay-Dale	CRCW040276K8FKED Series= CRCW..e3	1	\$0.01	Res= 76.8 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
22.	Rsense	Bourns	CRA2512-FZ-R010ELF Series= 385	1	\$0.17	Res= 10.0 mOhm Power= 3.0 W Tolerance= 1.0%	 2512 43mm2
23.	Rt	Vishay-Dale	CRCW040261K9FKED Series= CRCW..e3	1	\$0.01	Res= 61.9 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
24.	Ruv1	Vishay-Dale	CRCW040237K4FKED Series= CRCW..e3	1	\$0.01	Res= 37.4 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2

#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
25.	Ruv2	Vishay-Dale	CRCW04022K67FKED Series= CRCW..e3	1	\$0.01	Res= 2.67 kOhm Power= 63.0 mW Tolerance= 1.0%	 0402 8mm2
26.	U1	Texas Instruments	LM5118MH/NOPB	1	\$2.38	Switcher	 MXA20A 71mm2

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	2.465 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	713.008 m A	Current	Output capacitor RMS ripple current
3.	HS Ipk	8.375 A	Current	Peak switch current in IC
4.	Iin Avg	4.388 A	Current	Average input current
5.	L Ipp	2.47 A	Current	Peak-to-peak inductor ripple current
6.	L1 Irms	7.569 A	Current	Inductor ripple current
7.	LS Ipk	8.065 A	Current	Peak switch current in IC
8.	M1 Irms	5.79 A	Current	MOSFET RMS ripple current
9.	M2 Irms	3.978 A	Current	MOSFET RMS ripple current
10.	BOM Count	41.0	General	Total Design BOM count
11.	FootPrint	4.895 k mm2	General	Total Foot Print Area of BOM components
12.	Frequency	100.0 k Hz	General	Switching frequency
13.	IC Tolerance	18.0 m V	General	IC Feedback Tolerance
14.	M1 ThetaJA	40.0 degC/W	General	MOSFET junction-to-ambient thermal resistance
15.	M2 ThetaJA	55.0 degC/W	General	MOSFET junction-to-ambient thermal resistance
16.	Pout	140.0 W	General	Total output power
17.	Total BOM	\$0.0	General	Total BOM Cost
18.	Boost Duty Cycle	32.183 %	Op_point	Boost Duty cycle
19.	Buck Duty Cycle	58.371 %	Op_point	Buck Duty cycle
20.	Cross Freq	4.543 k Hz	Op_point	Bode plot crossover frequency
21.	Efficiency	93.844 %	Op_point	Steady state efficiency
22.	IC Tj	57.059 degC	Op_point	IC junction temperature
23.	ICThetaJA	40.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
24.	IOUT_OP	5.0 A	Op_point	Iout operating point
25.	M1 TJOP	39.216 degC	Op_point	MOSFET junction temperature
26.	M2 TJOP	33.319 degC	Op_point	MOSFET junction temperature
27.	Operating Topology	Transition	Op_point	The current operating topology of the device
28.	Phase Marg	30.946 deg	Op_point	Bode Plot Phase Margin
29.	VIN_OP	34.0 V	Op_point	Vin operating point
30.	Vout p-p	53.135 m V	Op_point	Peak-to-peak output ripple voltage
31.	Cin Pd	224.312 m W	Power	Input capacitor power dissipation
32.	Cout Pd	10.894 m W	Power	Output capacitor power dissipation
33.	IC Pd	926.472 m W	Power	IC power dissipation
34.	L Pd	1.764 W	Power	Inductor power dissipation
35.	M1 Pd	848.699 m W	Power	MOSFET power dissipation
36.	M1 PdCond	820.129 m W	Power	M1 MOSFET conduction losses
37.	M1 PdSw	28.569 m W	Power	M1 MOSFET switching losses
38.	M2 Pd	262.977 m W	Power	MOSFET power dissipation
39.	M2 PdCond	116.879 m W	Power	M2 MOSFET conduction losses
40.	M2 PdSw	146.098 m W	Power	M2 MOSFET switching losses
41.	Total Pd	9.184 W	Power	Total Power Dissipation
42.	Diode 1 Power Dissipation	728.503 m OpvalUnits.PD	Unknown	Power dissipation in the diode
43.	Diode 2 Power Dissipation	1.823 OpvalUnits.PD	Unknown	Power dissipation in the diode
44.	Diode 3 Power Dissipation	728.503 m OpvalUnits.PD	Unknown	Power dissipation in the diode
45.	Diode 4 Power Dissipation	1.823 OpvalUnits.PD	Unknown	Power dissipation in the diode

Design Inputs

#	Name	Value	Description
1.	Iout	5.0 A	Maximum Output Current
2.	Iout1	5.0 Amps	Output Current #1
3.	VinMax	34.0 V	Maximum input voltage
4.	VinMin	23.0 V	Minimum input voltage
5.	Vout	28.0 V	Output Voltage
6.	Vout1	28.0 Volt	Output Voltage #1
7.	base_pn	LM5118	National Based Product Number
8.	source	DC	Input Source Type
9.	Ta	20.0 degC	Ambient temperature

Design Assistance

1. The LM5118 is a wide range buck-boost controller which is operable in an ultra wide input range of 3 to 75V. A buck-boost regulator can maintain regulation for input voltages either higher or lower than the output voltage. The challenge is that buck-boost power converters are not as efficient as buck regulators. The LM5118 has been designed as a dual mode controller whereby the power converter acts as a buck regulator while the input voltage is above the output. As the input voltage approaches the output voltage, a gradual transition to the buck-boost mode occurs. This gradual transition between modes eliminates disturbances at the output during transitions.

2. **LM5118 Product Folder** : <http://www.ti.com/product/lm5118> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).