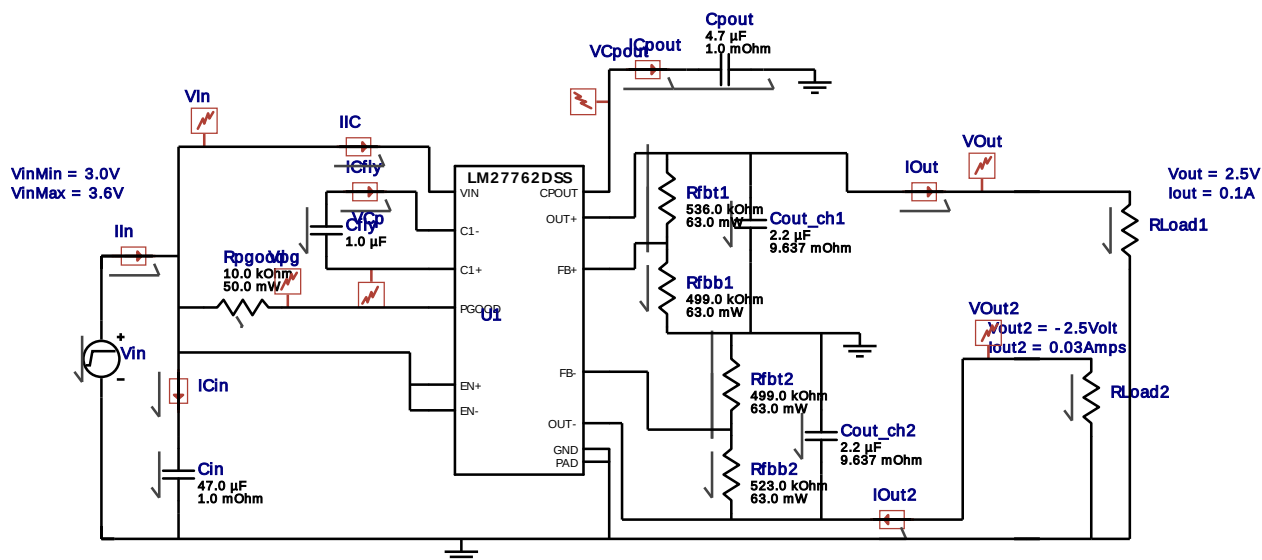


WEBENCH® Electrical Simulation Report



My Comments

No comments





Electrical BOM


#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cfly	Panasonic	ECPU1C105MA5 Series= ECPU(A)	Cap= 1.0 µF VDC= 16.0 V IRMS= 0.0 A	1	NA	1210 15 mm ²
2.	Cin	Taiyo Yuden	JMK212BJ476MG-T Series= X5R	Cap= 47.0 µF ESR= 1.0 mOhm VDC= 6.3 V IRMS= 0.0 A	1	\$0.15	0805 7 mm ²
3.	Cout_ch1	MuRata	GRM188R60J225KE19D Series= X5R	Cap= 2.2 µF ESR= 9.637 mOhm VDC= 6.3 V IRMS= 1.323 A	1	\$0.02	0603 5 mm ²
4.	Cout_ch2	MuRata	GRM188R60J225KE19D Series= X5R	Cap= 2.2 µF ESR= 9.637 mOhm VDC= 6.3 V IRMS= 1.323 A	1	\$0.02	0603 5 mm ²
5.	Cpout	MuRata	GRM155R60J475ME87D Series= X5R	Cap= 4.7 µF ESR= 1.0 mOhm VDC= 6.3 V IRMS= 0.0 A	1	\$0.02	0402_065 3 mm ²
6.	Rfbb1	Vishay-Dale	CRCW0402499KFKED Series= CRCW..e3	Res= 499.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
7.	Rfbb2	Vishay-Dale	CRCW0402523KFKED Series= CRCW..e3	Res= 523.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
8.	Rfbb1	Vishay-Dale	CRCW0402536KFKED Series= CRCW..e3	Res= 536.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
9.	Rfbb2	Vishay-Dale	CRCW0402499KFKED Series= CRCW..e3	Res= 499.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	Rpgood	Yageo America	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
11.	U1	Texas Instruments	LM27762DSSR	Switcher	1	\$0.79	DSS0012B 12 mm ²

Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Cfly	IC	Initial Condition	0 V
2.	Cout_ch1C		Initial Condition	0 V
3.	Cout_ch2C		Initial Condition	0 V
4.	RLoad1 R		Load resistance	25.0 Ohm
5.	RLoad2 R		Load Resistance	83.33333333333334 Ohm

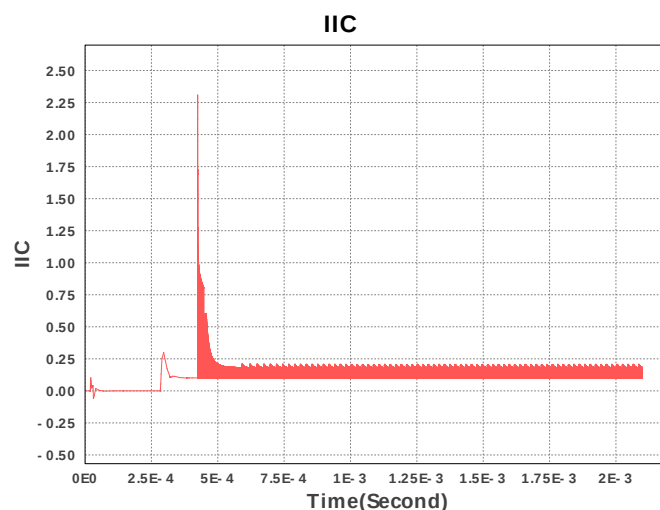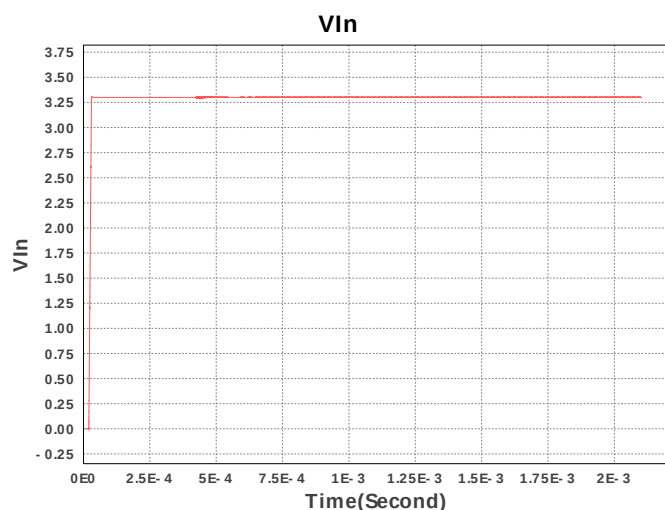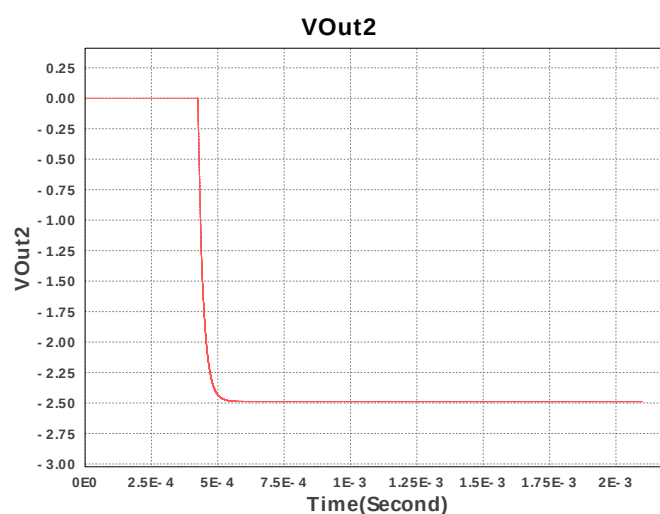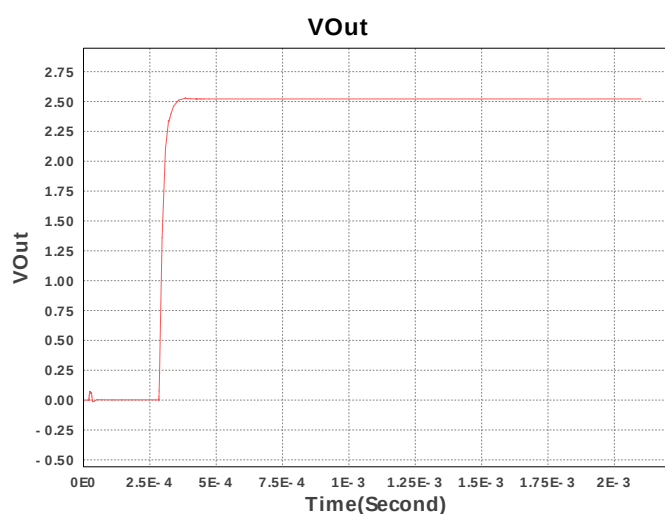

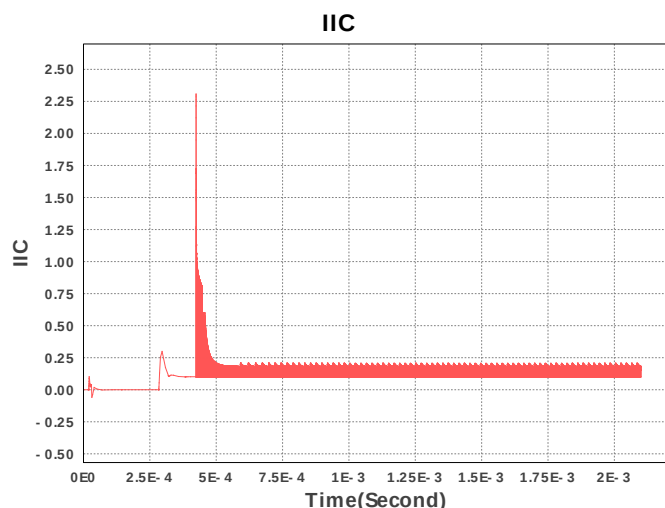

Design Inputs

#	Name	Value	Description
1.	Iout	100.0 mA	Maximum Output Current
2.	VinMax	3.6 V	Maximum input voltage
3.	VinMin	3.0 V	Minimum input voltage
4.	Vout	2.5 V	Output Voltage
5.	base_pn	LM27762	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0 degC	Ambient temperature

Operating Values

#	Name	Value	Category	Description
1.	Total BOM	\$0.0		Total BOM Cost
2.	BOM Count	5	General	Total Design BOM count
3.	FootPrint	60.0 mm ²	General	Total Foot Print Area of BOM components
4.	Frequency	2.0 MHz	General	Switching frequency
5.	Pout	324.96 mW	General	Total output power
6.	Efficiency	68.499 %	Op Point	Steady state efficiency
7.	IC Tj	38.984 degC	Op Point	IC junction temperature
8.	ICThetaJA	62.2 degC/W	Op Point	IC junction-to-ambient thermal resistance
9.	IOUT_OP	100.0 mA	Op Point	Iout operating point
10.	VIN_OP	3.6 V	Op Point	Vin operating point
11.	Vout OP	2.489 V	Op Point	Operational Output Voltage
12.	Vout p-p	694.365 μ V	Op Point	Peak-to-peak output ripple voltage
13.	Vout2 OP	-2.499 V	Op Point	Operational Voltage 2
14.	Vout2 p-p	208.309 μ V	Op Point	Peak-to-peak output voltage ripple channel 2
15.	IC Pd	144.444 mW	Power	IC power dissipation
16.	Total Pd	144.444 mW	Power	Total Power Dissipation

Design Assistance

-
- LM27762** Product Folder : <http://www.ti.com/product/LM27762> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).