

WEBENCH[®] Transformer Report

Design : 1243391/13351 UCC28740DR
UCC28740DR 85.0V-265.0V to 3.30V @ 3.3A

#	Name	Value
1.	Core Part Number	B66311G0000X127
2.	Core Manufacturer	TDK
3.	Coil Former Part Number	B66206B1110T001
4.	Coil Former Manufacturer	TDK

Transformer Electrical Diagram

Primary


Turns	88
AWG	32
Layers	2
Strands	1
Insulation Type	Heavy Insulated Magnet Wire

Auxiliary


Turns	18
AWG	24
Layers	1
Strands	1
Insulation Type	Heavy Insulated Magnet Wire

Secondary

Turns	4
AWG	26
Layers	1
Strands	4
Insulation Type	Triple Insulated

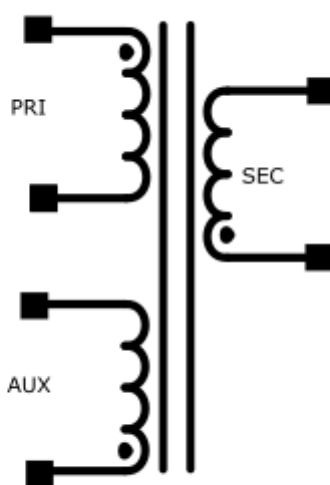

Transformer Construction Diagram

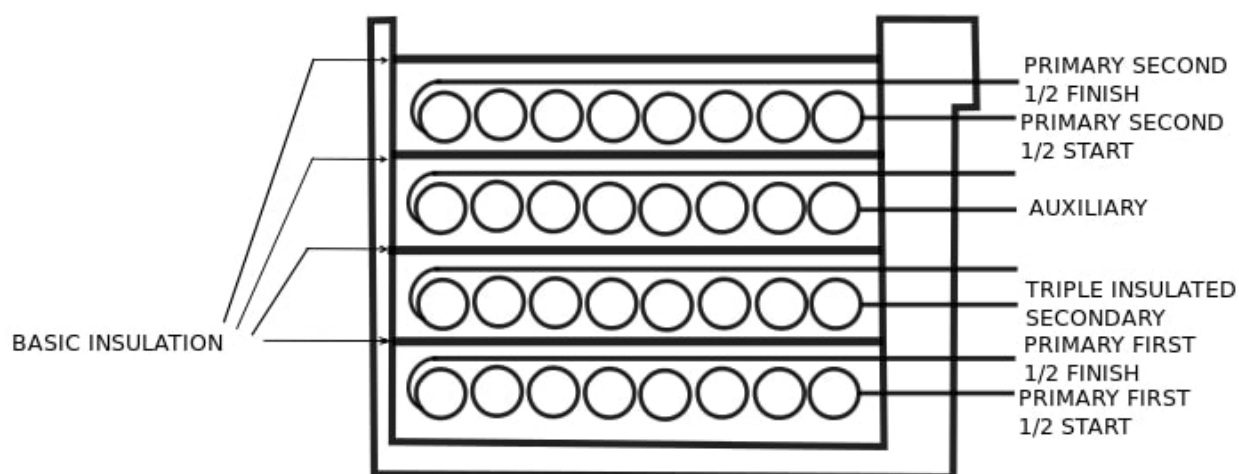

Winding Instruction

Winding	AWG	Turns	Winding Orientation
Primary First 1/2	32	44	Clockwise
Triple Insulated Secondary	26	4	Counter Clockwise
Auxiliary	24	18	Counter Clockwise
Primary Second 1/2	32	44	Clockwise

Transformer Parameters

#	Name	Value
1.	Lpri	0.00114H
2.	Inductance Factor(Al)	148nH
3.	Npri	88
4.	Nsec	4
5.	Naux	18
6.	Core Type	E20/10/6
7.	Core Material	N27
8.	Bmax	0.25T
9.	Switching Frequency	63.00kHz
10.	DMax	0.31
11.	Ipk(Primary)	0.62A
12.	Irms(Primary)	0.20A
13.	Ipk(Secondary)	13.50A
14.	Irms(Secondary)	5.09A

Design Assistance

1. Application Hints Rlc Rlc provides the function of feed-forward line compensation to eliminate change in IPP due to change in di/dt and the propagation delay of the internal comparator and MOSFET turn-off time. For best results the chosen value may need to be adjusted based on board, FET and transformer parasitics. Rtl Rtl is added to prevent excessive diode current and limit lopt to the maximum value necessary for regulation. The Rtl value may be adjusted for optimal limiting later during the prototype evaluation process. Rfbt & Rfbb The feedback resistors will set the output voltage of the circuit. The values chosen may need to be fine tuned based on the final Transformer turns ratios and the voltage across the output diode at close to zero current. Rfb3 & Cfb3 Rfb3 is necessary to limit the current into FB and to avoid excess draining of Cvdd during this type of transient situation. The value of Rfb3 is chosen to limit the excess Ifb and Rfb4 current to an acceptable level when the optocoupler is saturated. Cfb3 helps improve the transient response and is estimated initially by equating the time constant to 1ms. This can later be adjusted for optimal performance during prototype evaluation. Rfb4 Rfb4 speeds up the turnoff time of the optocoupler in the case of a heavy load-step transient condition. This value tends to fall within the range of 10k and 100k. A tradeoff must be made between a lower value for faster transient response and a higher value for lower standby power. Rfb4 also serves to set a minimum bias current for the optocoupler and to drain dark current. Part Description The UCC28740 isolated-flyback controller provides Constant-Voltage (CV) using an optical coupler to improve transient response. Constant-Current (CC) regulation is accomplished through Primary Side Regulation (PSR) techniques. Please see the datasheet for further design guidance. <http://www.ti.com/lit/ds/symlink/ucc28740.pdf>

2. **UCC28740** Product Folder : <http://www.ti.com/product/UCC28740> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).