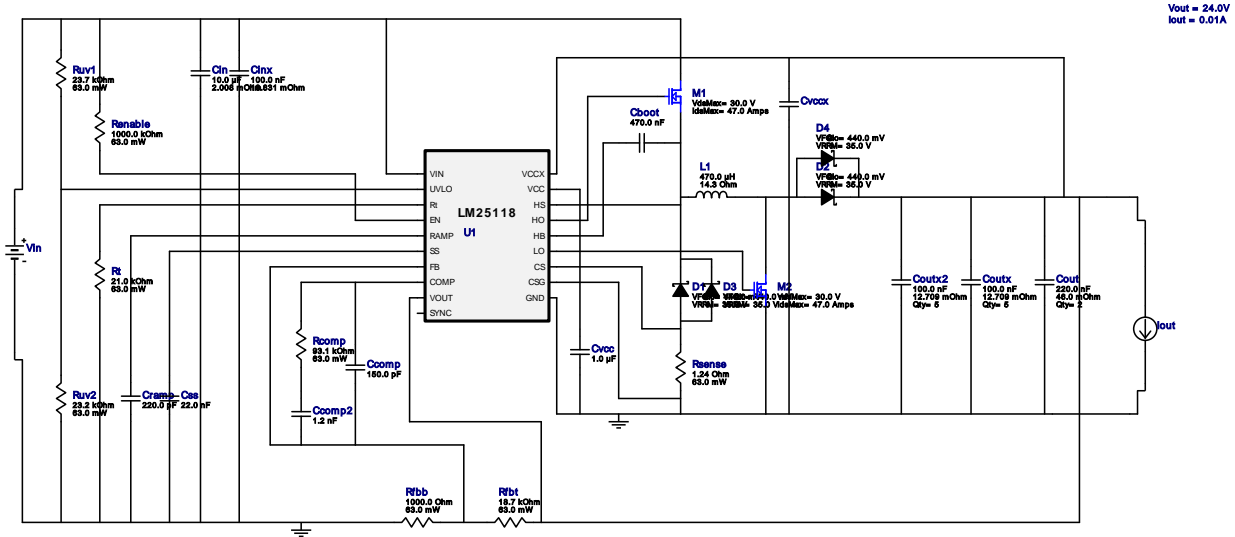

















WEBENCH® Design Report

 Design : 4461414/59 LM25118MH/NOPB
 LM25118MH/NOPB 3.0V-22.0V to 24.00V @ 0.01A

Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
1.	Cboot	MuRata	GRM155C80J474KE19D Series= X6S	Cap= 470.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
2.	Ccomp	AVX	0101YA150JAT2A Series= C0G/NP0	Cap= 150.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.04	01005 2 mm ²
3.	Ccomp2	MuRata	GRM033R71C122KA01D Series= X7R	Cap= 1.2 nF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
4.	Cin	MuRata	GRM32ER7YA106KA12L Series= X7R	Cap= 10.0 uF ESR= 2.008 mOhm VDC= 35.0 V IRMS= 4.6772 A	1	\$0.25	1210_280 15 mm ²
5.	Cinx	TDK	C1005X7R1H104K Series= X7R	Cap= 100.0 nF ESR= 19.831 mOhm VDC= 50.0 V IRMS= 0.0 A	1	\$0.02	1005 3 mm ²
6.	Cout	Kemet	C0805C224K5RACTU Series= X7R	Cap= 220.0 nF ESR= 46.0 mOhm VDC= 50.0 V IRMS= 2.65 A	2	\$0.02	0805 7 mm ²
7.	Coutx	TDK	C2012X8R1H104K Series= X8R	Cap= 100.0 nF ESR= 12.709 mOhm VDC= 50.0 V IRMS= 0.0 A	5	\$0.07	0805 7 mm ²
8.	Coutx2	TDK	C2012X8R1H104K Series= X8R	Cap= 100.0 nF ESR= 12.709 mOhm VDC= 50.0 V IRMS= 0.0 A	5	\$0.07	0805 7 mm ²
9.	Cramp	MuRata	GRM033R71C221KA01D Series= X7R	Cap= 220.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
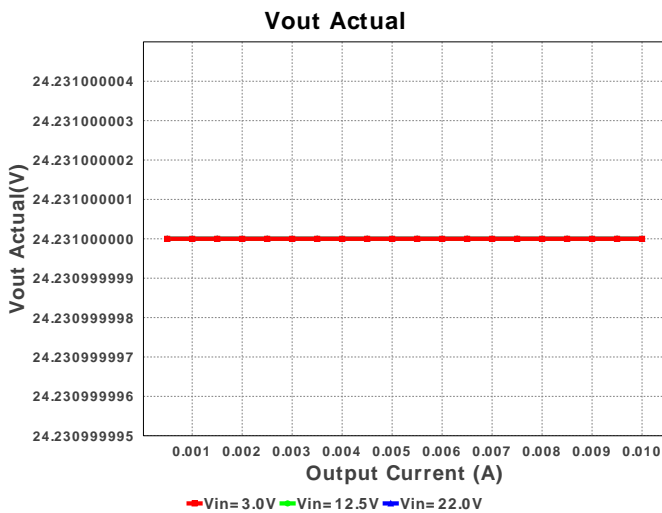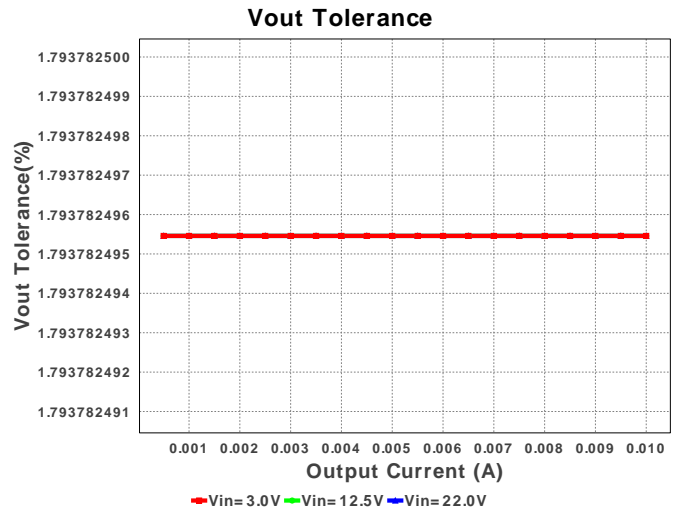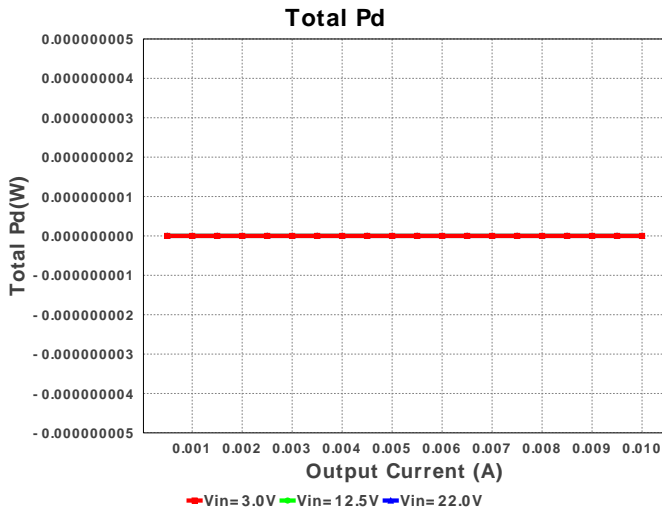
#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
10.	Css	MuRata	GRM033C80J223KE01D Series= X6S	Cap= 22.0 nF VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	 0201 2 mm ²
11.	Cvcc	Kemet	C0603C105K8PACTU Series= X5R	Cap= 1.0 uF VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0603 5 mm ²
12.	D1	Bourns	CD0603-B0130L	VF@Io= 440.0 mV VRRM= 35.0 V	1	\$0.09	 Diode_0603 5 mm ²
13.	D2	Bourns	CD0603-B0130L	VF@Io= 440.0 mV VRRM= 35.0 V	1	\$0.09	 Diode_0603 5 mm ²
14.	D3	Bourns	CD0603-B0130L	VF@Io= 440.0 mV VRRM= 35.0 V	1	\$0.09	 Diode_0603 5 mm ²
15.	D4	Bourns	CD0603-B0130L	VF@Io= 440.0 mV VRRM= 35.0 V	1	\$0.09	 Diode_0603 5 mm ²
16.	L1	Bourns	SDR0302-471KL	L= 470.0 uH DCR= 14.3 Ohm	1	\$0.18	 SDR0302 15 mm ²
17.	M1	Texas Instruments	CSD17308Q3	VdsMax= 30.0 V IdsMax= 47.0 Amps	1	\$0.34	 TRANS_NexFET_Q3 18 mm ²
18.	M2	Texas Instruments	CSD17308Q3	VdsMax= 30.0 V IdsMax= 47.0 Amps	1	\$0.34	 TRANS_NexFET_Q3 18 mm ²
19.	Rcomp	Vishay-Dale	CRCW040293K1FKED Series= CRCW..e3	Res= 93.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
20.	Renable	Vishay-Dale	CRCW04021M00FKED Series= CRCW..e3	Res= 1000.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
21.	Rfbb	Vishay-Dale	CRCW04021K00FKED Series= CRCW..e3	Res= 1000.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
22.	Rfbt	Vishay-Dale	CRCW040218K7FKED Series= CRCW..e3	Res= 18.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
23.	Rsense	Vishay-Dale	CRCW04021R24FKED Series= CRCW..e3	Res= 1.24 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
24.	Rt	Vishay-Dale	CRCW040221K0FKED Series= CRCW..e3	Res= 21.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
25.	Ruv1	Vishay-Dale	CRCW040223K7FKED Series= CRCW..e3	Res= 23.7 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
26.	Ruv2	Vishay-Dale	CRCW040223K2FKED Series= CRCW..e3	Res= 23.2 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm ²
27.	U1	Texas Instruments	LM25118MH/NOPB	Switcher	1	\$2.40	 MXA20A 71 mm ²



Operating Values

#	Name	Value	Category	Description
1.	BOM Count	36	General	Total Design BOM count
2.	FootPrint	282.0 mm ²	General	Total Foot Print Area of BOM components
3.	Frequency	266.445 kHz	General	Switching frequency
4.	IC Tolerance	18.0 mV	General	IC Feedback Tolerance
5.	Total BOM	\$4.78	General	Total BOM Cost
6.	Low Freq Gain	95.932 dB	Op_Point	Gain at 10Hz
7.	Vout Actual	24.231 V	Op_Point	Vout Actual calculated based on selected voltage divider resistors
8.	Cross Freq	5.333 kHz	Op_point	Bode plot crossover frequency
9.	Gain Marg	-6.071 dB	Op_point	Bode Plot Gain Margin
10.	IOUT_OP	10.0 mA	Op_point	Iout operating point
11.	Phase Marg	28.876 deg	Op_point	Bode Plot Phase Margin
12.	VIN_OP	22.0 V	Op_point	Vin operating point
13.	Total Pd	0.0 W	Power	Total Power Dissipation
14.	Vout Tolerance	1.794 %	Unknown	Vout Tolerance based on IC Tolerance and voltage divider resistors if applicable

Design Inputs

#	Name	Value	Description
1.	Iout	10.0 m	Maximum Output Current
2.	VinMax	22.0	Maximum input voltage
3.	VinMin	3.0	Minimum input voltage
4.	Vout	24.0	Output Voltage
5.	base_pn	LM25118	Base Product Number
6.	source	DC	Input Source Type
7.	Ta	30.0	Ambient temperature

Design Assistance

1. The LM25118 is a wide range buck-boost controller which is operable in an ultra wide input range of 3 to 75V. A buck-boost regulator can maintain regulation for input voltages either higher or lower than the output voltage. The challenge is that buck-boost power converters are not

as efficient as buck regulators. The LM5118 has been designed as a dual mode controller whereby the power converter acts as a buck regulator while the input voltage is above the output. As the input voltage approaches the output voltage, a gradual transition to the buck-boost mode occurs. This gradual transition between modes eliminates disturbances at the output during transitions.

2. **LM25118** Product Folder : <http://www.ti.com/product/LM25118> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).