

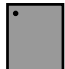


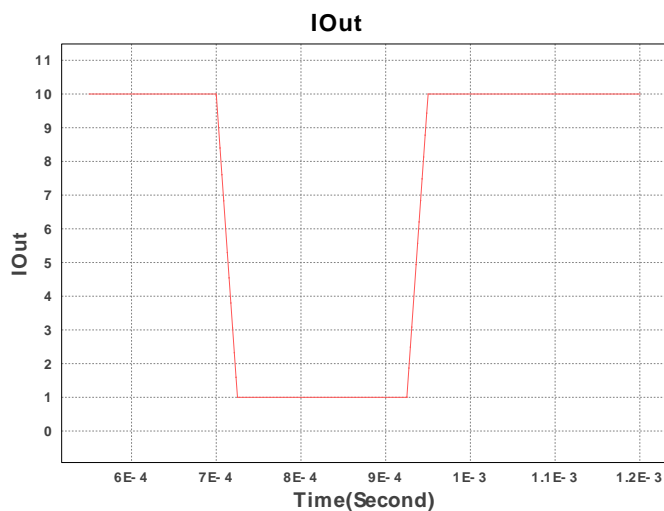

#	Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
9.	Ren	Vishay-Dale	CRCW0402976RFKED Series= CRCW...e3	Res= 976.0 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
10.	Renb	Vishay-Dale	CRCW040286K6FKED Series= CRCW...e3	Res= 86.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
11.	Rent	Vishay-Dale	CRCW04021M15FKED Series= CRCW...e3	Res= 1.15 MOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
12.	Rfbb	Susumu Co Ltd	RR1220P-103-D Series= RR12	Res= 10.0 kOhm Power= 100.0 mW Tolerance= 0.5%	1	\$0.01	0805 7 mm <sup>2</sup>
13.	Rfbt	Vishay-Dale	CRCW040269K8FKED Series= CRCW...e3	Res= 69.8 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
14.	Rlbst	Vishay-Dale	CRCW04021K82FKED Series= CRCW...e3	Res= 1.82 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
15.	Rmodeg	Vishay-Dale	CRCW040297K6FKED Series= CRCW...e3	Res= 97.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
16.	Rpg	Vishay-Dale	CRCW040297K6FKED Series= CRCW...e3	Res= 97.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
17.	Rtrip	Vishay-Dale	CRCW0402143KFKED Series= CRCW...e3	Res= 143.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
18.	U1	Texas Instruments	TPS53319DQPR	Switcher	1	\$3.00	 DQP0022A 56 mm <sup>2</sup>

### Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Cout	IC		5.0 V
2.	Iout	signal_type	Signal Type	PULSE
		I1	Initial Load Current	10.0 A
		I2	Minimum Load Current	1.0 A
		Td	Initial Time Delay	700u s
		Tf	Fall Time	25u s
		Tr	Rise Time	25u s
		Pw	Pulse Width	200u s

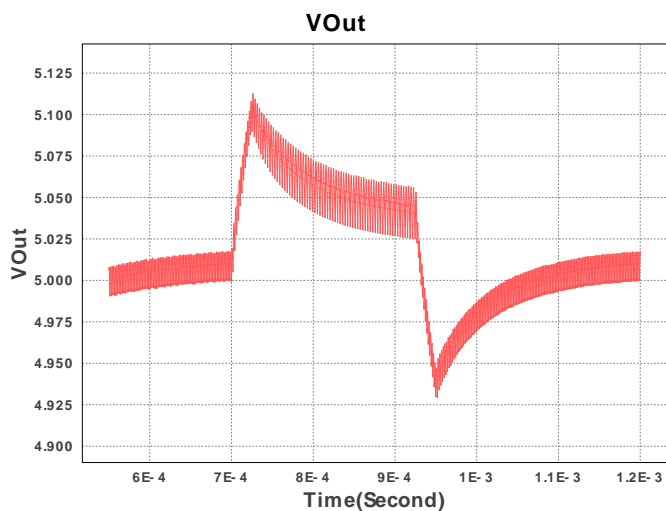

## Design Inputs

#	Name	Value	Description
1.	Iout	10.0 A	Maximum Output Current
2.	VinMax	19.0 V	Maximum input voltage
3.	VinMin	19.0 V	Minimum input voltage
4.	Vout	5.0 V	Output Voltage
5.	base_pn	TPS53319	Texas Instruments Base Part Number
6.	source	DC	Input Source Type
7.	ta	30.0 degC	Ambient temperature

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	4.454 A	Current	Input capacitor RMS ripple current
2.	Cout IRMS	1.002 A	Current	Output capacitor RMS ripple current
3.	IC Ipk	11.736 A	Current	Peak switch current in IC
4.	Iin Avg	2.793 A	Current	Average input current
5.	L Ipp	3.472 A	Current	Peak-to-peak inductor ripple current
6.	BOM Count	18	General	Total Design BOM count
7.	FootPrint	214.0 mm <sup>2</sup>	General	Total Foot Print Area of BOM components
8.	Frequency	500.0 kHz	General	Switching frequency
9.	Mode	CCM	General	Conduction Mode
10.	Pout	50.0 W	General	Total output power
11.	Total BOM	\$4.9	General	Total BOM Cost
12.	Duty Cycle	27.281 %	Op Point	Duty cycle
13.	Efficiency	94.216 %	Op Point	Steady state efficiency
14.	IC Tj	69.11 degC	Op Point	IC junction temperature
15.	ICThetaJA	27.2 degC/W	Op Point	IC junction-to-ambient thermal resistance
16.	IOUT_OP	10.0 A	Op Point	Iout operating point
17.	VIN_OP	19.0 V	Op Point	Vin operating point
18.	Vout Actual	4.788 V	Op Point	Vout Actual calculated based on selected voltage divider resistors
19.	Vout OP	5.0 V	Op Point	Operational Output Voltage
20.	Vout Tolerance	2.332 %	Op Point	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
21.	Vout p-p	19.962 mV	Op Point	Peak-to-peak output ripple voltage
22.	Cin Pd	41.304 mW	Power	Input capacitor power dissipation
23.	Cout Pd	2.851 mW	Power	Output capacitor power dissipation
24.	IC Iq Pd	7.98 mW	Power	IC Iq Pd
25.	IC Pd	1.438 W	Power	IC power dissipation
26.	L Pd	1.588 W	Power	Inductor power dissipation
27.	Total Pd	3.07 W	Power	Total Power Dissipation

## Design Assistance

1. TPS53319 Product Folder : <http://www.ti.com/product/TPS53319> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

**You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.**

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).